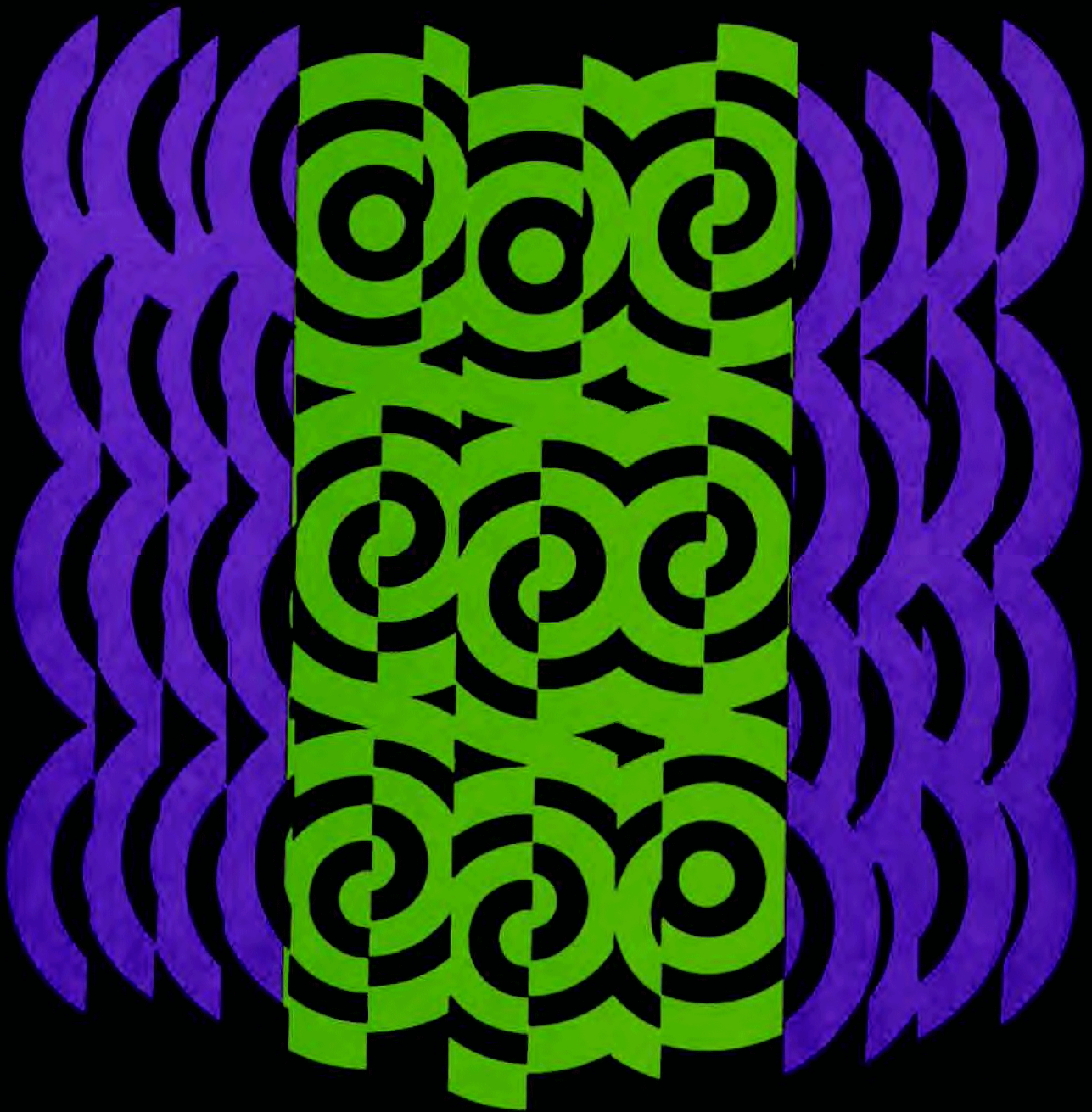


HANDBOOK OF ELECTRONIC DESIGN AND ANALYSIS PROCEDURES USING PROGRAMMABLE CALCULATORS

BRUCE K. MURDOCK



INTRODUCTION

This book provides programming techniques and programs to make the fully programmable calculator a valuable design tool for the working engineer. This book is not specifically intended to be a textbook on calculator programming, although documented programs can serve this purpose. Three books can be recommended for programming methods and algorithms: Jon M. Smith, "Scientific Analysis on the Pocket Calculator," Wiley 1975, John Ball, "Algorithms for RPN Calculators," Wiley 1978, and Richard W. Hamming, "Numerical Methods for Scientists and Engineers," McGraw-Hill 1973.

Many programs in this book are meant to be used in sets, i.e., the output of one program becomes the input for another through common storage register allocations. The description of each program is meant to stand alone, and consists of the following parts:

- 1) Problem description with pertinent equations,
- 2) Program operating instructions,
- 3) One or more program examples,
- 4) Equation and method derivation, or references,
- 5) Annotated program listing, which is its own flowchart.

Part 4 is not present in every program.

This program ordering was chosen so the variable definitions and operating instructions are immediately available to the experienced user. Should the user wish more information or background on the program and equations, or the details of the program operation, this material is also available, but is placed after the operating instructions.

Although the program language, and resulting program flow is tailored to the Hewlett-Packard (HP) fully programmable calculators, the HP-67/97, the annotated program listing/flowchart can be used as a basis for generating programs in other languages.

The language of the Texas Instruments (TI) fully programmable calculator, the TI-59, is not very different from the HP-67/97 language

when considered on a gross scale, therefore, the HP-67/97 programs may be easily translated into the language of the TI-59. While it is easy to write a program from equations and flowcharts, the new program must still be debugged. Translating a program that has already been tested and debugged can lead to a new program that has no bugs at all. The TI program translation will also closely follow the flow of the original HP program.

The differences between the HP and TI languages are mainly in format and not in form. Because the TI-59 has few merged keycodes, must use parentheses to set hierarchy, and must branch to a label or line number as the result of a true conditional test, the TI-59 program will be longer than the mating HP-67/97 program. This increased program length is generally not a detriment as it is accommodated by the larger program memory available in the TI-59. Because the TI-59 always starts label searches from the top of the program, the program execution time can also be longer unless direct addressing is used, or the labeled subroutines are placed at the beginning of the program.

Since the TI-59 does not have a stack to hold the results of an equals operation, a set of scratchpad registers must be set aside to hold those intermediate results normally retained in the HP-67/97 stack. Results residing in the TI-59 display register after the equals operation will permanently disappear unless stored before subsequent operations are performed.

The arithmetic hierarchy of the Algebraic Operating System (AOS) can sometimes be a problem which becomes particularly apparent when calling subroutines. If an equals operation does not precede the subroutine call, the subroutine hierarchy will be dependent on the hierarchy set up in the main program. To make the subroutine hierarchy independent of the main program, the subroutine should always start with an open parenthesis and terminate with a close parenthesis. This rule can be extended to the "go to" command also. The last statement prior to the unconditional jump should be an equals to terminate all pending operations. It will cause no harm to have an open parenthesis as the first statement after the label that is the jump destination. The TI-59 has enough program memory so that, whenever in doubt, parenthesis can be inserted to establish unconditional arithmetic hierarchy.

The TI-59 does not have the equivalent of the HP-67/97 flag 3 function where flag 3 is automatically set whenever numeric data

is entered from the keyboard. Because of this difference, the convenience feature existing in most of the HP-67/97 programs herein where the execution of a user definable key such as "A" without numeric entry results in the currently stored parameter value being displayed cannot be translated to the TI-59 program.

None of the TI-59 flags are test cleared, while flags 2 and 3 of the HP-67/97 are test cleared, thus, clear flag statements may be required in the TI-59 program and subroutines involving the use of flags 2 and 3.

The HP-67/97 and the TI-59 both have user definable labels A through E, and a through e (the latter are designated A' through E' on the TI-59). Executing these keys from the keyboard acts like a subroutine call on either machine: the program pointer jumps to the designated label, and program execution begins. The HP-67/97 and the TI-59 are different in the labels called "common labels" by TI, i.e., labels other than the user definable ones. HP uses the label designators 0 through 9, and a given label may be used more than once as label searches start from the present place in program memory, hence a "local label" such as label 6 in Program 2-4 is used many times within the program. The TI-59 cannot use numeric labels, but uses other function keys as labels, e.g., "sin," "fix," etc. There are 62 such keys available for labels. The TI-59 always starts label searches from the top of the program, hence, a given label can only be used once within the program.

The TI-59 is internally set up to be most efficient, time wise, when jumps and branches are made to line numbers rather than to labels. The HP-67/97 appears to be as fast in a label search as the TI-59 is in a line number search. The HP-67/97 cannot go to a specified line number under program control, hence, it is restricted to label searches only. There is a simple program trick shown on page IV-98 of the TI-59 owner's manual where a program is initially written with labels, and the label calls have "NOP" statements following so the program can easily be modified for line number addressing after the program is debugged and complete.

Care should be exercised when translating program coding containing rectangular-to-polar ($\rightarrow P$) and polar-to-rectangular ($\rightarrow R$) conversions as the TI-59 and HP-67/97 operate on the variables in opposite manner. The HP-67/97 takes the x and y coordinates from the x and y registers

and places the magnitude and angle equivalents back into the x and y registers respectively for the $\rightarrow P$ conversion, and vice-versa for the $\rightarrow R$ conversion. The TI-59 uses the t and x registers for the two variables, and takes the x and y coordinates from the t and x registers and places the equivalent magnitude and angle back into the t and x registers respectively for the $\rightarrow P$ conversion, and vice-versa for the $\rightarrow R$ conversion. Both machines display the contents of the x register, so the TI-59 will display angle or y coordinate whereas the HP-67/97 will display magnitude or x coordinate after respective $\rightarrow P$ or $\rightarrow R$ conversions.

To guide the reader in this translation, several programs in this book have been translated into the TI-59 language. These programs have user instructions, examples, and program coding in both languages. Program 1-1 has been flowcharted in addition to provide a common point of reference between the two program listings.

The preceding paragraphs mention anomalies in the TI-59 language. The HP-67/97 language has its idiosyncracies also. Reading the program listings, one will notice some "non-standard" program coding. The prime consideration was to fit the algorithm into the program memory. Within this constraint, the program coding was selected to minimize program execution time whenever possible. Numeric entries within the body of the program are to be avoided, and should be recalled from register storage. Entry of each numeric digit requires 72 milliseconds to execute while a register recall only requires 35 milliseconds typically. Numeric entries such as "10," "100," or any other power of 10 should be entered as a power of ten through the "EEX" key. The number "1" should be entered as "EEX" alone and requires only 48 milliseconds to execute. Similarly, the "CLX" function will result in a zero in the display, and only requires 30 milliseconds to execute. Multiplication of a number by two (2, x) requires 179 milliseconds to execute, while addition of a number to itself (ENT \uparrow , +) requires 82 milliseconds execution time and yields the same result. Register arithmetic is executed faster than stack arithmetic when the register recalls are considered, and register arithmetic can save program steps. Whenever the algorithm allows, subroutine calls should be minimized as they typically require 240 milliseconds for the label search and return. Likewise unconditional jumps such as GTOA require 160 milliseconds for the label search typically. By paying attention to small details such as these, the program

execution time can be shortened considerably especially when iteration or looping is required. For more information on execution times and programming hints with the HP-67/97, see "Better Programming on the HP-67/97" edited by William Kolb, John Kennedy, and Richard Nelson, and available from the PPC Club (new name for the HP-65 Users Club), 2541 W. Camden Place, Santa Ana, Calif. 92704.

Even though the program coding has been chosen for minimum execution time, the program LNAP may require more than a minute of computation time before output is provided when the number of branches is large. Likewise, the same time requirement may exist for the filter programs when the filter order is large.

An attempt has been made to choose self-explanatory label descriptions for the user definable keys; hence, once familiar with a particular program, the user need only refer to the magnetic card label markings to run the program.

To restate a point made in the preface of this book, it is not possible to include programs and descriptions covering all areas of engineering analysis and design. The programs herein are only representative of areas in networks and circuits (the terms "networks" and "circuits" may be used interchangeably). The 39 programs contained in this book have been selected from the author's library, and have proved to be quite useful to the author; hopefully, they will prove equally useful to the reader.

The program description not only shows the equations used by the program, but gives a reference, or has a derivation of the equations so these programs may serve as a base for the generation of other related programs as may be needed by the reader for his or her particular application.

Because the programs herein cover several different disciplines in electrical engineering, a problem with nomenclature arises. To the control systems oriented engineer, the term "transfer function" implies system output divided by system input. On the other hand, to the filter design engineer, "transfer function" implies system input divided by system output, or the reciprocal of the control system engineer's definition. To avoid confusion, the term "transmission function" is used to mean system output divided by input and "transfer function" is used to mean system input divided by output. This convention will be followed

throughout the book.

The appendix has a list of a list of abbreviations used, along with the bibliography give the reader an easily found place to go should confusion or uncertainty to variable or abbreviation meaning arise.

**HANDBOOK OF
ELECTRONIC DESIGN AND
ANALYSIS PROCEDURES USING
PROGRAMMABLE CALCULATORS**

Part 1

NETWORK ANALYSIS

PROGRAM 1-1 LOSSY TRANSMISSION LINE INPUT IMPEDANCE.

Program Description and Equations Used

This program uses Eq. (1-1.1) to determine the complex input impedance, Z_s , of a lossy transmission line of length l , loaded with a complex impedance Z_r , and having a characteristic impedance Z_0 , an attenuation constant α_{dB} in dB per unit length, and a phase constant β in radians per unit length (or velocity of propagation C_m). For solid dielectric cables, C_m is typically 1/2 to 2/3 the free-space speed of light, and is approximated by Eq. (1-1.9) for low loss coaxial cables, or calculated from Eqs. (1-1.5) and (1-1.6) if the cable impedance and admittance per unit length are known at the operating frequency. The unit of length has purposely not been given because it is to be selected by the user. As long as the same length unit is used throughout, length will cancel out of Eq. (1-1.1). Figure 1-1.1 shows the general circuit topology.

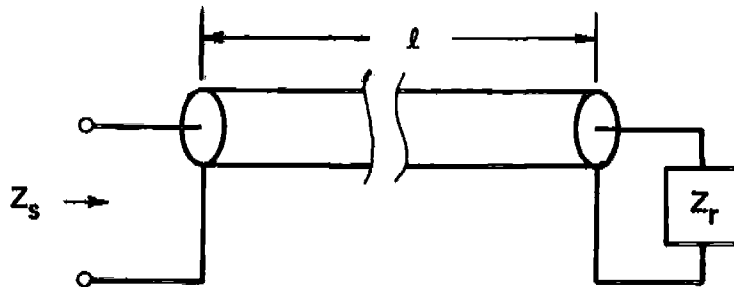


Figure 1-1.1 Transmission line setup.

The equation that describes the problem is:

$$Z_s = Z_o \frac{1 + \rho e^{-2\gamma \ell}}{1 - \rho e^{-2\gamma \ell}} \quad (1-1.1)$$

where ρ is the reflection coefficient and γ is the propagation function. These quantities are given by the following equations:

$$\rho = \frac{Z_r/Z_o - 1}{Z_r/Z_o + 1} \quad (1-1.2)$$

$$\gamma = \alpha + j\beta \quad (1-1.3)$$

$$\alpha = (\alpha_{db})/(20 \log e) \quad (1-1.4)$$

$$\beta = \frac{2\pi}{\lambda} = \frac{2\pi f}{C_m} \quad (1-1.5)$$

If the per unit length series impedance, $\bar{R} + j\omega\bar{L}$, and shunt admittance, $\bar{G} + j\omega\bar{C}$, are available at the frequency of operation, then the propagation function is given by:

$$\gamma = \sqrt{(\bar{R} + j\omega\bar{L})(\bar{G} + j\omega\bar{C})} \quad (1-1.6)$$

If Z_r is desired in terms of Z_s , Z_r is replaced by Z_s in Eq. (1-1.1), Z_s is replaced by Z_r in Eq. (1-1.2), and ℓ is replaced by $-\ell$ in Eq. (1-1.1).

This quasi-symmetrical property allows the use of the same program to calculate the transmission line input impedance with a complex load by using a positive line length, or to calculate the complex load that will provide a specified input impedance by using a negative line length.

A duality also exists with Eq. (1-1.1) and Eq. (1-1.2). The same equation form holds for the transmission line input or output admittance providing each Z is replaced by the corresponding Y , i.e., $Y_s = 1/Z_s$, $Y_r = 1/Z_r$, and $Y_o = 1/Z_o$. The admittance forms of Eqs. (1-1.1) and (1-1.2) are as follows:

$$Y_s = Y_o \frac{1 + \rho' e^{-2\gamma \ell}}{1 - \rho' e^{-2\gamma \ell}} \quad (1-1.7)$$

where

$$\rho' = \frac{Y_r/Y_o - 1}{Y_r/Y_o + 1} \quad (1-1.8)$$

$$(\rho' = -\rho)$$

Because the equation form is the same, the program will work with admittances as well as impedances.

In this HP-67/97 program, keys "A" through "E" and "a" through "c" on the calculator have a dual function role. Execution of these keys following a data entry from the keyboard is interpreted as data input by the program, and the numeric entry is stored. Execution of these keys following a nonnumeric entry, or following the "e" (clear) key is interpreted as an output request, and the currently stored values are printed (HP-97 only) and displayed. This feature cannot be translated into the TI-59 program.

The data required by the program is entered in either cartesian (real and imaginary) or polar (magnitude and angle) form through keys "b" and "c," or "B" and "C" respectively. On large coax cables such as underwater telephone cable, both the cable attenuation and phase constants are provided as a function of frequency by the manufacturer, and are loaded into the program using the units of dB per unit length and radians per unit length respectively. If β is unknown, it can be calculated from the velocity of propagation in the transmission line. If the transmission line has less than 1 dB loss in the length being used, and is of coaxial construction, the velocity in the medium (phase velocity) may be approximated by

$$C_m \approx \frac{\text{speed of light in free space}}{\sqrt{\epsilon_r \mu_r}} \quad (1-1.9)$$

where ϵ_r and μ_r are the relative dielectric constant and relative permeability of the cable dielectric and conductors respectively. For cables constructed of nonmagnetic parts, or for cables with a steel strength member within the center conductor of the cable and operating at frequencies where the skin effect keeps currents from flowing within the strength member, the relative permeability, μ_r becomes unity.

User Instructions

HP-67/97 PROGRAM

LOSSY TRANSMISSION LINE INPUT IMPEDANCE				
$f \uparrow C_m$	$Re Z_0 \uparrow Im Z_0$	$Re Z_r \uparrow Im Z_r$	compute $ Z_s , \angle Z_s$	clear entry mode
$\alpha_{dB} \uparrow \theta \uparrow f$	$ Z_0 \uparrow \angle Z_0$	$ Z_r \uparrow \angle Z_r$	$\rho, \angle \rho$	l

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card			
2	Enter transmission line parameters			
	line loss in dB/unit length	α_{dB}	$\boxed{\uparrow}$	
	phase constant in radians/unit length	θ	$\boxed{\uparrow}$	
	frequency in hertz	f	\boxed{A}	C_m
	If velocity of propagation is known instead of phase constant, enter dummy value of 1 for phase constant in step 3 above, then			
	Enter frequency in hertz	f	$\boxed{\uparrow}$	
	Enter propagation velocity*	C_m	$\boxed{f} \boxed{A}$	θ
	* note:			
	The units of length must be consistent throughout the data, i.e., all in meters, or feet, or miles, etc.			
3	Enter the transmission line characteristics at the chosen analysis frequency			
	magnitude of Z_0 in ohms	$ Z_0 $	$\boxed{\uparrow}$	
	phase angle of Z_0 in degrees	$\angle Z_0$	\boxed{B}	
	OR			
	real part of Z_0 in ohms	$Re Z_0$	$\boxed{\uparrow}$	
	imaginary part of Z_0 in ohms	$Im Z_0$	$\boxed{f} \boxed{B}$	
4	Enter load impedance			
	magnitude of load impedance in ohms	$ Z_r $	$\boxed{\uparrow}$	
	phase angle of load impedance in degrees	$\angle Z_r$	\boxed{C}	
	OR			
	real part of load impedance in ohms	$Re Z_r$	$\boxed{\uparrow}$	
	imaginary part of load impedance in Ω	$Im Z_r$	$\boxed{f} \boxed{C}$	

User Instructions

LOSSY TRANSMISSION LINE INPUT IMPEDANCE


HP-67/97

CONTINUED

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
5	Enter transmission line length	$\pm l$	<input type="button" value="E"/>	
	+l to calculate Z_s given Z_r			
	-l to calculate Z_r given Z_s			
6	Optional, printout or enter refl coef			
	ρ entry	$ \rho \uparrow \angle \rho^\circ$	<input type="button" value="D"/>	
	ρ printout		<input type="button" value="D"/>	$ \rho , \angle \rho^\circ$
	Of the three variables Z_0, Z_r , & ρ			
	either Z_0 & Z_r or Z_0 & ρ			
	are required.			
7	Compute $ Z_s , \angle Z_s$ (length positive)		<input type="button" value="f"/> <input type="button" value="D"/>	$ Z , \angle Z^\circ$
	$ Z_r , \angle Z_r$ (length negative)			
8	To clear input mode and initialize program		<input type="button" value="f"/> <input type="button" value="E"/>	
9	To review input data		<input type="button" value="f"/> <input type="button" value="E"/>	
			<input type="button" value="f"/> <input type="button" value="A"/>	f, C_m
			<input type="button" value="A"/>	α_{dB}, β, f
			<input type="button" value="f"/> <input type="button" value="B"/>	$\text{Re} Z_0, \text{Im} Z_0$
			<input type="button" value="B"/>	$ Z_0 , \angle Z_0^\circ$
			<input type="button" value="f"/> <input type="button" value="O"/>	$\text{Re} Z_r, \text{Im} Z_r$
			<input type="button" value="O"/>	$ Z_r , \angle Z_r^\circ$
			<input type="button" value="D"/>	$ \rho , \angle \rho^\circ$
			<input type="button" value="E"/>	l
	NOTE:			
	The angular mode of the program is degrees.			
	All angular data input and output is in			
	degrees with the exception of β . The			
	angular mode should not be changed as program			
	malfunction will occur because of R \leftrightarrow D and			
	D \leftrightarrow R conversions that are used.			

User Instructions

TI-59 TRANSLATION

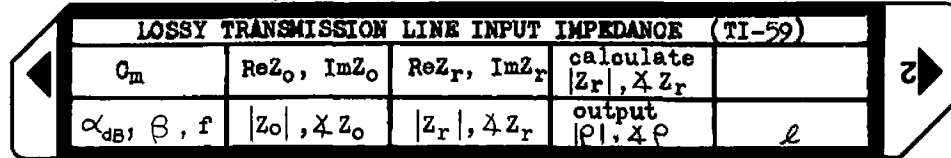

TI-59 TRANSLATION

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of magnetic card			
2	Load line loss in dB/unit length	α_{dB}	<input type="button" value="A"/>	
	Load line phase constant in rad/unit length	β	<input type="button" value="R/S"/>	
	If C_m , the velocity in the medium, is known instead, load dummy β of 1			
	Load analysis frequency in hertz	f	<input type="button" value="R/S"/>	
3	If C_m is known instead of β , load C_m	C_m	<input type="button" value="2nd"/> <input type="button" value="A"/>	
4	Enter Z_0 , the transmission line characteristic impedance in polar or rectangular co-ords			
	polar co-ordinates: magnitude	$ Z_0 , \Omega$	<input type="button" value="B"/>	
	phase angle	$\angle Z_0, ^\circ$	<input type="button" value="R/S"/>	
	rectangular co-ordinates: real part	$\text{Re } Z_0, \Omega$	<input type="button" value="2nd"/> <input type="button" value="B"/>	
	imaginary part	$\text{Im } Z_0, \Omega$	<input type="button" value="R/S"/>	
5	Enter load impedance at the analysis freq as either polar or rectangular data			
	polar co-ordinates:	$ Z_r , \Omega$	<input type="button" value="C"/>	
		$\angle Z_r, ^\circ$	<input type="button" value="R/S"/>	
	rectangular co-ordinates:	$\text{Re } Z_r, \Omega$	<input type="button" value="2nd"/> <input type="button" value="C"/>	
		$\text{Im } Z_r, \Omega$	<input type="button" value="R/S"/>	
6	Load transmission line length	$\pm \ell$	<input type="button" value="E"/>	
	$+\ell$ to calculate Z_s given Z_r			
	$-\ell$ to calculate Z_r given Z_s			
7	Optional: output reflection coefficient		<input type="button" value="D"/> <input type="button" value="R/S"/>	$ \rho $ $\angle \rho^\circ$
8	To calculate Z_s (or Z_r given negative length)		<input type="button" value="2nd"/> <input type="button" value="D"/> <input type="button" value="R/S"/>	$ Z , \Omega$ $\angle Z^\circ$
	* If the TI-59 is attached to the PO-100A printer, the second value will be printed without the R/S command.			

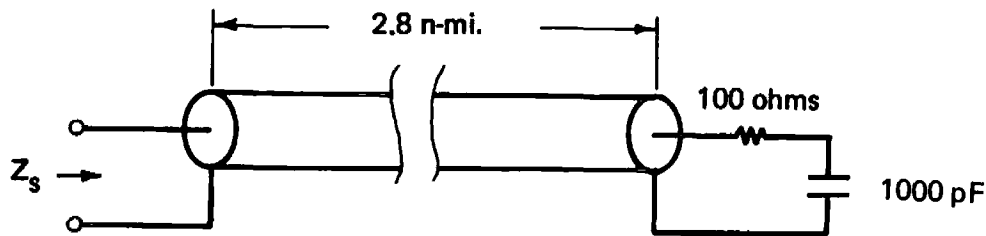
Example 1-1.1

Figure 1-1.2 SD coaxial cable circuit for Ex. 1-1.1.

Type SD underwater telephone coax is to be used at 0.72 MHz. The cable section is 2.8 nautical miles (n-mi.) long and is loaded by a series RC network of 100 ohms and 1000 pF as shown in Fig. 1-1.2. Find the cable input impedance, Z_s , at this frequency.

At 0.72 MHz the electrical parameters of SD coax are:

$$\alpha_{dB} = 2.070 \text{ dB/n-mi.}$$

$$\beta = 42.511 \text{ radians/n-mi.}$$

$$Z_o = 44.625 \text{ ohms at } -0.315 \text{ degree}$$

The RC load impedance is:

$$\text{Re } Z_r = 100 \text{ ohms}$$

$$\text{Im } Z_r = -j/(2\pi fC) = -j221 \text{ ohms}$$

The input impedance of the loaded coax is $66.902 + j11.167$ ohms as obtained from using the program and shown in the printout below:

PROGRAM INPUT	PROGRAM OUTPUT
2.070 ENT↑ α_{dB} , dB/n-mi.	GSBd calculate Z_s
42.511 ENT↑ β , rad/n-mi.	67.827 *** $ Z_s $, ohms
.72+06 GSBa frequency, Hz	9.476 *** $\angle Z_s$, degrees
44.265 ENT↑ $ Z_o $, ohms	XZY
-.315 GSBb $\angle Z_o$, degrees	→R convert to rect
100.000 ENT↑ Re Z_r , ohms	66.902 *** Re Z_s , ohms
-221.000 GSBc Im Z_r , "	11.167 *** Im Z_s , "
2.800 GSBd length, n-mi.	GSBa calculate C_m
	720000.000 *** frequency, Hz
	106417.008 *** C_m , n-mi./sec

Example 1-1.2

Using the type SD underwater telephone coax of Example 1-1.1, find the load impedance at 0.72 MHz that will result in an input impedance of $60 + j0$ ohms. The length of the coax is 2.8 n-mi. as in the previous example.

When using a lossy cable, a negative real part in Z_r will be required to obtain values of Z_s greatly different than Z_0 . Furthermore, if αl is greater than 30 dB, the input impedance will be nearly Z_0 , independent of the load impedance.

In this example, a negative line length is loaded to use the quasi-symmetric properties of Eqs. (1-1.1) and (1-1.2) for calculating Z_r given Z_s .

The HP-97 printout reproduced next shows a load impedance of $67.396 - j73.338$ ohms is required. The equivalent load network is also shown.

PROGRAM INPUT		PROGRAM OUTPUT	
2.070 ENT†	α dB, dB/n-mi.	GSBA calculate load Z_r	
42.511 ENT†	β , rad/n-mi.	99.603 *** $ Z_r $, ohms	
.72+06 GSBA	frequency, Hz	-47.418 *** $\angle Z_r$, degrees	
44.265 ENT†	$ Z_0 $, ohms	XZY	convert to rect
-.315 GSBB	$\angle Z_0$, degrees	→R	
60.000 ENT†	Re Z_s , ohms	67.396 *** Re Z_r , ohms	
0.000 GSBC	Im Z_s , "	-73.338 *** Im Z_r , "	
-2.800 GSBE		2.000 PI	
		X	calculate
		.72+06 X	equivalent
		X	capacitor
		1/X	
		3.014-09 *** C, farad	

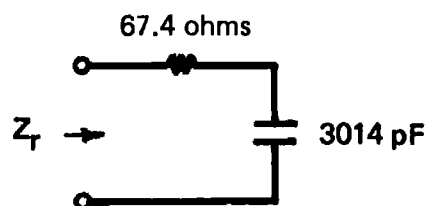


Figure 1-1.3 Equivalent load network.

Example 1-1.3, TI-59 Program Example

This example is the same as Example 1-1.2 where the problem is to determine load impedance, Z_r , that results in an input impedance, Z_s , of $60 + j0$ ohms. The line length is 2.8 n-mi. Because Z_r is to be calculated given Z_s , a negative line length is used. The PC-100A printer output is shown below.

PROGRAM INPUT


2.07	α_{dB} , dB/n-mi.
42.511	β , rad/n-mi.
7.2 05	frequency, Hz
106417.0079	C_m (output), n-mi./sec
44.265	$ Z_o $, ohms
-0.315	$\angle Z_o$, degrees
60.	Re Z_s , ohms
0.	Im Z_s , "
-2.8	line length, n-mi.

PROGRAM OUTPUT





.1509385583	$ \rho $, dimensionless
1.019762234	$\angle \rho$, degrees
99.60303649	$ Z_r $, ohms
-47.41754913	$\angle Z_r$, degrees

Note: the PC-100A printer will not print the mnemonic representing the input key. The HP-97 does this automatically when in the "norm" mode.


PROGRAM FLOW DIAGRAM

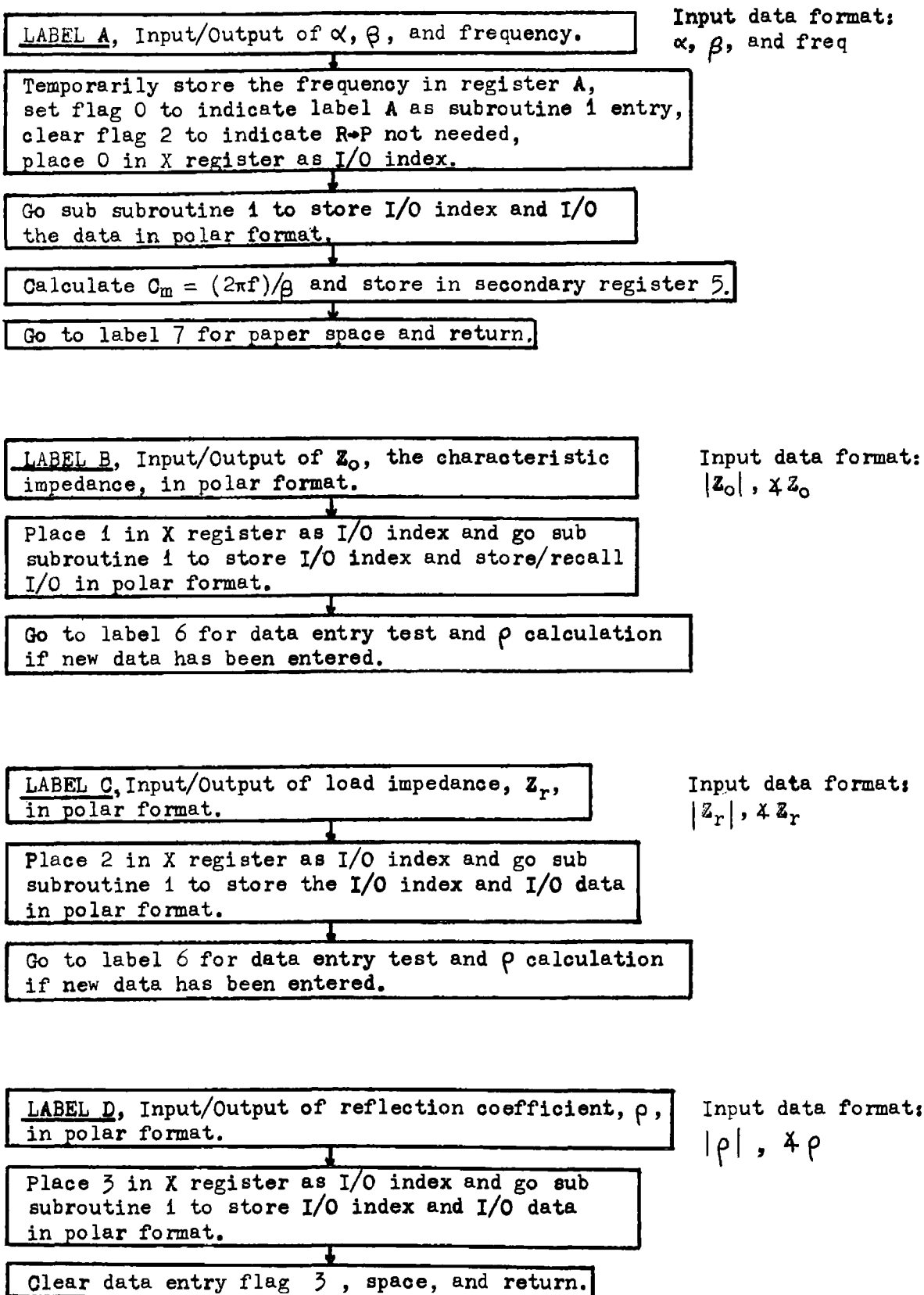



PROGRAM FLOW DIAGRAM

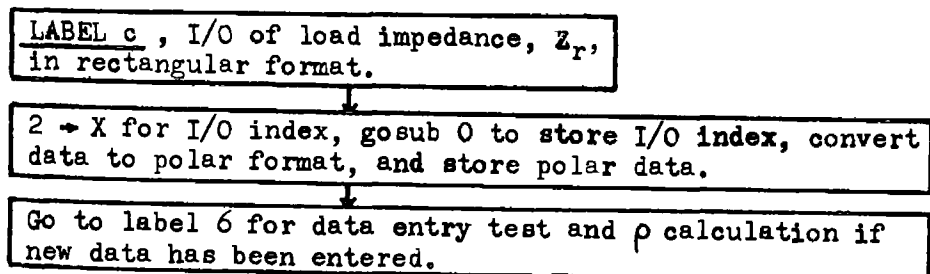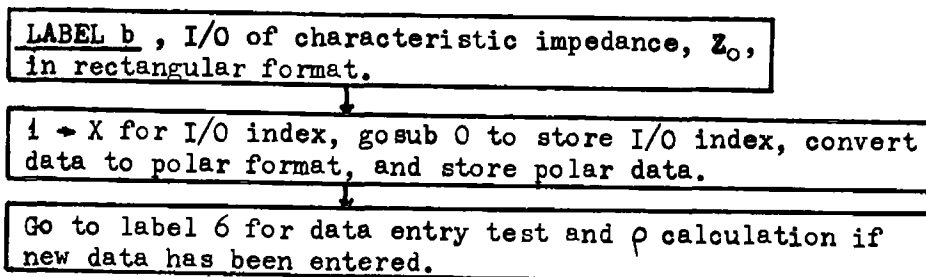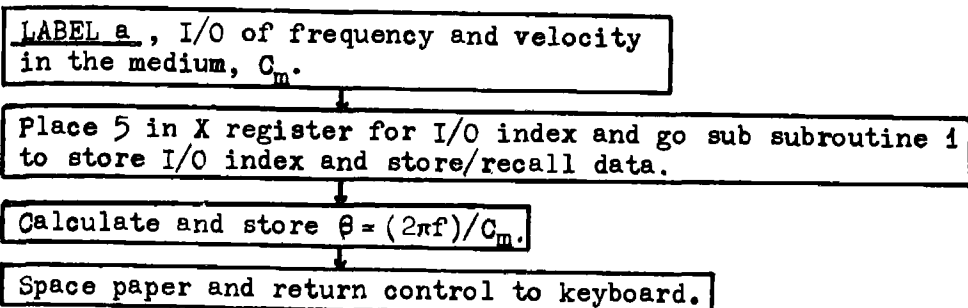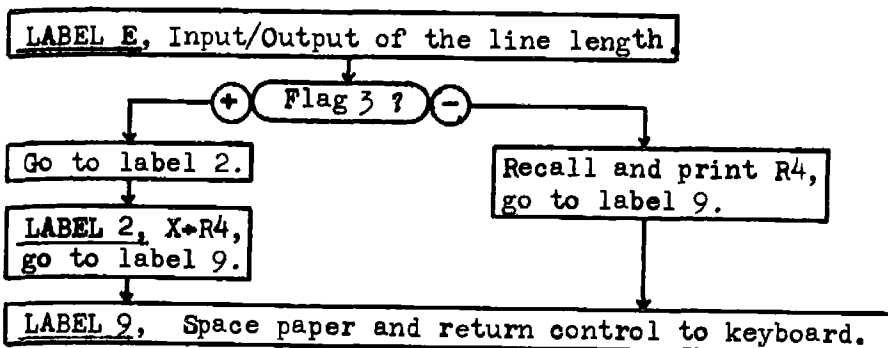

PROGRAM FLOW DIAGRAM

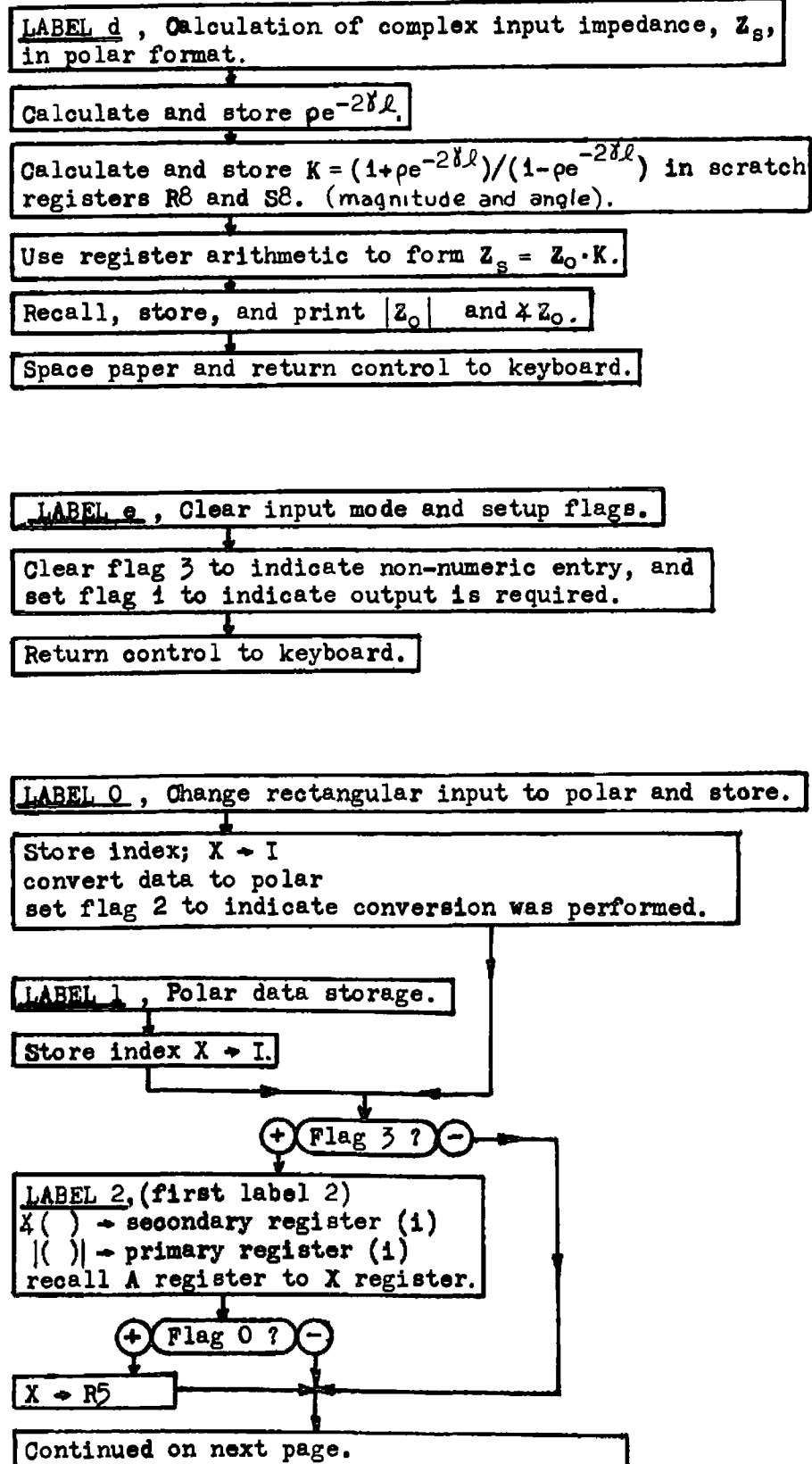

PROGRAM FLOW DIAGRAM

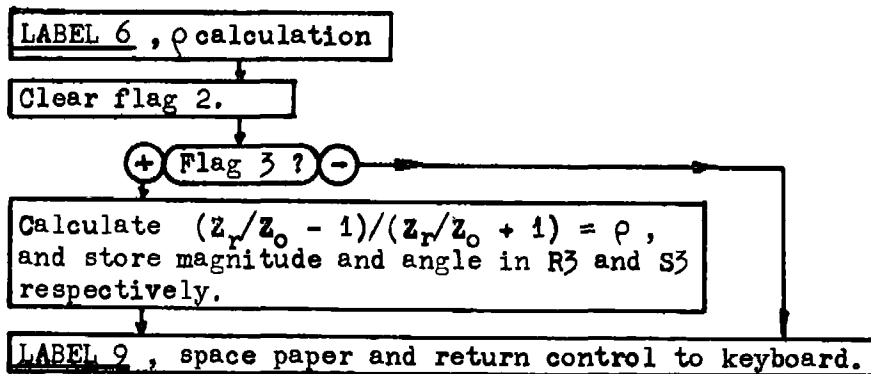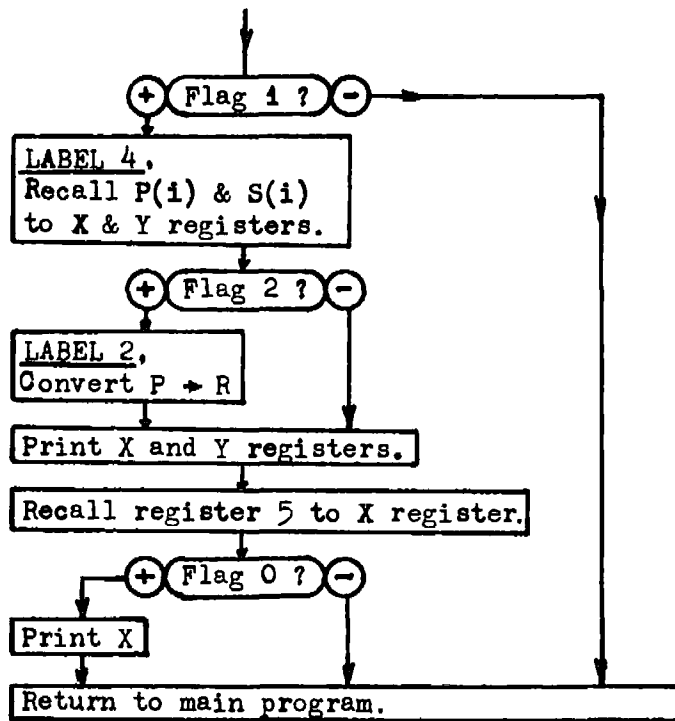

Program Listing I

001 *LBLA I/O OF α_{dB} , β , AND FREQ	057 GSB0 IN CARTESIAN CO-ORDINATES
002 ST0A	058 GT06
003 R↓	059 *LBLc I/O OF $\text{Re } Z_r$, $\text{Im } Z_r$, THE
004 SF0	060 2 LOAD IMPEDANCE IN
005 CF2	061 GSB0 CARTESIAN CO-ORDINATES
006 0	062 GT06
007 GSB1	063 *LBLd CALCULATION OF $ Z_s $, $\angle Z_s$,
008 CF0	064 RCL3 THE COMPLEX INPUT
009 CF3	065 RCL0 IMPEDANCE
010 P↑	066 RCL4
011 P↑	067 ×
012 +	068 EEX
013 RCL5	069 1
014 ×	070 ÷
015 P↔S	071 CHS
016 RCL0	072 10* $e^{-2\alpha l}$
017 ÷	073 ×
018 ST05	074 ST0A $ \rho \cdot e^{-2\alpha l} = \rho e^{-2\delta l} $
019 GT07	075 P↔S
020 *LBLB I/O OF $ Z_0 $, $\angle Z_0$, THE	076 RCL3 $\angle \rho$
021 EEX CHARACTERISTIC IMPEDANCE	077 RCL0 β , radians/length
022 GSB1 IN POLAR CO-ORDINATES	078 R→D β , degrees/length
023 GT06	079 P↔S
024 *LBLC I/O OF $ Z_r $, $\angle Z_r$, THE	080 RCL4 l
025 2 LOAD IMPEDANCE IN	081 ×
026 GSB1 POLAR CO-ORDINATES	082 ENT↑
027 GT06	083 + $2\beta l$
028 *LBLD I/O OF $ \rho $, $\angle \rho$, THE	084 - $\angle \rho - 2\beta l = \angle(\rho e^{-2\delta l})$
029 3 COMPLEX REFLECTION COEF	085 RCLA
030 GSB1 IN POLAR CO-ORDINATES	086 +R
031 CF3	087 ST0A $\text{Re}(\rho e^{-2\delta l})$
032 GT09	088 EEX
033 *LBLF I/O OF THE LINE LENGTH	089 + $1 + \text{Re}(\rho e^{-2\delta l})$
034 F↔?	090 X↔Y
035 GT02	091 ST0B $\text{Im}(\rho e^{-2\delta l})$
036 RCL4	092 X↔Y
037 GT08	093 +P
038 *LBL2	094 ST07 $ 1 + \rho e^{-2\delta l} $
039 ST04	095 X↔Y
040 GT09	096 ST09 $\angle(1 + \rho e^{-2\delta l})$
041 *LBLg I/O OF FREQUENCY AND	097 RCLB
042 5 VELOCITY IN THE MEDIUM, C_m	098 CHS $\text{Im}(1 - \rho e^{-2\delta l})$
043 GSB1	099 EEX
044 CF3	100 RCLA
045 RCL5	101 - $\text{Re}(1 - \rho e^{-2\delta l})$
046 ENT↑	102 +P
047 +	103 ST=7
048 P↑	104 X↔Y
049 ×	105 ST=9
050 P↔S	106 RCL1 $ Z_0 $
051 RCL5	107 ST×7
052 ÷	108 P↔S
053 ST00	109 RCL1 $\angle Z_0$
054 GT07	110 P↔S
055 *LBLh I/O OF $\text{Re } Z_0$, $\text{Im } Z_0$, THE	111 ST+9
056 EEX CHARACTERISTIC IMPEDANCE	112 RCL9 $\angle Z_s$

REGISTERS

0 α , dB/ℓ	1 $ Z_0 $	2 $ Z_r $	3 $ \rho $	4 l	5 freq	6 $\angle \rho$, scratch	7 $\pi Z $	8 $ Z $	9 $\sum \angle Z$
S0 $\beta \frac{\text{rad}}{Z}$	S1 $\angle Z_0$	S2 $\angle Z_r$	S3 $\angle \rho$	S4 .	S5 C_m	S6	S7	S8 $\angle Z$	S9
A scratchpad	B scratchpad	C scratchpad	D	E	I index				

Program Listing II

113 RCL7 $ Z_s $	168 RCL5 recall frequency
114 $\rightarrow R$ } eliminates neg magnitude	169 F0? print required ?
115 $\rightarrow P$ } $ Z_s $	170 PRTX print frequency
116 ST08	171 RTN
117 PRTX	172 *LBL2 convert polar data to
118 X \leftrightarrow Y rectangular format and	173 $\rightarrow R$ print results
119 P \leftrightarrow S	174 PRTX
120 ST08 $\times Z_s$	175 R \downarrow
121 P \leftrightarrow S	176 *LBL8 print and space subroutine
122 GSB8	177 PRTX
123 GT09	178 GT09 goto space subroutine
124 *LBL6 CLEAR INPUT MODE	179 *LBL6 ρ calculation
125 CF3 initialize and set flags	180 CF2
126 SF1	181 F3? ρ calculation needed ?
127 RTN	182 F3?
128 *LBL8 change rectangular input	183 GT09 goto space and return subr
129 ST01 to polar format	184 P \leftrightarrow S
130 R \downarrow	185 RCL2 $\times Z_r$
131 X \leftrightarrow Y	186 RCL1 $\times Z_o$
132 $\rightarrow P$	187 - $\times (Z_r - Z_o)$
133 X \leftrightarrow Y	188 P \leftrightarrow S
134 SF2	189 RCL2 $ Z_r $
135 GT02	190 RCL1 $ Z_o $
136 *LBL1 data I/O in polar mode	191 X=0? exit if $ Z_o $ is zero
137 ST01	192 GT09
138 R \downarrow	193 \div $ Z_r/Z_o $
139 *LBL2	194 $\rightarrow R$
140 F3? test for input	195 ST0A $\text{Re}(Z_r/Z_o)$
141 GSB2 goto input routine	196 EEX
142 F1? test for output	197 - $\text{Re}(Z_r/Z_o - 1)$
143 GSB4 goto output routine	198 X \leftrightarrow Y
144 SF1	199 ST0B $\text{Im}(Z_r/Z_o - 1)$
145 RTN	200 X \leftrightarrow Y
146 *LBL2 input data storage routine	201 $\rightarrow P$
147 SF3 (data stored in polar form)	202 ST03 $ Z_r/Z_o - 1 $
148 P \leftrightarrow S	203 X \leftrightarrow Y
149 ST01	204 ST06 $\times (Z_r/Z_o - 1)$
150 P \leftrightarrow S	205 RCLB $\text{Im}(Z_r/Z_o)$
151 R \downarrow	206 RCLA $\text{Re}(Z_r/Z_o)$
152 ST01	207 EEX
153 RCLA	208 + $\text{Re}(Z_r/Z_o + 1)$
154 F0?	209 $\rightarrow P$
155 ST05	210 ST \div 3 $ \rho $
156 CF1	211 X \leftrightarrow Y
157 RTN	212 ST-6 $\times \rho$
158 *LBL4 data output routine	213 RCL6
159 P \leftrightarrow S	214 P \leftrightarrow S
160 RCL1	215 ST03
161 P \leftrightarrow S	216 *LBL7 P \leftrightarrow S & space subroutine
162 RCL1	217 P \leftrightarrow S
163 F2? P \leftrightarrow R required ?	218 *LBL9 space and return subr
164 GT02	219 SPC
165 PRTX	220 RTN
166 R \downarrow	
167 PRTX	

LABELS					FLAGS	SET STATUS		
^A I/O: α, β, θ, f	^B I/O: $1, 1, \times Z_o$	^C I/O: $1, 1, \times Z_r$	^D I/O: $1, 1, \times \rho$	^E I/O: length	⁰ label A ?	FLAGS	TRIG	DISP
^a I/O: $f, 0, m$	^b I/O: $\text{ReIm} Z_o$	^c I/O: $\text{ReIm} Z_r$	^d calc. Z_s	^e clear input mode	¹ input or output	0 ON OFF	DEG	FIX
⁰ P \rightarrow R	¹ I/O index	² local lbl	³	⁴ print in polar	² cartesian data fmt	1	GRAD	SCI
⁵	⁶ calc ρ	⁷ p \leftrightarrow s, spc, rt	⁸ prt, spc, r	⁹ spc, rtn	³ data entry	2	RAD	ENG
						3		n <u>2</u>

000	76	LBL	LOAD α_{dB}	050	10	10	
001	11	A		051	71	SBR	go to print or R/S routine
002	42	STD	store and print	052	68	NOP	
003	00	00	α_{dB}	053	98	ADV	
004	99	PRT		054	92	RTN	
005	91	R/S	LOAD β	055	76	LBL	LOAD $ Z_o $
006	42	STD	store and print	056	12	B	
007	10	10	β	057	42	STD	store and print
008	99	PRT		058	01	01	$ Z_o $
009	91	R/S	LOAD FREQUENCY	059	99	PRT	
010	42	STD	store and print	060	91	R/S	LOAD $\angle Z_o$
011	05	05	frequency	061	42	STD	store and print
012	99	PRT		062	11	11	$\angle Z_o$
013	65	X	calculate and	063	99	PRT	
014	02	2	store $2\pi f$	064	98	ADV	
015	65	X		065	61	GTO	goto ρ calculation subroutine
016	89	π		066	70	RAD	
017	95	=		067	76	LBL	LOAD Re Z_o
018	42	STD		068	17	B	
019	26	26		069	99	PRT	print and store
020	55	÷	calculate and	070	32	XIT	Re Z_o
021	43	RCL	store C_m	071	91	R/S	LOAD Im Z_o
022	10	10		072	22	INV	convert to polar
023	95	=	$C_m = \frac{2\pi f}{\beta}$	073	37	P/R	
024	42	STD		074	42	STD	store $\angle Z_o$
025	15	15		075	11	11	
026	02	2	set flag 7 if	076	32	XIT	recall and store
027	00	0	calculator	077	42	STD	$ Z_o $
028	69	OP	attached to	078	01	01	
029	07	07	printer	079	98	ADV	go to ρ calculation subroutine
030	69	OP		080	61	GTO	
031	19	19		081	70	RAD	
032	25	CLR		082	76	LBL	LOAD $ Z_r $
033	43	RCL	recall C_m and go	083	13	C	
034	15	15	to R/S or print	084	42	STD	store and print
035	71	SBR	routine	085	02	02	$ Z_r $
036	68	NOP		086	99	PRT	
037	98	ADV		087	91	R/S	LOAD $\angle Z_r$
038	92	RTN		088	42	STD	store and print
039	76	LBL	LOAD C_m	089	12	12	$\angle Z_r$
040	16	A		090	99	PRT	
041	42	STD	store and print	091	98	ADV	
042	15	15	C_m	092	61	GTO	goto ρ calculation subroutine
043	99	PRT		093	70	RAD	
044	35	1/X	calculate and	094	76	LBL	LOAD Re Z_r
045	65	X	store β	095	18	C	
046	43	RCL	$\beta = \frac{2\pi f}{C_m}$	096	99	PRT	store and print
047	26	26		097	32	XIT	Re Z_r
048	95	=		098	91	R/S	LOAD Im Z_r
049	42	STD		099	99	PRT	print Im Z_r

NOTE: The register assignments are the same as the HP-97 program.
Read S0 as R10, and RA as R20, etc. R26 - R28 are scratchpads

1-1

TI-59 PROGRAM LISTING

100	98	ADV		150	37	P/R	
101	22	INV	convert to polar	151	22	INV	use register
102	37	P/R		152	44	SUM	arithmetic to form:
103	42	STD	store ΔZ_r	153	13	13	$\Delta \rho$
104	12	12		154	32	XIT	use register
105	32	XIT	store $ Z_r $	155	22	INV	arithmetic to form:
106	42	STD		156	49	PRD	$ \rho $
107	02	02		157	03	03	
108	76	LBL	ρ calculation	158	92	RTN	rtn to main pgm
109	70	RAD		159	76	LBL	ρ OUTPUT ROUTINE
110	43	RCL	calculate & store:	160	14	II	
111	12	12		161	43	RCL	recall $ \rho $
112	75	-	$\Delta(Z_r - Z_0)$	162	03	03	
113	43	RCL		163	71	SBR	goto print or R/S
114	11	11		164	68	NDP	
115	95	-		165	43	RCL	recall $\Delta \rho$
116	32	XIT		166	13	13	
117	43	RCL	calculate & store:	167	71	SBR	goto print or R/S
118	02	02		168	68	NDP	
119	55	÷	$ Z_r / Z_0 $	169	98	ADV	space and return
120	43	RCL		170	92	RTN	
121	01	01		171	76	LBL	CALCULATE Z_s
122	95	=		172	19	D'	
123	32	XIT		173	43	RCL	form αl in dB
124	37	P/R	convert to rect.	174	00	00	
125	42	STD	store $\text{Im}(Z_r/Z_0)$	175	65	x	
126	27	27		176	43	RCL	
127	32	XIT		177	04	04	
128	42	STD	store $\text{Re}(Z_r/Z_0)$	178	55	+	convert to nepers
129	28	28		179	53	(
130	75	-	calculate & store:	180	01	1	
131	01	1		181	22	INV	
132	95	=	$Z_r/Z_0 - 1$	182	23	LNK	
133	32	XIT		183	28	LOG	
134	22	INV	convert to polar	184	65	x	
135	37	P/R		185	01	1	
136	42	STD	store $\Delta(Z_r/Z_0 - 1)$	186	00	0	
137	13	13		187	54)	
138	43	RCL	recall & store:	188	95	=	
139	27	27	$\text{Im}(Z_r/Z_0 + 1)$	189	94	+/-	calculate:
140	32	XIT		190	22	INV	$e^{-2\alpha l}$
141	42	STD	store $ Z_r/Z_0 - 1 $	191	23	LNK	
142	03	03		192	65	x	calculate & store:
143	43	RCL		193	43	RCL	$ \rho e^{-2\alpha l} $
144	28	28	form $Z_r/Z_0 + 1$	194	03	03	
145	85	+		195	95	=	
146	01	1		196	32	XIT	
147	95	=		197	43	RCL	recall $\Delta \rho$
148	32	XIT		198	13	13	
149	22	INV	convert to polar	199	75	-	

200	53	(
201	43	RCL	form βl in radians
202	10	10	
203	65	x	
204	43	RCL	
205	04	04	
206	65	x	
207	03	3	form $2\beta l$ in degrees
208	06	6	
209	00	0	
210	55	÷	
211	89	↵	
212	54)	
213	95	=	form $4\phi = 2\beta l$
214	37	P/R	convert to rect
215	42	STD	store $\text{Im}(\rho e^{-2\beta l})$
216	21	21	
217	32	X↵T	
218	42	STD	store $\text{Re}(\rho e^{-2\beta l})$
219	20	20	
220	85	+	form:
221	01	1	$1 + \rho e^{-2\beta l}$
222	95	=	
223	32	X↵T	
224	22	INV	convert to polar
225	37	P/R	
226	42	STD	store $4(1 + \rho e^{-2\beta l})$
227	09	09	
228	32	X↵T	
229	42	STD	store $ 1 + \rho e^{-2\beta l} $
230	07	07	
231	01	1	form and store:
232	75	-	
233	43	RCL	$\text{Re}(1 - \rho e^{-2\beta l})$
234	20	20	
235	95	=	
236	32	X↵T	
237	43	RCL	form:
238	21	21	$\text{Im}(1 - \rho e^{-2\beta l})$
239	94	+/-	
240	22	INV	convert to polar
241	37	P/R	
242	22	INV	
243	44	SUM	divide to memory
244	09	09	
245	32	X↵T	
246	22	INV	subtract from
247	49	PRD	memory
248	07	07	
249	43	RCL	recall $ Z_0 $
250	01	01	use register arith
251	49	PRD	to form $ Z_r $
252	07	07	
253	43	RCL	use register arith
254	11	11	to form $4Z_r$
255	44	SUM	
256	09	09	
257	43	RCL	recall $ Z_r $
258	07	07	
259	32	X↵T	
260	43	RCL	recall $4Z_r$
261	09	09	
262	37	P/R	eliminate negative
263	22	INV	magnitude
264	37	P/R	
265	42	STD	store $4Z$
266	18	18	
267	32	X↵T	store $ Z $
268	42	STD	
269	08	08	
270	71	SBR	goto print or R/S
271	68	NDF	
272	43	RCL	recall $4Z$
273	18	18	
274	71	SBR	goto print or R/S
275	68	NDF	
276	98	ADV	space & return
277	92	RTN	
278	76	LBL	print or R/S
279	68	NDF	subroutine
280	87	IFF	jump if flag 7 set
281	07	07	
282	38	SIN	
283	91	R/S	stop & await start
284	92	RTN	return to main pgm
285	76	LBL	
286	38	SIN	
287	99	PRT	print
288	92	RTN	rtm to main program
289	76	LBL	LOAD LINE LENGTH
290	15	E	
291	42	STD	store line length
292	04	04	
293	99	PRT	print line length
294	98	ADV	
295	92	RTN	rtm to keyboard

PROGRAM 1-2 VOLTAGE ALONG A LOSSY LOADED TRANSMISSION LINE.

Program Description and Equations Used

This program calculates the voltage $V(x)$ in dBV, at any distance, x , along a doubly loaded transmission line (a line with terminating Y's or Z's at both ends). Both the source and load impedances are allowed to be complex quantities. This program is parasitic to Program 1-1, and that program must be run first to properly load the registers for this program. The same line length and units must be used with both programs.

Given a section of transmission line of length ℓ (Fig. 1-2.1) which may be a coax as shown, or open wire line, stripline, microstrip, or other, the input impedance, Z_s , can be expressed in terms of the load impedance, Z_r , and the cable parameters as given by Eqs. (1-1.1) and (1-1.2). With the input impedance, Z_s known, and given the transmitter source impedance, Z_t , the voltage at the input of the transmission line, V_s , is given by:

$$V_s = V_t \left[\frac{Z_s}{Z_s + Z_t} \right] \quad (1-2.1)$$

where Z_s is given by Eq. (1-1.1).

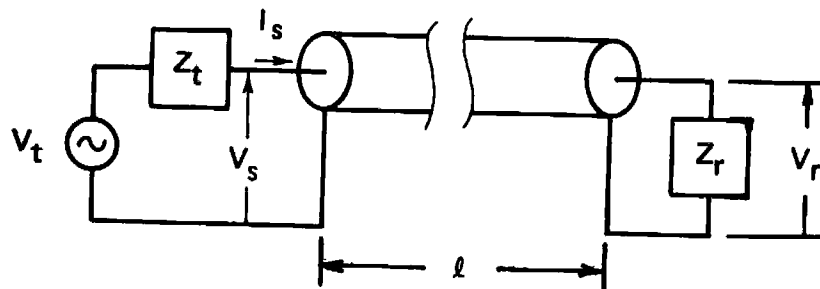


Figure 1-2.1 Transmission line circuit topology.

The voltage and current distribution of the transmission line can be written in terms of the voltage and current at any point along the transmission line as the reference. Most commonly, the voltage at the receiving end is taken as the reference, but for this problem, the voltage and current at the transmitting end are more convenient references. The voltage at any distance, x , from the transmitting end is given by Eq. (1-2.2), where the reflection coefficient at the transmitter is designated ρ_t and is defined by Eq. (1-2.3). The derivation of Eq. (1-2.2) is given later.

$$V(x) = \frac{V_s}{1 + \rho_t} \cdot \left[e^{-\gamma x} + \rho_t e^{\gamma x} \right] \quad (1-2.2)$$

$$\rho_t = \frac{Z_s/Z_o - 1}{Z_s/Z_o + 1} \quad (1-2.3)$$

In Eq. (1-2.2), γ is as defined in Eq. (1-1.3). With these equations in mind, the program operation is now described (Program 1-1 has already calculated and stored Z_s using Eq. (1-1.1)).

The routines under labels "A," "a," and "B" provide for data entry and storage. All impedances are stored in polar form; hence, impedances entered in cartesian form (real and imaginary) under label "a" are converted to polar form and stored using the routine under label "A," which is the polar impedance entry and storage routine. The routine under label "B" causes the source voltage strength in volts to be stored.

Label "E" is the start of the data output routine. On the first execution of label "E" after program loading and data entry, ρ_t is calculated and stored. Flag 2 is tested on each execution of label "E" to determine if the reflection coefficient calculation is needed (ρ_t). Since flag 2 is test cleared, and is only set by card loading, the ρ_t calculation is skipped after the first execution of label "E."

Following the ρ_t calculation decision, is a routine to evaluate Eq. (1-2.2) without the V_s term (lines 050 and 096 in the program listing). V_s is calculated using Eq. (1-2.1) in lines 097 through 118 and combined with the results of Eq. (1-2.2) in lines 119 to 125. The output is provided as magnitude (in dBV) of $V(x)$ and its angle.

Label 9 is a space and return subroutine used by labels "a," "A," "B," and "E."

[illegible]

Example 1-2.1

Given the coax cable with source and load impedances as shown in Fig. 1-2.2, find the voltages on the cable at the transmitting end, the receiving end, and 1 n-mi. from the transmitting end.

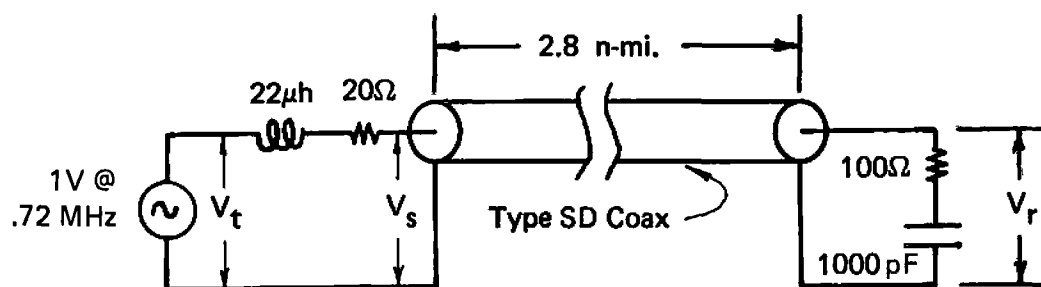


Figure 1-2.2 Doubly loaded coaxial cable for Ex. 1-2.1.

At 0.72 MHz, the characteristics of the SD coax cable are:

$$\begin{aligned}\alpha_{\text{dB}} &= 2.070 \text{ dB/n-mi.} \\ \beta &= 42.511 \text{ radians/n-mi.} \\ Z_0 &= 44.265 \Omega @ -0.315 \text{ degree}\end{aligned}$$

At the same frequency, the complex source and load impedances are:

$$\begin{aligned}\text{Re } Z_t &= 20 \text{ ohms} \\ \text{Im } Z_t &= j2\pi fL = j99.53 \text{ ohms} \\ \text{Re } Z_r &= 100 \text{ ohms} \\ \text{Im } Z_r &= -j/(2\pi fC) = -j221 \text{ ohms}\end{aligned}$$

Since this program is parasitic to Program 1-1, that program is run first with the line length required here (2.8 n-mi.). The print-out from that program is included here for clarity.

HP-97 printout for Example 1-2.1

First, Program 1-1 is run to calculate and store Z_s and to load the registers.

```

2.070 ENT↑ load  $\alpha_{dB}$  in dB/n-mi.
42.511 ENT↑ load  $\beta$  in radians/n-mi.
.72+06 GSBA load frequency in hertz

44.265 ENT↑ load  $|Z_o|$  in ohms
-.315 GSBB load  $\angle Z_o$  in degrees

100.000 ENT↑ load Re  $Z_r$  in ohms
-221.000 GSBB load Im  $Z_r$  in ohms

2.800 GSBE load line length in nautical miles

        GSBD calculate  $Z_s$  (will be automatically stored)
67.827 ***  $|Z_s|$ , ohms
9.476 ***  $\angle Z_s$ , degrees

```

Second, load and run this program.

```

20.00 ENT↑ load Re  $Z_t$ 
39.57 GSBB load Im  $Z_t$ 

1.00 GSBE load source voltage in volts

0.00 GSBE load line length to transmitting end and start
-6.34 ***  $20 \log |V_s|$ , dBV
-42.39 ***  $\angle V_s$ , degrees

2.00 GSBE load line length to receiving end and start
-8.54 ***  $20 \log |V_r|$ , dBV
-34.98 ***  $\angle V_r$ , degrees

1.00 GSBE load line length to 1 n-mi. from xmit end and start
-12.95 ***  $20 \log |V(x)|$ , dBV
22.15 ***  $\angle V(x)$ , degrees

```

Derivation of Equations Used

A transmission line provides a conduit for the propagation of electrical power. If the transmission line is not terminated in the characteristic impedance of the line, Z_0 , then not all of the power that propagates down the line is absorbed in the termination, and thus some is reflected into the line and propagates back to the source. The "reflection coefficient," ρ , is a measure of the amount of power that is reflected. A reflection coefficient of zero ($\rho = 0$) implies no power is reflected, and all of it is absorbed by the load. When $\rho = \pm 1$, all the power is reflected. The reflection coefficient in terms of the characteristic impedance (Z_0) and the load impedance (Z_r) is given by Eq. (1-1.2).

If the transmission line is doubly terminated, then there will be a reflection coefficient for both ends, and Eq. (1-1.2) is used with Z_r replaced by Z_s , the cable input impedance at the transmitter end. This is the transmitter reflection coefficient and is designated ρ_t . The receiver reflection coefficient is left unsubscripted.

The power propagates along the transmission line as a voltage wave and a current wave. Considering both the voltage wave from the transmitter directly, and the reflected wave from the receiver, there exist points along the cable where these waves are in phase, and constructively add together; while there are other points where the waves are 180° out of phase and produce a voltage null.

Reference [43] (chapters 8 and 9) contains the solution to the wave equation for voltage and current waves traveling along a transmission line. The voltage and current along the transmission line can conveniently be expressed in terms of hyperbolic functions and a reference voltage and current taken at any point on the line. If x represents the distance from the transmitter (or source) to the point under observation, then the voltage and current ($V(x)$ and $I(x)$) at this point are:

$$\begin{bmatrix} V(x) \\ I(x) \end{bmatrix} = \begin{bmatrix} \{\cosh(\gamma x)\} & \{-Z_0 \sinh(\gamma x)\} \\ \{-\frac{1}{Z_0} \sinh(\gamma x)\} & \{\cosh(\gamma x)\} \end{bmatrix} \cdot \begin{bmatrix} V_s \\ I_s \end{bmatrix} \quad (1-2.4)$$

where the hyperbolic functions are defined by:

$$\text{Sinh } (\gamma x) = \frac{e^{\gamma x} - e^{-\gamma x}}{2} \quad (1-2.5)$$

$$\text{Cosh } (\gamma x) = \frac{e^{\gamma x} + e^{-\gamma x}}{2} \quad (1-2.6)$$

Remembering that $I_s = V_s / Z_s$, and using the transmitter reflection coefficient defined by:

$$\rho_t = \frac{Z_s / Z_o - 1}{Z_s / Z_o + 1} \quad (1-2.3)$$

Equation (1-2.4) may be solved for $V(x)$ yielding:

$$V(x) = \frac{V_s}{1 + \rho_t} \cdot \left[e^{-\gamma x} + \rho_t e^{\gamma x} \right] \quad (1-2.2)$$

REGISTERS									
0	1	2	3	4	5	6	7	8	9
α_{dB}	$ Z_0 $	$ Z_r $	$ \rho_t $	l	freq	$\angle \rho_t$	scratch	$ Z_s $	scratch
S0 β	S1 $\angle Z_0$	S2 $\angle Z_r$	S3 $\angle \rho$	S4	S5 Ω_m	S6 $ Z_t $	S7 $\angle Z_t$	S8 $\angle Z_s$	S9 V_t
A scratchpad	B scratchpad	C scratchpad	D $20 \log e$	E 2π	I index				

```

111  →R
112  RCLA
113  +      Re(Zs + Zt)
114  XZY
115  RCLB
116  +      Im(Zs + Zt)
117  XZY
118  →P
119  ST=7   |Zs + Zt|
120  XZY
121  ST=9   √(Zs + Zt)
122  PZS
123  RCL9   Vt
124  PZS
125  STX7   complete |V(x)| calculation
126  RCL7
127  LOG
128  2
129  0
130  x
131  PRTX   20 log V(x)
132  RCL9
133  PRTX   √ V(x)
134  *LBL9  space and return subroutine
135  SPC
136  RTN

```

NOTE FLAG SET STATUS

LABELS					FLAGS	SET STATUS		
A	B	C	D	E		FLAGS	TRIG	DISP
Z _t √ Z _t	source voltage			calc V(x)	0	ON OFF	DEG ■	FIX ■
Re Z _t Im Z _t					1		GRAD ■	SCI ■
0	∅ calc jump	2	3	∅ calc ?	2	■	RAD ■	ENG ■
5		7	8	spc & rtn	3	3		n 2

PROGRAM 1-3 SECOND ORDER ACTIVE NETWORK TRANSMISSION FUNCTION.

Program Description and Equations Used

This program provides the coefficients of the numerator and denominator polynomials of the transmission function $T(s) = N(s)/D(s)$, of the generalized second order active network shown in Fig. 1-3.1. A second part of the program provides the polynomial roots. If a real (non-ideal) operational amplifier (op-amp) is used, the amplifier will have both finite gain and bandwidth. The compensation pole of the op-amp will introduce a parasitic pole causing $D(s)$ to become third order even though the RC network is set up to provide second order response. This program accepts the gain and 3 dB bandwidth of the amplifier and calculates the resulting third order transmission function.

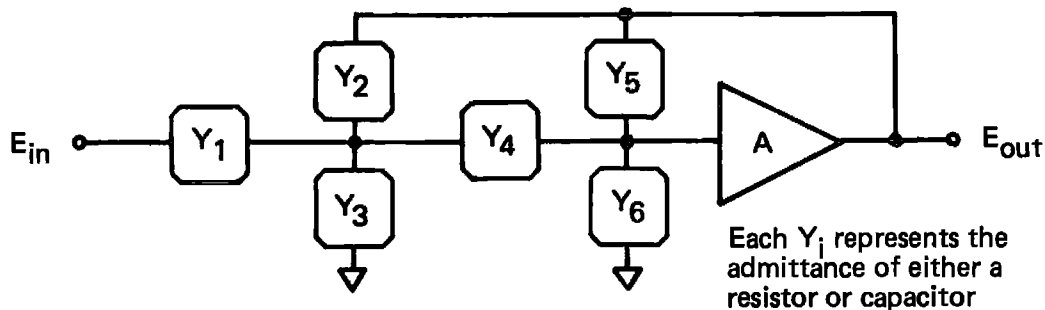


Figure 1-3.1 Generalized second order circuit.

If the natural frequencies of the response governed by the RC network alone are many decades removed from the amplifier unity gain crossover frequency, then the transmission function $T(s)$, will be practically equal to the transmission function of the second order network with an ideal infinite bandwidth amplifier. The component values dictated by many active filter references assume ideal operational amplifier characteristics.

When the natural frequencies are within a decade or two of the amplifier unity gain crossover frequency, then the parasitic pole will cause a noticeable shift in the natural frequencies governed by the RC network alone. The network can be predistorted so the natural frequencies shift to the desired positions (see Program 2-11).

The transmission function is determined by writing the nodal equations for the network, and solving for E_{out} in terms of E_{in} . This derivation is done later and provides:

$$E_{out} = \frac{A_0 Y_1 Y_4}{D(s)} \quad (1-3.1)$$

where

$$D(s) = (Y_1 + Y_2 + Y_3) \left[(Y_4 + Y_6)(1 + \tau s) + Y_5 (1 - A_0 + \tau s) \right] + Y_4 \left[Y_6 + (1 + \tau s) + Y_5 (1 - A_0 + \tau s) - A_0 Y_2 \right]$$

and where a one-pole model of the amplifier is assumed:

$$A = \frac{A_0}{1 + \tau s} \quad (1-3.2)$$

The sign of A_0 may be either positive or negative depending upon the amplifier characteristics (see examples). The first program uses Eq. (1-3.1) to form the numerator and denominator polynomials, and the second program finds the zeros of these polynomials (polynomial roots).

When the element values are loaded, capacitors are signified by a negative mantissa. The subroutine under label 8 tests the sign of the entry; if it is negative, the absolute value is stored; if it is positive, it is a resistor, and the reciprocal is taken to convert to conductance, and then multiplied by 10^{50} before storage.

The magnitude of the stored element value is used to signal whether the element is a resistor or a capacitor. Other programs use the sign of the stored value to differentiate between resistors and capacitors, but that indicator cannot be used in this program because algebraic operations are performed on the element values in the main program before the element type subroutine is entered and the resistor/capacitor test is done, i.e., the term $Y_5 (1 - A_0)$ can have either sign depending upon the magnitude and sign of A_0 , and Y_5 can legitimately represent the admittance of either a resistor or a capacitor.

The magnitude test is done in the summing routine under label 0.

If the absolute value of the coefficient is greater than 10^{30} , it is assumed to be a conductance (s^0 term), the value is divided by 10^{50} to undo the original storage operation, and the summation is done in the stack. If the absolute value of the coefficient is less than 10^{30} , it is assumed to be a capacitance (s^1 term), and the summation is done in the designated i register.

Some terms in the denominator of Eq. (1-3.1) contain the factor τs . These terms generate s^1 and s^2 coefficients. Subroutine 3 is used to perform multiplication by τs and to append the s^1 and s^2 terms to the presently stored s^0 and s^1 terms to form the complete admittance sum set for the denominator segment being evaluated.

After each set of admittance sums (s^0 , s^1 , & s^2) are calculated and stored, polynomial multiplication is done to generate the coefficients of the various powers of s in the denominator polynomial. This multiplication is accomplished by the routine under label 6. If flag 0 is set, the polynomial coefficient registers are cleared before multiplication. This condition exists for the first product-of-sums. Flag 0 is cleared for the second product-of-sums to indicate continued summation into the polynomial coefficient registers.

After the denominator has been calculated, the polynomial coefficients are normalized by dividing by the s^0 polynomial coefficient. The numerator coefficient is likewise normalized, and the polynomial coefficients are provided as output. This normalization process can cause the program to halt displaying "ERROR" for certain classes of degenerate networks, e.g., a differentiator constructed with capacitors in locations 1 and 4, no elements in locations 2, 3, and 6, and feedback resistor in location 5. The series capacitors should be combined into a single capacitor in location 1 or 4 with the feedback resistor in location 2 or 5 and no elements in locations 3 and 6. The unspecified series elements can be 1 ohm resistors.

The second program finds the zeros of the denominator polynomial (poles of the transmission function). The numerator polynomial will be either a constant, a single zero at the origin, or a double zero at the origin depending on whether the filter is lowpass, bandpass, or highpass, respectively. The second program also indicates the degree of the zero, and the gain constant of the second order pair, K , after the third order root has been removed (if any), i.e.:


$$\text{Lowpass:} \quad T(s) = K \frac{1}{\frac{s^2}{\omega_n^2} + \frac{s}{\omega_n Q} + 1} \quad (1-3.3)$$

$$\text{Bandpass:} \quad T(s) = K \frac{\frac{s}{\omega_n Q}}{\frac{s^2}{\omega_n^2} + \frac{s}{\omega_n Q} + 1} \quad (1-3.4)$$

$$\text{Highpass:} \quad T(s) = K \frac{\frac{s^2}{\omega_n^2}}{\frac{s^2}{\omega_n^2} + \frac{s}{\omega_n Q} + 1} \quad (1-3.5)$$

If the denominator polynomial is second order, the quadratic formula is used to find the zeros. If it is third order, a Newton-Raphson iterative technique is used to find the real third order zero (there will be at least one), then the third order polynomial is deflated to second order, and the quadratic formula is used to find the remaining zeros of the polynomial. If the zeros of the denominator polynomial are complex, the program will also calculate the natural frequency, $f_n = \omega_n/2\pi$, and the Q, or quality factor of the complex pair (see the equation derivation part of this description for equations and details).

User Instructions

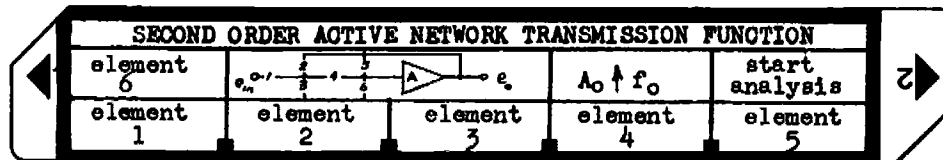

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card			
2	Enter element 1			
	a) if resistor (value $\neq 0$)	R, ohms	<input type="text" value="A"/>	
	b) if capacitor, enter negative value	C, farad	<input type="text" value="chs"/> <input type="text" value="A"/>	
3	Enter element 2			
	a) if resistor	R, ohms	<input type="text" value="B"/>	
	b) if capacitor	C, farad	<input type="text" value="chs"/> <input type="text" value="B"/>	
	c) if no element present	zero	<input type="text" value="B"/>	
4	Enter element 3			
	a) if resistor	R, ohms	<input type="text" value="C"/>	
	b) if capacitor	C, farad	<input type="text" value="chs"/> <input type="text" value="C"/>	
	c) if no element present	zero	<input type="text" value="C"/>	
5	Enter element 4			
	a) if resistor (value $\neq 0$)	R, ohms	<input type="text" value="D"/>	
	b) if capacitor	C, farad	<input type="text" value="chs"/> <input type="text" value="D"/>	
6	Enter element 5			
	a) if resistor	R, ohms	<input type="text" value="E"/>	
	b) if capacitor	C, farad	<input type="text" value="chs"/> <input type="text" value="E"/>	
	c) if no element present	zero	<input type="text" value="E"/>	
7	Enter element 6			
	a) if resistor	R, ohms	<input type="text" value="f"/> <input type="text" value="A"/>	
	b) if capacitor	C, farad	<input type="text" value="chs"/> <input type="text" value="f"/> <input type="text" value="A"/>	
	c) if no element present	zero	<input type="text" value="f"/> <input type="text" value="A"/>	
8	Enter operational amplifier parameters	A_o	<input type="text" value="↑"/>	
		f_o , Hz	<input type="text" value="f"/> <input type="text" value="D"/>	
9	Start analysis		<input type="text" value="f"/> <input type="text" value="E"/>	Den coeffs Num coeffs
10	Go back and change any element then rerun step 9, or load second card to find denominator pole locations, f_n , and Q			

User Instructions


SECOND AND THIRD ORDER ROOT FINDER PROGRAM
USE AFTER TRANSMISSION FUNCTION PROGRAM

START

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card when display flashes, program execution begins unaided			
2	Program output			
2a	If three real roots, $(s+a)(s+b)(s+c)$			-a -b -c
2b	If one real root and a complex conjugate pair, $(s+a)(s+\alpha+j\beta)(s+\alpha-j\beta)$			-a β $-\alpha$ -B $-\alpha$ of second order pair { f_n (Hz) Q midband gain num zero locations
2c	If two real roots: $(s+a)(s+b)$			-a -b
2c	A complex conjugate pair, $(s+\alpha+j\beta)(s+\alpha-j\beta)$			β $-\alpha$ -B $-\alpha$ of second order pair { f_n (Hz) Q midband gain num zero locations

User Instructions

TI-59 TRANSLATION

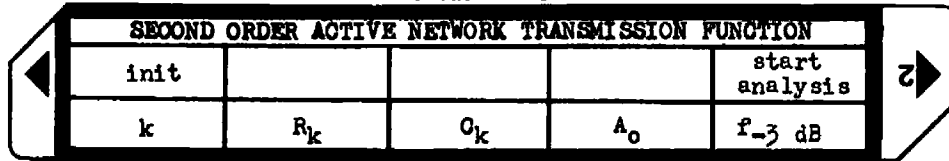

TI-59 TRANSLATION

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card one			
2	Initialize and clear registers		2nd A	0
3	Load elements			
	a) load element number (1 to 6)	k	A	k
	b) load element values:			
	if resistor	R_k , ohms	B	R_k
	if capacitor	C_k , F	C	C_k
	if no element present	0	C	0
	Repeat step 3 until all elements have been entered.			
4	Load amplifier dc gain (load negative gain for inverting op-amp)	A_o	D	A_o
5	Load -3 dB rolloff frequency of amplifier	$f_{-3} \text{ dB, Hz}$	E	$f_{-3} \text{ dB}$
6	Start analysis		2nd E	den coeffs
			R/S*	b_3
			R/S*	b_2
			R/S*	b_1
			R/S*	1
				num coeffs
			R/S*	a_2
			R/S*	a_1
			R/S*	a_o
	* "R/S" not necessary if the TI-59 is attached to the PC-100A printer. All results will be printed automatically after the program is started.			

User Instructions

TI-59 TRANSLATION

SECOND AND THIRD ORDER ROOT FINDER PROGRAM use with 1-3				
				start

TI-59 TRANSLATION

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
7	Load both sides of program card 2			
8	Start second program		E	
	a) If three real roots: (s+a)(s+b)(s+b)		R/S*	-a
			R/S*	-b
			R/S*	-c
	b) If one real root and a complex conjugate pair: (s+a)(s+α+jβ)(s+α-jβ)		R/S*	-a
			R/S*	β
			R/S*	-α
			R/S*	-β
			R/S*	-α
			R/S*	f _n , Hz
			R/S*	Q
			R/S*	midband gain
	c) If two real roots: (s+a)(s+b)		R/S*	-a
			R/S*	-b
	d) If a complex conjugate pair: (s+α+jβ)(s+α-jβ)		R/S*	β
			R/S*	-α
			R/S*	-β
			R/S*	-α
			R/S*	f _n , Hz
			R/S*	Q
			R/S*	midband gain
	* "R/S" not necessary if the TI-59 is attached to the PC-100A printer. All results will be automatically printed after the program is started.			

Example 1-3.1

The schematic in Fig. 1-3.2 represents a second order active band-pass filter using the infinite gain, multiple feedback topology. The filter element values were designed assuming the op-amp to be ideal, i.e., having infinite gain and bandwidth. The type 741 op-amp is not ideal in that it has both finite gain and bandwidth. This example will use the program to show that the element values provide the desired specification when the op-amp has very large gain (-10^9) and infinite bandwidth ($\tau = 0$). The program will then be run with the gain and bandwidth values for the 741 type op-amp to show that both the pole natural frequency and "Q" have shifted away from the desired values. The 741 has a typical gain of -100,000, and open loop break frequency of 5 Hz.

The design specifications for the filter are:

center frequency:	10 kHz
midband gain:	10
quality factor, Q:	10
capacitor value:	1000 pF

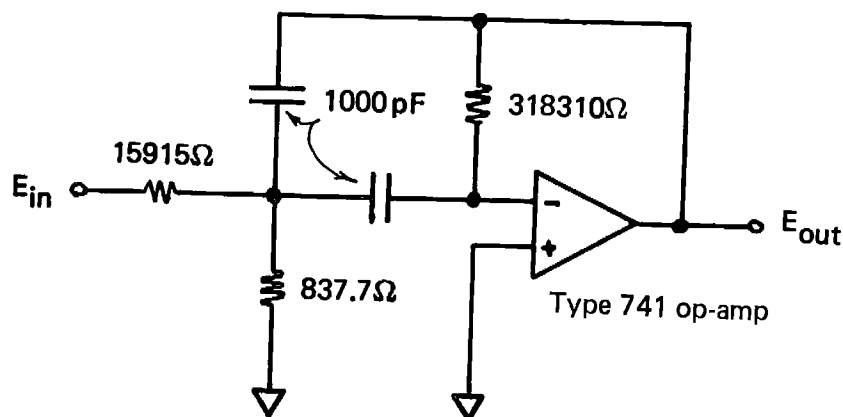


Figure 1-3.2 Second order bandpass active filter, infinite gain-multiple feedback topology.

HP-97 PRINTOUT FOR EXAMPLE 1-3.1

load first program and
enter element values

15915. GSBA element 1, resistor
-1.-09 GSBB element 2, cap
837.7 GSBC element 3, resistor
-1.-09 GSBD element 4, cap
318310. GSBE element 5, resistor
0. GSBA element 6, missing

-1.+09 ST00 enter infinite gain app
0. ST07 set γ to zero ($BW=\infty$)

GSBe start analysis

0.000+00 *** s³ denominator coef
253.3-12 *** s² " "
1.592-06 *** s¹ " "
1.000+00 *** s⁰ " "

0.000+00 *** s² numerator coef
-15.92-06 *** s¹ " "
0.000+00 *** s⁰ " "

load second card and
start analysis

62.75+03 *** imag
-3.142+03 *** real } complex
 conjugate
-62.75+03 *** imag } poles
-3.142+03 *** real }

10.00+03 *** f_n } of second
10.00+00 *** Q } order pole
 pair

-10.00+00 *** midband gain

0.000+00 *** numerator zero
 location

reload first card

-100000. ENT† 741 do gain
5. GSBA 741 break freq

GSBe start analysis

80.63-18 *** s³
355.1-12 *** s²
1.913-06 *** s¹
1.000+00 *** s⁰

0.000+00 *** s²
-15.92-06 *** s¹
0.000+00 *** s⁰

load second card
& start analysis

-4.400+06 *** real pole location

53.04+03 *** imag
-2.376+03 *** real } complex
 conjugate
-53.04+03 *** imag } poles
-2.376+03 *** real }

8.450+03 *** f_n } of second
11.17+00 *** Q } order pole
 pair

-9.441+00 *** midband gain

0.000+00 *** numerator zero
 location

TI-59 PRINTOUT FOR EXAMPLE 1-3.1

load first program and enter element values			
1.	element #		
15 15.	R resistor		
2.	element #		
1. -09	C capacitor		
3.	element #		
887.7	R resistor		
4.	element #		
1. -09	C capacitor		
5.	element #		
3183 10.	R resistor		
-1. 09	A amplifier gain (ideal)		
1. 25	F amplifier BW (ideal)		
1.00 00	s ³ den coef		
253.31-12	s ² " "		
1.59-06	s ¹ " "		
1.00 00	s ⁰ " "		
0.00 00	s ² num coef		
-15.92-06	s ¹ " "		
0.00 00	s ⁰ " "		
load second card			
62.75 03	imag		
-3.14 03	real		
	complex		
	conj.		
-62.75 03	imag		
-3.14 03	real		
	pole pair		
10.00 03	f _n		
10.00 00	Q _n		
-10.00 00	midband gain		
		reload first card	
		-100. 03	A 741 dc gain
		5. 00	F 741 break freq
		80.63-18	s ³ den coef
		355.14-12	s ² " "
		1.91-06	s ¹ " "
		1.00 00	s ⁰ " "
		0.00 00	s ² num coef
		-15.92-06	s ¹ " "
		0.00 00	s ⁰ " "
		load second card	
		-4.3997 06	real pole location
		53.03 03	imag
		-2.3760 03	real
			complex
			conj.
		-53.03 03	imag
		-2.3760 03	real
			pole pair
		8.4499 03	f _n
		11.17 00	Q _n
		-9.4414 00	midband gain

Example 1-3.2

Figure 1-3.3 is the schematic of a second order highpass filter using the Sallen and Key controlled source topology. An operational amplifier is connected in the voltage follower configuration to provide the unity gain non-inverting buffer amplifier required. The design procedure assumes infinite bandwidth in this buffer, but physical op-amps, such as the 741 type have finite bandwidth (BW). This example will show how this finite bandwidth affects the filter performance. The design specifications are:

natural frequency, f_o :	10000 Hz
quality factor, Q :	$1/\sqrt{2} = 0.707$
capacitor value, C_1, C_4 :	1 nF
asymptotic high frequency gain:	unity

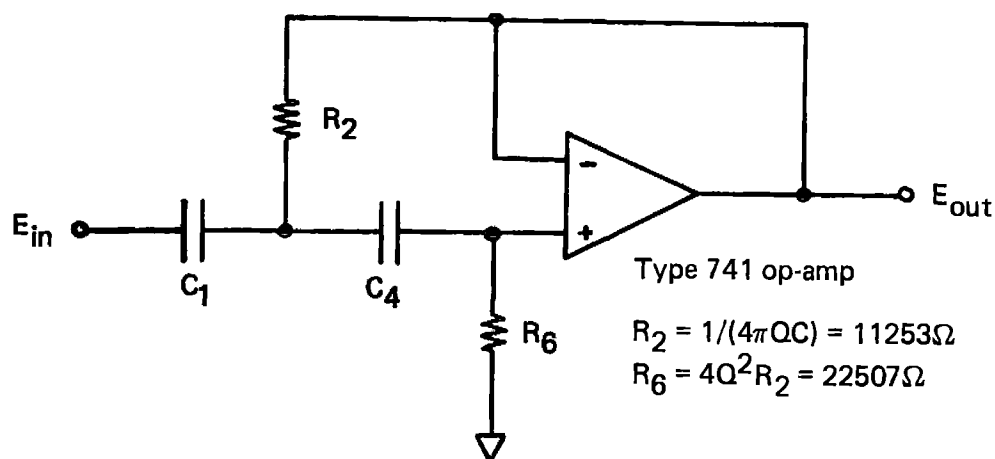


Figure 1-3.3 Sallen and Key type second order highpass filter.

The HP-97 printout is shown on the next page. Again, two runs were made; first the amplifier was assumed to be ideal, and the program output verifies the design specifications; second, the finite gain and bandwidth characteristics of the 741 operational amplifier were used. The program output for the second case shows the non-ideal (finite) characteristics of the 741 have caused the second order pole positions to shift away from the desired positions, and a real pole has also been introduced.

HP-97 PRINTOUT FOR EXAMPLE 1-3.2

load first program and
enter element values

-1.-09 GSBA element 1, capacitor
11253. GSBB element 2, resistor
0. GSBC element 3, missing
-1.-09 GSBD element 4, capacitor
0. GSBE element 5, missing
22507. GSBA element 6, resistor

1. ST00 set $A_0 = 1$
0. ST07 set $\tau = 0$ ($BW = \infty$)

GSBe start analysis
0.000+00 *** s^3
253.3-12 *** s^2
22.51-06 *** s^1
1.000+00 *** s^0

253.3-12 *** s^2
0.000+00 *** s^1
0.000+00 *** s^0

load second card &
start analysis

44.43+03 *** imag
-44.43+03 *** real } { complex
-44.43+03 *** imag } { conjugate
-44.43+03 *** real } { poles

10.00+03 *** f_n } { of second
707.1-03 *** Q } { order pole
pair

1.000+00 *** asymptotic gain
0.000+00 *** numerator zero
0.000+00 *** locations

Reload first card and
enter op-amp parameters

1. ENT↑ gain
500000. GSBA bandwidth } type 741

GSBe start analysis
80.62-18 *** s^2 denominator coef
267.6-12 *** s^2 " "
22.82-06 *** s^1 " "
1.000+00 *** s^0 " "

253.3-12 *** s^2 numerator coef
0.000+00 *** s^1 " "
0.000+00 *** s^0 " "

load second card &
start analysis

-3.233+06 *** real pole location

44.40+03 *** imag
-43.19+03 *** real } { complex
-44.40+03 *** imag } { conjugate
-43.19+03 *** real } { poles

9.858+03 *** f_n } { of second
717.0-03 *** Q } { order pole
pair

971.7-03 *** asymptotic gain
0.000+00 *** numerator zero
0.000+00 *** locations

TI-59 PRINTOUT FOR EXAMPLE 1-3.2

load first program and enter element values			
1.	1. -09	C	element # capacitor
2.	11253.	R	element # resistor
4.	1. -09	C	element # capacitor
6.	22507.	R	element # resistor
1.		A	amplifier gain (ideal)
1. 25		F	amplifier BW (ideal)
0.00 00		s ³	den coef
253.27-12		s ²	" "
22.51-06		s ¹	" "
1.00 00		s ⁰	" "
253.27-12		s ²	num coef
0.00 00		s ¹	" "
0.00 00		s ⁰	" "
load second card			
44.43 03	imag		complex
-44.43 03	real		
-44.43 03	imag		pole pair
-44.43 03	real		
10.00 03	f _n		of second order
707.12-03	Q		
			pole pair
1.00 00	asymptotic gain		
reload first card			
	1. 00	A	741 gain
	500. 03	F	741 BW
	80.62-18	s ³	den coef
	267.60-12	s ²	" "
	22.82-06	s ¹	" "
	1.00 00	s ⁰	" "
	253.27-12	s ²	num coef
	0.00 00	s ¹	" "
	0.00 00	s ⁰	" "
load second card			
	-3.23 06	real pole location	
	44.40 03	imag	
	-43.19 03	real	
	-44.40 03	imag	
	-43.19 03	real	
	9.86 03	f _n	
	717.04-03	Q	
			of second order
	971.75-03		pole pair
			asymptotic gain

Derivation of Equations and Algorithms Used

Active network transfer function: The schematic of the generalized second order active network is shown in Fig. 1-3.1. Let the junction of Y_1 , Y_2 , Y_3 , and Y_4 be designated node 1. Furthermore, let the junction of Y_4 , Y_5 , and Y_6 be designated as node 2. The nodal equations for this circuit may be written in matrix form in terms of the voltages at node 1 (E_1), and at node 2 (E_2):

$$\begin{bmatrix} \{Y_1 + Y_2 + Y_3 + Y_4\} & \{-Y_4\} \\ \{-Y_4\} & \{Y_4 + Y_5 + Y_6\} \end{bmatrix} \cdot \begin{bmatrix} E_1 \\ E_2 \end{bmatrix} = \begin{bmatrix} Y_1 & Y_2 \\ 0 & Y_5 \end{bmatrix} \cdot \begin{bmatrix} E_{in} \\ E_{out} \end{bmatrix} \quad (1-3.6)$$

Since $E_2 = E_{out}/A$, this expression is substituted into Eq. (1-3.6), and the dependent variables brought to the left hand side.

$$\begin{bmatrix} \{Y_1 + Y_2 + Y_3 + Y_4\} & \left\{\frac{Y_4}{A} - Y_2\right\} \\ \{-Y_4\} & \left\{\frac{Y_4 + Y_5 + Y_6}{A} - Y_5\right\} \end{bmatrix} \cdot \begin{bmatrix} E_1 \\ E_{out} \end{bmatrix} = \begin{bmatrix} Y_1 \\ 0 \end{bmatrix} (E_{in}) \quad (1-3.7)$$

$T(s) = E_{out}/E_{in}$ may be obtained from Eq. (1-3.7) using Cramer's rule. To this end, the determinant of the coefficient matrix (Δ) is needed:

$$\Delta = (Y_1 + Y_2 + Y_3 + Y_4) \cdot \left[\frac{Y_4 + Y_5 + Y_6}{A} - Y_5 \right] - Y_4 \left[\frac{Y_4}{A} - Y_2 \right] \quad (1-3.8)$$

After clearing fractions and eliminating term subtraction,

$$\begin{aligned} A \cdot \Delta &= (Y_1 + Y_2 + Y_3)[Y_4 + Y_6 + Y_5(1 - A)] + \\ &Y_4 [Y_5(1 - A) - AY_2 + Y_6] \end{aligned} \quad (1-3.9)$$

Substituting $A = A_0/(1 + \tau s)$ as the amplifier gain, and clearing fractions, Eq. (1-3.9) becomes:

$$\begin{aligned} A_0 \cdot \Delta &= (Y_1 + Y_2 + Y_3)[(Y_4 + Y_5)(1 + \tau s) + Y_5(1 - A_0 + \tau s)] + \\ &Y_4 [Y_6(1 + \tau s) + Y_5(1 - A_0 + \tau s) - A_0 \cdot Y_2] \end{aligned} \quad (1.3.10)$$

Using Cramer's rule, the transmission function becomes:

$$T(s) = E_{\text{out}}/E_{\text{in}} = (Y_1 \cdot Y_4)/\Delta \quad (1-3.11)$$

Newton-Raphson solution for finding real zeros of third order polynomials:

The Newton-Raphson solution is an iterative procedure for finding the values of x where $f(x)$ becomes zero, hence, these values of x are called the zeros of $f(x)$. If the mathematical operations are restricted to real numbers, then the procedure will only find the real zeros of the function, $f(x)$. All odd ordered polynomials with real coefficients have at least one real zero. The third order polynomial generated by this program falls into this class, therefore real arithmetic is used to extract the real zero.

Given the function $f(x) = 0$, the Newton-Raphson solution provides a new estimate, x_{i+1} , based on the present estimate, x_i , and the tangent to $f(x_i)$. The value of x_{i+1} is determined by calculating the intercept of the tangent, $f'(x_i)$ on the x axis as shown in Fig. 1-3.2.

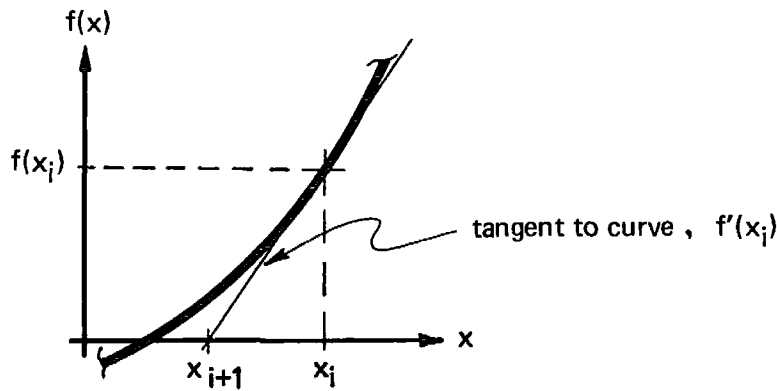


Figure 1-3.2 Newton-Raphson solution method.

$$f'(x_i) = \Delta f(x_i) / \Delta x_i = (f(x_i) - 0) / (x_i - x_{i+1})$$

Solving for x_{i+1} :

$$x_{i+1} = x_i - f(x_i) / f'(x_i)$$

The iteration is stopped when the absolute value of the correction term, $f(x_i) / f'(x_i)$ becomes smaller than the desired error limit, $x_i \cdot 10^{-8}$.

Once the real zero of the third order polynomial has been found, a polynomial division is done to deflate the polynomial to second order. The quadratic equation is used to obtain the zeros of the second order

polynomial, and these zeros may be complex. If $s = a$ is a zero of $f(s)$, then $s-a$ must be a factor of $f(s)$, and can be removed:

$$\begin{array}{r}
 b_3 s^2 + (ab_3 + b_2)s + (a(ab_3 + b_2) + b_1) \\
 s-a \overline{) b_3 s^3 + b_2 s^2 + b_1 s + 1} \\
 \underline{-(b_3 s^3 - ab_3 s^2)} \\
 (ab_3 + b_2)s^2 + b_1 s + 1 \\
 \underline{-[(ab_3 + b_2)s^2 - a(ab_3 + b_2)s]} \\
 a(ab_3 + b_2)s + b_1 s + 1 \\
 \underline{-(a(ab_3 + b_2)s + b_1 s - a[a(ab_3 + b_2) + b_1])} \\
 0*
 \end{array} \tag{1-3.14}$$

The third order polynomial is evaluated in nested form, i.e.:

$$D(s) = (((b_3)s + b_2)s + b_1)s + 1 \tag{1-3.15}$$

When $s = a$, the intermediate products in $D(s)$ are the same as the second order polynomial coefficients in Eq. (1-3.14). These intermediate products are stored at lines 027 and 031 of the program on the second card. The numbers stored only have value in the last iteration loop before loop exit, at which time $s = a$, and $f(s) = 0$, the desired result.

The second order polynomial is normalized so $c_0 = 1$ (lines 064 to 066). This normalization places the second order polynomial in the same form as the third order polynomial was originally. The quadratic formula is now used to find the zeros of the second order polynomial, $c_2 s^2 + c_1 s + 1$.

$$s_{1,2} = -c_1 / (2c_2) \pm \sqrt{(c_1 / (2c_2))^2 - 1/c_2} \tag{1-3.16}$$

If the discriminant, $(c_1 / (2c_2))^2 - 1/c_2$, is positive, then two real zeros exist, if it is zero, a double zero exists, and if it is negative, a complex conjugate pair of zeros exist. Steps 067 through 102 find the zeros of the second order polynomial.

* By definition since $s = a$ is a zero of the polynomial.

If the zeros of the second order polynomial are complex conjugates, then the poles of the transmission function are also complex conjugates, and a natural frequency, f_n , and quality factor, Q , may be calculated:

$$f_n = 1/(2\pi\sqrt{c_2}) \quad (1-3.17)$$

$$Q = \sqrt{c_2}/c_1 \quad (1-3.18)$$

These calculations are performed by steps 103 through 113 of the program. Assuming the third order real pole of the transmission function (parasitic pole caused by the op-amp characteristics) to be large compared to the other poles, then the gain term, K , can be defined in terms of the numerator and denominator coefficients:

$$T(s) = \frac{a_2s^2 + a_1s + a_0}{(s/a + 1)(c_2s^2 + c_1s + 1)} \quad (1-3.19)$$

$$\text{lowpass case: } K = a_0 \quad (1-3.20)$$

$$\text{bandpass case: } K = a_1/c_1 \quad (1-3.21)$$

$$\text{highpass case: } K = a_2/c_2 \quad (1-3.22)$$

The gain term is calculated by steps 114 through 137 of the program.

Program Listing I

001 *LBL1	LOAD ELEMENT 1	057 RCL6	
002 EEV		058 GSB0	
003 ST09		059 RCL5	calculate and store s^0 and
004 *LBL2	LOAD ELEMENT 2	060 EEV	s^1 terms of:
005 2		061 RCL0	
006 ST09		062 -	
007 *LBL3	LOAD ELEMENT 3	063 x	$Y_4 + Y_6 + Y_5(1 - A_0)$
008 3		064 ST09	
009 ST09		065 GSB2	
010 *LBL4	LOAD ELEMENT 4	066 RCL4	
011 4		067 GSB0	calculate and store s^1 and
012 ST09		068 RCL5	s^2 terms of:
013 *LBL5	LOAD ELEMENT 5	069 GSB0	
014 5		070 RCL6	$\gamma s(Y_4 + Y_5 + Y_6)$
015 ST09		071 GSB0	
016 *LBL6	LOAD ELEMENT 6	072 GSB3	
017 6		073 SF0	calculate and store:
018 *LBL8	element load subroutine	074 GSB6	$(Y_4 + Y_5 + Y_6)\{Y_4 + Y_5(1 + \gamma s) + Y_6(1 - A_0 + \gamma s)\}$
019 ST01	store register index	075 GSB1	initialize index counter
020 R4	recover and store	076 RCL4	calculate and store Y_4
021 ST09	element value	077 GSB2	
022 X000	test for resistor	078 RCL6	calculate s^0 and s^1 terms
023 ST09		079 GSB0	of:
024 CHS		080 RCL9	
025 ST01	store capacitor value	081 GSB0	$Y_6 + Y_5(1 - A_0) - A_0 Y_2$
026 *LBL8		082 RCL2	
027 1/X	calculate conductance,	083 RCL0	
028 EEV	multiply by 10^{50} , and store	084 x	
029 5		085 CHS	
030 0		086 GSB2	
031 ST09	store 10^{50} for later use	087 RCL6	
032 x		088 GSB0	calculate and store s^1 and
033 *LBL7		089 RCL5	s^2 terms of $\gamma s(Y_5 + Y_6)$
034 ST01	store modified element value	090 GSB0	
035 RCL9	recall original element to	091 GSB3	
036 RTN	display and return to keybd	092 CF0	clear flag 0 to indicate
037 *LBL9	LOAD A_0 AND f_0 OF AMPLIFIER	093 GSB6	additional summing and
038 P1		094 P1S	calculate and store:
039 x		095 RCL0	$\gamma Y_4 \{Y_4(1 + \gamma s) + Y_5(1 - A_0 + \gamma s) - A_0 Y_6\}$
040 ENT1	calculate and store	096 ST0A	normalize denominator terms:
041 +	$\gamma = 1/(2\pi f_0)$	097 ST=1	
042 1/X		098 ST=2	$\frac{a_3}{a_0} s^3 + \frac{a_2}{a_0} s^2 + \frac{a_1}{a_0} s + 1$
043 ST07		099 ST=3	
044 R4	recover and store A_0	100 RCL3	recall, store, and print
045 ST00		101 PRTX	normalized denominator terms
046 RTN	return control to keyboard	102 ST0D	
047 *LBL8	START ANALYSIS	103 RCL2	$a_3/a_0 \rightarrow R_D$
048 GSB1		104 PRTX	
049 RCL1	calculate s^0 and s^1 terms	105 ST0C	$a_2/a_0 \rightarrow R_C$
050 GSB0		106 RCL1	
051 RCL2	of $Y_1 + Y_2 + Y_3$	107 P1S	$a_1/a_0 \rightarrow R_B$
052 GSB0		108 PRTX	
053 RCL3		109 ST0B	
054 GSB2		110 EEV	
055 RCL4		111 ENT1	
056 GSB0		112 PRTX	

REGISTERS									
0 A_0	1 Y_1	2 Y_2	3 Y_3	4 Y_4	5 Y_5	6 Y_6	7 γ	8 10^{50}	9 scratch
S0 $\sum s^0$ terms	S1 $\sum s^1$ terms	S2 $\sum s^2$ terms	S3 $\sum s^3$ terms	S4	S5 s_1^2	S6 s_1^0	S7 s_1^1	S8 s_2^0	S9 s_2^1
A b_0	B D_1	C D_2	D D_3	E scratchpad	I index				

LABELS					FLAGS	SET STATUS		
A	B	C	D	E	0 continued summation	FLAGS	TRIG	DISP
Load Y_1	Load Y_2	Load Y_3	Load Y_4	Load Y_5	1	ON OFF	USERS CHOICE	
load Y_6	second card wait loop		load $A_0 + f_0$	start analysis	2	0	DEG	FIX
sum $R \leftarrow sC$	initialize	2 loop terminate	3 calculate $s^0 \& s^1$	4 summation subroutine	3	1	GRAD	SCI
5 summation initialize	6 polynomial multiplication	7 input routine	8 input routine	9 recall subroutine		2	RAD	ENG
						3		n

Program Listing I

```

001 *LBLE  START ANALYSIS
002   SPC
003   P=S
004   RCLD  if s3 coefficient is not
005   X#0?  zero go to 3rd order soln
006   GT00  otherwise store remaining
007   RCLC  second order coefficients
008   ST09  and go to second order
009   RCLB  solution
010   ST08
011   GT02

```

```

012 *LBLE  third order solution
013   RCLC
014   X=Y  calculate initial guess
015   =    for real 3rd order root
016   CHS
017   ST06

```

```

018 *LBL1  Newton-Raphson start
019   RCL6
020   ENT↑
021   ENT↑
022   ENT↑

```

```

023   RCLD
024   x
025   RCLC
026   +
027   ST08
028   x
029   RCLB  calculate f(x1)
030   +
031   ST07
032   x
033   EEX
034   +
035   ST05
036   CLX

```

```

037   RCLD
038   3
039   x
040   x
041   RCLC
042   ENT1  calculate f'(x1)
043   +
044   +
045   x
046   RCLB
047   +
048   X#0?  f'(x1) = 0 escape
049   ST=5  calc f(x1)/f'(x1)
050   RCL5  apply correction to x1
051   ST-6
052   ABS
053   RCL6
054   EEX
055   8
056   ÷      test for loop exit
057   ABS
058   X<Y?
059   GT01
060   RCL6  print real root
061   GSB9
062   RCLD
063   ST09  normalize remaining
064   RCL7  second order coefficients
065   ST=8
066   ST=9

```

REGISTERS

0	1	2	3	4	5	6	7	8	9
A ₀	Y ₁	Y ₂	Y ₃	Y ₄	Y ₅	Y ₆	τ	scratch	scratch
S ₀ ∑ s _n ⁰	S ₁ ∑ s _n ¹	S ₂ ∑ s _n ²	S ₃	S ₄	S ₅ scratch	S ₆ σ	S ₇ c ₀ , 1/c ₂	S ₈ c ₁ , c ₁ /2c ₂	S ₉ c ₂
A b ₀	B D ₁	C D ₂	D D ₃	E	I				

Program Listing II

067	*LBL2	second order solution
068	RCL9	c ₂
069	ENT↑	
070	+	2*c ₂
071	ST=8	c ₁ /(2c ₂)
072	RCL8	
073	X²	
074	RCL9	
075	1/X	
076	ST07	
077	-	(c ₁ /(2c ₂))² - 1/c ₂
078	X<0?	if discriminant is negative,
079	GT03	go to imaginary solution
080	JX	
081	ST05	
082	RCL8	calculate and print
083	-	one real root
084	GSB9	
085	RCL5	
086	RCL8	calculate and print
087	+	other real root
088	CHS	
089	GT00	
090	*LBL3	imaginary solution routine
091	CHS	
092	JX	
093	ST05	
094	PRTX	calculate and print
095	RCL8	one imaginary root
096	CHS	
097	GSB9	
098	RCL5	
099	CHS	
100	PRTX	calculate and print
101	X*Y	other imaginary root
102	GSB9	
103	RCL7	ω ² _n
104	JX	
105	2	
106	÷	
107	ST05	ω _n /2
108	P↑	
109	÷	
110	PRTX	f _n , the natural frequency
111	RCL5	
112	RCL8	
113	÷	Q, the quality factor

114	*LBL0	
115	GSB9	print Q, or second real root
116	RCL9	
117	ST×7	restore second order
118	ENT↑	coefficients
119	+	
120	ST×8	
121	SPC	
122	RCL2	is numerator second order?
123	X#0?	
124	GT00	
125	RCL0	is numerator a constant?
126	X#0?	
127	GT08	
128	RCL1	numerator is first order
129	RCL8	calculate and print the
130	÷	gain term, K
131	GSB9	
132	CLX	print location of numerator
133	GT08	zero and exit program
134	*LBL0	numerator is second order
135	RCL9	calculate and print the
136	÷	gain term, K
137	GSB9	
138	CLX	print location of the
139	PRTX	numerator zeros
140	*LBL8	program exit, restore
141	P↑S	registers to original order
142	*LBL9	
143	PRTX	print and space subroutine
144	SPC	
145	RTN	

LABELS					FLAGS	SET STATUS			
A	B	C	D	E start analysis	0	FLAGS		TRIG	DISP
a	b	c	d	e	1	ON OFF			
0 local label	1 local label	2 2nd order solution	3 imag roots	4	2	0		DEG ■	FIX
						1		GRAD	SCI
						2		RAD	ENG ■
5	6	7	8 P↑S, prt & space	9 print & space	3	3			n 3

Suggested program changes for the HP-67: Program space does not allow the inclusion of a print, R/S toggle and associated output routine. To cause the program execution to stop at the data output points, replace the "print" statements with "R/S" statements at the following line numbers: 101, 104, 108, 112, 131, 133, and 136 in program one, and at lines 094, 100, 110, 139, and 143 in program two.

If these changes are made, the program will stop at each output point. To continue program execution, key a "R/S" command from the keyboard.

TI-59 PROGRAM LISTING

1-3 card 1

000	76	LBL	subroutine to sum	050	05	05	
001	44	SUM	conductance & susceptance	051	00	0	
002	42	STD	store entry in scratchpad	052	72	ST*	clear next set of storage registers
003	09	09		053	04	04	
004	50	IXI	test for conductance:	054	72	ST*	
005	32	XIT	If entry is smaller than	055	05	05	
006	01	1	10^{30} , then it is a	056	92	RTH	return to main program
007	52	EE	susceptance and program	057	76	LBL	LOAD ELEMENT INDEX
008	03	3	execution jumps to	058	11	A	
009	00	0	step 24.	059	98	ADV	space paper in printer
010	77	GE		060	22	INV	
011	00	00		061	52	EE	set fix 0 format
012	24	24		062	22	INV	
013	43	RCL	recover entry	063	57	ENG	
014	09	09		064	99	PRT	print element index
015	55	÷	remove conductance	065	85	+	
016	01	1	scaling	066	32	XIT	save index entry
017	52	EE		067	01	1	
018	05	5		068	00	0	calculate storage
019	00	0		069	95	=	register location
020	95	=		070	42	STD	
021	74	SM*	sum conductance	071	04	04	
022	05	05		072	32	XIT	recover index to display
023	92	RTH	return to main program	073	91	R/S	stop program execution
024	43	RCL	recover entry	074	76	LBL	LOAD RESISTOR VALUE
025	09	09		075	12	B	
026	74	SM*	sum susceptance	076	35	1/X	form conductance
027	04	04		077	65	X	
028	92	RTH	return to main program	078	32	XIT	save conductance
029	76	LBL	initialization	079	01	1	
030	59	INT	subroutine	080	52	EE	multiply conductance by
031	02	2		081	05	5	10^{30} and indirectly store
032	00	0	initialize susceptance	082	00	0	
033	42	STD	storage register index	083	95	=	
034	04	04		084	72	ST*	
035	02	2		085	04	04	
036	01	1	initialize conductance	086	03	3	setup to print "R" as
037	42	STD	storage register index	087	05	5	annotation on right
038	05	05		088	69	DP	hand edge of printout
039	61	GTO	jump to step 51 and	089	04	04	
040	00	00	continue program	090	32	XIT	
041	51	51	execution	091	35	1/X	recover resistor entry
042	76	LBL	subroutine to complete	092	22	INV	and print annotated
043	85	+	summation	093	52	EE	value
044	71	SBR	gosub subroutine "sum"	094	69	DP	
045	44	SUM		095	06	06	
046	02	2		096	91	R/S	stop program execution
047	44	SUM	increment storage	097	76	LBL	LOAD CAPACITOR VALUE
048	04	04	register indices	098	13	C	
049	44	SUM		099	72	ST*	

Note: This translation was provided by Mr. Roger Junk.

TI - 59 PROGRAM LISTING

1-3 card 1

100	04	04	indirectly store cap	150	32	XIT	recover entry
101	32	XIT	save entry	151	98	ADV	space paper and
102	01	1		152	69	DP	print annotated entry
103	05	5	setup to print "C" on	153	06	06	
104	69	DP	right hand edge of paper	154	91	R/S	stop program execution
105	04	04		155	76	LBL	INITIALIZE
106	32	XIT		156	16	R*	
107	57	ENG	print capacitor value in	157	00	0	
108	69	DP	engineering format along	158	42	STO	zero elements 2, 3, 5, & 6
109	06	06	with annotation	159	12	12	
110	91	R/S	stop program execution	160	42	STO	
111	76	LBL	LOAD OP-AMP DC GAIN, A ₀	161	13	13	
112	14	D		162	42	STO	
113	42	STO	store A ₀	163	15	15	
114	10	10		164	42	STO	
115	32	XIT	save entry	165	16	16	
116	01	1		166	91	R/S	stop program execution
117	03	3	setup to print "A" on	167	76	LBL	START ANALYSIS
118	69	DP	right hand edge of paper	168	10	E*	
119	04	04		169	71	SBR	test for printer attached
120	32	XIT	recover entry,	170	04	04	to calculator
121	98	ADV	space paper, and	171	75	75	
122	69	DP	print entry and notation	172	71	SBR	initialize counters and
123	06	06		173	59	INT	registers
124	91	R/S	stop program execution	174	43	RCL	
125	76	LBL	LOAD OP-AMP BREAK	175	11	11	
126	15	E	FREQUENCY (-3 dB point)	176	71	SBR	
127	65	x		177	44	SUM	
128	32	XIT	save entry	178	43	RCL	calculate and store
129	02	2		179	12	12	s ₀ and s ₁ terms of:
130	65	x		180	71	SBR	
131	89	n	form and store:	181	44	SUM	Y ₁ + Y ₂ + Y ₃
132	95	=	$\gamma = \frac{1}{2\pi f_{-3 \text{ dB}}}$	182	43	RCL	
133	35	1/X		183	13	13	
134	42	STO		184	71	SBR	
135	17	17		185	85	+	
136	01	1		186	43	RCL	
137	52	EE	if entry is larger than	187	14	14	
138	02	2	10 ²⁰ set γ to zero	188	71	SBR	
139	00	0		189	44	SUM	calculate and store
140	77	GE		190	43	RCL	s ₀ and s ₁ terms of:
141	01	01		191	16	16	
142	46	46		192	71	SBR	Y ₄ + Y ₆ + Y ₅ (1 - A ₀)
143	00	0		193	44	SUM	
144	42	STO		194	01	1	
145	17	17		195	75	-	
146	02	2		196	43	RCL	
147	01	1	setup to print "F" on	197	10	10	
148	69	DP	right hand edge of paper	198	95	=	
149	04	04		199	65	x	

TI-59 PROGRAM LISTING

1-3 card 1

200	43	RCL		250	71	SBR	
201	15	15		251	44	SUM	
202	95	=		252	43	RCL	calculate and store
203	42	STD		253	15	15	s^1 and s^2 terms of:
204	19	19		254	71	SBR	
205	71	SBR		255	44	SUM	$\tau s(Y_5 + Y_6)$
206	85	+		256	71	SBR	
207	43	RCL	-----	257	49	PRD	-----
208	14	14		258	22	INV	calculate and store:
209	71	SBR		259	86	STF	
210	44	SUM	calculate and store	260	00	00	$D_1 + Y_4 \{ Y_6(1 + \tau s) +$
211	43	RCL	s^1 and s^2 terms of:	261	71	SBR	$Y_5(1 - A_0 + \tau s) - A_0 Y_2 \}$
212	15	15		262	65	x	
213	71	SBR	$\tau s(Y_4 + Y_5 + Y_6)$	263	29	CP	-----
214	44	SUM		264	43	RCL	test for non-zero
215	43	RCL		265	00	00	denominator coeffs
216	16	16		266	22	INV	
217	71	SBR		267	67	EQ	
218	44	SUM		268	02	02	
219	71	SBR		269	78	78	
220	49	PRD		270	43	RCL	non-zero test continued
221	86	STF	calculate and store:	271	01	01	
222	00	00		272	22	INV	
223	71	SBR	$(Y_1 + Y_2 + Y_3) \{ (Y_4 + Y_6 X(1 + \tau s) + Y_5(1 - A_0 + \tau s)) \}$	273	67	EQ	
224	65	x	$= D_1$	274	02	02	
225	71	SBR		275	78	78	
226	59	INT	initialize indices	276	43	RCL	non-zero test concluded
227	43	RCL		277	02	02	
228	14	14	calculate and store	278	42	STD	
229	71	SBR	s^0 and s^1 terms of	279	18	18	
230	85	+	Y_4	280	35	1/X	normalize denominator
231	43	RCL	-----	281	49	PRD	terms
232	16	16		282	00	00	
233	71	SBR		283	49	PRD	
234	44	SUM		284	01	01	
235	43	RCL	calculate and store	285	49	PRD	
236	19	19	s^0 and s^1 terms of:	286	02	02	
237	71	SBR		287	49	PRD	
238	44	SUM	$Y_6 + Y_5(1 - A_0) + A_0 Y_2$	288	03	03	
239	43	RCL		289	43	RCL	recall and print s^3
240	12	12		290	03	03	denominator coefficient
241	65	x		291	71	SBR	(program will stop if
242	43	RCL		292	98	ADV	printer is not attached)
243	10	10		293	42	STD	
244	95	=		294	29	29	
245	94	+/-		295	43	RCL	recall and print s^2
246	71	SBR		296	02	02	denominator coefficient
247	85	+		297	71	SBR	
248	43	RCL	-----	298	04	04	
249	16	16		299	64	64	

TI-59 PROGRAM LISTING

1-3 card 1

300	42	STD		350	04	04	
301	28	28		351	64	64	
302	43	RCL		352	43	RCL	
303	01	01	recall and print s^1	353	00	00	recall and print s^0
304	71	SBR	denominator coefficient	354	71	SBR	numerator coefficient
305	99	PRT		355	04	04	
306	42	STD		356	64	64	
307	27	27		357	91	R/S	stop program execution
308	43	RCL		358	00	0	
309	00	00	recall and print s^0	359	00	0	unused program memory
310	71	SBR	denominator coefficient	360	00	0	
311	99	PRT		361	00	0	
312	42	STD		362	00	0	
313	26	26		363	00	0	
314	86	STF	indicate first product	364	00	0	
315	00	00	of sums	365	00	0	
316	71	SBR	initialize indices	366	00	0	
317	59	INT		367	00	0	
318	43	RCL		368	76	LBL	subroutine to multiply
319	11	11	calculate and store	369	49	PRD	by γ s to form s^2 and
320	71	SBR	s^0 , s^1 , and s^2 terms	370	43	RCL	additional s^1 terms, and
321	85	+	of $Y_1 \cdot Y_4$	371	17	17	add to presently stored
322	43	RCL		372	49	PRD	terms
323	14	14		373	24	24	
324	71	SBR		374	65	x	
325	85	+		375	43	RCL	
326	00	0		376	25	25	
327	72	ST*		377	95	=	
328	04	04		378	44	SUM	
329	71	SBR		379	22	22	
330	65	x		380	92	RTN	
331	43	RCL		381	76	LBL	polynomial multiplication
332	10	10		382	65	x	subroutine
333	55	÷	normalize numerator	383	00	0	
334	43	RCL	coefficients	384	71	SBR	
335	18	18		385	04	04	
336	95	=		386	48	48	
337	49	PRD		387	43	RCL	
338	02	02		388	23	23	s^0 term calculation
339	49	PRD		389	65	x	
340	01	01		390	43	RCL	
341	49	PRD		391	21	21	
342	00	00		392	95	=	
343	43	RCL		393	74	SM*	
344	02	02	recall and print s^2	394	05	05	
345	71	SBR	numerator coefficient	395	01	1	
346	98	ADV		396	71	SBR	
347	43	RCL		397	04	04	s^1 term calculation
348	01	01	recall and print s^1	398	48	48	
349	71	SBR	numerator coefficient	399	43	RCL	

TI-59 PROGRAM LISTING 1-3 card 1

400	22	22	s ¹ term calculation continued	450	22	INV	subroutine to print and continue if calculator attached to PC-100A printer, or else to stop program execution and display answer				
401	65	x		451	87	IFF					
402	43	RCL		452	00	00					
403	21	21		453	04	04					
404	95	=		454	58	58					
405	74	SM*		455	00	0					
406	05	05		456	72	ST*					
407	43	RCL		457	05	05					
408	23	23		458	92	RTN					
409	65	x		459	76	LBL					
410	43	RCL	460	98	ADV	subroutine to sense PC-100A printer is attached to calculator					
411	20	20	461	98	ADV						
412	95	=	462	76	LBL						
413	74	SM*	463	99	PRT						
414	05	05	464	57	ENG						
415	02	2	465	99	PRT						
416	71	SBR	466	22	INV						
417	04	04	467	87	IFF						
418	48	48	468	01	01						
419	43	RCL	469	04	04						
420	22	22	470	74	74						
421	65	x	471	91	R/S						
422	43	RCL	472	22	INV						
423	20	20	473	57	ENG						
424	95	=	474	92	RTN						
425	74	SM*	475	69	DP						
426	05	05	476	08	08						
427	43	RCL	477	86	STF						
428	24	24	478	01	01						
429	65	x	479	92	RTN						
430	43	RCL									
431	21	21									
432	95	=									
433	74	SM*									
434	05	05									
435	03	3									
436	71	SBR									
437	04	04									
438	48	48									
439	43	RCL									
440	24	24	s ³ term calculation								
441	65	x									
442	43	RCL									
443	20	20									
444	95	=									
445	74	SM*									
446	05	05									
447	92	RTN									
448	42	STD						polynomial multiplication storage subroutine			
449	05	05									

REGISTER ALLOCATIONS FOR TI-59 1-3 card 1

register number	contents
0	sum of s^0 terms
1	sum of s^1 terms
2	sum of s^2 terms
3	sum of s^3 terms
4	indirect storage register index
5	indirect storage register index
6	
7	
8	
9	
10	A_0 , the op-amp dc gain
11	Y_1
12	Y_2
13	Y_3
14	Y_4
15	Y_5
16	Y_6
17	τ
18	b_0
19	$Y_5(1-A_0)$
20	----- s_2^1
21	----- s_2^0
22	----- s_1^1
23	----- s_1^0
24	----- s_1^2
25	
26	D_0
27	D_1
28	D_2
29	D_3
30	

TI-59 PROGRAM LISTING

1-3 card 2

000	76	LBL	START	050	43	RCL	
001	15	E		051	29	29	
002	71	SBR	test for PO-100A printer	052	65	x	
003	04	04	attached to calculator	053	43	RCL	
004	75	75		054	23	23	
005	43	RCL		055	85	+	
006	29	29	if s^3 coefficient is zero,	056	02	2	calculate $f'(x_1)$
007	29	CP	go to second order	057	65	x	
008	67	EQ	solution routine	058	43	RCL	
009	01	01		059	28	28	
010	19	19		060	95	=	
011	55	÷		061	65	x	
012	43	RCL	calculate initial guess	062	43	RCL	
013	28	28	for real third order root	063	23	23	
014	95	=		064	85	+	
015	35	1/X	$x_0 = D_2/D_3$	065	43	RCL	
016	94	+/-		066	27	27	
017	42	STO		067	95	=	
018	23	23		068	29	CP	
019	43	RCL	Newton-Raphson start	069	67	EQ	$f'(x_1) = 0$ escape
020	23	23		070	00	00	
021	65	x		071	75	75	
022	43	RCL		072	35	1/X	
023	29	29		073	49	PRD	calc $f(x_1)/f'(x_1)$
024	85	+		074	25	25	
025	43	RCL		075	43	RCL	
026	28	28		076	25	25	
027	95	=		077	94	+/-	apply correction to x_1
028	42	STO		078	44	SUM	
029	21	21		079	23	23	
030	65	x		080	50	I×I	
031	43	RCL		081	32	X↓T	
032	23	23	calculate $f(x_1)$	082	43	RCL	
033	85	+		083	23	23	
034	43	RCL		084	55	÷	
035	27	27		085	01	1	
036	95	=		086	52	EE	test for loop exit
037	42	STO		087	08	8	
038	22	22		088	95	=	
039	65	x		089	50	I×I	
040	43	RCL		090	22	INV	
041	23	23		091	77	GE	
042	85	+		092	00	00	
043	43	RCL		093	19	19	
044	26	26		094	43	RCL	
045	95	=		095	23	23	
046	42	STO		096	71	SBR	print real root
047	25	25		097	04	04	
048	03	3		098	65	65	
049	65	x		099	43	RCL	

TI-59 PROGRAM LISTING

1-3 card 2

100	29	29		150	77	GE	
101	42	STD		151	01	01	
102	20	20		152	75	75	
103	43	RCL		153	34	FX	
104	22	22		154	42	STD	
105	29	CP		155	25	25	
106	67	EQ	normalize second order coefficients	156	75	-	
107	01	01		157	43	RCL	calculate and print one real root
108	31	31		158	21	21	
109	35	1/X		159	95	=	
110	49	PRD		160	71	SBR	
111	20	20		161	04	04	
112	49	PRD		162	65	65	
113	21	21		163	43	RCL	
114	49	PRD		164	25	25	
115	22	22		165	85	+	
116	61	STD		166	43	RCL	
117	01	01		167	08	08	calculate and print other real root
118	31	31		168	94	+/-	
119	43	RCL		169	71	SBR	
120	28	28		170	04	04	
121	42	STD	store second order coefficients	171	65	65	
122	20	20		172	61	STD	
123	43	RCL		173	02	02	
124	27	27		174	25	25	
125	42	STD		175	94	+/-	imaginary solution:
126	21	21		176	34	FX	
127	43	RCL		177	42	STD	
128	26	26		178	25	25	
129	42	STD		179	71	SBR	
130	22	22		180	04	04	
131	43	RCL	second order solution:	181	65	65	calculate and print one complex root
132	20	20		182	43	RCL	
133	35	1/X		183	21	21	
134	49	PRD		184	94	+/-	
135	22	22		185	71	SBR	
136	55	+		186	04	04	
137	02	2		187	66	66	
138	95	=	calculate discriminant,	188	43	RCL	
139	49	PRD		189	25	25	
140	21	21	$b^2 - 4ac$	190	94	+/-	
141	43	RCL		191	71	SBR	
142	21	21		192	04	04	
143	33	X ²		193	65	65	
144	75	-		194	43	RCL	calculate and print the other complex root
145	43	RCL		195	21	21	
146	22	22		196	94	+/-	
147	95	=		197	71	SBR	
148	29	CP	test for negative discriminant	198	04	04	
149	22	INV		199	66	66	

TI-59 PROGRAM LISTING

1-3 card 2

200	68	NOP		250	21	21	
201	68	NOP		251	95	=	
202	43	RCL		252	61	GTO	
203	22	22		253	02	02	
204	34	FX		254	59	59	
205	55	÷		255	55	÷	
206	02	2		256	43	RCL	calculate and print
207	95	=		257	20	20	the gain term, K
208	42	STO	calculate and print	258	95	=	
209	25	25	f _n , the natural	259	71	SBR	
210	55	÷	frequency	260	04	04	
211	89	IF		261	65	65	
212	95	=		262	61	GTO	
213	71	SBR		263	91	R/S	
214	04	04		264	00	0	
215	65	65		265	00	0	
216	43	RCL		266	00	0	
217	25	25		267	00	0	
218	55	÷		268	00	0	
219	43	RCL		269	00	0	
220	21	21	calculate and print Q	270	00	0	
221	95	=					
222	71	SBR					
223	04	04					
224	66	66					
225	43	RCL		457	00	0	
226	20	20		458	00	0	
227	49	PRD		459	00	0	
228	22	22	restore second order				
229	65	x	coefficients				
230	02	2		460	76	LBL	subroutine to lock up
231	95	=		461	91	R/S	"R/S" command-prevents
232	49	PRD		462	61	GTO	further program execution
233	21	21		463	04	04	via the "R/S" command
234	43	RCL		464	61	61	
235	02	02		465	98	ADV	
236	22	INV	is numerator second order	466	99	PRT	print or display
237	67	EQ		467	68	NOP	subroutine
238	02	02		468	22	INV	
239	55	55		469	87	IFF	
240	43	RCL		470	01	01	
241	00	00		471	04	04	
242	22	INV	is numerator a constant?	472	74	74	
243	67	EQ		473	91	R/S	
244	02	02		474	92	RTN	
245	59	59		475	69	OP	
246	43	RCL		476	08	08	PC-100A sense routine
247	01	01		477	86	STF	
248	55	÷		478	01	01	
249	43	RCL		479	92	RTN	

REGISTER ALLOCATIONS FOR TI - 59 1-3 card 2

register number	contents
0	N_0
1	N_1
2	N_2
3	
4	
5	
6	
7	
8	
9	
10	A_0
11	Y_1
12	Y_2
13	Y_3
14	Y_4
15	Y_5
16	Y_6
17	τ
18	b_0
19	
20	c_2
21	$c_1, c_1/2c_2$
22	$c_0, 1/c_2$
23	x_1
24	
25	$f(x_1)/f'(x_1)$
26	D_0
27	D_1
28	D_2
29	D_3

PROGRAM 1-4 L N A P , LADDER NETWORK ANALYSIS PROGRAM.

Program Description and Equations Used

This program evaluates the frequency response and input impedance of a RLC ladder network containing up to 4 nodes and 8 branches using a sweep of discrete evaluation frequencies. The frequency response is provided as magnitude (dB) and phase (degrees, radians, or grads), and the input impedance is provided as real and imaginary parts (ohms). The evaluation frequency may be incremented in a linear manner using an additive increment or in a logarithmic manner using a multiplicative increment.

Each branch of the ladder may contain a resistor (R), a capacitor (C), an inductor (L), a series RC, a parallel RC, a series RL, or a parallel RL network. All element values are stored, and may be reviewed at any time to check or correct the component values and interconnection.

Because of the number of available storage registers in the HP-67/97, the number of nodes cannot exceed four, while the TI-59 can accommodate the data for ten nodes. Elements that inhibit signal flow through the network are not allowed, and will cause the program execution to halt displaying "Error." Examples of these inhibiting elements are a shunt resistor or a shunt inductor having zero value, or series capacitors in series branches having zero values.

The algorithm used by this program assumes 1 volt at the output of the ladder network (see Fig. 1-4.1). From the knowledge of the last branch admittance, the complex branch current may be determined. Since no current flows out of the last node, the last shunt branch current must also flow through the preceding series branch. The complex voltage drop across this branch may be determined by multiplying the branch impedance and the branch current. By adding the series branch voltage to the last node voltage, the next lower node voltage may be obtained. This node voltage times the shunt node admittance will yield the shunt node current. Adding this shunt node current to the previous series

branch current will yield the next lower series branch current.

This loop is repeated until the input voltage source is reached (node 0). The frequency response is found from Eq. (1-4.1) and the input impedance from Eq. (1-4.2), i.e.:

$$T(j\omega) = E_{\text{out}}/E_{\text{in}} = 1/E_0 \quad (1-4.1)$$

$$Z_{\text{in}}(j\omega) = E_0/I_0 \quad (1-4.2)$$

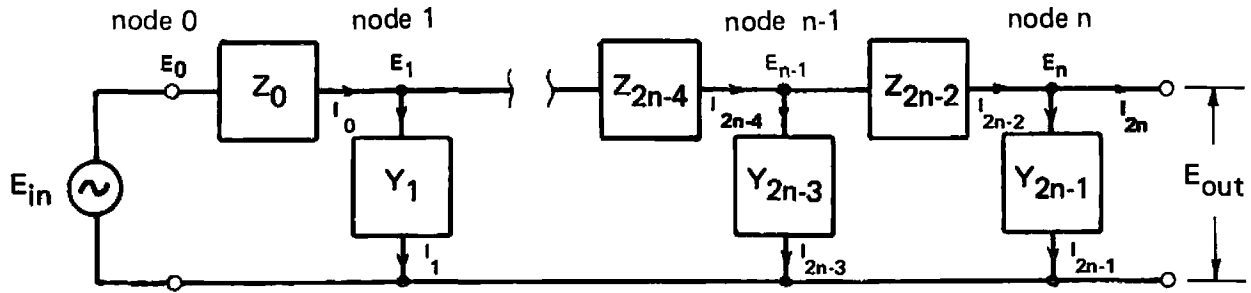


Figure 1-4.1 General ladder network topology.

The preceding algorithm may be expressed in mathematical shorthand using indices:

$$I_{2k-2} = (E_k)(Y_{2k-1}) + I_{2k} \quad (1-4.3)$$

$$E_{k-1} = (I_{2k-2})(Z_{2k-2}) + E_k \quad (1-4.5)$$

where $k = n, n-1, n-2, \dots, 1$, and n is the highest numbered node. The initial conditions for the n -th node are given by:

$$I_{2n} = 0 \quad (1-4.5)$$

$$E_n = 1 + j0 \quad (1-4.6)$$


Equation (1-4.3) is evaluated for I_{2k-2} and substituted into Eq. (1-4.4) to obtain the next lower numbered node voltage. The index, k , is decremented by one, and Eqs. (1-4.3) and (1-4.4) are again evaluated. This process is continued until the voltage at node 0 is obtained. Equation (1-4.1) is used to find the frequency response, $T(j\omega)$, from the node 0 voltage, and Eq. (1-4.2) is used to find the input impedance.

User Instructions

L N A P, LADDER NETWORK ANALYSIS PROGRAM				
# of nodes	linear sweep	log sweep	data review	start analysis
load R	load L	load 0	load start freq	load freq increment

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of the magnetic card			
2	Load the number of nodes in the network The number of nodes cannot exceed four	# nodes	<input type="text" value="f"/> <input type="text" value="A"/>	# branches
3	Enter data starting with the highest numbered node: a) If parallel RC or RL: key in resistance and change sign* key in inductance OR key in capacitance b) If series RC or RL: key in resistance OR key in inductance key in capacitance	R, ohms L, henry C, farad R, ohms L, henry C, farad	<input type="text" value="chs*"/> <input type="text" value="A"/> <input type="text" value="B"/> <input type="text" value="C"/> <input type="text" value="A"/> <input type="text" value="B"/> <input type="text" value="C"/>	branch # br # - 1 br # - 1 branch # br # - 1 br # - 1
	<p>For resistance, inductance, or capacitance alone in one branch, use step 3b with zero resistance for L or 0 entry, or use zero inductance for resistance entry. A zero or positive resistance is interpreted as a series branch indication.</p> <p>Alternately, step 3a may be used to enter single inductors or capacitors by entering a very large negative resistance like -10^{20} ohms.</p> <p>Fastest program execution will result if the zero resistance method with step 3b is used for series branches, and the large negative resistance method with step 3a is used for shunt branches. By observing this convention, the program will not use the series to parallel conversion subroutine which requires about 2 seconds to execute each time it is called.</p> <p>Repeat step 3 until all branches including branch 0 have been entered.</p> <p>* The sign change must affect the mantissa and not the exponent on numbers entered using scientific notation.</p>			

User Instructions

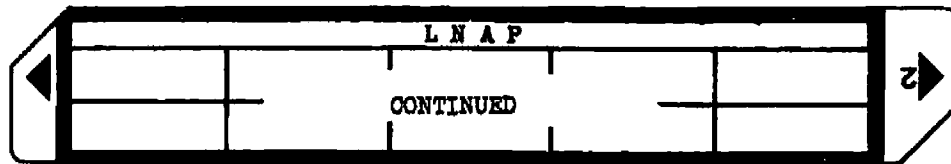

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
4	To review stored element values		f D	branch # R _n * L _n or C _n ** space R _{n-1} * L 0 ** : : R ₀ * L ₀ or C ₀ **
	* A negative resistance value indicates a parallel connection of elements			
	** A negative value for the reactive element indicates the element is a capacitor. The capacitance value is the absolute value of the number given.			
5	To change the value of a stored element:			
	a) Key in branch number to be changed	branch #	STO I	
	b) Key in correct resistance	R	A	
	c) Key in correct reactive element value	L OR C	B OR C	
	Repeat step 4 or 5 if desired.			
6	To run analysis:			
	a) Load start frequency in hertz	f _{start}	D	
	b) Load frequency increment (for linear sweep, the new frequency will be the old frequency plus the increment, and for log sweep, the new frequency will be the old frequency times the increment)	f _{incr}	E	
	c) Select linear or logarithmic sweep For linear sweep For logarithmic sweep		f B f C	"0" "1"
	Steps 6a, 6b, and 6c may be executed in any order.			
	d) Start analysis run		f E	see Ex. (1-4.1)

[illegible]

Example 1-4.1

Figure 1-4.2 is the schematic of a predistorted 8th order Butterworth lowpass filter with a -3 dB cutoff frequency of 1000 Hz, and a design impedance level of 1000 ohms. Determine the frequency response and input impedance of this filter over a frequency range of 100 Hz to 10 kHz using a logarithmic sweep with 10 points per decade.

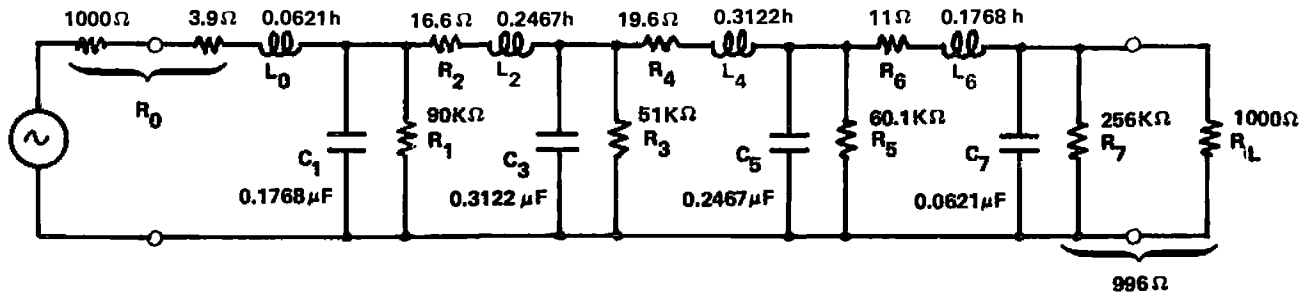


Figure 1-4.2 Predistorted 8th order Butterworth LP filter.

HP-97 PRINTOUT FOR EXAMPLE 1-4.1

PROGRAM INPUT			DATA REVIEW		
4.00 GSBA	load # of nodes		GSBd	start data review	
-996. GSBA	R7*		7.000+00	***	branch number
.0621-06 GSBC	07		-996.0+00	***	resistive part*
11. GSBA	R6		-62.10-09	***	reactive part**
.1768 GSBB	L6				
-60100. GSBA	R5		6.000+00	***	
.2647-06 GSBC	05		11.00+00	***	
			176.8-03	***	
19.6 GSBA	R4		5.000+00	***	
.3122 GSBB	L4		-60.10+03	***	
			-264.7-09	***	
-51000. GSBA	R3				
.3122-06 GSBC	03		4.000+00	***	
			19.60+00	***	
16.6 GSBA	R2		312.2-03	***	
.2647 GSBB	L2				
			3.000+00	***	
-90000. GSBA	R1		-51.00+03	***	
.1768-06 GSBC	01		-312.2-09	***	
1003.5 GSBA	R0		2.000+00	***	
.0621 GSBB	00		16.60+00	***	
			264.7-03	***	
			1.000+00	***	
			-90.00+03	***	
			-176.8-09	***	
			0.000+00	***	
			1.004+03	***	
			62.10-03	***	

* A negative sign indicates a parallel connection of elements.

** A negative sign indicates a capacitor as the reactive element.

HP-97 PRINTOUT FOR EXAMPLE 1-4.1

```

        GSBc  select log sweep
100. GSBd  load start frequency

        .1 10x calculate freq increment for 10 points per decade
1.259+00 *** multiplicative increment (manual print command)
        GSBF  load multiplicative increment

        GSBg  start analysis

```

PROGRAM OUTPUT

100.0+00	freq, Hz	316.2+00	1.000+03	3.162+03
-6.467+00	gain, dB	-6.482+00	-9.816+00	-86.07+00
-29.40+00	phase, °	-94.00+00	2.263+00	95.46+00
2.000+03	Re Z_{in}, Ω	2.000+03	5.622+03	1.005+03
208.2-03	Im Z_{in}, Ω	115.0-03	-415.8+00	932.4+00
125.9+00		398.1+00	1.259+03	3.981+03
-6.468+00		-6.493+00	-22.54+00	-102.0+00
-37.04+00		-119.2+00	-98.07+00	75.48+00
2.000+03		2.000+03	1.049+03	1.005+03
250.4-03		-723.8-03	-813.0+00	1.319+03
158.5+00		501.2+00	1.585+03	5.012+03
-6.470+00		-6.513+00	-38.24+00	-118.0+00
-46.68+00		-152.0+00	-161.3+00	59.79+00
2.000+03		1.993+03	1.013+03	1.004+03
292.3-03		-2.388+00	-139.0+00	1.772+03
199.5+00		631.0+00	1.995+03	6.310+03
-6.472+00		-6.557+00	-54.14+00	-134.0+00
-58.87+00		164.2+00	154.3+00	47.41+00
2.000+03		1.957+03	1.008+03	1.004+03
322.3-03		17.75+00	248.9+00	2.317+03
251.2+00		794.3+00	2.512+03	7.943+03
-6.476+00		-6.770+00	-70.09+00	-150.0+00
-74.33+00		101.8+00	121.1+00	37.62+00
2.000+03		1.931+03	1.006+03	1.004+03
305.9-03		275.6+00	586.1+00	2.985+03
				10.00+03
				-166.0+00
				29.86+00
				1.004+03
				3.811+03

Example 1-4.2

Over a frequency range of 8 Hz to 12 Hz using a linear sweep with 0.2 Hz steps, evaluate the transmission function and input impedance of the network shown in Fig. 1-4.3.

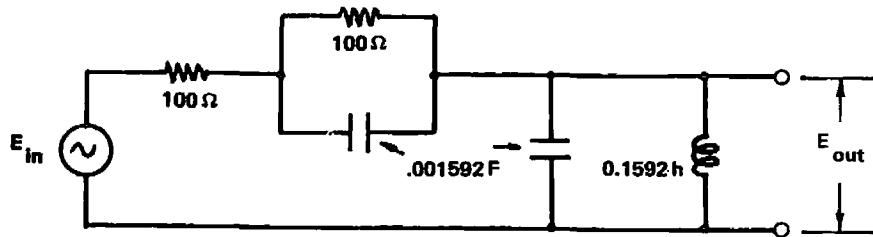


Figure 1-4.3 Network for Example 1-4.2.

The network must be redrawn with the insertion of dummy elements to place it in the ladder format meeting the program input requirements, i.e., only parallel RC or RL networks can be accommodated, not parallel LC networks. The redrawn network is shown in Fig. 1-4.4.

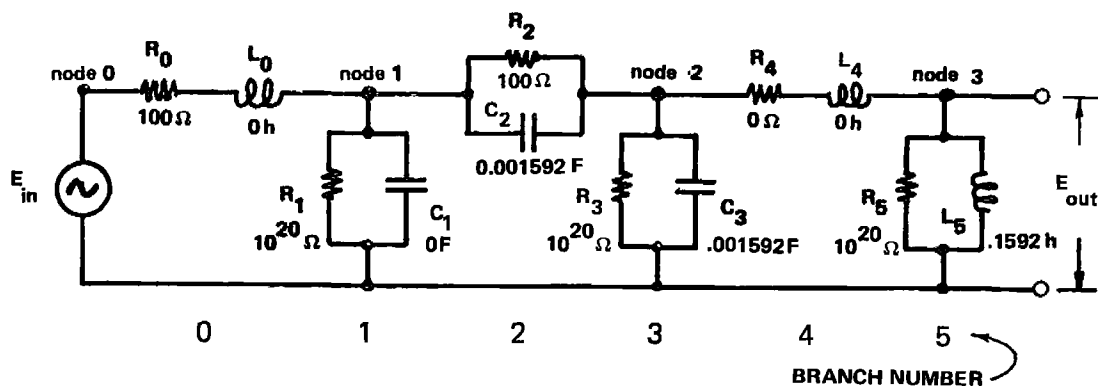


Figure 1-4.4 Network of Fig. 1-4.3 redrawn with dummy elements.

HP-97 PRINTOUT FOR EXAMPLE 1-4.2

PROGRAM INPUT	DATA REVIEW
3.00 GSBA enter # of nodes	GSBd start data review
-1.+20 GSBA R ₅ *	5.000+00 *** branch number
.159155 GSBB L ₅	-100.0+18 *** resistive part *
0. GSBA R ₄	159.2-63 *** reactive part **
0. GSBB L ₄	4.000+00 ***
-1.+20 GSBA R ₃	0.000+00 ***
1.59155-03 GSBC C ₃	0.000+00 ***
-100. GSBA R ₂	3.000+00 ***
1.59155-03 GSBC C ₂	-100.0+18 ***
-1.+20 GSBA R ₁	-1.592-03 ***
0. GSBC C ₁	2.000+00 ***
100. GSBA R ₀	-100.0+00 ***
0. GSBB L ₀	-1.592-03 ***
	1.000+00 ***
	-100.0+18 ***
	0.000+00 ***
	0.000+00 ***
	100.0+00 ***
	0.000+00 ***

* A negative sign indicates parallel connection of elements.

** A negative sign indicates a capacitor.

8. GSB _D	start frequency	} Analysis Particulars
.2 GSB _E	frequency increment	
GSB _b	select linear sweep	
GSB _e	start analysis	

PROGRAM OUTPUT

8.000+00	freq, Hz	9.000+00	10.00+00	11.00+00
-13.24+00	gain, dB	-7.123+00	-6.158-06	-7.057+00
84.42+00	phase, °	70.22+00	-414.3-06	-58.65+00
101.5+00	Re Z _{in} , Ω	101.2+00	101.0+00	100.8+00
9.915+00	Im Z _{in} , Ω	36.39+00	-13.97+06	-61.40+00
8.200+00		9.200+00	10.20+00	11.20+00
-12.23+00		-5.473+00	-928.2-03	-8.251+00
82.69+00		64.09+00	-21.06+00	-62.31+00
101.5+00		101.2+00	101.0+00	100.8+00
13.01+00		49.15+00	-262.2+00	-52.88+00
8.400+00		9.400+00	10.40+00	11.40+00
-11.13+00		-3.663+00	-2.509+00	-9.306+00
80.60+00		55.22+00	-36.38+00	-65.11+00
101.4+00		101.1+00	100.9+00	100.8+00
16.79+00		70.24+00	-137.0+00	-46.76+00
8.600+00		9.600+00	10.60+00	11.60+00
-9.930+00		-1.819+00	-4.173+00	-10.25+00
77.99+00		42.03+00	-46.69+00	-67.31+00
101.3+00		101.1+00	100.9+00	100.7+00
21.55+00		112.1+00	-95.11+00	-42.12+00
8.800+00		9.800+00	10.80+00	11.80+00
-8.602+00		-361.1-03	-5.702+00	-11.09+00
74.66+00		23.05+00	-53.70+00	-69.09+00
101.3+00		101.0+00	100.9+00	100.7+00
27.79+00		237.4+00	-74.08+00	-38.49+00
				12.00+00
				-11.86+00
				-70.55+00
				100.7+00
				-35.55+00

TI-59 PRINTOUT FOR EXAMPLE 1-4.2

DATA REVIEW		PROGRAM OUTPUT	
		0.10	freq, Hz
5.	branch #	-267.18	phase, °
-1.	20 resistive part *	-65.99	gain, dB
0.159155	reactive part **	199.01	Re Z_{in} , Ω
		-9.80	Im Z_{in} , Ω
4.			
0.		0.13	
0.		-268.46	
3.		-63.97	
-1.	20	198.44	
-0.00159155		-12.27	
2.			
-100.		0.16	
-0.00159155		-265.57	
		-61.94	
1.		197.55	
-1.	20	-15.30	
0.			
0.		0.20	
100.		-264.47	
0.		-59.89	
		196.17	
		-18.99	
		0.25	
		-263.13	
		-57.82	
		194.06	
		-23.38	
		0.32	
		-261.53	
		-55.70	
		190.91	
		-28.43	

References and Equation Derivation

The algorithm is completely described in the program description section. This particular analysis method is widely referenced. The earliest reference known to the author is T.R. Bashkow [4].

Program Listing I

001 *LBLA	LOAD RESISTOR VALUE	056 *LBLd	INPUT DATA REVIEW
002 GSB5	odd or even branch?	057 GSB4	initialize
003 F0?		058 *LBL8	review loop start
004 1/X	if odd numbered branch,	059 GSB5	odd numbered branch?
005 F0?	form $G = -1/R$	060 RCLi	recall and print branch #
006 CHS		061 PRTX	
007 ST0?	store value	062 RCLi	recall branch R or G
008 RCLi	recall branch # to display	063 F0?	
009 RTN	return control to keyboard	064 1/X	if odd branch (flag 0 set)
010 *LBLC	LOAD CAPACITOR VALUE	065 F0?	form $-1/R(1)$
011 CHS	change sign of entry	066 CHS	
012 *LBLB	LOAD INDUCTOR VALUE	067 PRTX	print branch resistance
013 GSB5	odd numbered branch?	068 P?S	
014 F0?	change sign of entry if	069 RCLi	recall branch L or C
015 CHS	branch number is odd	070 P?S	
016 P?S		071 F0?	
017 ST0?	indirectly store reactive	072 CHS	change sign if branch odd
018 P?S	element values	073 PRTX	print L or -C
019 DSZi	decrement branch number	074 SPC	
020 CF3	clr flag 3 (a NOP statement)	075 F3?	test for loop exit
021 RCLi	recall branch number	076 RTN	
022 GT0?	goto space and return	077 SF3	decrement index register
023 *LBLD	LOAD START FREQUENCY	078 DSZi	and SF3 if index is zero
024 ST08		079 CF3	
025 GT0?		080 GT08	
026 *LBLB	LOAD FREQUENCY INCREMENT	081 *LBLB	LNAP ANALYSIS START
027 ST09		082 GSB4	goto initialization
028 GT0?		083 *LBL9	analysis loop start
029 *LBLA	LOAD NUMBER OF NODES	084 GSB3	recall shunt branch elements
030 ST0E	store number of nodes	085 RCLB	recall complex node voltages
031 *LBL4	initialization routine	086 RCLA	and execute complex multiply
032 EEX		087 GSB1	
033 ST0A	$E_n = 1 + j0$	088 RCLD	recall previous complex
034 CLX		089 RCLC	branch current and perform
035 ST0B		090 GSB2	complex addition
036 ST0C		091 ST0C	
037 ST0D	$I_{2n} = 0 + j0$	092 X*Y	store complex branch
038 RCLB		093 ST0D	currents for present branch
039 ENT?	calculate and store	094 X*Y	
040 +	highest branch number	095 CF0	
041 EEX		096 DSZi	decrement index register
042 -	$Br\# = 2(\# \text{ nodes}) - 1$	097 SF0	& SF0 if index is zero
043 ST0I		098 GSB3	recall series branch elts.
044 CF3	clear data entry flag and	099 GSB1	execute complex multiply
045 GT0?	goto space and return	100 RCLB	recall complex node voltage
046 *LBLB	SET LINEAR SWEEP	101 RCLA	and add to branch voltage
047 CF1		102 GSB2	
048 CLX	place "zero" in display	103 X*Y	store new complex node
049 GT0?	goto space and return	104 ST0B	voltage
050 *LBLC	SET LOGARITHMIC SWEEP	105 X*Y	
051 SF1		106 ST0A	
052 EEX		107 DSZi	decrement branch number and
053 *LBL7	space and return subroutine	108 F0?	test for loop exit
054 SPC		109 GT09	
055 RTN		110 *P	convert to magnitude & angle

REGISTERS									
0 R ₀	1 G ₁	2 R ₂	3 G ₃	4 R ₄	5 G ₅	6 R ₆	7 G ₇	8 start	9 freq
S ₀	S ₁	S ₂	S ₃	S ₄	S ₅	S ₆	S ₇	S ₈ cmplx	S ₉ cmplx
-C ₀ or L ₀	C ₁ or -L ₁	-C ₂ or L ₂	C ₃ or -L ₃	-C ₄ or L ₄	C ₅ or -L ₅	-C ₆ or L ₆	C ₇ or -L ₇	multiply	multiply
A Re E _k	B Im E _k	C Re I _k	D Im I _k	E number of nodes	F index				

Program Listing II

111	STOA	temporarily store E_{in}	166	ST+9	ad + bc in register 9
112	LOG		167	RCL9	rc1 f = ac + bc
113	2	convert to dB	168	RCL8	rc1 e, ac - bd = e
114	0		169	P+S	restore register order
115	X		170	RTN	return to main program
116	RCL8		171	*LBL2	complex add subroutine
117	RND	recall and print present	172	X*Y	
118	PRTX	analysis frequency	173	R+	
119	R+		174	+	
120	CHS	recover and print -dB	175	R+	
121	RND		176	+	
122	PRTX		177	R+	
123	R+	recover phase angle	178	RTN	return to main program
124	STOB	temporarily store E_{in}	179	*LBL3	complex recall subroutine
125	CHS		180	RCL8	calculate $\omega = 2\pi f$
126	RND	print -(phase angle)	181	P+	
127	PRTX		182	X	
128	RCLD	recall I_0	183	ENT+	
129	RCLC		184	+	
130	+P		185	P+S	recall reactive branch
131	RCLA		186	RCLi	element, b_x , and form
132	X*Y		187	P+S	$2\pi f b_x$
133	=		188	X	
134	X*Y	perform complex division:	189	X<0?	form reciprocal if $b_x < 0$
135	RCLB		190	1/X	
136	X*Y	$Z_{in} = E_{in}/I_0$	191	RCLi	recall resistive element
137	-		192	X<0?	if <0, perform parallel
138	X*Y		193	GT03	series conversion
139	+R		194	RTN	return to main program
140	PRTX	print Re Z_{in}	195	*LBL3	parallel series conversion
141	X*Y		196	ABS	conductance \rightarrow resistance
142	PRTX	print Im Z_{in}	197	1/X	
143	PSE		198	X*Y	
144	RCL9	recall frequency increment	199	1/X	susceptance \rightarrow reactance
145	F1?		200	X*Y	
146	STX8	use multiplicative increment	201	+P	
147	F1?	if logarithmic sweep selected	202	1/X	calculate complex inverse
148	GT0e		203	+R	
149	ST+8	use additive increment if	204	RTN	return to main program
150	GT0e	linear sweep selected	205	*LBL5	odd or even branch subr
151	*LBL1	complex multiplication	206	RCL1	
152	P+S	$(a+jb)(c+jd) = e+jf$	207	2	form 0 if branch even
153	ST08	a	208	=	or 0.5 if branch odd
154	ST09	a	209	FRC	
155	R+		210	SF0	
156	ENT+		211	X=0?	set flag 0 if branch is odd
157	R+		212	CF0	
158	R+	c	213	R+	restore x register in stack
159	STX8	ac in register 8	214	RTN	return to main program
160	R+	d			
161	STX9	ad in register 9			
162	X	bd in stack			
163	ST-8	ac - bd in register 8			
164	R+				
165	X	bc in stack			

LABELS					FLAGS	SET STATUS		
A load R	B load L	C load C	D load	E load freq	0 odd	FLAGS		DISP
a load #	b set linear	c set log	d start freq	e start	1 log/lin	ON OFF	TRIG	
of nodes	sweep	sweep	data revu	analysis		0 <input type="checkbox"/>	DEG <input type="checkbox"/>	FIX
0	1 complex	2 complex	3 complex	4 initialize	2	1 <input type="checkbox"/>	GRAD <input type="checkbox"/>	SCI
	multiply	add	recall		3 data	2 <input type="checkbox"/>	RAD <input type="checkbox"/>	ENG <input type="checkbox"/>
5 odd/even	6 series \rightarrow	7 log sweep	8	9	entry	3 <input type="checkbox"/>		n 3
branch	parallel							

1-4

TI-59 PROGRAM LISTING

000	76	LBL	LOAD RESISTOR VALUE	050	44	SUM	
001	11	R		051	56	56	
002	42	STO	temporarily store	052	43	RCL	
003	57	57		053	58	58	recall reactive element to display
004	71	SBR	set flag 0 if branch number is odd	054	92	RTN	
005	04	04		055	76	LBL	LOAD SWEEP STARTING FREQ
006	18	18		056	14	5	
007	43	RCL	recall entry	057	42	STO	
008	57	57		058	55	55	
009	87	IFF	if odd branch, form $G = -1/R$	059	92	RTN	
010	00	00		060	76	LBL	LOAD FREQ INCREMENT
011	00	00		061	15	E	
012	18	18		062	42	STO	
013	12	ST*	store R or G	063	54	54	
014	59	59		064	92	RTN	
015	43	RCL	recall resistor value to display	065	76	LBL	SELECT LINEAR SWEEP
016	57	57		066	17	B'	
017	92	RTN		067	22	INV	
018	04	+	routine for $G = -1/R$	068	86	STF	
019	35	1 X		069	01	01	
020	61	GTO		070	00	0	display 0
021	00	00		071	92	RTN	
022	13	13		072	76	LBL	SELECT LOG SWEEP
023	76	LBL	LOAD CAPACITOR VALUE	073	18	C'	
024	13	C		074	86	STF	
025	54			075	01	01	
026	94	+	change sign and temporarily store	076	01	1	display 1
027	42	STO		077	92	RTN	
028	58	58		078	76	LBL	INPUT DATA REVIEW
029	76	LBL	LOAD INDUCTOR VALUE	079	19	D'	
030	12	B		080	71	SBR	
031	42	STO		081	03	03	initialize
032	58	58		082	80	80	
033	71	SBR	set flag 0 if branch number is odd	083	71	SBR	
034	04	04		084	04	04	set flag 0 if branch number is odd
035	18	18		085	18	18	
036	43	RCL	recall entry	086	53	(
037	58	58		087	43	RCL	recall branch number
038	22	INV	if branch number is odd, change the sign of the entry	088	59	59	
039	87	IFF		089	75	.	
040	00	00		090	01	1	
041	00	00		091	00	0	
042	44	44		092	54)	
043	94	+/-		093	98	ADV	
044	72	ST*	store reactive element	094	71	SBR	
045	56	56		095	04	04	print or display branch number
046	01	1	decrement index of resistive and reactive storage registers	096	66	66	
047	94	+/-		097	73	RC*	recall resistive element
048	44	SUM		098	59	59	
049	59	59		099	22	INV	

This translation was provided by Mr. Walter Ware

1-4

TI-59 PROGRAM LISTING

100	87	IFF	if odd branch, form	150	03	03	
101	00	00	R = -1/G	151	68	NOP	
102	01	01		152	68	NOP	
103	06	06		153	68	NOP	
104	35	1/X		154	61	GTO	
105	94	+/-		155	00	00	goto loop start
106	71	SBR		156	83	83	
107	04	04	display or print	157	29	CP	complex recall subr
108	66	66	resistance	158	53	(
109	73	RC*	recall reactive element	159	43	RCL	
110	56	56		160	55	55	calculate $\omega=2\pi f$
111	22	INV		161	65	X	
112	87	IFF	if odd branch,	162	89	+	
113	00	00	change sign	163	65	X	
114	01	01		164	02	2	
115	17	17		165	65	X	
116	94	+/-		166	73	RC*	recall reactive branch
117	71	SBR		167	56	56	element value and
118	04	04	print or display	168	54)	form branch immittance
119	66	66	L or C	169	77	GE	
120	87	IFF		170	01	01	if immittance is nega-
121	03	03		171	73	73	tive, form reciprocal
122	01	01	test for loop exit	172	35	1/X	
123	47	47		173	42	STD	store immittance
124	86	STF		174	58	58	
125	03	03		175	73	RC*	
126	01	1	decrement indirect	176	59	59	recall branch
127	94	+/-	storage register	177	42	STD	resistance and store
128	44	SUM	indices	178	57	57	
129	56	56		179	22	INV	
130	44	SUM		180	77	GE	if resistance negative,
131	59	59		181	01	01	perform series \rightleftharpoons parallel
132	43	RCL		182	84	84	conversion
133	09	09		183	92	RTH	
134	85	+	set t = 10	184	43	RCL	series \rightleftharpoons parallel
135	01	1		185	57	57	conversion subroutine
136	95	=		186	50	1/X	
137	32	X/T		187	35	1/X	conductance \rightleftharpoons resistance
138	43	RCL		188	32	X/T	
139	59	59	recall register index	189	43	RCL	
140	22	INV		190	58	58	
141	67	EQ	if index - 10, execute	191	35	1/X	susceptance \rightleftharpoons reactance
142	01	01	one more loop	192	94	+/-	
143	48	48		193	22	INV	
144	61	GTO		194	37	P R	
145	00	00		195	94	+	calculate complex
146	83	83		196	32	X/T	inverse
147	92	RTH		197	35	1/X	
148	22	INV	clear flag 3	198	32	X/T	
149	86	STF		199	37	P R	

1-4

TI-59 PROGRAM LISTING

200	42	STD	temporarily store	250	59	59	
201	58	58	immittance	251	71	SBR	
202	32	XIT	temporarily store	252	01	01	recall series branch
203	42	STD	resistance or cond	253	57	57	elements
204	57	57		254	43	RCL	
205	92	RTN	return to main program	255	57	57	
206	76	LBL	LNAP ANALYSIS START	256	42	STD	multiply series
207	10	E ⁴		257	01	01	impedance by complex
208	58	FIX	set display mode	258	43	RCL	branch current to
209	02	02		259	58	58	obtain series branch
210	98	ADV	advance paper	260	42	STD	voltage drop
211	98	ADV		261	02	02	
212	71	SBR		262	43	RCL	
213	03	03	initialize	263	51	51	
214	83	83		264	42	STD	
215	71	SBR		265	03	03	
216	01	01	recall shunt branch	266	43	RCL	
217	57	57		267	52	52	
218	43	RCL		268	42	STD	
219	57	57	recall complex node	269	04	04	
220	42	STD	voltage and execute	270	36	PGM	
221	01	01	complex multiply to	271	04	04	
222	43	RCL	obtain complex branch	272	13	C	
223	58	58	current	273	43	RCL	
224	42	STD		274	01	01	add complex series
225	02	02		275	44	SUM	voltage drop to previous
226	43	RCL		276	49	49	node voltage to obtain
227	49	49		277	43	RCL	next node voltage and
228	42	STD		278	02	02	store result
229	03	03		279	44	SUM	
230	43	RCL		280	50	50	
231	50	50		281	01	i	
232	42	STD		282	94	+/-	decrement indirect
233	04	04		283	44	SUM	recall indices
234	36	PGM		284	56	56	
235	04	04		285	44	SUM	
236	13	C		286	59	59	
237	43	RCL		287	43	RCL	
238	01	01	recall previous complex	288	09	09	
239	44	SUM	branch current, perform	289	32	XIT	test for loop exit
240	51	51	complex add and store	290	43	RCL	
241	43	RCL	result	291	59	59	
242	02	02		292	67	EQ	
243	44	SUM		293	02	02	
244	52	52		294	98	98	
245	01	i		295	61	GTO	
246	94	+/-	decrement indirect	296	02	02	repeat loop
247	44	SUM	recall indices	297	15	15	
248	56	56		298	43	RCL	recall present freq
249	44	SUM		299	55	55	

14

TI-59 PROGRAM LISTING

300	71	SBR	print or display frequency	350	04	04	
301	04	04		351	66	66	
302	66	66		352	43	RCL	
303	49	RCL		353	02	02	
304	49	49	recall complex input voltage	354	71	SBR	print or display $\text{Im } Z_{in}$
305	32	X/T		355	04	04	
306	3	RCL		356	66	66	
307	50	50		357	43	RCL	recall frequency increment
308	22	INT	convert to polar	358	54	54	
309	4	P/R		359	37	IFF	
310	04	+	change sign of angle and store	360	01	01	jump if log sweep selected
311	42	STD		361	03	03	
312	05	05		362	68	68	
313	71	SBR	print or display angle of network transmission function	363	44	SUM	
314	04	04		364	55	55	add frequency increment for linear sweep
315	66	66		365	61	GTO	
316	32	X/T		366	02	02	
317	28	LOG	calculate 20 log of network transmission function magnitude	367	06	06	
318	94	+/-		368	49	PRD	
319	65	x		369	55	55	multiply by frequency increment for log sweep
320	02	2		370	61	GTO	
321	00	0		371	02	02	
322	95	=		372	06	06	
323	42	STD		373	76	LBL	LOAD NUMBER OF NODES
324	06	06		374	16	A ²	
325	71	SBR	print or display dB response	375	71	SBR	
326	04	04		376	04	04	test for printer
327	66	66		377	75	75	
328	43	RCL		378	42	STD	store number of nodes
329	49	49		379	53	53	
330	42	STD	recall complex network input voltage	380	09	9	initialization subr
331	01	01		381	42	STD	set minimum loop counter value allowed
332	43	RCL		382	09	09	
333	50	50		383	53	(
334	42	STD		384	43	RCL	
335	02	02		385	53	53	
336	43	RCL		386	65	x	calculate highest branch number storage index for real immittance storage
337	51	51		387	02	2	
338	42	STD	recall complex network input current	388	75	-	
339	03	03		389	01	1	
340	43	RCL		390	85	+	
341	52	52		391	01	1	
342	42	STD		392	00	0	
343	04	04		393	54)	
344	36	PGM		394	42	STD	
345	04	04	perform complex division	395	59	59	
346	18	C ²		396	85	+	calculate highest branch number storage index for imaginary immittance storage
347	43	RCL		397	01	1	
348	01	01	print or display $\text{Re } Z_{in}$	398	00	0	
349	71	SBR		399	54)	

1-4

TI-59 PROGRAM LISTING

400	42	STD		450	00	0	
401	56	56		451	00	0	
402	01	1		452	00	0	
403	42	STD	initialize node voltage	453	00	0	
404	49	49	of highest node:	454	00	0	
405	00	0		455	00	0	
406	42	STD	$E_n = 1 + j0$	456	00	0	
407	50	50		457	00	0	
408	42	STD	initialize $I_{2n} = 0 + j0$	458	00	0	
409	51	51		459	00	0	
410	42	STD		460	00	0	
411	52	52		461	00	0	
412	22	INV		462	00	0	
413	86	STF	clear flag 3	463	00	0	
414	03	03		464	00	0	
415	43	RCL	recall number of nodes	465	00	0	
416	53	53		466	22	INV	print or R/S routine
417	92	RTN	return to main program	467	87	IFF	
418	29	CP	odd or even branch subr	468	05	05	
419	22	INV		469	04	04	
420	86	STF	clear flag 0	470	73	73	
421	00	00		471	91	R/S	
422	43	RCL		472	92	RTN	
423	59	59		473	99	PRT	
424	55			474	92	RTN	printer sense routine
425	02	2		475	69	DP	
426	54			476	08	08	
427	22	INV		477	86	STF	
428	59	INT		478	05	05	
429	67	EQ		479	92	RTN	
430	04	04					
431	34	34					
432	86	STF	set flag 0 if branch				
433	00	00	number is odd				
434	92	RTN					
435	00	0	unused program memory				
436	00	0					
437	00	0					
438	00	0					
439	00	0					
440	00	0					
441	00	0					
442	00	0					
443	00	0					
444	00	0					
445	00	0					
446	00	0					
447	00	0					
448	00	0					
449	00	0					
450	00	0					

REGISTER ALLOCATIONS FOR TI-59

register number	contents	
0		40
1	Re	41
2	Im	42
3	Re	43
4	Im	44
5		45
6	xmsn fcn magnitude	46
7		47
8		48
9	loop counter	49
10		50
11		51
12		52
13		53
14		54
15		55
16		56
17		57
18		58
19		59
20		
21		
22		
23		
24		
25		
26		
27		
28		
29		
30		
31		
32		
33		
34		
35		
36		
37		
38		
39		
40		

complex arith
temp storage

loop counter

real
immittance
storage

imaginary
immittance
storage

Re node V sum
Im node V sum
Re branch I
Im branch I
of nodes
freq increment
start freq
Im storage index
temp store
temp store
Re storage index

PROGRAM 1-5 LC - L N A P , LC LADDER NETWORK ANALYSIS PROGRAM.

Program Description and Equations Used

This program evaluates the frequency response and input impedance of a resistively terminated lossless (LC) ladder network having up to seven branches. The frequency response is provided as magnitude (dB) and phase (degrees, radians, or grads), and the input impedance is provided as real and imaginary parts.

The input impedance is the impedance seen by the voltage generator in the source. It is more common to calculate the input impedance at the input terminals of the lossless ladder network, but this way was not implemented because program steps are not available for the coding to recall the source resistor value and subtract it from the real part of the input impedance. If the program feature of allowing the number of branches to be entered via a user definable key (key "a") is sacrificed, and the number of branches is stored into register E, then the additional coding for calculating the network input impedance can be added to the program by deleting steps 028 and 029 and adding "RCL0," "-" after step 097 (099 before deletions).

The frequency response and input impedance evaluation frequency can be incremented in either a linear manner using an additive increment, or a logarithmic manner using a multiplicative increment. Each branch of the network may contain an inductor (L), a capacitor (C), a series LC network, or a parallel LC network. All element values and interconnection topology are stored, and can be reviewed at any time to check or correct the component values or interconnection.

Because of the available number of HP-67/97 registers, the number of branches cannot exceed seven. The TI-59 can accommodate data for 20 branches. Elements that inhibit signal flow through the network are not allowed, and will cause the program execution to halt displaying "Error." Examples of elements that inhibit signal flow are single shunt resistors or inductors that have zero value, or series capacitors in series

branches that have zero value.

The algorithm used by this program is the same as used in Program 1-4 where 1 volt is assumed at the network output, and the required input voltage is calculated. In this program, the branch immittances (impedances or admittances) are purely imaginary, and the branch numbers start with branch #1 instead of branch #0. This changes all indices by +1. The difference is necessary to let the DSZ instruction operation allow the source resistance to be added to branch #1 with minimum coding. The load resistance is combined with the last branch immittance. If the number of branches is odd, the last branch consists of the load resistor alone.

User Instructions

LC-LNAP, LC LADDER NETWORK ANALYSIS PROGRAM				
load # of branches	linear sweep?	log sweep?	review input data	start analysis
load R_L , R_S	load br C	load br L	load start frequency	load freq increment

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of magnetic card			
2	Load the number of branches in the network	# branches	<input type="button" value="f"/> <input type="button" value="A"/>	
3	Enter the load and source resistances in ohms	R_L R_S	<input type="button" value="ENT ↑"/> <input type="button" value="A"/>	
4	Load branch capacitance; If a parallel tank in a series branch, or a series tank in a shunt branch, change the sign of the mantissa in the capacitor value	$\pm C_{\text{branch}}$ (farads)	<input type="button" value="B"/>	
	Start loading network capacitors (and inductors) from the highest numbered branch (load resistor end)			
5	Load branch inductance; If a parallel tank in a series branch, or a series tank in a shunt branch, change the sign of the mantissa in the inductor value	$\pm L_{\text{branch}}$ (henries)	<input type="button" value="C"/>	
6	Input data review (optional)		<input type="button" value="f"/> <input type="button" value="D"/>	R_{load} space highest branch # $\pm C$ $\pm L$ space : R_{source}
	Negative element values indicate series tanks in shunt branches, or parallel tanks in series branches			
7	Select frequency sweep mode: a) linear sweep b) logarithmic sweep		<input type="button" value="f"/> <input type="button" value="B"/> <input type="button" value="f"/> <input type="button" value="O"/>	
8	Load start frequency for sweep in hertz	f_{start}	<input type="button" value="D"/>	

LC-LNAP, LC LADDER NETWORK ANALYSIS PROGRAM			
	CONTINUED		2

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
9	Load frequency increment	f_{incr}	E	
	If linear sweep, the increment is added to the present frequency to obtain the next frequency.			
	If logarithmic sweep, the increment is multiplied by the present frequency to obtain the next frequency.			
10	Start analysis		f E	freq (Hz) gain (dB) phase* () Re $Z_{in, \Omega}$ Im $Z_{in, \Omega}$ space : :
	* The phase units will be in whatever trig mode the calculator is set. The trig mode is at the discretion of the user.			
11	Stop analysis: Press R/S when the printer starts to print.			
	Pressing R/S at other times may leave the registers interchanged. To determine if an interchange has occurred, goto step 6 and review input data. If L and C values are reversed, execute a P \rightarrow S instruction from the keyboard.			

Example 1-5.1

Bartlett's bisection theorem [53], [56], [57] has been applied to an equally terminated (1000 ohm) third order Butterworth bandpass filter with 10 kHz center frequency and 1 kHz bandwidth to produce the unequally terminated LC filter shown in Fig. 1-5.1. The source resistance is 1000 ohms and the load resistance is 10000 ohms. Determine the frequency response and input impedance of this LC network over a frequency range of 9000 Hz to 10900 Hz using a linear sweep with 100 Hz steps.

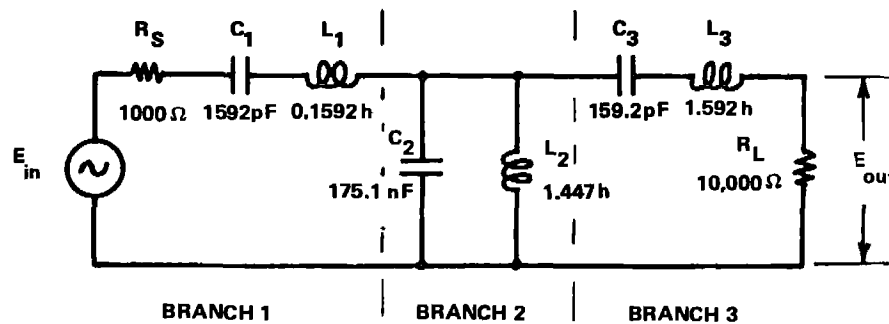


Figure 1-5.2 Network for Example 1-5.1.

PROGRAM INPUT		DATA REVIEW	
3.00 GSBa	number of branches	GSBd	start review
10000. ENTt	R _L	10.00+03 ***	load resistance
1000. GSBA	R _S	3.000+00 ***	branch number
159.2-12 GSBB	C ₃	159.2-12 ***	C
1.592 GSBC	L ₃	1.592+00 ***	L
.1751-06 GSBB	C ₂	2.000+06 ***	branch number
1.447-03 GSBC	L ₂	175.1-09 ***	C
		1.447-03 ***	L
1592.-12 GSBB	C ₁	1.000+00 ***	branch number
.1592 GSBC	L ₁	1.592-09 ***	C
		159.2-05 ***	L
GSBb	linear sweep	1.000+03 ***	source resistance
9000.00 GSED	start freq , Hz		
100.00 GSBE	freq incr , Hz		

HP-97 PRINTOUT FOR EXAMPLE 1-5.1

GSBe start analysis

PROGRAM OUTPUT

9000.00 freq, Hz	9500.00	10000.00	10500.00
-20.29 gain, dB	-4.14	-0.83	-3.58
-146.92 phase, °	138.09	-0.48	-132.20
1003.54 Re Z_{in} , Ω	1042.21	10994.89	1048.18
-1666.97 Im Z_{in} , Ω	-93.28	-227.42	10.31
9100.00	9600.00	10100.00	10600.00
-17.44	-1.93	-0.83	-6.35
-154.43	106.39	-23.45	-157.06
1005.32	1083.75	2916.29	1027.54
-1391.66	364.31	-3831.85	363.73
9200.00	9700.00	10200.00	10700.00
-14.32	-1.04	-0.84	-9.45
-164.23	74.86	-47.28	-175.59
1008.28	1186.21	1504.60	1016.80
-1105.20	979.39	-1965.91	668.18
9300.00	9800.00	10300.00	10800.00
-10.93	-0.85	-1.01	-12.47
-177.51	47.27	-73.45	170.95
1013.48	1498.05	1195.73	1010.80
-801.44	1951.68	-1020.61	941.35
9400.00	9900.00	10400.00	10900.00
-7.40	-0.83	-1.76	-15.27
163.89	22.71	-102.68	160.95
1023.10	2964.18	1091.62	1007.25
-470.17	3870.77	-426.27	1193.23

Example 1-5.2

The filter shown in Fig. 1-5.3 is a 5th order, 30° modular angle, 50% reflection coefficient elliptic filter designed for 10 kHz cutoff frequency and 1000 ohm impedance level. This example shows how dummy elements are inserted to place the filter in proper ladder format for this program. The frequency response and input impedance are calculated with the analysis frequency being logarithmically swept from 1 kHz to 100 kHz using 10 points per decade.

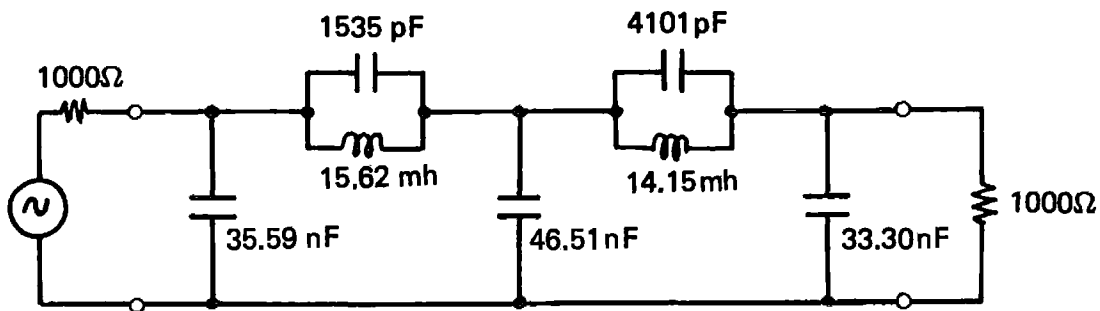


Figure 1-5.3 Elliptic filter for Example 1-5.2.

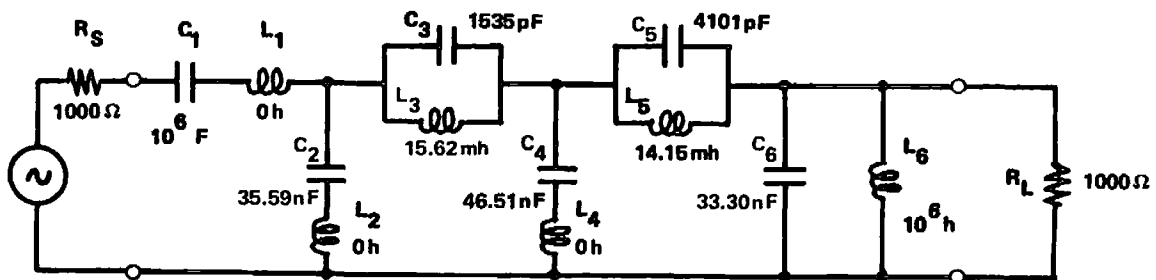


Figure 1-5.4 Network of Fig. 1-5.3 redrawn with dummy elements to place in proper ladder format for program input.

HP-97 PRINTOUT FOR EXAMPLE 1-5.2

PROGRAM INPUT	DATA REVIEW
6.00 GSBa # of branches	GSBd start review
1000. ENT↑ enter load R	1.000+03 *** load resistance
GSBA enter source R	6.000+00 *** branch number
.03330-06 GSBb C ₆	33.30-09 *** C
1.+06 GSBC L ₆ (dummy)	1.000+06 *** L
-4101.-12 GSBb C ₅ (note minus)	5.000+00 *** branch number
-14.15-03 GSBC L ₅ " "	-4.101-09 *** C
-04651-06 GSBb C ₄	-14.15-03 *** L
0. GSBC L ₄ (dummy)	4.000+00 *** branch number
-1535.-12 GSBb C ₃ (note minus)	-46.51-09 *** C
-15.62-03 GSBC L ₃ " "	0.000+00 *** L
-03559-06 GSBb C ₂	3.000+00 *** branch number
0. GSBC L ₂ (dummy)	-1.535-09 *** C
1.+06 GSBb C ₁ (dummy)	-15.62-03 *** L
0. GSBC L ₁ (dummy)	2.000+00 *** branch number
GSBc log sweep	-35.59-09 *** C
1000. GSBd start freq	0.000+00 *** L
.10 10 ^x increment for	1.000+00 *** branch number
GSBE 10 points per	1.000+06 *** C
decade	0.000+00 *** L
	1.000+03 *** source resistance

HP-97 PRINTOUT FOR EXAMPLE 1-5.2

DSF3 set display format
GSBe start analysis

PROGRAM OUTPUT			
1000.000	freq, Hz	3162.278	10000.000
-6.304	gain, dB	-7.265	31622.777
-25.492	phase, °	-71.409	-95.872
1731.945	Re Z_{in} , Ω	46.462	106.137
-354.815	Im Z_{in} , Ω	2425.429	1000.000
		-1314.534	-141.760
1258.925		3981.072	12589.254
-6.445		-7.140	39810.717
-31.679		-29.301	-80.704
1641.443		-87.812	-77.360
-367.449		-34.999	1000.000
		1001.496	1000.000
		-520.507	-110.753
1584.893		5011.872	15848.932
-6.636		-6.543	50118.724
-39.149		-48.256	-77.037
1545.329		-53.026	-80.045
-354.383		1000.017	1000.000
		-334.325	-87.088
1995.262		6309.573	19952.623
-6.872		-6.035	63095.735
-48.061		-75.897	-76.495
1455.184		-62.745	-82.135
-312.318		1000.000	1000.000
		-242.424	-68.745
2511.886		7943.282	25118.864
-7.114		-7.176	79432.824
-58.642		-76.839	-77.128
1383.210		110.795	-83.773
-242.073		1466.092	1000.000
		-532.050	1000.000
			-54.393
			100000.000
			-78.338
			-85.064
			1000.000
			-43.101

Program Listing I

001 *LBLP	LOAD R _L +R _s	057 GSB2	add complex branch currents
002 ST00	store R _s	058 ST0C	store next lower branch
003 R _L		059 XZY	current (complex)
004 PZS		060 ST0D	
005 ST00	store R _L	061 DSZ1	decrement branch number
006 PZS		062 GSB3	recall series branch Z
007 GT07	goto space and return	063 CLX	
008 *LBLC	LOAD BRANCH INDUCTANCE	064 RCL0	
009 CHS	indicate inductance by chs	065 CF0	
010 PZS	interchange registers and	066 DSZ1	If branch 1, add
011 GSB6	goto capacitor load routine	067 SF0	source resistance to
012 PZS		068 F0?	branch impedance
013 DSZ1	decrement and recall branch	069 CLX	
014 RCL1		070 ENT↑	
015 ST07	goto space and return	071 RCLD	recall present
016 *LBLB	LOAD BRANCH CAPACITANCE	072 RCLC	branch current
017 GSB5	odd/even branch?	073 GSB1	calculate branch voltage
018 F0?	change sign of entry if	074 RCLA	recall next higher
019 CHS	branch number is odd	075 RCLB	branch voltage
020 ST01	store entry	076 GSB2	add branch voltages
021 RTN	return control to keyboard	077 ST0A	
022 *LBLD	LOAD START FREQUENCY	078 XZY	store next lower
023 ST08		079 ST0B	node voltage
024 GT07		080 F0?	test for loop exit
025 *LBLE	LOAD FREQUENCY INCREMENT	081 GT09	
026 ST09		082 XZY	
027 GT07		083 →P	convert to magnitude & angle
028 *LBLA	LOAD NUMBER OF BRANCHES	084 LOG	
029 ST0E		085 2	
030 *LBL4	initialization routine	086 0	calculate magnitude in dB
031 EEX		087 X	
032 ST0A	$E_n = 1 + j0$	088 RCL8	recall present frequency
033 CLX		089 SF0	indicate sign change in p/o
034 ST0B		090 GSB0	gosub printout (p/o) routine
035 ST0C		091 RCLD	
036 ST0D	$I_{2n+1} = 0 + j0$	092 CHS	
037 RCLC	set index to	093 RCLC	recall branch 1 current (I_0)
038 ST01	highest branch number	094 →P	and form complex inverse
039 SF2	initialize flags	095 1/X	
040 CF3		096 →R	
041 GT07	goto space and return	097 RCLB	recall node 0 voltage (E_{in})
042 *LBL6	SELECT LINEAR SWEEP	098 RCLA	
043 CF1		099 GSB1	perform complex multiply
044 GT07		100 PRTX	print Re Z_{in}
045 *LBLC	SELECT LOGARITHMIC SWEEP	101 XZY	
046 SF1		102 PRTX	print Im Z_{in}
047 GT07		103 RCL9	recall frequency increment
048 *LBLE	START ANALYSIS	104 F1?	
049 GSB4	initialize	105 STX8	multiply present frequency
050 *LBL9	analysis loop start	106 F1?	by increment if log sweep
051 GSB3	recall shunt branch Y	107 GT0E	
052 RCLB	recall complex node voltage	108 ST+8	add increment to present
053 RCLA		109 GT0E	frequency if linear sweep
054 GSB1	calculate shunt branch I	110 *LBLJ	INPUT DATA REVIEW
055 RCLC	recall next higher (series)	111 GSB4	initialize registers & flags
056 RCLD	branch current	112 PZS	

REGISTERS									
0 R _s	1 O ₁	2 O ₂	3 O ₃	4 O ₄	5 O ₅	6 O ₆	7 O ₇	8 present frequency	9 freq increment
S0 R _L	S1 L ₁	S2 L ₂	S3 L ₃	S4 L ₄	S5 L ₅	S6 L ₆	S7 L ₇	S8 cmplx multiply	S9 cmplx multiply
A Re E _k	B Im E _k	C Re I _j	D Im I _j	E number of branches	F index				

A-1000 Program									
LABELS					FLAGS		SET STATUS		
A load R _L + R _s	B load C _i	C load L _i	D load start freq	E load freq incr	0 odd br	1 log swp	2 first time thru loop	3	
113 RCL0	114 P+S	115 PRTX	116 *LBL8 data review loop start	117 GSB5 odd/even branch?	118 P+S	119 RCLi	120 P+S	121 CHS	122 RCLi
123 PCLi	124 SPC	125 GSB0	126 DSZi	127 GT08	128 RCL0	129 SPC	130 PRTX	131 *LBL7	132 SPC
133 RTN	134 *LBL0	135 PRTX	136 GSB0	137 *LBL0	138 R↓	139 F0?	140 CHS	141 PRTX	142 RTN
143 *LBL1	144 P+S	145 ST08	146 ST09	147 R↓	148 ENT↑	149 R↓	150 R↓	151 ST×8	152 R↓
153 ST×9	154 ×	155 ST-8	156 R↓	157 ×	158 ST+9	159 RCL9	160 RCL8	161 P+S	162 RTN
163 *LBL2	164 R↓	165 +	166 R↓	167 +	168 R↓				
169 RTN	170 *LBL7	171 GSB5	172 RCL8	173 Pi	174 ×	175 ENT↑	176 +	177 ENT↑	178 ENT↑
179 RCLi	180 X<0?	181 SF3	182 ×	183 X<0?	184 1/X	185 X×Y	186 P+S	187 RCLi	188 P+S
189 ×	190 X<0?	191 1/X	192 +	193 F0?	194 F3?	195 F3?	196 GSB3	197 F2?	198 GT08
199 0	200 RTN	201 *LBL3	202 1/X	203 CHS	204 RTN	205 *LBL0	206 F0?	207 0	208 P+S
209 RCL0	210 P+S	211 1/X	212 F0?	213 ISZi	214 RTN	215 *LBL5	216 RCLi	217 2	218 =
219 FRC	220 SF0	221 X=0?	222 CF0	223 R↓	224 RTN				

PROGRAM 1-6 EQUIVALENT INPUT NOISE OF AN AMPLIFIER WITH GENERALIZED INPUT COUPLING NETWORK

Program Description and Equations Used

When low noise amplifiers are designed, the amplifier equivalent current and voltage noise densities (noise in a 1 Hz band), and the coupling network noise sources, response, and impedance behavior must be considered. This program calculates the total noise voltage density that is reflected to the amplifier input which is coupled to a sensor by means of a transformer (Fig. 1-6.1).

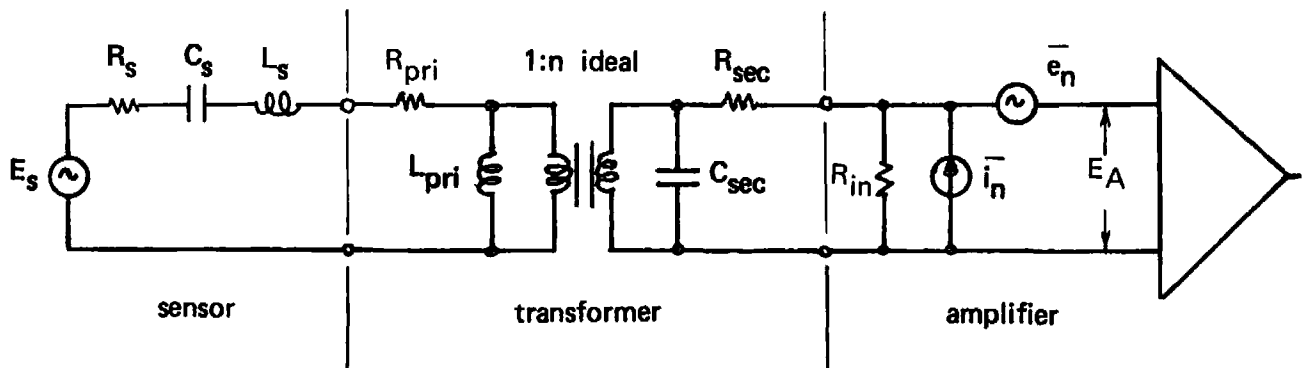


Figure 1-6.1 Generalized input coupling network.

The transformer model includes the turns ratio (1:n), the primary and secondary resistances (R_{pri} and R_{sec}), the primary inductance (L_{pri}), and the secondary capacitance (C_{sec}). The coupling network noise sources include: the thermal noise densities (Johnson noise) of the transformer primary and secondary resistances and of the source resistance, the amplifier equivalent voltage noise density (\bar{e}_n), and the equivalent noise voltage density generated by the amplifier current noise density (\bar{i}_n) flowing through the coupling network impedance presented to the amplifier input.

The noise voltage density of each noise source is reflected to the amplifier input through the network gain (at the analysis frequency) from the noise source location to the amplifier input. The total noise reflected to the amplifier input is calculated from the root-sum-squared (RSS) values of the individual contributions.


The sensor is represented by a voltage source (E_s) and a series LRC network (L_s , R_s , and C_s). The inductance may be set to zero if not needed, and the capacitor may be set to 10^{50} farads to remove its contribution. The sensor resistance may be zero if the transformer primary resistance is not zero and vice-versa.

The equivalent circuit can be modified to reflect the transformer secondary capacitance to the primary if desired by deleting steps 059, 060, and 061 in the program. The primary capacitance is now loaded in step 2f of the users' instructions. This modification allows piezoelectric transducer elements to be modeled as the source. R_{pri} is set to zero, and the transformer primary capacitance is used to represent the clamped capacity of the piezoelectric element.

If the transformer is not wanted in the circuit, the turns ratio should be set to one.

The equations are derived using nodal analysis, and the user is referred to the section following Example 1-6.2 for details.

User Instructions

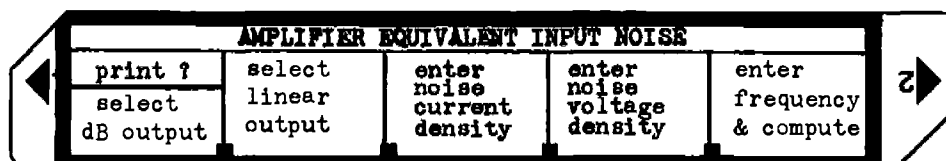

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of the program card			
2	Load network element values			
	a) sensor resistance, ohms	R_s	<input type="button" value="STO"/> <input type="text" value="0"/>	
	b) sensor capacitance, farads	C_s	<input type="button" value="STO"/> <input type="text" value="1"/>	
	c) sensor inductance, henries	L_s	<input type="button" value="STO"/> <input type="text" value="2"/>	
	d) transformer primary resistance, Ω	R_{pri}	<input type="button" value="STO"/> <input type="text" value="3"/>	
	e) transformer primary inductance, h	L_{pri}	<input type="button" value="STO"/> <input type="text" value="4"/>	
	f) xfmr secondary capacitance, farads	C_{sec}	<input type="button" value="STO"/> <input type="text" value="5"/>	
	g) xfmr secondary resistance, ohms	R_{sec}	<input type="button" value="STO"/> <input type="text" value="6"/>	
	h) amplifier input resistance, ohms	R_{in}	<input type="button" value="STO"/> <input type="text" value="7"/>	
	i) transformer turns ratio	n	<input type="button" value="STO"/> <input type="text" value="8"/>	
3	Select output mode			
	a) for voltages in dBV and network gain in dB		<input type="button" value="A"/>	
	b) for voltages in volts, and network gain as a voltage ratio		<input type="button" value="B"/>	
4	Select print (1) / run-stop (0) option		<input type="button" value="f"/> <input type="text" value="A"/>	0,1
5	Enter amplifier input noise current density	$\bar{i}_n, A/\sqrt{Hz}$	<input type="button" value="C"/>	
6	Enter amplifier input noise voltage density	$\bar{e}_n, V/\sqrt{Hz}$	<input type="button" value="D"/>	
7	Enter analysis frequency and compute output	f, Hz	<input type="button" value="E"/>	gain space \bar{e}_1 \bar{e}_2 \bar{e}_3 \bar{e}_n, amp $\bar{i}_n * Z, amp$ space RSS noise space space
	Note: All noise voltages are reflected to the amplifier input, i.e., the gain of the network from the noise voltage source to the amplifier input is taken into account.			
8	For another case, go back to steps 2 thru 6 as required			

Example 1-6.1

A type 2N4867A low-noise field effect transistor (FET) is to be used as a preamplifier for a piezoelectric hydrophone. A frequency range of 10 Hz to 1000 Hz is to be covered. The hydrophone is operating well below its self-resonant frequency, hence, its equivalent circuit is accurately represented by a 4000 pF capacitor in series with a 10 ohm resistor. To avoid preamplifier overload problems from cable flutter and other subsonic signals, the input resistance of the preamplifier is chosen to provide a 50 Hz low frequency break with the hydrophone capacity. The hydrophone will be coupled to the preamp without using a transformer, therefore a dummy turns ratio of 1:1 will be used in the program. The current and voltage noise densities for the 2N4867A are listed in Table 1-6.1.

Table 1-6.1 Current and voltage noise densities of
2N4867A operating at drain current I_{dss} .

Frequency, Hz	\bar{i}_n , noise A/ $\sqrt{\text{Hz}}$	\bar{e}_n , noise V/ $\sqrt{\text{Hz}}$
10	6×10^{-16}	7.0×10^{-9}
20	6×10^{-16}	5.3×10^{-9}
50	6×10^{-16}	4.1×10^{-9}
100	6×10^{-16}	3.6×10^{-9}
200	6.1×10^{-16}	3.2×10^{-9}
500	6.2×10^{-16}	2.8×10^{-9}
1000	6.3×10^{-16}	2.7×10^{-9}

The HP-97 printout is shown on the next page. Dummy values have been entered for unused components to remove their contribution.

HP-97 PRINTOUT FOR EXAMPLE 1-6.1

PROGRAM INPUT

```

10.0 ST00 sensor resistance
4.-09 ST01 sensor capacitance
0.0 ST02 sensor inductance
0.0 ST03 primary resistance
1.+50 ST04 primary inductance
0.0 ST05 secondary capacitance
1.0 ST06 secondary resistance
RCL1
50.0 X
    Pi
    4
    2.2 X
    1/X
795774.7 ***
ST07
1.0 ST08 n, xfmr turns ratio
GSBA select dB/dBV output

```

PROGRAM OUTPUT

```

6.-16 GSBC  $\bar{I}_n$  @ 10 Hz.
7.-09 GSBD  $\bar{e}_n$  @ 10 Hz
10.0 GSBE frequency

-14.1 ***  $A_v$ , network gain, dB

-202.1 ***  $R_s + R_{pri}$  thermal noise, dBV
-212.1 ***  $R_{sec}$  thermal noise, dBV
-139.1 ***  $R_{in}$  thermal noise, dBV
-163.1 ***  $\bar{e}_n$ , transistor
-186.6 ***  $\bar{I}_n * Z$  equiv noise, dBV

-139.1 *** total noise (RSS), dBV

```

```

5.3-09 GSBD  $\bar{e}_n$  @ 20 Hz *
20.0 GSBE frequency

-8.6 ***

-196.5 ***
-206.5 ***
-139.5 ***
-165.5 ***
-187.1 ***

-139.5 *** total noise at 20 Hz

```

```

4.1-09 GSBD  $\bar{e}_n$  @ 50 Hz
50.0 GSBE frequency

-3.0 ***

-190.9 ***
-200.9 ***
-141.9 ***
-167.7 ***
-189.4 ***

-141.9 *** total noise at 50 Hz

```

```

3.6-09 GSBD  $\bar{e}_n$  @ 100 Hz.
100.0 GSBE frequency

```

```

-1.0 ***

-188.9 ***
-198.9 ***
-145.9 ***
-168.9 ***
-193.4 ***

-145.9 *** total noise at 100 Hz

```

```

6.1-16 GSBC  $\bar{I}_n$  @ 200 Hz
3.2-09 GSBD  $\bar{e}_n$  @ 200 Hz
200.0 GSBE frequency

```

```

-0.3 ***

-168.2 ***
-198.2 ***
-151.2 ***
-169.9 ***
-196.6 ***

-151.1 *** total noise at 200 Hz

```

```

6.2-16 GSBC  $\bar{I}_n$  @ 500 Hz
2.8-09 GSBD  $\bar{e}_n$  @ 500 Hz
500.0 GSBE frequency

```

```

0.0 ***

-188.0 ***
-198.0 ***
-158.9 ***
-171.1 ***
-206.2 ***

-158.7 *** total noise at 500 Hz.

```

```

6.3-16 GSBC  $\bar{I}_n$  @ 1000 Hz
2.7-09 GSBD  $\bar{e}_n$  @ 1000 Hz
1000.0 GSBE frequency

```

```

0.0 ***

-187.9 ***
-197.9 ***
-164.9 ***
-171.4 ***
-212.0 ***

-164.0 *** total noise at 1000 Hz

```

Example 1-6.1 continued

This example points up one of the problems associated with using the characteristics of the sensor impedance along with the amplifier input resistance to effect frequency shaping. It will be noticed that the dominant source of noise comes from the thermal noise of the input resistor. The low noise characteristics of the input transistor are buried by the input resistor noise contribution.

If the input resistor is made larger, the noise contribution of the input resistor will be less. Although this statement may seem backwards, the logic may be seen by looking at the input resistor and its noise generator as a Norton equivalent source instead of a Thevenin equivalent as is presently used. In this light, one can see that the injected noise current is proportional to $1/\sqrt{R}$. Since other circuit impedances are unchanged, lower injected noise current means lower input resistor noise contribution.

The input resistor noise contribution may also be reduced by lowering the sensor impedance to lower the noise voltage resulting from the input resistor noise current.

To illustrate the above point, the example is rerun using a larger input resistor; 100 megohms is used instead of 796 kilohms. The HP-97 printout for this case is shown on the next page. The noise contribution of the input resistor loses dominance above 500 Hz in this case.

Fortunately, the ocean self noise is greatest at low frequencies, and low noise performance is less critical here.

EXAMPLE 1-6.1 CONTINUED

PROGRAM INPUT		
100.+06	ST07	store new R_{in}
	PREG	print registers to show currently stored values
10.00+00	0	sensor resistance
4.000-09	1	sensor capacitance
0.000+00	2	sensor inductance
0.000+00	3	primary resistance
100.0+48	4	primary inductance
0.000+00	5	secondary capacitance
1.000+00	6	secondary resistance
100.0+06	7	input resistance
1.000+00	8	xfr turns ratio
PROGRAM OUTPUT		
6.-16	GSEC	\bar{i}_n @ 10 Hz
7.-09	GSBD	\bar{e}_n @ 10 Hz
10.	GSBE	frequency
0.0	***	A_v , network gain, dB
-187.9	***	$R_s + R_{pri}$ thermal noise, dBV
-197.9	***	R_{sec} thermal noise, dBV
-145.9	***	R_{in} thermal noise, dBV
-163.1	***	\bar{e}_n , transistor, dBV
-172.4	***	$\bar{i}_n \times 2$ equiv. noise, dBV
-145.6	***	total noise (RSS), dBV
3.6-09	GSBD	\bar{e}_n @ 100 Hz
100.0	GSBE	frequency
0.0	***	
-187.9	***	
-197.9	***	
-165.9	***	
-168.9	***	
-192.4	***	
-164.1	***	total noise at 100 Hz
6.1-16	GSEC	\bar{i}_n @ 200 Hz
3.2-09	GSBD	\bar{e}_n @ 200 Hz
200.0	GSBE	frequency
0.0	***	
-187.9	***	
-197.9	***	
-171.9	***	
-169.9	***	
-198.3	***	
-167.7	***	total noise at 200 Hz
5.3-09	GSBD	\bar{e}_n @ 20 Hz *
20.0	GSBE	frequency
0.0	***	
		* \bar{i}_n is unchanged from the last entry.
-187.9	***	
-197.9	***	
-151.9	***	
-165.5	***	
-178.5	***	
-151.7	***	total noise at 20 Hz
6.2-16	GSEC	\bar{i}_n @ 500 Hz
2.3-09	GSBD	\bar{e}_n @ 500 Hz
500.0	GSBE	frequency
0.0	***	
-187.9	***	
-197.9	***	
-179.9	***	
-171.1	***	
-206.1	***	
-170.4	***	total noise at 500 Hz
4.1-09	GSBD	\bar{e}_n @ 50 Hz
50.0	GSBE	frequency
0.0	***	
-187.9	***	
-197.9	***	
-159.5	***	
-167.7	***	
-166.4	***	
-159.2	***	total noise at 50 Hz
6.3-16	GSEC	\bar{i}_n @ 1000 Hz
2.7-09	GSBD	\bar{e}_n @ 1000 Hz
1000.0	GSBE	frequency
0.0	***	
-187.9	***	
-197.9	***	
-165.9	***	
-171.4	***	
-212.0	***	
-171.1	***	total noise at 1000 Hz

Example 1-6.2

A small hydrophone is to be matched to a low-noise preamplifier for optimum noise performance at 30 kHz. The hydrophone equivalent circuit is shown in Fig. 1-6.2. The amplifier input transistor will be a 2N4867A FET operating at a drain current of I_{dss} .

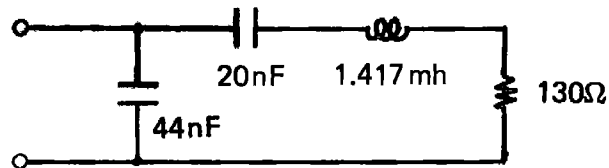


Figure 1-6.2 Hydrophone equivalent circuit.

Table 1-6.2 Current and voltage noise densities of 2N4867A operating at I_{dss} .

Frequency, kHz	$\overline{i_n},$ A/ $\sqrt{\text{Hz}}$	$\overline{e_n},$ V/ $\sqrt{\text{Hz}}$
10	8.0×10^{-16}	2.3×10^{-9}
15	1.0×10^{-15}	
20	1.2×10^{-15}	
25	1.4×10^{-15}	
30	1.6×10^{-15}	2.3×10^{-9}
35	1.75×10^{-15}	2.2×10^{-9}
40	1.9×10^{-15}	
45	2.15×10^{-15}	
50	2.4×10^{-15}	
55	2.7×10^{-15}	
60	3.0×10^{-15}	2.2×10^{-9}

Before the analysis is started, the transformer turns ratio, primary inductance, and amplifier input resistance must be chosen. The transformer ratio should be kept low to minimize the current noise contribution of the input transistor.

The parallel equivalent circuit of the hydrophone at 30 kHz is required. The capacitive part will be resonated by the transformer

primary inductance, leaving only the resistive part. Figure 1-6.3 shows the parallel equivalent circuit before resonating, and Fig. 1-6.4 shows the HP-97 calculations used to obtain the parallel equivalent circuit.

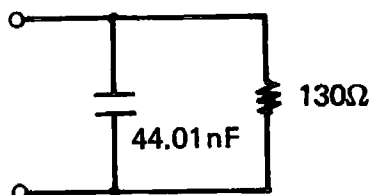


Figure 1-6.3 Parallel equivalent circuit of hydrophone at 30 kHz.

30000.	PI	enter frequency and
x		calculate and store
2.	x	$\omega = 2\pi f \Rightarrow R_E$
STOE		
1.407-03	x	form ωL
RCLE		
20000.-12	x	form $1/(\omega C)$
1/X		
-		form and print
-44.99-03	***	$\omega L - 1/(\omega C) = \text{Im } Z$
130.	+P	load $\text{Re } Z$
1/X		
X \rightarrow Y		convert impedance
CH5		to admittance
X \rightarrow Y		
+R		
1/X		
130.0+00	***	$\frac{1}{\text{Re } Y}$ in ohms
1/X		
X \rightarrow Y		$\text{Re } Y$ back in mhos
		$\text{Im } Y$
44000.-12	RCLE	
x		add clamp capacity
+		susceptance
RCLE		convert total
=		susceptance to
44.01-09	***	capacitance & print

Figure 1-6.4 HP-97 printout showing calculations used to find the parallel equivalent circuit at 30 kHz.

The thermal noise of the equivalent parallel resistor in a one Hz band is:

$$\bar{e}_n (130 \Omega) = \sqrt{4KT(130)} = 1.45 \times 10^{-9} \text{ V}/\sqrt{\text{Hz}}$$

If the transformer raises this noise to 6 dB above the transistor noise, the RSS sum of both resistor and transistor noises will be 1 dB higher

than the resistor noise alone. The transformer turns-ratio necessary to meet this condition is:

$$n = \frac{2(2.2 \times 10^{-9})}{1.45 \times 10^{-9}} = 3.03$$

The noise current contribution to the total noise voltage also may be calculated (only $\text{Re } Z_{\text{in}}$ is used as $\text{Im } Z_{\text{in}}$ is resonated out):

$$\bar{e}_n = \bar{i}_n \cdot n^2 \cdot |Z_{\text{in}}| = (1.6 \times 10^{-15})(10^2)(130) = 20.8 \times 10^{-12} \text{ V}/\sqrt{\text{Hz}}$$

This contribution is insignificant compared to the voltage noise term, and the transformer ratio may be raised to make the dominant noise source that of the hydrophone resistance only. This will be the best noise performance obtainable.

With a transformer ratio of 10:1, the equivalent hydrophone resistor noise is $1.45 \times 10^{-8} \text{ V}/\sqrt{\text{Hz}}$ at the transistor input, and the RSS of both the transistor and resistor noises is 1.467×10^{-8} . This RSS voltage is only 0.1 dB above the resistor noise alone!

To represent the equivalent hydrophone shunt capacity (44.01 nF), the transformer secondary capacitance term, C_{sec} is used. This equivalent secondary capacity is the primary capacity (hydrophone capacity) divided by the square of the turns ratio:

$$C_{\text{sec}} = (44.01 \text{ nF})/(10^2) = 440 \text{ pF}$$

The primary inductance is chosen to parallel resonate with the equivalent hydrophone capacity, 44.01 nF, at the design frequency of 30 kHz. This primary inductance is:

$$L_{\text{pri}} = 1/((2\pi f)^2 C) = 1/((2\pi 30000)^2 \cdot 44.01 \times 10^{-9})$$

$$L_{\text{pri}} = 639.5 \text{ } \mu\text{h}$$

The "Q" of the network is $R/(2\pi fL) = 1.078$, which means the approximate bandwidth of the network is $30000/1.078 = 27829 \text{ Hz}$. Additional broadbanding using the shunting effect of an amplifier input resistor is not necessary. This input resistor may be removed altogether as the transformer secondary provides the dc return for the transistor gate connection. The input resistor will be omitted by making its value 10^{50} ohms .

The HP-97 printout for this example is shown on the next page, and the equivalent circuit is shown in Fig. 1-6.5.

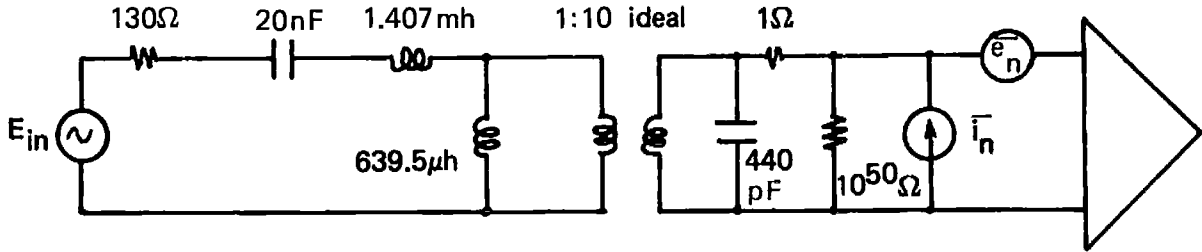


Figure 1-6.5 Equivalent circuit for hydrophone and amplifier.

HP-97 PRINTOUT FOR EXAMPLE 1-6.2

130.0 ST00 R _s 20000.-12 ST01 C _s 1.407-03 ST02 L _s 0.0 ST03 R _{pri} 639.5-06 ST04 L _{pri} 440.-12 ST05 C _{sec} 1.0 ST06 R _{sec} 1.+50 ST07 R _{in} 10.0 ST08 ntransformer GSBH select dB mode for p/d	1.4-15 GSBC I _n @ 25 kHz 25000.0 GSBE freq & start 21.9 *** -154.9 *** -197.9 *** -611.8 *** -172.8 *** -211.0 *** -154.8 *** \bar{e}_n tot @ 25kHz	2.15-15 GSBC I _n @ 45 kHz 45000.0 GSBE freq & start 19.6 *** -157.1 *** -197.9 *** -610.1 *** -173.2 *** -205.5 *** -157.0 *** \bar{e}_n tot @ 45kHz
PROGRAM OUTPUT 8.-16 GSBC load I _n @10kHz 2.3-09 GSBD load e _n @ " 10000.0 GSBE load freq & start -3.5 *** A _v dB -186.3 *** -197.9 *** -624.3 *** -172.8 *** -228.3 *** -172.0 *** RSS of all noise e's,dBV	1.6-15 GSBC I _n @ 30 kHz 30000.0 GSBE freq & start 20.0 *** -156.8 *** -197.9 *** -615.6 *** -172.8 *** -213.6 *** -156.7 *** \bar{e}_n tot @ 30kHz	2.4-15 GSBC I _n @ 50 kHz 50000.0 GSBE freq & start 14.5 *** -162.3 *** -197.9 *** -613.6 *** -173.2 *** -208.1 *** -162.0 *** \bar{e}_n tot @ 50kHz
1.-15 GSBC I _n @ 15 kHz * 15000.0 GSBE freq & start (*e _n unchanged) 7.4 *** -169.4 *** -197.9 *** -618.1 *** -172.8 *** -220.2 *** -167.7 *** \bar{e}_n tot @ 15kHz	1.75-15 GSBC I _n @ 35 kHz 2.2-09 GSBD e _n @ " 35000.0 GSBE freq & start 21.3 *** -155.4 *** -197.9 *** -612.8 *** -173.2 *** -210.1 *** -155.4 *** \bar{e}_n tot @ 35kHz	2.7-15 GSBC I _n @ 55 kHz 55000.0 GSBE freq & start 10.5 *** -166.3 *** -197.9 *** -616.2 *** -173.2 *** -209.6 *** -165.5 *** \bar{e}_n tot @ 55kHz
1.2-15 GSBC I _n @ 20 kHz 20000.0 GSBE freq & start 19.6 *** -157.1 *** -197.9 *** -610.1 *** -172.8 *** -210.6 *** -157.0 *** \bar{e}_n tot @ 20kHz	1.9-15 GSBC I _n @ 40 kHz 40000.0 GSBE freq & start 23.4 *** -153.4 *** -197.9 *** -608.4 *** -173.2 *** -204.9 *** -153.3 *** \bar{e}_n tot @ 40kHz	3.-15 GSBC I _n @ 60 kHz 60000.0 GSBE freq & start 7.4 *** -169.4 *** -197.9 *** -618.1 *** -173.2 *** -210.6 *** -167.8 *** \bar{e}_n tot @ 60kHz

Example 1-6.2 is meant to illustrate both the program functioning and to give some insight on hydrophone matching. The gain versus frequency response has two peaks, which is characteristic of doubly tuned networks.

The whole subject of optimum hydrophone matching is beyond the scope of this program and discussion. Equiripple passband response and optimum noise performance may be simultaneously obtained with higher order matching networks which represent bandpass filter like structures and include the hydrophone equivalent circuit in the filter structure. Typical broadbanding networks are fifth order and have Chebyshev responses. These networks are an extension of the work of Fano [23] and Matthaei [37].

Derivation of Equations Used

The network shown in Fig. 1-6.1 is redrawn with the components on the secondary side of the transformer reflected to the primary side, and the thermal noise sources of the resistors added. This new network is shown in Fig. 1-6.6.

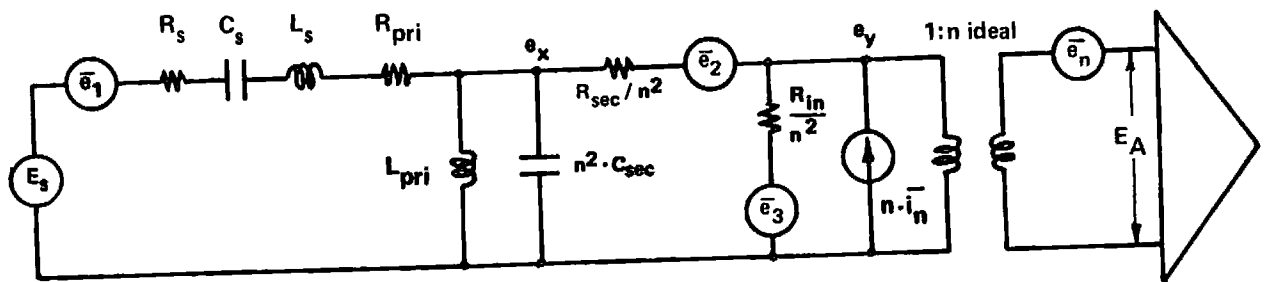


Fig. 1-6.6 Network of Fig. 1-6.1 redrawn with the transformer moved to the right side.

The network of Fig. 1-6.6 is shown in Fig. 1-6.7 with the individual element groups replaced by generalized admittance blocks. The noise voltage densities of the noise generators are defined by Eqs. (1-6.1) through (1-6.3), and the admittance blocks are defined by Eqs. (1-6.4) through (1-6.7).

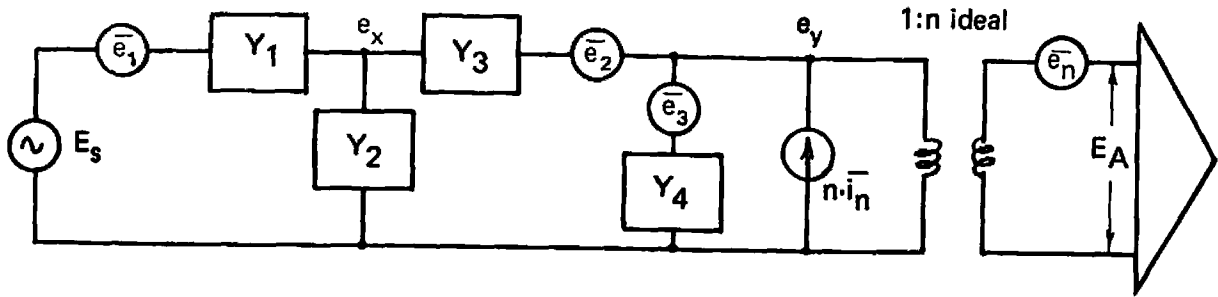


Figure 1-6.7 Network of Fig. 1-6.6 redrawn with generalized admittance blocks.

$$\bar{e}_1 = \sqrt{4KT(R_s + R_{pri})} \quad (1-6.1)$$

$$\bar{e}_2 = (1/n) \sqrt{4KTR_{sec}} \quad (1-6.2)$$

$$\bar{e}_3 = (1/n) \sqrt{4KTR_{in}} \quad (1-6.3)$$

$$Y_1 = \frac{1}{R_s + R_{pri} + sL_s + 1/(sC_s)} \quad (1-6.4)$$

$$Y_2 = s(n^2 \cdot C_{sec}) + 1/(sL_{pri}) \quad (1-6.5)$$

$$Y_3 = n^2/R_{sec} \quad s = j\omega \quad (1-6.6)$$

$$Y_4 = n^2/R_{in}$$

Where K is Boltzmann's constant (1.380×10^{-23} Joules/K), and T is the temperature in Kelvin (290 K at room temperature).

The nodal equations are written from Fig. 1-6.7:

$$\begin{bmatrix} (Y_1 + Y_2 + Y_3) & (-Y_3) \\ (-Y_3) & (Y_3 + Y_4) \end{bmatrix} \cdot \begin{bmatrix} e_x \\ e_y \end{bmatrix} = \begin{bmatrix} Y_1(\bar{e}_1 + e_s) - Y_3\bar{e}_2 \\ Y_3\bar{e}_2 + Y_4\bar{e}_3 + n \cdot \bar{i}_n \end{bmatrix} \quad (1-6.8)$$

The variable, e_y , is obtained using Cramer's rule. The determinant of the coefficient matrix is designated Δ .

$$\Delta = (Y_1 + Y_2 + Y_3)(Y_3 + Y_4) - Y_3^2$$

which upon rearranging yields:

$$\Delta = (Y_1 + Y_2 + Y_3)(Y_4) + (Y_1 + Y_2)(Y_3) \quad (1-6.9)$$

Substituting the constant matrix (right hand side) into the second column of the coefficient matrix, and evaluating the determinant yields the following:

$$n \cdot e_y = (n/\Delta) \left[(Y_1 + Y_2 + Y_3)(Y_3 \bar{e}_2 + Y_4 \bar{e}_3 + n \cdot \bar{i}_n) + (Y_1 Y_3)(\bar{e}_1 + E_s) - (Y_3^2)(\bar{e}_2) \right] \quad (1-6.10)$$

Simplifying and removing term subtraction yields:

$$n \cdot e_y = (n/\Delta) \left[(Y_1 + Y_2 + Y_3)(Y_4 \bar{e}_3 + n \cdot \bar{i}_n) + (Y_1 Y_3)(\bar{e}_1 + E_s) + (Y_1 - Y_2)(Y_3 \bar{e}_2) \right] \quad (1-6.11)$$

The voltage gain of the network is: $n \frac{\partial e_y}{\partial E_s} = \frac{\partial e_A}{\partial E_s} = A_v$, or: (1-6.12)

$$A_v = (n Y_1 Y_3) / (\Delta), \quad (1-6.13)$$

In terms of magnitude only:

$$A_v = n \cdot |Y_1| \cdot |Y_3| / |\Delta| \quad (1-6.14)$$

Since the noise voltages \bar{e}_2 , \bar{e}_3 , and \bar{e}_n , and the current \bar{i}_n are random in nature, their addition must be done in RSS fashion to obtain the overall RMS noise voltage at the amplifier input, e_A , i.e.,

$$\bar{e}_A^2 = \bar{e}_n^2 + n^2 \cdot \bar{e}_y^2 \quad (1-6.15)$$

Upon expanding:

$$\bar{e}_A^2 = \bar{e}_n^2 + \frac{n^2}{|\Delta|^2} \left(|Y_1 + Y_2 + Y_3|^2 \cdot (\bar{e}_3^2 |Y_4|^2 + n^2 \bar{i}_n^2) + |Y_1 Y_3|^2 \cdot \bar{e}_1^2 + |Y_1 + Y_2|^2 Y_3^2 \bar{e}_2^2 \right) \quad (1-6.16)$$

This program uses Eqs. (1-6.14) and (1-6.16) to calculate the overall noise voltage density.

Program Listing I

001 *LBLA	SELECT OUTPUT IN dB & dBV	056 STOA	store $\text{Re}(Y_1 + Y_2)$ $\text{Re } Y_2$
002 CF1		057 XZY	calculate and store
003 RTN		058 RCL5	$\text{Im}(Y_1 + Y_2)$
004 *LBLB	SELECT OUTPUT IN RATIO	059 RCL8	
005 SF1	AND VOLTS	060 X2	calculate $n^2 \omega C_{\text{sec}}$
006 RTN		061 X	
007 *LBLC	LOAD AMPLIFIER INPUT CURRENT	062 RCLE	
008 P2S	NOISE DENSITY IN $\text{A}/\sqrt{\text{Hz}}$	063 X	
009 F3?	if numeric entry, jump to	064 +	
010 GT00	storage routine	065 RCLE	calculate $1/(\omega L_{\text{pri}})$
011 RCL0	recall presently stored value	066 RCL4	
012 P2S	jump to print and space	067 X	
013 GT02	routine	068 1/X	
014 *LBL0	store entered value of I_n ,	069 -	
015 ST00	and return control to	070 ST0B	form and store $\text{Im}(Y_1 + Y_2)$
016 P2S	keyboard	071 RCLA	take $Y_1 + Y_2$ to polar
017 RTN		072 +P	
018 *LBLD	LOAD AMPLIFIER INPUT VOLTAGE	073 RCL8	calculate and store:
019 F3?	NOISE DENSITY IN $\text{V}/\sqrt{\text{Hz}}$	074 X2	$Y_3 = n^2/R_{\text{sec}}$
020 GT00	if numeric entry, jump	075 RCL6	
021 RCL9	recall presently stored value	076 ÷	
022 *LBL2	print and space routine	077 STOC	
023 PRTX		078 X	form and store $ Y_3 \cdot Y_1 + Y_2 $
024 SPC		079 P2S	
025 RTN	return control to keyboard	080 ST02	
026 *LBL0	store entered value of \bar{e}_n	081 P2S	
027 ST09		082 RCLB	$\text{Im}(Y_1 + Y_2 + Y_3)$ $\text{Im}(Y_1 + Y_2)$
028 RTN	return control to keyboard	083 RCLA	calculate $\text{Re}(Y_1 + Y_2 + Y_3)$
029 *LBL E	LOAD ANALYSIS FREQ & START	084 RCLC	
030 F3?	if numeric entry, store it	085 +	
031 ST01		086 +P	form and store $Y_1 + Y_2 + Y_3$
032 RCL1	recall present stored freq	087 STOE	
033 GSB3	if flag 0, space	088 RCL8	form $ Y_4 \cdot Y_1 + Y_2 + Y_3 $
034 ENT+		089 X2	
035 +	form and store $\omega = 2\pi f$	090 X	
036 Pi		091 RCL7	
037 X		092 ÷	
038 STOE		093 +R	form $\text{Re} \& \text{Im}(Y_4(Y_1 + Y_2 + Y_3))$
039 RCL2	form ωL_{sens}	094 RCLA	form $\text{Re}(Y_3(Y_1 + Y_2))$
040 X		095 RCLC	
041 RCLE		096 X	
042 RCL1	form $1/(\omega C_{\text{sens}})$	097 +	form $\text{Re } \Delta$
043 X		098 XZY	form $\text{Im}(Y_3(Y_1 + Y_2))$
044 1/X		099 RCLB	
045 -	$\text{Im } Z_4 = \omega L_s - 1/(\omega C_s)$	100 RCLC	
046 RCL0		101 X	
047 RCL3	$\text{Re } Z_4 = R_s + R_{\text{pri}}$	102 +	form $\text{Im } \Delta$
048 +		103 +P	form $ \Delta $
049 +P	convert rectangular to polar	104 RCL8	form and store $n/ \Delta $
050 1/X	form and store $ Y_1 $	105 ÷	
051 ST0D		106 1/X	
052 XZY	finish complex inverse,	107 STOA	
053 CHS	and return output in	108 RCLD	form $ Y_1 Y_3 $
054 XZY	rectangular co-ordinates	109 RCLC	
055 +R		110 X	

REGISTERS

0 R_s	1 C_s	2 L_s	3 R_{pri}	4 L_{pri}	5 C_{sec}	6 R_{sec}	7 R_{in}	8 n	9 $\bar{e}_{n_{\text{amp}}}$
S0 $I_{n_{\text{amp}}}$	S1 $\sum V^2$	S2 $ Y_3(Y_1 + Y_2) $	S3	S4	S5	S6	S7	S8	S9
A $\text{Re } Y_1, \frac{n}{ \Delta }$	B $\text{Im}(Y_1 + Y_2), 4KT$	C $ Y_3 , Y_1 Y_3 $	D $ Y_1 , A_v $	E $2\pi f, Y_1 + Y_2 + Y_3 $	F the freq for analysis				

Program Listing II

111	STOC	calculate and store:	166	GSB1		167	P+S	calculate and output the
112	x		168	RCL0	voltage noise density	169	P+S	caused by the amplifier
113	STOD	$ A_v = n \cdot Y_1 Y_3 / \Delta $	170	RCL8	input current noise density	171	x	acting on the equivalent
114	GSB1	print A_v or $20 \cdot \log A_v$	172	RCL6	circuit impedance	173	x	
115	0	initialize ΣV^2 register	174	GSB1		175	GSB3	space if flag 0 is set
116	P+S		176	P+S		177	RCL1	recall and output the RSS
117	STO1		178	P+S	of all the above noise	179	JX	voltage densities
118	P+S		180	GSB1	($\sqrt{\Sigma V^2}$)	181	GSB3	
119	GSB3	space if flag 0 is set	182	GTO3		183	*LBL1	output subroutine:
120	1	form and store $4KT$	184	X ²	store ΣV^2	185	P+S	
121	.		186	ST+1		187	P+S	
122	6		188	LSTX	recall V	189	F1?	if flag 1, output voltage
123	1		190	GTO1	in engineering format	191	FIX	flag 1 is cleared; output
124	7		192	DSP1	20 log V in fix 1 format	193	LOG	
125	3		194	2		195	0	
126	6		196	x		197	RND	
127	EEX		198	GTO2		199	*LBL1	
128	CHS		200	ENG		201	DSP3	
129	2		202	*LBL2	print-R/S subroutine	203	F0?	
130	0		204	PRTX		205	F0?	
131	STOB		206	RTN		207	R/S	
132	RCL0	calculate and output:	208	RTN		209	*LBL3	space if flag 0 subroutine
133	RCL3	$A_v \cdot \sqrt{4KT(R_s + R_{pri})}$	210	F0?		211	SPC	
134	+	which is the transformer	212	RTN		213	*LBL0	print - R/S toggle
135	x	primary resistance and	214	CF0		215	0	a "0" displayed indicates
136	JX	sensor resistance thermal	216	RTN	R/S mode selected	217	*LBL0	
137	RCLD	voltage noise density	218	SF0		219	1	a "1" displayed indicates
138	x		220	RTN	print mode selected			
139	GSB1							
140	RCLB	calculate and output:						
141	RCL6	$ Y_3(Y_1+Y_2)/\Delta \cdot \sqrt{4KTR_{sec}}$						
142	x	which is the transformer						
143	JX	secondary resistance thermal						
144	RCL8	voltage noise density						
145	÷							
146	P+S							
147	RCL2							
148	P+S							
149	x							
150	RCLA							
151	x							
152	GSB1							
153	RCLB	calculate and output:						
154	RCL7	$\frac{n}{ \Delta } Y_4(Y_1+Y_2+Y_3) \cdot \sqrt{4KTR_{in}}$						
155	÷	which is the thermal noise						
156	JX	voltage density due to the						
157	RCL8	amplifier input resistance						
158	x							
159	RCLA							
160	RCL6							
161	x							
162	STOE							
163	x							
164	GSB1							
165	RCL9	recall and output the						
		amplifier noise voltage dens						

LABELS					FLAGS	SET STATUS		
A select dB	B select linear	C load I_n	D load \bar{e}_n	E input freq & go	F R/S, prt	FLAGS	TRIG	DISP
a	b	c	d	e	1dB/ linear	ON OFF		
						0 <input type="checkbox"/>	DEG <input type="checkbox"/>	FIX
						1 <input type="checkbox"/>	GRAD	SCI
						2 <input type="checkbox"/>	RAD	ENG
						3 <input type="checkbox"/>		n_____

Part 2

FILTER DESIGN

PROGRAM 2-1 BUTTERWORTH AND CHEBYSHEV FILTER ORDER CALCULATION.

Program Description and Equations Used

This program calculates the minimum filter order required to meet specifications for maximum passband attenuation ($A_{p_{dB}}$) and minimum stopband attenuation ($A_{s_{dB}}$) for the Butterworth or Chebyshev filter approximations. A second part of the program calculates the stopband-to-passband frequency ratio, λ , if the filter order and type are given. Furthermore, a third part of the program predicts the stopband attenuation if n , λ , $A_{p_{dB}}$, and the filter order are provided.

Figures 2-1.1 and 2-1.2 are nomographs adapted from Kawakami [34], and can prove useful to rough out the problem and provide tradeoffs. Once the desired parameters have been estimated, this program may be used to fine-tune the results.

Equation (2.1.1) is the analytic expression for the Butterworth amplitude response characteristic.

$$A_s^2 - 1 = (A_p^2 - 1) \lambda^{2n} \quad (2-1.1)$$

where

$$A_s^2 = 10^{0.1 A_{s_{dB}}} \quad (2-1.2)$$

and

$$A_p^2 = 10^{0.1 A_{p_{dB}}} \quad (2-1.3)$$

The quantities A_s and A_p are ratios greater than one (it is the convention to express attenuation as positive decibels).

Equations (2-1.1), (2-1.2), and (2-1.3) can be used to find expressions for $A_{s_{dB}}$, λ , or n :

$$A_{s_{dB}} = 10 \cdot \log \left[(A_p^2 - 1) \lambda^{2n} + 1 \right] \quad (2-1.4)$$

$$\lambda = \left[\frac{A_s^2 - 1}{A_p^2 - 1} \right]^{\frac{1}{2n}} = \left[\sqrt{\frac{A_s^2 - 1}{A_p^2 - 1}} \right]^{\frac{1}{n}} \quad (2-1.5)$$

$$n = \frac{\ln \sqrt{\frac{A_s^2 - 1}{A_p^2 - 1}}}{\ln \lambda} \quad (2-1.6)$$

Equation (2-1.7) is the analytic expression for the Chebyshev amplitude characteristic where A_s^2 and A_p^2 are defined by Eqs. (2-1.2) and (2-1.3). Equation (2-1.7) can also yield expressions for $A_{s_{dB}}$, λ , or n :

$$A_s^2 - 1 = (A_p^2 - 1) [\cosh (n \cosh^{-1} \lambda)]^2 \quad (2-1.7)$$

$$A_{s_{dB}} = 10 \cdot \log \left[(A_p^2 - 1) (\cosh (n \cdot \cosh^{-1} \lambda))^2 + 1 \right]^2 \quad (2-1.8)$$

$$\lambda = \cosh \left(\frac{1}{n} \cosh^{-1} \sqrt{\frac{A_s^2 - 1}{A_p^2 - 1}} \right) \quad (2-1.9)$$

$$n = \frac{\cosh^{-1} \sqrt{\frac{A_s^2 - 1}{A_p^2 - 1}}}{\cosh^{-1} \lambda} \quad (2-1.10)$$

A certain degree of similarity can be noticed between the Butterworth and Chebyshev equations. Keeping in mind that \ln and \exp are complementary operations as are \cosh and \cosh^{-1} , and noticing that y^x can be expressed as $\exp (x \cdot \ln y)$, then replacing \ln with \cosh and \exp with \cosh^{-1} will convert the Butterworth formulas to the Chebyshev

formulas. This technique is used by this program where flag 1 indicates the function to be used (set for Butterworth).

A separate subprogram is also included to aid in the specification of bandpass or bandstop filters. The characteristics of these filters are symmetrical when plotted on logarithmic frequency scales (log paper). This characteristic implies geometric symmetry of the various defining frequencies (-3dB, etc.) about the filter center frequency, i.e., the center frequency is the square root of the product of similar response frequencies located above and below the center frequency.

To use the bandstop and bandpass programs in this section, the filter center frequency (f_o) and bandwidth (BW) are needed, however, when specifying the filter initially, the bandedge frequencies may be of greater interest. The separate subprogram provides the conversion between center frequency and bandwidth, and upper and lower bandedge frequencies (f_{upr} and f_{lwr}), and vice-versa. The definition of "bandedge frequencies" in the present context means a pair of frequencies (one on either side of the center frequency) where the filter attenuation is the same, i.e., -0.01 dB, -3 dB, -60 dB, etc.

To convert from center frequency and bandwidth to upper and lower bandedge frequencies, Eqs. (2-1.11) and (2-1.12) apply.

$$f_{upr} = (BW/2) + \sqrt{(BW/2)^2 + f_o^2} \quad (2-1.11)$$

$$f_{lwr} = (f_o^2)/f_{upr} \quad (2-1.12)$$


To do the reverse conversion, i.e., to go from upper and lower bandedge frequencies to center frequency and bandwidth, Eqs. (2-1.13) and (2-1.14) apply.

$$f_o = \sqrt{(f_{upr})(f_{lwr})} \quad (2-1.13)$$

$$BW = f_{upr} - f_{lwr} \quad (2-1.14)$$

In the case of a bandpass or bandstop filter, the stopband-to-passband frequency ratio, λ , still holds. The user should remember to use bandwidths, and not bandedge frequencies. This is an easy trap to fall into since bandedge frequencies and bandwidths can be one and the same for lowpass filters.

User Instructions

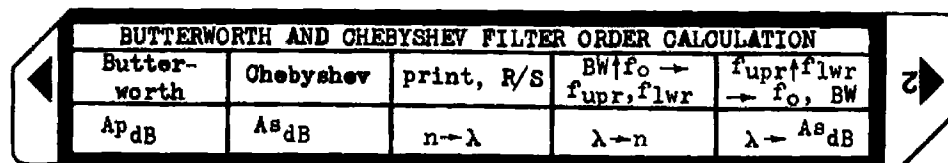

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load program card (either side)			
2	Select print (HP-97), or R/S (HP-67) option		<div>f</div> <div>C</div> <div>f</div> <div>C</div> <div>f</div> <div>C</div>	1 (print) 0 (R/S) 1 :
3	Select filter type: Butterworth Chebyshev		<div>f</div> <div>A</div> <div>f</div> <div>B</div>	
4	Load the maximum passband attenuation in dB	A_{pdB}	<div>A</div>	
5	Load the minimum stopband attenuation in dB	A_{sdB}	<div>B</div>	
6	To find filter order, n , given the frequency ratio, λ , load λ	λ	<div>D</div>	n
7	To find the frequency ratio, λ , given the filter order, n : load n (n must be integer)	n	<div>C</div>	λ
8	After finding n , to find A_s (dB) given λ a) perform step 7 to store n b) load λ Step 8b may be repeated with other values of λ without having to repeat step 8a.	λ	<div>E</div>	A_{sdB}
9	A separate program section to aid with bandpass filter selection, enter bandwidth and center frequency and calculate the upper and lower bandedge frequencies, or vice-versa load bandwidth (for any dB down points) load center frequency load upper bandedge frequency load lower bandedge frequency	BW, Hz f_o, Hz f_{upr}, Hz f_{lwr}, Hz	<div>ENT</div> <div>f</div> <div>D</div> <div>ENT</div> <div>f</div> <div>E</div>	f_{upr}, Hz f_{lwr}, Hz f_o, Hz BW, Hz

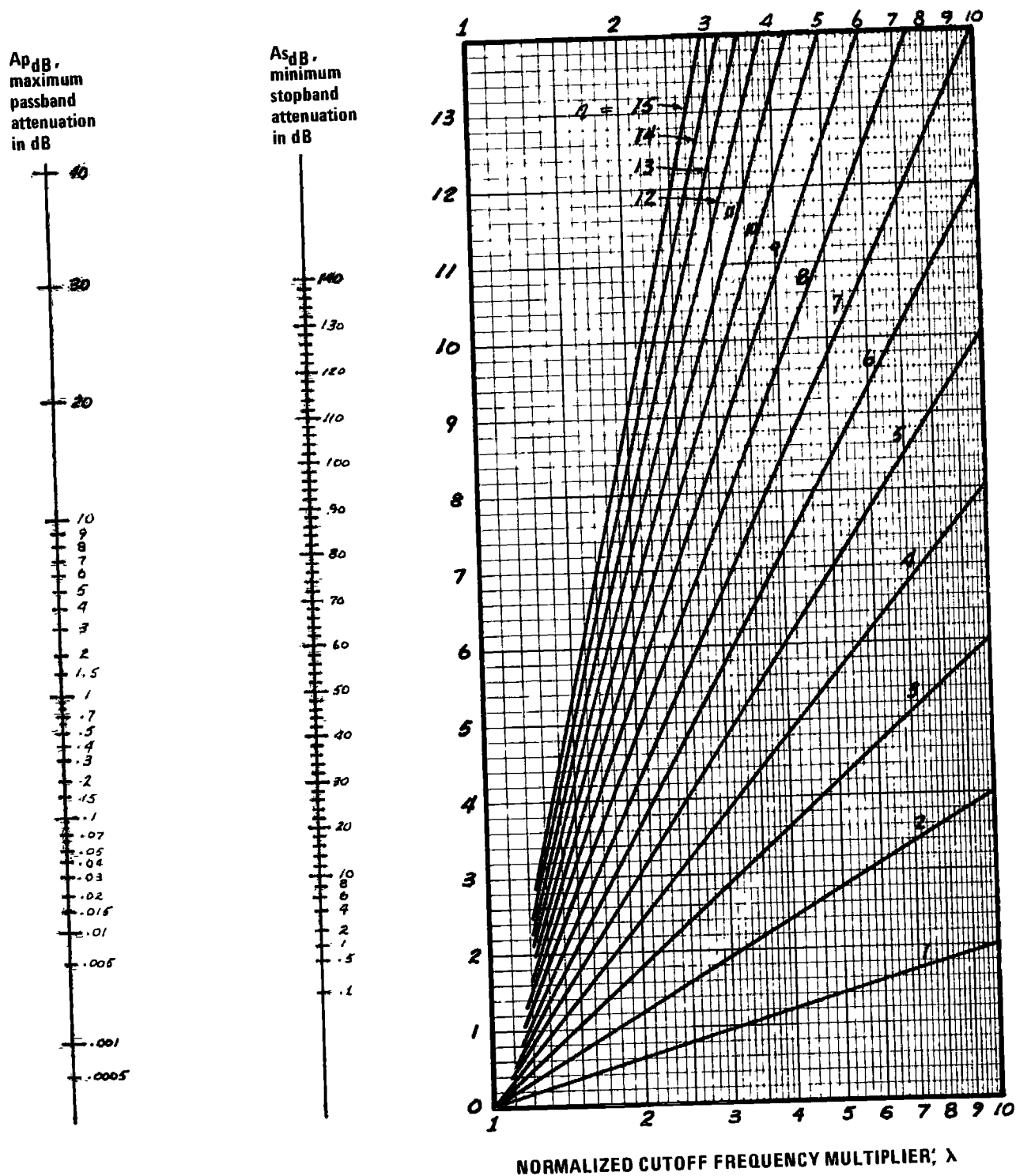


Figure 2-1.1 Butterworth filter nomograph.

$$A_s^2 - 1 = (A_p^2 - 1)\lambda^{2n}.$$

Adapted from Kawakami [34]

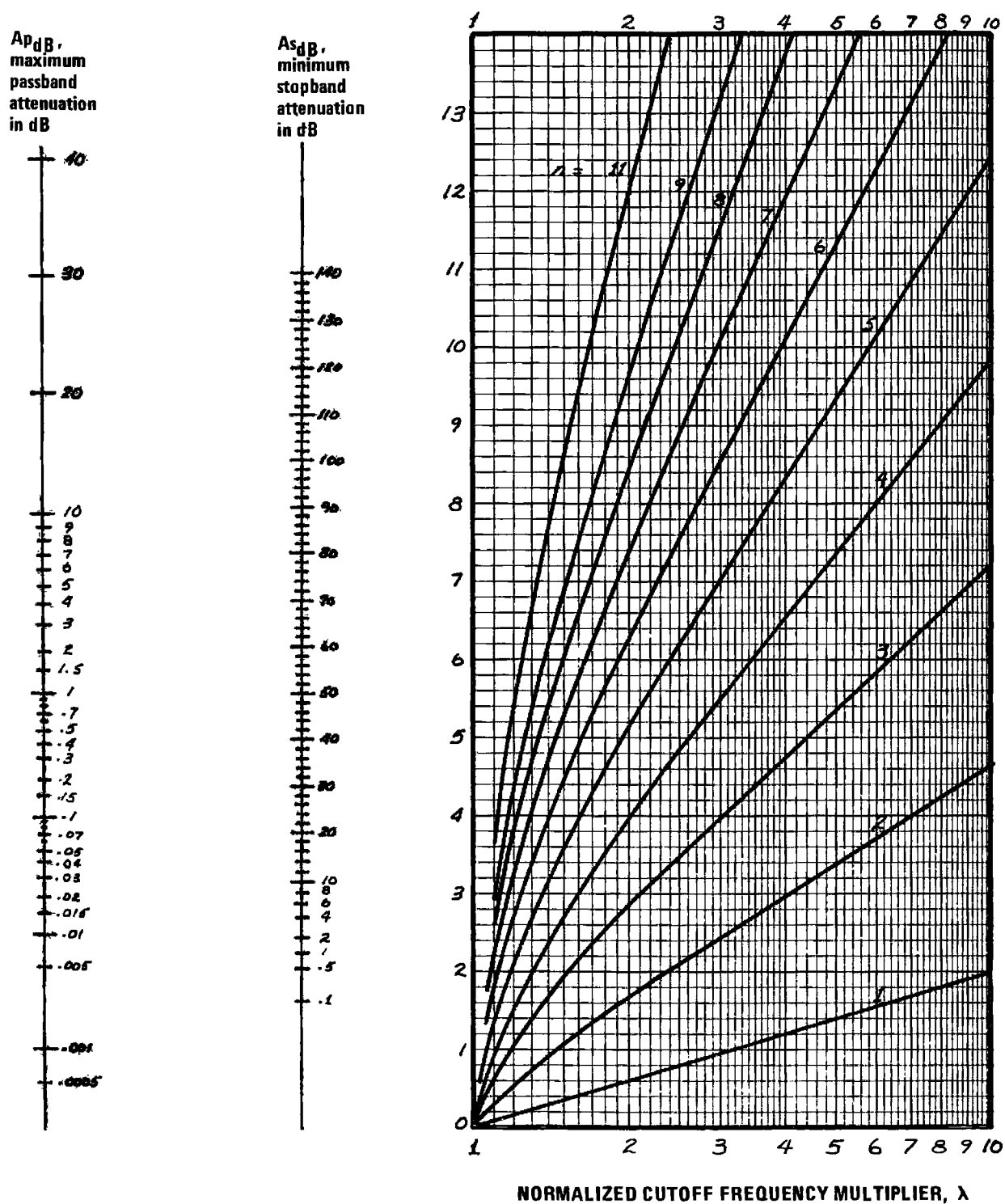


Figure 2-1.2 Chebyshev filter nomograph.

$$A_s^2 - 1 = (A_p^2 - 1) \{ \cosh(n \cdot \cosh^{-1} \lambda) \}$$

Adapted from Kawakami [34]

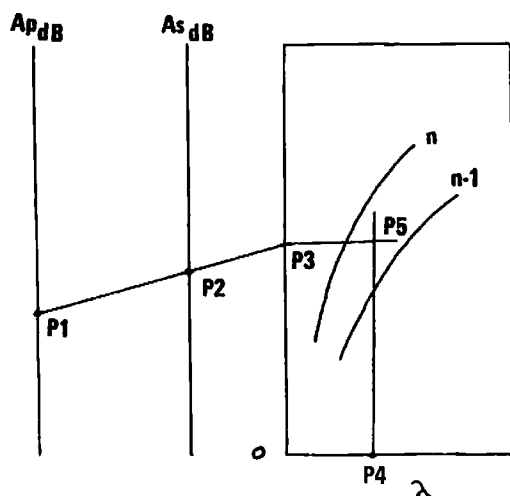
How to Use the Nomographs

Figure 2-1.3 Nomograph use.

P1 and P2 are the required passband and stopband attenuation, P3 is a turning point, P4 represents the ratio between the frequencies where the stopband attenuation and the passband attenuation are specified, and P5 represents the required filter order, n .

Since n must be an integer, and P5 will generally lie between two integral numbers, always choose the larger of the two integers. Furthermore, if any of the narrowband approximations to bandpass filters are going to be generated, and Chebyshev response is specified, n must be an odd integer. This requirement occurs as even ordered Chebyshev filters have unequal termination resistances, and the narrowband bandpass approximations require equal termination resistances.

These nomographs are also contained in Zverev, however, the two vertical scales appear to be misregistered slightly, and in some applications will give inaccurate results.

These nomographs may also be used in other ways. If the filter order is known, then the filter response may be predicted. In this case, P5 would lie directly on one of the filter order lines, λ and P1, or P2 are the input variables, with P2, or P1 being the output quantity.

Example 2-1.1 Highpass filter

A Butterworth filter is to pass 20 kHz and higher with 3 dB or less attenuation, and reject 10 kHz and lower with at least 40 dB of attenuation. Find the minimum filter order to meet these specifications.

```

      55E:  select Butterworth
5.00  55E-  load  $A_{p\text{dB}}$ 
40.00 55EE  load  $A_{s\text{dB}}$ 
2.00  55EE  load  $\lambda = \frac{\text{dB}}{(20 \text{ kHz})/(10 \text{ kHz})} = 2$ , & calculate n
0.65  **   filter order, n (use n = 7)

```

Example 2-1.2 Bandpass filter

A Chebyshev bandpass filter is centered at 100 kHz (center frequency is not a parameter of the filter order calculation). Frequencies in a 20 kHz passband (geometrically centered about the center frequency) must be passed with 0.5 dB attenuation or less, and frequencies outside a 40 kHz bandwidth (again geometrically centered) must be rejected with at least 40 dB attenuation. Find the minimum filter order to meet these requirements.

```

      55E:  select Chebyshev
.50  55E-  load passband ripple in dB ( $A_{p\text{dB}}$ )
40.00 55EE  load minimum stopband attenuation in dB ( $A_{s\text{dB}}$ )
2.00  55EE  load  $\lambda = (40 \text{ kHz})/(20 \text{ kHz}) = 2$ , and calculate n
4.62  **   filter order, n (use n = 5 as smallest integer
              value to meet specs)

```

Example 2-1.3 Bandstop example

A maximally flat (Butterworth) bandstop filter is centered at 20 kHz. Frequencies lying outside a 10 kHz band geometrically centered on the center frequency should be attenuated by 3 dB or less. Frequencies inside a band of 1 kHz geometrically centered on the center frequency should be attenuated by at least 60 dB. Find the minimum filter order meeting these specifications.

```

      GSBa select Butterworth
3.00 GSBa load ApdB
60.00 GSBb load AsdB
10.00 GSBd load  $\lambda = (10 \text{ kHz})/(1 \text{ kHz}) = 10$  & calculate n
3.00 *** filter order required

      DSP4 display 4 figures past the decimal point
3.0010 *** the filter order required is greater than 3

      3.0000 GSBc enter filter order of exactly three & calc.  $\lambda$ 
10.0079 ***  $\lambda$  where filter is 60 dB down

      10.0000 GSBF enter  $\lambda$  and calculate AsdB
55.9754 *** AsdB at  $\lambda = 10$ 
           dB

```

This bandstop example shows other features of this program. Given n , the ratio, λ , where A_s is met is calculated, and alternately, given λ , A_s for this ratio is calculated.

As an aside, Butterworth filters are not exactly three dB down at the bandedge, but are $10 \cdot \log_{10} 2 = 3.010299957$ dB. If this number had been entered for A_p , the calculated filter order would have been three (to seven significant figures).

Example 2-1.4 Lowpass filter

Find the frequency where a 2 dB ripple, 7th order Chebyshev lowpass filter will be 60 dB down when the cutoff (-2dB) frequency is 1000 Hz.

```

      GSBk select Chebyshev
2.00 GSBk load ApdB, the passband ripple
60.00 GSBb load AsdB, the minimum stopband rejection
7.00 GSBc load the filter order, n, and calculate  $\lambda$ 
1.70 ***  $\lambda$  to meet above requirements

      1000.00 .. cutoff frequency of filter times  $\lambda$ 
1701.27 *** frequency where the filter is 60 dB down

```

Program Listing I

```

001 *LBLA  LOAD ApdB
002 GSB0
003 ST01  store  $A_p^2 - 1$ 
004 RTN
005 *LBLB  LOAD AsdB
006 GSB0
007 ST02  store  $A_s^2 - 1$ 
008 RTN
009 *LBL0  subroutine to convert dB to
010 EEX    (magnitude)2 - 1
011 1
012 ÷
013 10x
014 EEX
015 -
016 RTN
017 *LBLE  LOAD n, THE FILTER ORDER
018 ST03  AND CALCULATE  $\lambda$ 
019 RCL2
020 RCL1  calculate  $k = \sqrt{\frac{A_s^2 - 1}{A_p^2 - 1}}$ 
021 ÷
022 JX
023 FI?   jump if Butterworth
024 GT03  calculate cosh k
025 GSB2
026 RCL3
027 ÷
028 GSB1  calc  $\lambda = \cosh^{-1}(\frac{1}{n} \cosh k)$ 
029 ST04
030 GT08  goto the print/stop routine
031 *LBL3  calculate  $\lambda$  for Butterworth
032 RCL3
033 1/X
034 YX     $\lambda = (k)^{\frac{1}{n}}$ 
035 ST04
036 GT08

```

```

037 *LBLD  LOAD  $\lambda$  AND CALCULATE n
038 ST04
039 RCL2
040 RCL1  calculate k
041 ÷
042 JX
043 FI?   jump if Butterworth
044 GT03
045 GSB2
046 RCL4
047 GSB2  for Chebyshev:
048 ÷       $n = \frac{\cosh^{-1} k}{\cosh^{-1} \lambda}$ 
049 ST03
050 GT08
051 *LBL3
052 LN
053 RCL4
054 LN
055 ÷       $n = \frac{\ln k}{\ln \lambda}$ 
056 ST03
057 GT08
058 *LBLE  LOAD  $\lambda$  AND CALCULATE AsdB
059 FI?   jump if Butterworth
060 GT03
061 GSB2
062 RCL3  for Chebyshev:
063 x
064 GSB1   $q = \cosh(n \cdot \cosh^{-1} \lambda)$ 
065 GT04
066 *LBL3  for Butterworth:
067 RCL3
068 YX     $q = (\lambda)^n$ 
069 *LBL4  common part for Buttr & Cheb
070 X2
071 RCL1
072 x
073 EEX
074 +
075 LOG
076 EEX
077 1
078 x
079 GT08

```

REGISTERS

0	1 $A_p^2 - 1$	2 $A_s^2 - 1$	3 n	4 λ	5	6	7	8	9
S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
A	B	C	D	E	I				

080 *LBL1 cosh x subroutine	113 *LBLd BANDPASS; enter BW, f _o and
081 e ^x	114 X ² calculate f _{upr} and f _{lwr}
082 ENT↑	115 ST05
083 1/X cosh x = $\frac{e^x + e^{-x}}{2}$	116 XZY
084 +	117 2
085 2	118 ÷
086 ÷	119 ENT↑
087 RTN	120 X ² f _{upr} = $\left(\frac{BW}{2}\right) + \sqrt{\left(\frac{BW}{2}\right)^2 + f_o^2}$
088 *LBL2 cosh ⁻¹ x subroutine	121 RCL5
089 ENT↑	122 +
090 X ²	123 JX
091 EEX	124 +
092 -	125 ENT↑
093 JX cosh ⁻¹ x = ln(x + $\sqrt{x^2 - 1}$)	126 GSB9 f _{lwr} = (f _o) ² /f _{upr}
094 +	127 RCL5
095 LN	128 XZY
096 RTN	129 ÷
097 *LBLa SELECT BUTTERWORTH	130 GT08
098 SF1	131 *LBLe BANDPASS; enter f _{upr} & f _{lwr}
099 RTN	132 ST05 calculate f _o and BW
100 *LBLb SELECT CHEBYSHEV	133 XZY
101 CF1	134 ST06
102 RTN	135 x f _o = ((f _{upr})(f _{lwr})) ^{1/2}
103 *LBLc SELECT PRINT OR R/S	136 JX
104 F0? jump if flag 0 is set	137 GSB9
105 GT03	138 RCL6
106 SF0	139 RCL5
107 1 set flag 0 to indicate print	140 -
108 RTN	141 *LBL8 print or R/S subroutine
109 *LBL3	142 GSB9
110 CF0 clear flag 1 to indicate R/S	143 F0? if flag 0, space
111 0	144 SPC
112 RTN	145 RTN
	146 *LBL9
	147 F0? if flag 0, go to print
	148 GT09
	149 R/S flag 0 not set, R/S
	150 RTN
	151 *LBL9
	152 PRTX
	153 RTN

LABELS					FLAGS	SET STATUS		
A A _p dB	B A _s dB	C n → λ	D λ → n	E λ → A _s dB	0 print?	FLAGS	TRIG	DISP
a set	b set	c print,	d f _o & BW →	e	1 Buttr	--USERS CHOICE--		
Buttr	Chebyshev	no-print	f _u , f _l		2	0	DEG	FIX
0 dB → ² -1	1 cosh x	2 cosh ⁻¹ x	3	4	3	1	GRAD	SCI
5	6	7	8 print & space	9 print		2	RAD	ENG
						3		n

PROGRAM 2-2 BUTTERWORTH AND CHEBYSHEV FILTER FREQUENCY RESPONSE AND GROUP DELAY.

Program Description and Equations Used

This program calculates the frequency response (magnitude in dB and phase in degrees) and the un-normalized group delay in seconds for the Butterworth or Chebyshev all pole filter approximations. The response may be in lowpass, highpass, bandpass, or bandstop form (the lowpass and highpass responses are special cases of the bandpass and bandstop responses respectively in that the center frequency is zero). Both single frequency analysis and frequency sweeps may be done. The sweep can be linear using an additive increment, or logarithmic using a multiplicative increment.

The actual analysis routine that is buried within the program analyzes a normalized lowpass filter. The input data is normalized and transformed as required to place it in normalized lowpass form. The phase and gain response (frequency response) of the normalized lowpass filter is the same as the original filter type before transformation; hence, no reverse transformation is necessary for output. The group delay is the rate of change of phase with respect to frequency (derivative of the phase function) and is affected by the transformation to normalized lowpass form, therefore, an output transformation from the normalized lowpass group delay is required.

The logarithm of the normalized lowpass filter transmission function, $T(j\Omega)$ is composed of two components, the attenuation, a , and the phase, b . As a complex number, these two components represent the constant, g :

$$T(j\Omega) = \prod_k \frac{K}{\sigma_k + j(\omega_k - \Omega)} \quad (2.2.1)$$

$$g = \ln(T(j\Omega)) = a + jb \quad (2-2.2)$$

$$\Omega = F(\omega) \quad (2-2.3)$$

$$\omega = 2\pi f \quad (2-2.4)$$

where $F(\omega)$ represents the transformation to normalized lowpass, and σ_k and ω_k are the pole locations of the Butterworth or Chebyshev normalized lowpass transfer function (see the equation derivation section following the examples for pole location details).

The group delay of the normalized lowpass filter is the derivative of the phase function, b , taken with respect to radian frequency:

$$b = \sum_{k=1}^n \tan^{-1} \left\{ \frac{\omega_k - \Omega}{\sigma_k} \right\} \quad (2-2.5)$$

$$\tau_{g_{\text{nor}}} = \frac{db}{d\Omega} = \sum_{k=1}^n \frac{|\sigma_k|}{\sigma_k^2 + (\omega_k - \Omega)^2} \quad (2-2.6)$$

The group delay is denormalized by multiplying the normalized group delay, Eq. (2-2.6), by the derivative of the transformation function, Eq. (2-2.3), taken with respect to the un-normalized radian frequency, ω .

$$\tau_g = \tau_{g_{\text{nor}}} \cdot \frac{d\Omega}{d\omega} \quad (2-2.7)$$

The transform functions for the bandpass and lowpass cases are:

$$\Omega_{\text{BP}} = \left| \frac{1}{\text{BW}} \left\{ f - \frac{f_o^2}{f} \right\} \right| \quad (2-2.8)$$

$$\frac{d\Omega_{\text{BP}}}{d\omega} = \frac{1}{2\pi\text{BW}} \left\{ 1 + \frac{f_o^2}{f^2} \right\} \quad (2-2.9)$$

where "BW" and " f_o " are the bandwidth and center frequency of the bandpass filter in hertz, and " f " is the frequency to be transformed (in hertz). The center frequency is zero for the lowpass case.

The transform functions for the bandstop and highpass cases are:

$$\Omega_{\text{BS}} = \frac{1}{\Omega_{\text{BP}}} = \left| \frac{\text{BW}}{f - \frac{f_o^2}{f}} \right| \quad (2-2.10)$$

$$\frac{d\Omega_{\text{BS}}}{d\omega} = \frac{\text{BW}}{2\pi} \left\{ \frac{f^2 + f_o^2}{(f^2 - f_o^2)^2} \right\} \quad (2-2.11)$$

The definitions of the terms are the same as above, and the highpass case has zero center frequency also.

The program uses Eqs. (2-2.8) and (2-2.10) to transform the input data to normalized lowpass, and then evaluates Eqs. (2-2.1) and (2-2.6) to obtain the frequency response and normalized lowpass group delay. The group delay is denormalized using Eqs. (2-2.9) or (2-2.11), and the frequency response and group delay are printed (HP-97 only) and displayed.

User Instructions

BUTTERWORTH AND CHEBYSHEV FILTER GROUP DELAY				
C: n DBR	HP: f_o	BP: BW f_o	lin: 0 log: 1	f_{start} Δf
B: n	LP: f_o	BS: BW f_o	start sweep	single freq analysis

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of magnetic card			
2	a) if Butterworth, enter filter order	n	A	
	b) if Chebyshev:			
	enter passband ripple in dB	DBR	ENT↑	
	enter filter order	n	f A	
3	Select filter type and enter characteristics			
	a) if lowpass: enter cutoff frequency*	BW, Hz	B	
	b) if highpass: enter cutoff frequency*	BW, Hz	f B	
	c) if bandstop:			
	enter bandwidth**	BW, Hz	ENT↑	
	enter center frequency	f_o , Hz	C	
	d) if bandpass:			
	enter bandwidth**	BW, Hz	ENT↑	
	enter center frequency	f_o , Hz	f C	
4	If sweep of frequencies is desired:			
	a) select linear or logarithmic sweep (toggle)		f D	0
			f D	1
			f D	0
				:
	b) enter sweep starting frequency in hertz	f_{start}	ENT↑	
	c) enter frequency increment:	f	f E	
	if linear sweep, the increment is additive; if logarithmic, the increment is multiplicative.			
	d) start sweep		D	f, Hz loss, dB phase, deg group delay, sec
5	for analysis at a single frequency	f, Hz	E	analysis above
	NOTE (* & **)			
	The LP & HP cutoff frequency and the BP & BS bandwidth are defined as the -3dB point for Butterworth, and the -DBR point for Chebyshev			

Example 2-2.1

Calculate the amplitude, phase, and group delay characteristics of a third order, 1 dB ripple Chebyshev bandpass filter with 1000 Hz bandwidth and 10000 Hz center frequency. Calculate these characteristics from 8000 Hz to 12000 Hz in linear increments of 100 Hz.

PROGRAM INPUT	PROGRAM OUTPUT				
3. ENT↑ n 1. GSBa DBR 1000. ENT↑ BW 10000. GSBc fo bandpass GSBd } linear 0.000+00 *** } sweep 8000. ENT↑ fstart 100. GSBc Δ f GSBd start analysis	8.000+03	9.000+03	10.00+03	11.00+03	12.00+03
	-45.04+00	-24.06+00	0.000+00	-21.06+00	-39.53+00
	-257.1+00	-240.1+00	0.000+00	-235.9+00	-254.0+00
	21.23-06	110.6-06	802.3-06	121.1-06	21.89-06
	8.100+03	9.100+03	10.10+03	11.10+03	frequency
	-43.48+00	-20.73+00	-345.5-03	-23.78+00	20 log H(jω)
	-256.3+00	-235.4+00	-27.82+00	-239.7+00	∠ H(jω), deg
	23.69-06	151.2-06	723.6-06	92.14-06	τ _g , sec
	8.200+03	9.200+03	10.20+03	11.20+03	
	-41.85+00	-16.90+00	-894.2-03	-26.20+00	
	-255.4+00	-228.8+00	-51.87+00	-242.6+00	
	26.62-06	223.1-06	624.7-06	72.90-06	
	8.300+03	9.300+03	10.30+03	11.30+03	
	-40.13+00	-12.35+00	-906.8-03	-28.38+00	
	-254.4+00	-218.5+00	-74.49+00	-245.0+00	
	30.17-06	371.0-06	667.2-06	59.38-06	
	8.400+03	9.400+03	10.40+03	11.40+03	
	-38.31+00	-6.901+00	-195.5-03	-30.36+00	
	-253.3+00	-199.6+00	-103.5+00	-247.0+00	
	34.53-06	731.4-06	1.006-03	49.47-06	
	8.500+03	9.500+03	10.50+03	11.50+03	
	-36.37+00	-1.466+00	-654.3-03	-32.17+00	
	-251.9+00	-160.9+00	-148.3+00	-248.6+00	
	39.96-06	1.430-03	1.371-03	41.94-06	
	8.600+03	9.600+03	10.60+03	11.60+03	
	-34.30+00	-82.00-03	-4.904+00	-33.85+00	
	-250.4+00	-109.8+00	-189.4+00	-250.0+00	
	46.88-06	1.189-03	844.2-06	36.08-06	
	8.700+03	9.700+03	10.70+03	11.70+03	
	-32.07+00	-865.9-03	-9.967+00	-35.42+00	
	-246.5+00	-76.75+00	-211.4+00	-251.2+00	
	55.92-06	726.3-06	432.4-06	31.41-06	
	8.800+03	9.800+03	10.80+03	11.80+03	
	-29.66+00	-909.1-03	-14.30+00	-36.87+00	
	-246.3+00	-52.79+00	-223.3+00	-252.3+00	
	68.11-06	648.4-06	253.9-06	27.62-06	
	8.900+03	9.900+03	10.90+03	11.90+03	
	-27.01+00	-351.4-03	-17.94+00	-38.24+00	
	-243.6+00	-28.08+00	-230.8+00	-253.2+00	
	85.24-06	737.1-06	168.4-06	24.50-06	

Equations Used and Pole Locations

Butterworth pole locations: The pole locations of a normalized lowpass Butterworth filter lie on a circle in the complex plane. Odd ordered filters have a real pole plus complex conjugate pairs. Even order filters have only complex conjugate pairs. No poles ever lie directly on the $j\omega$ axis. Figure 2-2.1 shows the pole locations for a 5th order normalized Butterworth lowpass filter, and Eqs. (2-2.12) and (2-2.13) show the generalized pole locations.

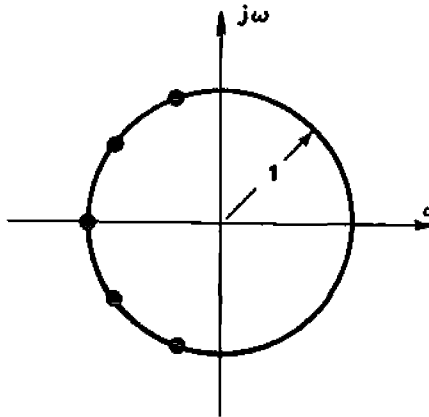


Figure 2-2.1 Butterworth pole locations.

Pole locations:

$$\text{Real part, } \sigma_k = -\sin\left(\frac{2k-1}{2n}\pi\right) \quad (2-2.12)$$

$$\text{Imag part, } \omega_k = \cos\left(\frac{2k-1}{2n}\pi\right) \quad (2-2.13)$$

$$k = 1, 2, \dots, n$$

(trig argument is in radians)

The attenuation of the normalized Butterworth lowpass filter is 3 dB at $\omega = 1$. At other frequencies, the attenuation in dB is expressed by:

$$A_{\text{dB}} = 10 \log(1 + \omega^{2n}) \quad (2-2.14)$$

As shown by this equation, the attenuation monotonically increases as frequency increases. Figure 2-2.2 shows the general shape of the Butterworth response.

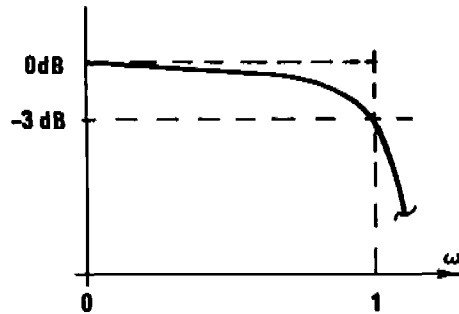


Figure 2-2.2 Normalized Butterworth amplitude response.

Chebyshev pole locations: The normalized lowpass pole locations of a Chebyshev lowpass filter lie on an ellipse with major axis dimension $\cosh a$, and minor axis dimension $\sinh a$ where a is defined by:

$$a = 1/n \sinh^{-1}(1/\epsilon) \quad (2-2.15)$$

The parameter ϵ is related to the passband ripple in dB by:

$$\epsilon = (10^{0.1\epsilon_{dB}} - 1)^{1/2} \quad (2-2.16)$$

Using these quantities, the real and imaginary parts of the pole locations are given by Eqs. (2-2.17) and (2-2.18). Figure 2-2.3 shows the pole locations for a fifth order Chebyshev filter.

$$\text{Real part, } \sigma_k = -(\sinh a) \left(\sin \frac{2k-1}{2n} \pi \right) \quad (2-2.17)$$

$$\text{Imag part, } \omega_k = (\cosh a) \left(\cos \frac{2k-1}{2n} \pi \right) \quad (2-2.18)$$

$$k = 1, 2, \dots, n$$

(trig argument is in radians)

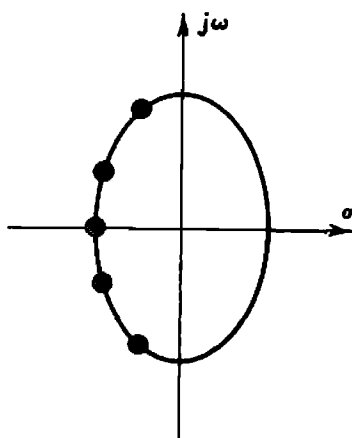


Figure 2-2.3 Chebyshev pole locations (5th order).

The passband edge of a Chebyshev filter is defined as the highest frequency where the response is ϵ_{dB} down. Remember, the Chebyshev passband response oscillates within a band of ϵ_{dB} . Fourth and fifth order Chebyshev responses are shown in Fig. 2-2.4.

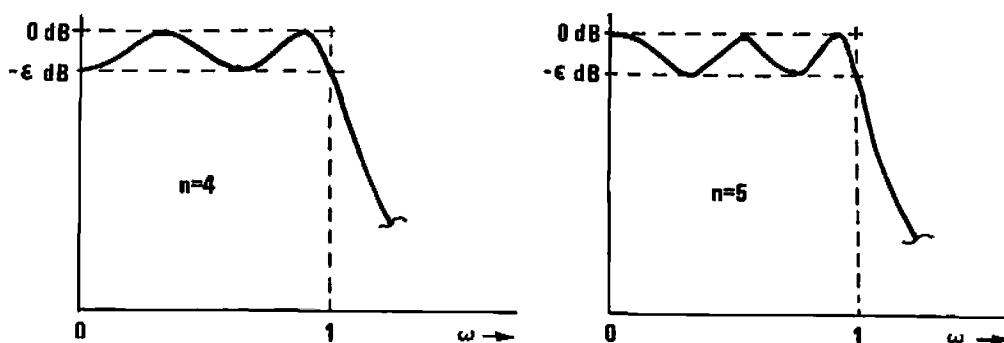


Figure 2-2.4 Chebyshev normalized lowpass filter responses.

The normalized frequency where the Chebyshev filter response is 3 dB down is given by the expression:

$$f_{-3\text{dB}} = \cosh \left\{ \frac{1}{n} \cosh^{-1} \left(\frac{1}{\epsilon} \right) \right\} \quad (2-2.19)$$

Comparing the equations that define the pole locations for the Butterworth and Chebyshev filters, one will notice that the only difference is the Chebyshev poles are modified by hyperbolic functions. If the $\sinh a$ and $\cosh a$ functions are defined to be unity, then the

Chebyshev equations become the Butterworth equations. This technique is used in the program. Chebyshev poles are always calculated; however, if Butterworth response is selected, the hyperbolic functions are not calculated, but are set equal to one in register storage.

Another difference between Butterworth and Chebyshev filters lies in the definition of the bandedge. Butterworth response is 3 dB down at the bandedge, and Chebyshev response is ϵ_{dB} down at the bandedge where ϵ_{dB} is the passband ripple in dB. Flag 1 is used to indicate the filter type, and is set for Butterworth. When the pole locations are calculated, flag 1 is tested to see what equation, if any, is to be used to convert the given passband edge frequency into the appropriate frequency for the filter type being used.

Program Listing I

001 *LBLA LOAD BUTTERWORTH FILTER ORDER				055 *LBLC LOAD BW AND f_o FOR BANDSTOP			
002 ST01 store n				056 SF0			
003 EEX				057 GT01			
004 ST05 cosh=1 for Butterworth				058 *LBLc LOAD BW AND f_o FOR BANDPASS			
005 ST06 sinh=1 " "				059 CF0			
006 RCL1 recall n to display				060 *LBL1			
007 RTN				061 X ² calc & store f_o^2			
008 *LBLa LOAD CHEB ORDER AND DB RIPPLE				062 ST02			
009 ST0C store dB ripple				063 R↓			
010 R↓				064 ST03 store bandwidth			
011 ST01 store n				065 RTN			
012 RCLC calculate epsilon, ϵ				066 *LBLD START SWEEP			
013 EEX				067 SPC			
014 1 $\epsilon = \sqrt{10^{0.4 A_{max}} - 1}$				068 *LBL7			
015 ÷				069 RCL8			
016 10 ^x				070 PRTX			
017 EEX				071 GSBE			
018 -				072 RCL9			
019 JX				073 F1?			
020 1/X calculate $\sinh^{-1}(1/\epsilon)$				074 GT01			
021 ENT↑				075 ST+8 linear sweep increment			
022 X ²				076 GT07			
023 EEX				077 *LBL1			
024 +				078 ST×8 log sweep increment			
025 JX				079 GT07			
026 +				080 *LBLd SELECT LIN/LOG SWEEP			
027 RCL1 calculate $\sinh(\frac{1}{n} \sinh^{-1}(\frac{1}{\epsilon}))$				081 F1?			
028 1/X				082 GT01			
029 Y ^x				083 SF1			
030 ENT↑ $\sinh^{-1} x = \ln(x + \sqrt{x^2 + 1})$				084 EEX			
031 ENT↑ $Y^{\frac{1}{n}x} = e^{\frac{1}{n} \ln x}$				085 RTN			
032 ENT↑				086 *LBL1			
033 1/X $\sinh x = \frac{e^x - e^{-x}}{2}$				087 CF1			
034 -				088 CLX			
035 ST06				089 RTN			
036 R↓ calculate $\cosh(\frac{1}{n} \sinh^{-1}(\frac{1}{\epsilon}))$				090 *LBLc LOAD SWEEP f_{start} AND Δf			
037 1/X				091 ST09			
038 + $\cosh x = \frac{e^x + e^{-x}}{2}$				092 R↓			
039 ST05				093 ST08			
040 2				094 RTN			
041 ST=5							
042 ST=6							
043 RTN							
044 *LBLb LOAD f_o FOR LOWPASS CASE							
045 CF0							
046 GT01							
047 *LBLb LOAD f_o FOR HIGHPASS CASE							
048 SF0							
049 *LBL1							
050 ST03 store f_o							
051 CLX $f_o^2 = 0$ for lowpass and							
052 ST02 highpass cases							
053 RCL3							
054 RTN							

REGISTERS									
0 present frequency	1 n	2 f_o^2	3 bandwidth	4 f	5 cosh	6 sinh	7 Σ delay	8 $\prod \frac{\sigma^2 + \omega^2}{\sigma^2 + (\omega - \omega_c)^2}$	9 Σ phase
S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
A σ_R	B ω_R	C A_{max}	D Δf	E Ω	I index				

Program Listing II

095	*LBL5	LOAD ANALYSIS FREQUENCY	147	RCLA		form in R8:
096	STO4		148	X2		
097	RCL2	store frequency and form:	149	RCLB		
098	RCL4		150	X2		
099	=		151	+		
100	-	$\Omega = \frac{1}{BW} \left\{ f - \frac{f_o^2}{f} \right\}$	152	STX8		
101	RCL3		153	DSZ1		
102	=		154	GT00		decrement k and test for loop exit
103	F0?	if bandstop, $\frac{1}{\Omega} \rightarrow \Omega$	155	RCL7		
104	1/X		156	Pi		
105	ABS	store $ \Omega $	157	ENT1		calculate: $\frac{\sum \gamma}{2\pi}$
106	STOE		158	+		
107	RCL1		159	=		
108	STO1	initialize loop:	160	RCL3		
109	CLX	$n \rightarrow RI$	161	F0?		jump if highpass or bandstop
110	STO7	$\Sigma_7 = 0$	162	GT08		
111	STO9	$\Pi_9 = 1$	163	=		
112	EEX	$\Sigma_9 = 0$	164	RCL2		
113	STO8		165	RCL4		lowpass or bandpass $\frac{d\Omega}{d\omega}$
114	*LBL0		166	X2		
115	RCL1		167	=		
116	ENT1		168	EEX		$\gamma_g = \left\{ 1 + \frac{f_o^2}{f^2} \right\} \frac{\Sigma_7}{2\pi BW}$
117	+		169	+		
118	EEX	calculate angle:	170	X		
119	-		171	GT09		
120	RCL1	$\theta_k = 90 \left(\frac{2k-1}{n} \right)$	172	*LBL8		
121	=		173	X		
122	9		174	RCL4		
123	0		175	X2		highpass or bandstop $\frac{d\Omega}{d\omega}$
124	X		176	RCL2		
125	EEX	calculate $\sin \theta_k$ & $\cos \theta_k$	177	+		
126	+R		178	X		
127	RCL5		179	RCL4		$\gamma_g = \left\{ \frac{f^2 + f_o^2}{(f^2 - f_o^2)^2} \right\} \frac{BW}{2\pi} \cdot \Sigma_7$
128	X	form and store ω_k	180	X2		
129	STO8		181	RCL2		
130	RCL5	form: $\omega_k - \Omega$	182	-		
131	-		183	X2		
132	X2Y		184	=		
133	RCL6	form and store σ_k	185	*LBL9		
134	X		186	RCL8		
135	STO4		187	LOG		calculate and print amplitude response in dB
136	+P		188	EEX		
137	X2	form and sum:	189	1		
138	RCLA		190	X		
139	X2Y	σ_k	191	PRTX		
140	=		192	R4		
141	ST+7	$\sigma_k^2 + (\omega_k - \Omega)^2$	193	RCL9		calculate and print phase response in degrees
142	RCLA		194	F0?		
143	=	form: $\frac{1}{\sigma_k^2 + (\omega_k - \Omega)^2}$	195	CHS		
144	STX8		196	PRTX		
145	X2Y		197	R4		print group delay
146	ST+9	sum phase element	198	PRTX		
			199	SPC		
			200	RTH		

LABELS					FLAGS	SET STATUS		
A BUTTERWORTH	B LP: f_o	C BS: BW $\uparrow f_o$	D START SWEEP	E $f \rightarrow \gamma_g, etc$	0 CLR: LP or BP SET: HP or BS	FLAGS	TRIG	DISP
a CHEBYCHEV	b HP: f_o	c BP: BW $\uparrow f_o$	d SELECT LOG/LIN SWP	e $f_{START} \uparrow \Delta f$	1 CLR: LINEAR SET: LOG	ON OFF	DEG	FIX
0 SUMMATION	1 MULTIPLE LABEL	2	3	4	2	0	GRAD	SCI
LOOP START						1	RAD	ENG
5		7 SWEEP START	8 BS, HP OUTPUT	9 PRINT & SPACE SUBROUTINE	3	2		n <u>3</u>

Suggested HP-67 program changes. The "print" command is used to output data in the program listing. These print commands are located at the following line numbers: 070, 191, 196, and 198. HP-67 users may prefer either a "pause" or "R/S" command replacing the "print" command at the above line numbers. If the R/S change is made, the program execution will stop at each data output point. To resume program execution, execute a "R/S" command from the keyboard.

PROGRAM 2-3 BUTTERWORTH AND CHEBYSHEV LOWPASS NORMALIZED COEFFICIENTS.

Program Description and Equations Used

This program calculates the normalized (1 ohm, 1 radian/second cut-off) element values for either the Butterworth (maximally flat) or Chebyshev (equal ripple passband) all pole lowpass filter approximations. The filters can be either doubly terminated (resistors at both ends) or singly terminated (driven from a voltage or current source, i.e., R_T approaches infinity). Because of duality, two filter topologies exist for the ladder filter as shown in Fig. 2-3.1. These topologies are bilateral and passive; therefore, the voltage source can be placed in series with the left-hand termination resistor as shown, or in series with the right-hand termination resistor. By proper selection of the filter topology and input port designation, the singly terminated filter can be driven from either a current or voltage source and resistively terminated, or driven from a Thevenin (or Norton) equivalent source and terminated in either a short or open circuit.

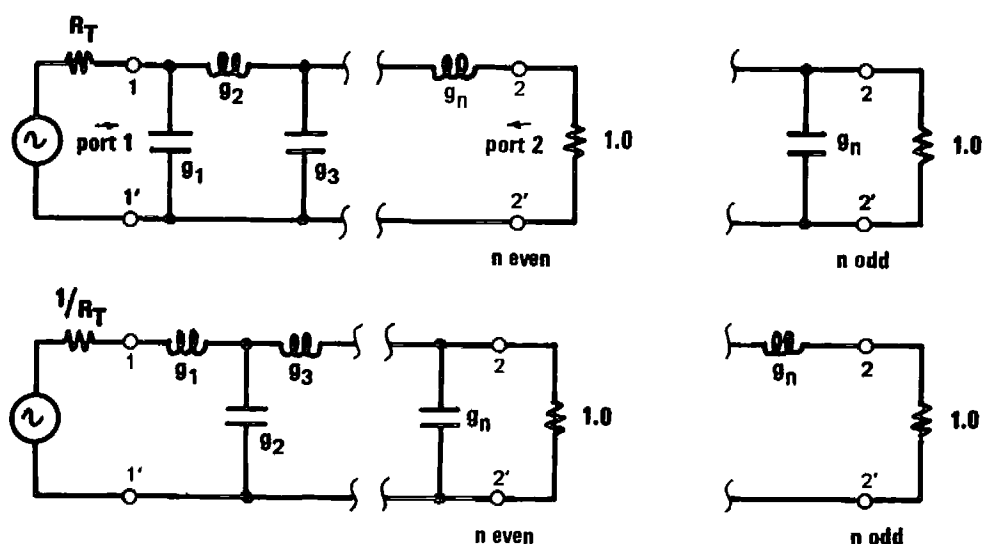


Figure 2-3.1 Lowpass ladder filter topologies.

The search for explicit formulas for ladder filter element values has extended over four decades. Bennett [7] provided the remarkably simple formula for equally terminated Butterworth filters in 1932. Norton [39] provided the formulas for the open circuited Butterworth case in 1937. Belevitch [5] published formulas for the doubly terminated Chebyshev case in 1952. Orchard [40] gathered together this previous work and provided the missing fourth formula set for the open circuited Chebyshev case in 1953. Green [28] went on to generalize these formulas for any ratio of resistive terminations in 1954. These formulas had been numerically tested, but never formally proved. Doyle [22] provided a "hammer and tongs" brute force proof for the Butterworth case with arbitrary terminations. Meanwhile, in Japan, Takahasi [51], had made an ingenious proof of the formulas for the arbitrarily terminated Chebyshev case and extended it to the Butterworth case by a limiting process. Takahasi published his independent work in 1951 (in Japanese), but it was not discovered by the rest of the world until 1957. Weinberg and Slepian [54] discuss Takahasi's results. Takahasi's results can also be found in the back of Weinberg's book [53].

The recursion relations given by Eqs. (2-3.1) through (2-3.16) are adapted from Takahasi. If the filter order is odd, the filter can be terminated by 1 ohm at one port and by any resistance 1 ohm or larger at the other port. By using the dual topology, the termination resistance can be any resistance 1 ohm or smaller (including 0 ohms). If the filter is an even ordered Chebyshev design, then the first port termination resistance must be larger than 1 ohm. The minimum value of this termination resistance is given by Eq. (2-3.18).

Takahasi's recursion relationships:

$$g_{r+1} = \frac{A \cdot s_{r-\frac{1}{2}} \cdot s_{r+\frac{1}{2}}}{g_r (\xi^2 + \eta^2 - \xi \eta c_r + s_r^2)} \quad (2-3.1)$$

where

$$r = 1, 2, \dots, n-1$$

$$g_1 = \frac{\sqrt{A} \cdot s_{\frac{1}{2}}}{R_T (\xi - \eta)} \quad (2-3.2)$$

$$s_q = 2 \cdot \sin\left(\frac{\pi \cdot q}{n}\right) \quad (2-3.3)$$

$$c_q = 2 \cdot \cos\left(\frac{\pi \cdot q}{n}\right) \quad (2-3.4)$$

For normalized lowpass Butterworth coefficients:

$$A = 1 \quad (2-3.5)$$

$$\xi = 1 \quad (2-3.6)$$

$$\eta = \left(\frac{R_T - 1}{R_T + 1} \right)^{1/n} \quad (2-3.7)$$

$$s_r^2 \equiv 0 \quad (2-3.8)$$

For normalized lowpass Chebyshev coefficients:

$$A = 4 \quad (2-3.9)$$

$$\xi = F(1) \quad (2-3.10)$$

$$\eta = F \left(1 - \frac{4 \cdot v R_T}{(1 + R_T)^2} \right) \quad (2-3.11)$$

$$v = \begin{cases} 1 + \xi^2, & n \text{ even} \\ 1, & n \text{ odd} \end{cases} \quad (2-3.12)$$

$$F(x) = u - \frac{1}{u} \quad (2-3.13)$$

$$u = \left(\sqrt{\frac{x}{\epsilon^2}} + \sqrt{\frac{x}{\epsilon^2} + 1} \right)^{1/n} \quad (2-3.14)$$

$$y = 10^{\epsilon \text{ dB}/20} \quad (2-3.15)$$

$$\epsilon^2 = y^2 - 1 \quad (2-3.16)$$

$$\omega_{-3\text{dB}} = \cosh \left(\frac{1}{n} \cosh^{-1} \frac{1}{\epsilon} \right) \quad (2-3.17)$$

$$R_L \Big|_{\substack{\text{min} \\ n \text{ even}}} = \left(\frac{\sqrt{\frac{y+1}{y-1}} - 1}{\sqrt{\frac{y+1}{y-1}} + 1} \right)^2 \quad (2-3.18)$$

When the termination ratio is neither 0, ∞ , or as close as possible to 1, there are more than one possible set of ladder element values for the same filtering function. These alternate sets are synthesized by realizing the reflection zeros in the RHP, or RHP-LHP alternating rather than in the LHP. The closed form formulas realize the LHP reflection zero case. This realization generally results in a ladder filter with minimum sensitivity to component value changes. For a more comprehensive discussion of reflection zeros and order of realization, see Weinberg [53], chapter 13.

The program is set up to calculate the minimum termination resistance, and if the value loaded by the user is less than the minimum, the minimum value replaces the user loaded value.

When the termination resistance is allowed to approach infinity (or 0 using the dual topology), the filter only has one termination resistor, and is called "singly terminated." These singly terminated filters are used where it is inconvenient, or wasteful of power, to use the doubly terminated filter. Because the loaded Q's of the resonant circuits become higher as the unloaded end of the filter is approached, the singly terminated design is more difficult to align.

Often, the LC filter is used as a basis for an active filter design such as Szentirmai's leapfrog topology [48], Bruton's frequency dependent negative resistor (FDNR) approach [10], or Orchard and Sheahans' type 11 active simulation [42]. Using the doubly terminated LC topologies for the active filter basis, will also mean that the active filters will be less critical toward alignment.

User Instructions

BUTTERWORTH AND CHEBYSHEV LP NORMALIZED COEFFICIENTS				
Load n	Load R_T ($R_T \geq 1$)	calculate Butterworth values	calculate ϵ_{dB} Cheb values	calculate -3_{dB} Cheb values

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of magnetic card			
2	Load filter order ($n \leq 12$ maximum) If the normalized lowpass prototype is to be transformed to bandpass types 6, 7, 8, 9, 10, or 11, and Chebyshev response is desired, the filter order must be odd so the terminations will be equal resistance.	n	A	n
3	Load the termination resistance desired The termination resistance must be 1 or larger. For terminations less than 1 ohm (normalized) load the reciprocal value and use the dual topology. See note after step 7.	R_T	B	
4	For Butterworth coefficients		C	R_T space ϵ_1 ϵ_2 : ϵ_n space $R_L = 1$
5	For Chebyshev coefficients that define a filter that is $- \epsilon_{dB}$ down at $\omega = 1$ If even ordered Chebyshev has been selected, the minimum source resistance is calculated and is used if the resistance loaded in step 3 is smaller.	ϵ_{dB}	D	$\omega - 3_{dB}$ space R_T space ϵ_1 ϵ_2 : ϵ_n space $R_L = 1$

BUTTERWORTH AND CHEBYSHEV LP NORMALIZED COEFFICIENTS				2
		CONTINUED		

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
6	<p>For Chebyshev coefficients that define a filter that is 3 dB down at $\omega=1$</p> <p>The minimum source resistance comment for even ordered Chebyshev filters in step 5 also applies here.</p>	εdB	E	ω -ε dB space R_T space ξ_1 ξ_2 : ξ_n space R_L 1
7	<p>Go back and repeat any step.</p> <p>The last calculated coefficients will be in storage for use by other programs in this section.</p>			
	<p>Notes on termination resistance:</p> <p>To enable the program to output coefficients for the singly terminated case, load 10^5 ohms for R_T if Chebyshev response is going to be selected, or load 10^9 ohms if Butterworth response is going to be selected. Either one of these values is a reasonable approximation to infinity when compared to one ohm. The maximum termination resistance in the Chebyshev case is limited to 10^5 ohms because of a small difference between big numbers problem. 10^5 ohms is a compromise between an approximation to infinity and the number of significant digits in the coefficients. With 10^5 ohms, the answers are significant to five places.</p>			

Example 2-3.1

Find the normalized lowpass coefficients for a 4th order, $\frac{1}{2}$ dB ripple Chebyshev filter that is doubly terminated, and has the minimum termination resistance. The filter response should be 3 dB down at the pass-band edge ($\omega = 1$) relative to the response at dc.

HP-97 printout

```

      4. 6554  load filter order
      1. 6585  load termination resistance desired
      .5 6882  enter passband ripple in dB and calculate
                Chebyshev coefficients
914.828-03 ***  $\omega_{-3dB}$  (output)
1.98406+00 *** minimum termination resistance allowed at port 1
920.243-03 ***  $g_1$ 
2.58640+00 ***  $g_2$ 
1.30355+00 ***  $g_3$ 
1.82581+00 ***  $g_4$ 

1.00000-00 *** port 2 termination resistance

```

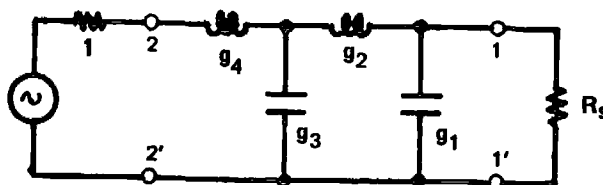


Figure 2-3.2 One topology for normalized lowpass filter (port ordering reversed).

Example 2-3.2

Find the normalized lowpass coefficients for a 10th order Butterworth filter that is singly terminated.

HP-97 printout

```

10. 6:ET  load filter order
1.705 6:EE  load termination resistance (use 105 for Chebyshev)
6:EC      calculate Butterworth coefficients

1.000000+0j  ***  termination resistance at port 1

1.56434+0j  ***  g1
1.85516+0j  ***  g2
1.81211+0j  ***  g3
1.55665+0j  ***  g4
1.51062+0j  ***  g5
1.5203+0j   ***  g6
1.24962+0j  ***  g7
762.517-0j  ***  g8
465.375-0j  ***  g9
156.434-0j  ***  g10

1.000000+0j  ***  termination resistance at port 2

```

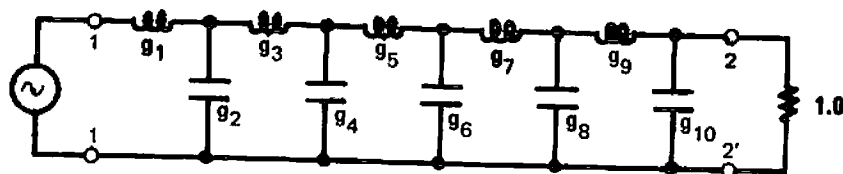


Figure 2-3.3 One form for normalized lowpass filter (dual topology used).

Address	Operation	Comment
001	*LBLA	LOAD FILTER ORDER
002	ST06	store filter order
003	PI	
004	XZY	calculate and store π/n
005	÷	
006	ST01	
007	ROLE	
008	RTN	
009	*LBLB	LOAD DESIRED TERMINATION
010	ST0D	RESISTANCE
011	RTN	
012	*LBLC	CALCULATE BUTTERWORTH COEFS
013	CF1	
014	EEX	set $\omega_{-3dB} = 1$
015	ST02	
016	ST02	set $\xi = 1$
017	RCLD	
018	EEX	calculate and store:
019	-	
020	RCLD	
021	EEX	
022	+	
023	÷	
024	GSB4	
025	ST03	
026	ST08	jump around Cheb setup
027	*LBLB	CALCULATE -3dB CHEBYSHEV
028	SF0	COEFFICIENTS
029	ST02	
030	*LBLD	CALCULATE - dB CHEBYSHEV
031	CF0	COEFFICIENTS
032	*LBLB	
033	SF1	indicate Chebyshev
034	EEX	
035	1	calculate and store:
036	÷	
037	10X	
038	EEX	$\epsilon^2 = 10^{\epsilon_{dB}/40} - 1 \rightarrow R_3$
039	-	
040	ST05	
041	EEX	calculate and store:
042	+	
043	JX	$y = 10^{\epsilon_{dB}/20} \rightarrow R_E$
044	ST0E	
045	EEX	calculate:
046	+	
047	ROLE	
048	EEX	
049	-	
050	÷	
051	JX	
052	ST0E	
053	EEX	
054	+	
055	ROLE	
056	EEX	
057	-	
058	÷	
059	XZ	
060	RCLD	if filter order is even,
061	XZY0	and R_T desired is less than
062	R4	R_{Tmin} , replace R_T desired
063	GSB6	by R_{Tmin}
064	F29	
065	F29	
066	ST0D	
067	EEX	calculate and store:
068	GSB7	$\xi = F(1) \rightarrow R_2$
069	ST02	
070	RCL7	calculate and store:
071	1/X	
072	JT	
073	LSTX	
074	EEX	
075	-	
076	JY	$\omega_{-3dB} = \cosh\left(\frac{1}{n} \cosh^{-1} \frac{1}{\epsilon}\right) \rightarrow R_0$
077	+	
078	GSB4	
079	1/X	
080	+	
081	2	
082	-	
083	ST08	
084	F07	calculate $\omega_{\epsilon dB}$ if ω_{-3dB}
085	1/X	coefficients requested
086	GSB7	print ω_{-3dB} , or $\omega_{\epsilon dB}$
087	GSB6	
088	RCL3	calculate
089	EEX	$v = \begin{cases} 1 + \epsilon^2, & n \text{ even} \\ 1, & n \text{ odd} \end{cases}$
090	÷	
091	F29	
092	LSTX	
093	4	
094	+	calculate and store:
095	RCLD	
096	X	
097	RCLD	
098	EEX	
099	+	
100	XZ	
101	÷	
102	CHS	$\eta = F\left(1 - \frac{4vR_T}{(1+R_T)^2}\right) \rightarrow R_3$
103	EEX	
104	+	
105	X<0?	X<0 default
106	CLX	
107	GSB7	
108	ST03	
109	*LBL0	
110	RCLD	
111	PZS	
112	CLRG	clear coefficient registers

Program Listing II

NOTE TRIG MODE

113	P25		169	GT01	
114	ST00		170	SPC	$R_L = 1$
115	GSB3	print actual termination R	171	EEX	
116	1/X		172	*LBL3	print and space subroutine
117	ST04	initialize registers	173	PRTX	
118	EEX		174	SPC	
119	1		175	RTN	
120	ST01		176	*LBL5	subroutine to finish g_{r+1}
121	EEX		177	-	
122	ST07		178	ST÷4	calculation, store result,
123	.		179	RCL0	
124	5		180	PCL4	and setup g_r for next
125	ST08	calculate and store:	181	ST÷4	
126	GSB8		182	ST÷4	iteration
127	ST09		183	F00	
128	ENT↑	$g_1 = \frac{A^{1/2} \cdot g_{1/2}}{R_T (\xi - \eta)}$	184	x	
129	F1?		185	ST01	
130	+		186	PRTX	
131	ST×4	if Chebyshev use A = 4,	187	RTN	
132	RCL2	otherwise use A = 1	188	*LBL6	subroutine to set flag 2
133	RCL3		189	RCL6	if filter order is odd
134	GSB5		190	2	
135	*LBL1	recursion loop start	191	÷	
136	ISZ↑	increment register index	192	FRC	
137	RCL9	$s_{r+1/2}$ start g_{r+1} calculation	193	X≠0?	
138	ST×4		194	SF2	
139	EEX		195	R4	
140	ST+8		196	RTN	
141	RCL8		197	*LBL7	subroutine to calculate:
142	GSB8	$s_{r+1/2}$	198	RCL3	
143	ST×4		199	÷	
144	ST03		200	JX	$F(x) = u - \frac{1}{u}$
145	4		201	ENT↑	
146	F1?	if Chebyshev, use A = 4	202	X²	
147	ST×4		203	EEX	
148	RCL7	finish g_{r+1} calculation	204	+	
149	GSB8		205	JX	$u = \left\{ \sqrt{\frac{x}{\epsilon^2}} + \sqrt{\frac{x}{\epsilon^2} + 1} \right\}^{1/n}$
150	X²		206	÷	
151	RCL2		207	GSB4	
152	X²		208	1/X	
153	F1?	add s_r^2 if Chebyshev	209	-	
154	+		210	RTN	
155	RCL3		211	*LBL4	subroutine to calculate:
156	X²		212	RCL6	
157	+		213	1/X	$()^{1/n} \rightarrow R_x \rightarrow R_y$
158	RCL6		214	yx	
159	RCL2		215	ENT↑	
160	x		216	RTN	
161	RCL3		217	*LBL8	subroutine to calculate:
162	x		218	RCL1	
163	GSB5		219	x	$s_q = 2 \sin \left(\frac{\pi q}{n} \right) \rightarrow R_x$
164	EEX	increment r	220	2	
165	ST+7		221	+R	
166	RCL7		222	ST0E	$c_q = 2 \cos \left(\frac{\pi q}{n} \right) \rightarrow R_E$
167	RCL6	test for loop exit	223	R↓	
168	X>Y?		224	RTN	

LABELS					FLAGS	SET STATUS		
A filter order	B R_T	C Butterworth coefficients	D -6dB Cheb coefficients	E -3dB Cheb coefficients	0 -3dB Cheb	FLAGS		
a	b	c	d	e	1 Chebyshev	ON OFF	DEG	FIX
0 recursion loop setup	1 recursion loop start	2 Chebyshev -3dB jump	3 print & space	4 $()^{1/n}$	2 add number	0 <input type="checkbox"/>	GRAD	SCI
5 store g_{r+1}	6 SF2 if n odd	7 $F(x)$	8 s_q & c_q	9	3	1 <input type="checkbox"/>	RAD <input type="checkbox"/>	ENG <input type="checkbox"/>
						2 <input type="checkbox"/>		n <u>5</u>
						3 <input type="checkbox"/>		

PROGRAM 2-4 NORMALIZED LOWPASS TO BANDSTOP, LOWPASS, OR HIGHPASS LC LADDER TRANSFORMATIONS.

Program Description and Equations Used

This program transforms the normalized lowpass coefficients (1 ohm, 1 radian/sec) into the frequency and impedance scaled lowpass, highpass, or bandstop topologies. The normalized lowpass coefficients are obtained from register storage and either must be loaded by the user (for other than Butterworth and Chebyshev filters), or are generated and stored by Program 2-3 for the Butterworth and Chebyshev approximations.

Every linear, passive, lumped, time-invariant, bilateral electrical network has a dual topology. LC filters are a member of this class of networks; hence, two electrically equivalent networks can be formed from the transformation or scaling of the normalized lowpass structure. These two forms are designated as form 1, and form 2 in the program. Having two forms available provides the designer some relief from awkward component values, or the opportunity to choose the minimum inductor topology.


The program is separated into three parts which share common sub-routines. These sections are 1) de-normalization parameter input (bandwidth, termination resistance level, and center frequency), 2) bandstop denormalization and transformation, and 3) lowpass and highpass denormalization and transformation. In analytical form, these transformations are discussed next.

Lowpass filters: No transformation is necessary for converting the normalized lowpass to the un-normalized lowpass filters. The normalized lowpass values need only be scaled to the desired operating impedance level and cutoff frequency. The object of the scaling procedure is to end up with filter elements that have the same impedance ratios to the termination resistance at the cutoff frequency as the normalized filter has at 1 radian/second to 1 ohm. The mechanics of this scaling procedure are:


$$L, \text{ scaled} = (L, \text{ normalized}) \cdot (R / (2\pi \cdot BW)) \quad (2-4.1)$$

$$C, \text{ scaled} = (C, \text{ normalized}) / (2\pi \cdot BW \cdot R) \quad (2-4.2)$$

The normalized L's and C's are equal to the g's from Program 2-3, and BW and R represent the cutoff frequency in Hz and the load resistance in ohms respectively. Figure 2-4.1 shows the two forms of the low-pass filter; either port can be designated as input, i.e., the input voltage source can go in series with either termination resistor.

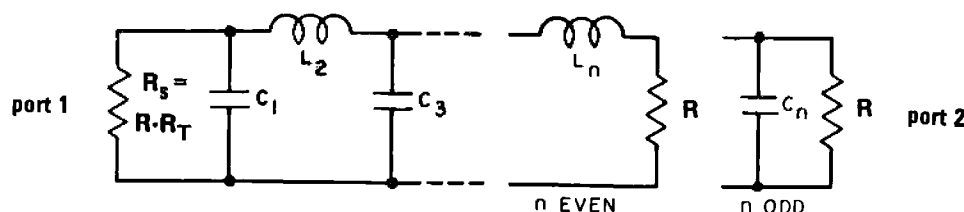

FORM 1

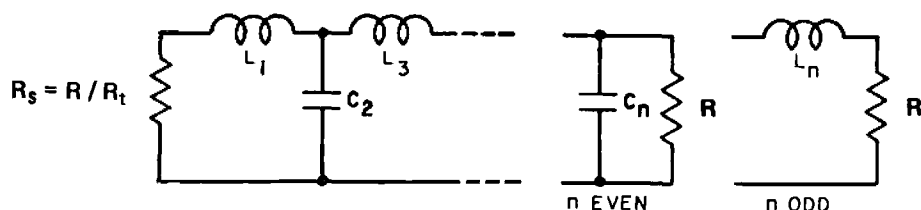

FORM 2

Figure 2-4.1 Two forms of lowpass filter.

Highpass filters: The highpass transformation is accomplished by replacing s by $1/s$. Since sinusoidal frequencies are of primary interest, s may be replaced by $j\omega$, or $1/s$ by $-j/\omega$. Conceptually, this operation is equivalent to replacing each normalized lowpass capacitor with an inductor and vice-versa. The normalized values of the highpass elements are the reciprocals of the lowpass values, i.e., the g's calculated in Program 2-3 become $1/g$'s when converted to normalized highpass coefficients. Fig. 2-4.2 shows the two forms of the highpass filter, and the element values are calculated using Eqs. (2-4.1) and (2-4.2) with the normalized highpass coefficients. Either port can be designated as the input as in the lowpass case (or in any other passive LC case).

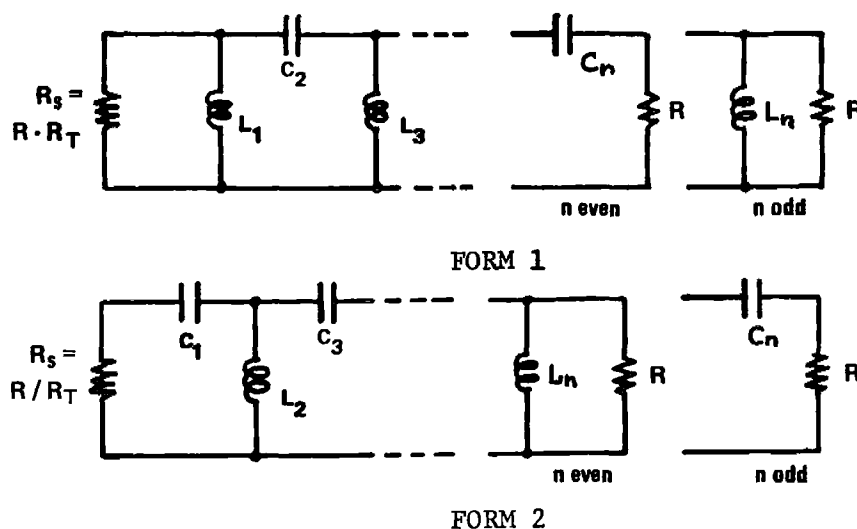


Figure 2-4.2 Two forms of highpass filter.

The highpass transformation may also be applied analytically; for example, the transformation is applied to the Butterworth normalized lowpass magnitude response equation (Eq. (2-4.3)) to convert it to the normalized highpass form (Eq. (2-4.4)).

$$|A(\omega)|_{LP} = \frac{1}{\sqrt{1 + \omega^{2n}}} \quad (2-4.3)$$

$$|A(\omega)|_{HP} = \frac{\omega^n}{\sqrt{1 + \omega^{2n}}} \quad (2-4.4)$$

For more information, see Weinberg [53]. Blinchikoff and Zverev [8] also has an excellent discussion of transformations both conventional as used herein, and unconventional to preserve LP transient characteristics.

Bandpass filters: The bandpass filter is a combination of a highpass and a lowpass filter. The loaded Q , Q_L , of the filter is a measure of the separation between the highpass and lowpass portions. To accomplish the transformation from normalized lowpass to un-normalized bandpass, s in the normalized lowpass expression is replaced by the function of s shown in Eq. (2-4.5).

$$s \Rightarrow Q_L \left\{ \frac{s}{\omega_o} + \frac{\omega_o}{s} \right\} \quad (2-4.5)$$

$$Q_L = \frac{f_o}{BW} \quad (2-4.6)$$

Where f_o and BW are the center frequency and bandwidth in hertz.

Conceptually, the lowpass elements are replaced with new elements that exhibit the same impedance behavior at the bandpass filter center frequency as did the original elements at dc. Ideal inductors have zero reactance at dc, and are replaced with series resonant tank circuits which resonate at the bandpass filter center frequency, f_o . Ideal (lossless) series tank circuits have zero reactance at resonance. Likewise, each lowpass capacitor is replaced with a parallel resonant tank circuit which resonates at the bandpass filter center frequency. When the loaded Q is greater than 10 or so, the bandpass filter is called narrowband. In this case, other tank circuits can be synthesized to approximate the impedance behavior of the series and parallel resonant tank circuits for frequencies within the vicinity of the passband. Bandpass filters and narrowband transformations are discussed in Programs 2-5, 2-6, and 2-11.

Bandstop filters: The bandstop transformation is the reciprocal of the bandpass transformation, and is analogous to the lowpass-highpass transformation. Highpass filters are actually bandstop filters which have zero center frequency. To accomplish the bandstop transformation, s is replaced by:

$$s \Rightarrow \frac{1}{Q_L \left\{ \frac{s}{\omega_o} + \frac{\omega_o}{s} \right\}} \quad (2-4.7)$$

Conceptually the bandstop transformation is accomplished by designing a highpass filter whose cutoff frequency equals the bandwidth of the desired bandstop filter. Each shunt inductor in the highpass filter is series resonated with a capacitor at the desired center frequency of the filter. Likewise, each series capacitor is parallel resonated with an inductor at the desired filter center frequency.

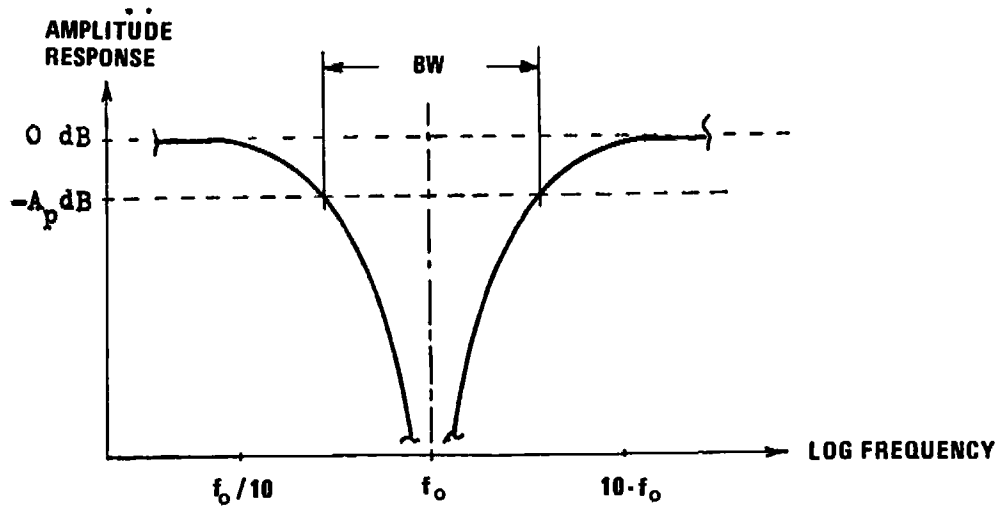


Figure 2-4.1 Bandstop filter parameters.

If g_1, g_2, \dots, g_n are the normalized lowpass coefficients and R_T is the normalized termination resistance, then one form of the bandstop filter is shown by Fig. 2-4.2 .

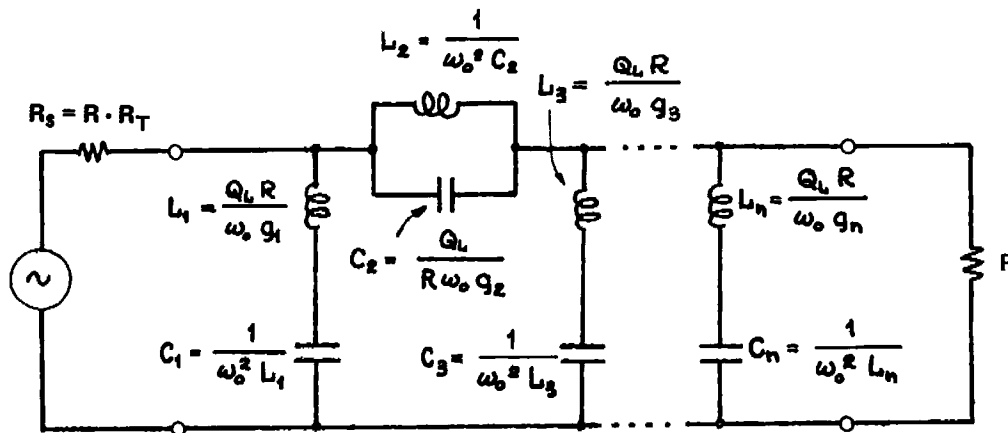


Figure 2-4.2 Bandstop filter form 1 (program output heading "21"), odd order filter shown; even order filter lacks last series tank circuit.

The other form of this filter is the dual of the first:

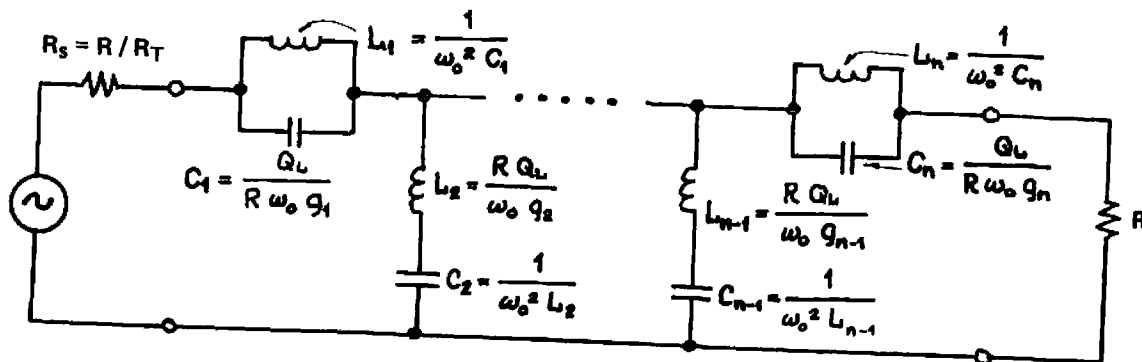


Figure 2-4.3 Bandstop form 2 (program output heading "22"), odd order filter shown; even order filter lacks last parallel tank circuit.

The program calculates both forms of these bandstop filters.

Filter physical realizability. The preceding transformations are used by this program and result in LC network schematics that will produce the desired response. Not all LC networks that can be drawn on paper as schematics are physically realizable. For example, a network branch consisting of a 1 μF capacitor in series with a 10 nh inductor would be nearly impossible to realize since the self inductance of the capacitor is much larger than the total required inductance. Table 2-4.1 is a reproduction of Table 7.1 from White [56], and shows the degree of physical realizability of lowpass and highpass filters. The physical realizability of a filter is assigned one of four possible scores. These scores are defined as follows:

Readily realizable (R):	$1 \mu\text{h} \leq L \leq 1 \text{ h}$ $5 \text{ pF} \leq C \leq 1 \mu\text{F}$
Practical (P):	$200 \text{ nh} \leq L \leq 10 \text{ h}$ $2 \text{ pF} \leq C \leq 10 \mu\text{F}$
Marginally practical (M):	$50 \text{ nh} \leq L \leq 100 \text{ h}$ $0.5 \text{ pF} \leq C \leq 500 \mu\text{F}$

Impractical (I): All element values that lie outside the marginal range, i.e.,

$L < 50$	nh
$L > 100$	h
$C < 0.5$	pF
$C > 500$	μF

The table headings are meant to indicate ranges of filter cutoff frequency and termination impedance level. These ranges are defined as follows:

Frequency,

$$\begin{aligned} f_o = 10 \text{ Hz implies: } 3 \text{ Hz} \leq f_o < 30 \text{ Hz} \\ f_o = 100 \text{ Hz implies: } 30 \text{ Hz} \leq f_o < 300 \text{ Hz} \\ f_o = 1 \text{ kHz implies: } 300 \text{ Hz} \leq f_o < 3 \text{ kHz} \\ f_o = 10 \text{ kHz implies: } 3 \text{ kHz} \leq f_o < 30 \text{ kHz} \\ f_o = 100 \text{ kHz implies: } 30 \text{ kHz} \leq f_o < 300 \text{ kHz} \\ f_o = 1 \text{ MHz implies: } 300 \text{ kHz} \leq f_o < 3 \text{ MHz} \\ f_o = 10 \text{ MHz implies: } 3 \text{ MHz} \leq f_o < 30 \text{ MHz} \\ f_o = 100 \text{ MHz implies: } 30 \text{ MHz} \leq f_o < 300 \text{ MHz} \end{aligned}$$

At frequencies above 300 MHz, lumped element filters are generally replaced with transmission line type filters.

Impedance Level (source and load resistances equal)

$$\begin{aligned} R = 3 \text{ ohms implies: } 1 \leq R < 10 \text{ (power filters)} \\ R = 50 \text{ ohms implies: } 10 \leq R < 150 \\ R = 500 \text{ ohms implies: } 150 \leq R < 2.5k \\ R = 10k \text{ ohms implies: } 2.5k \leq R < 50k \end{aligned}$$

Table 2-4.1 Physical realizability of lowpass and highpass filters.

R in ohms	Cutoff Frequency, f_c							
	10 Hz	100 Hz	1 kHz	10 kHz	100 kHz	1 MHz	10 MHz	100 MHz
3	I	M	M	P	R	P	M	I
50	M	M	M	R	R	R	R	M
500	M	P	R	R	R	R	R	R
10k	I	M	P	R	R	R	P	I

Courtesy, Don White Consultants, Inc.

Bandstop filter physical realizability must include one additional parameter, the loaded Q of the filter, Q_L . As Q_L becomes higher (filter

becomes more narrow) the separation in element value between the series tank elements and the parallel tank elements increases as Q_L . Table 2-4.2 is adapted from Table 7.2 in White and assigns realizability scores to bandstop (and bandpass) filters. The loaded Q ranges are defined as follows:

Loaded Q (Q_L), for bandpass and bandstop,

$$Q_L = 5 \text{ implies: } 3 \leq Q_L < 10$$

$$Q_L = 15 \text{ implies: } 10 \leq Q_L < 30$$

$$Q_L = 50 \text{ implies: } 30 \leq Q_L \leq 100$$

Table 2-4.2 Physical realizability of bandstop filters.

Filter Prototype		$f_0 = 1 \text{ kHz}$									$f_0 = 10 \text{ kHz}$								
		$Q_L = 5$			$Q_L = 15$			$Q_L = 50$			$Q_L = 5$			$Q_L = 15$			$Q_L = 50$		
Type		50	500	10K	50	500	10K	50	500	10K	50	500	10K	50	500	10K	50	500	10K
1st		I	P	P	I	I	I	I	I	I	M	R	P	I	M	P	I	M	P
2nd		I	P	P	I	I	I	I	I	I	M	R	P	I	M	P	I	M	P
Filter Prototype		$f_0 = 100 \text{ kHz}$									$f_0 = 1 \text{ MHz}$								
		$Q_L = 5$			$Q_L = 15$			$Q_L = 50$			$Q_L = 5$			$Q_L = 15$			$Q_L = 50$		
Type		50	500	10K	50	500	10K	50	500	10K	50	500	10K	50	500	10K	50	500	10K
1st		P	R	R	P	P	I	M	M	I	P	R	P	P	P	I	M	P	I
2nd		P	R	R	P	P	I	M	M	I	P	R	P	P	P	I	M	P	I
Filter Prototype		$f_0 = 10 \text{ MHz}$									$f_0 = 100 \text{ MHz}$								
		$Q_L = 5$			$Q_L = 15$			$Q_L = 50$			$Q_L = 5$			$Q_L = 15$			$Q_L = 50$		
Type		50	500	10K	50	500	10K	50	500	10K	50	500	10K	50	500	10K	50	500	10K
1st		M	P	M	I	P	I	I	I	I	I	I	I	I	I	I	I	I	I
2nd		M	P	M	I	P	I	I	I	I	I	I	I	I	I	I	I	I	I

Courtesy Don White Consultants Inc.


As the loaded Q increases, the element value spread can become unmanageable. This problem can be reduced by using narrowband transformations which are used in Programs 2-5 and 2-6 for the bandpass case. Narrowband transformation schematics for the bandstop case may be found on p. 217 of the ITT handbook [44]. The concept of coupling and narrowband transformations was introduced by Milton Dishal [21], and expanded by Seymour Cohn [16] for the bandpass case.

User Instructions

BANDSTOP, LOWPASS, OR HIGHPASS TRANSFORMATIONS				
Lowpass Type 1	Lowpass Type 2	Highpass Type 1	Highpass Type 2	
Center Frequency	Bandwidth, Cutoff freq	Termination Resistance	Bandstop Type 1	Bandstop Type 2

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of magnetic card			
2	For lowpass filter component values:			
	a) load cutoff frequency in hertz	f_{cutoff}	<input type="text" value="B"/>	
	b) load termination resistance in ohms	R	<input type="text" value="C"/>	
	c) for type 1 filter (capacitor first)*		<input type="text" value="f"/> <input type="text" value="A"/>	R_s
				C_1
				L_2
				\vdots
				$C_n \text{ or } L_n$
				R
	d) for type 2 filter (inductor first)*		<input type="text" value="f"/> <input type="text" value="B"/>	R_s
				L_1
				C_2
				\vdots
				$L_n \text{ or } C_n$
				R
3	For highpass filter component values:			
	a) load cutoff frequency in hertz		<input type="text" value="B"/>	
	b) load termination resistance in ohms		<input type="text" value="C"/>	
	c) for type 1 filter (inductor first)*		<input type="text" value="f"/> <input type="text" value="C"/>	R_s
				L_1
				C_2
				\vdots
				$C_n \text{ or } L_n$
				R

User Instructions

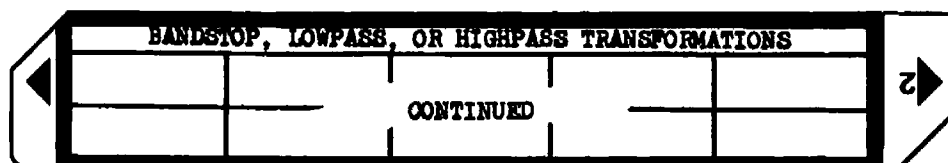

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
3	Highpass component values continued b) for type 2 filter (capacitor first)*		<input type="text" value="f"/> <input type="text" value="D"/>	R_s C_1 L_2 \vdots L_n or C_n R
4	For bandstop filter component values: a) load filter center frequency in hertz b) load filter bandwidth in hertz c) load termination resistance in ohms d) for type 1 filter (series tank first)* e) for type 2 filter (parallel tank first)*	f_o BW R	<input type="text" value="A"/> <input type="text" value="B"/> <input type="text" value="C"/> <input type="text" value="D"/> <input type="text" value="E"/>	R_s C_1^{**} L_1 C_2 L_2 \vdots C_n L_n R
	NOTES: * All capacitor values are in farads, all inductor values are in henries and all resistor values are in ohms. ** In all section 2 programs where resonant tank components are printed, the capacitor is always printed first.			C_1 L_1 \vdots C_n L_n R

Example 2-4.1 Singly terminated lowpass filter

A maximally flat (Butterworth) lowpass filter must pass a 1 kHz signal with 1 dB or less attenuation relative to the filter response at dc, and must reject a 12 kHz signal by at least 75 dB. Program 2-1 is used to predict the required filter order, and -3 dB cutoff frequency (Butterworth cutoff frequency) with $A_{p_{dB}} = 1$ dB, $A_{s_{dB}} = 75$ dB, and $\lambda = 12$. A filter order of 3.75 is calculated, which is rounded to the next largest integer, 4. Re-entering the program with $A_{s_{dB}} = 3$ and $n = 4$, yields $\lambda = 1.183301$, which means the 3 dB cutoff frequency is $(1000)(1.183301) = 1183.301$ Hz.

Next, Program 2-3 is loaded to obtain the normalized lowpass coefficients for a singly terminated 4th order Butterworth filter. The coefficients are automatically stored for use by this program.

Load this program, load the above cutoff frequency, and select an operating impedance level from Table 2-4.1. An impedance level of 500 ohms will result in a readily realizable filter. Both the type 1 and type 2 topologies can be calculated and the most attractive one selected. The HP-97 printout for the above operations is shown on the next page.

Programs 3-1 and 3-2 can be used to design the inductors needed for this design. If an active filter approach can be considered, see Program 2-9 for a lowpass active filter design.

HP-97 printout for Example 2-4.1, lowpass filter design.

Load Program 2-1 to calculate required filter order:

```

        GSBL select Butterworth
1.00 GSBA load  $A_{p\text{dB}}$ 
75.00 GSBB load  $A_{s\text{dB}}$ 
12.00 GSBC load  $\lambda$ , and calculate n, the filter order
3.75 *** n (output)

3.00 GSBE load new  $A_{s\text{dB}}$ 
4.00 GSBF load integral filter order, n, and calculate  $\lambda$ 
1.183381 ***  $\lambda$  (output)

```

Load Program 2-3 to generate and store the normalized lowpass coeffs.

```

4. GSBH load filter order
1.+05 GSBI load termination resistance desired
        GSBJ calculate Butterworth coefficients
1.000000+09 ***  $R_T$  (normalized)

1.53073+00 ***  $g_1$ 
1.57716+00 ***  $g_2$ 
1.08239+00 ***  $g_3$ 
382.683-03 ***  $g_4$ 
        } lowpass normalized coefficients

1.000000+00 *** R (normalized)

```

Load this program (Program 2-4) to obtain un-normalized filter.

```

1181.301 GSBE load un-normalized cutoff frequency
500. GSBC load termination resistance, R
        GSBA calculate type 1 lowpass filter (capacitor first)

```

31. lowpass type 1 output code


500.0+03 *** R_s (open circuit)

```

412.5-09 ***  $C_1$ 
106.2-03 ***  $L_2$ 
291.7-05 ***  $C_3$ 
25.78-03 ***  $L_4$ 

```

500.0+00 *** R

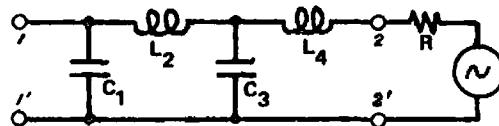

GSB_K calculate type 2 lowpass filter (inductor first)

32. lowpass type 2 output code


500.0-09 *** R_s (short circuit)

```

103.1-03 ***  $L_1$ 
425.0-09 ***  $C_2$ 
72.91-03 ***  $L_3$ 
103.1-09 ***  $C_4$ 

```

500.0+00 *** R

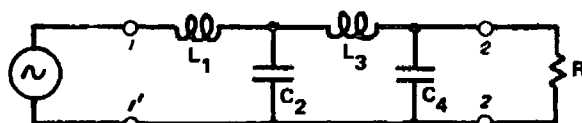

Example 2-4.2 Doubly terminated highpass filter

A highpass filter is required to keep the signal from a local CB transmitter from causing cross modulation interference in the tuner of a TV set. The filter will be placed in series with the 300 ohm balanced line from the antenna to the TV set, hence, the filter will be designed for a 300 ohm terminating impedance level. The filter must pass the TV spectrum which starts at 54 MHz, but must reject the CB radio band at 27 MHz. One dB of ripple is allowed across the TV spectrum, and at least 60 dB rejection is needed at the CB band frequencies. Because of the allowed ripple, a Chebyshev filter will be used. Program 2-1 calculates a minimum filter order of 7 as shown below along with the rest of the HP-97 printout for this design:

Load Program 2-1 to obtain minimum filter order required:

```

      6350 select Chebyshev
1.00 6354 load ApdB
60.00 6355 load AsdB
2.00 6357 load  $\lambda$  and calculate filter order, n
6.32 *** n (output)

7.00 6359 load integral filter order, n
1.78 ***  $\lambda$  where filter is 60 dB down ( $54/1.78 = 30.3$ )

2.00 6355 load  $\lambda$  and calculate AsdB
60.15 *** AsdB at 27 MHz

```

Load Program 2-3 to generate and store the normalized lowpass coefficients:

```

7. 6354 load filter order
1. 6355 load termination resistance ratio
1. 6357 load Chebyshev passband ripple in dB and start
1.01721+00 *** normalized -3 dB frequency (output)

1.00000+00 ***  $R_T$  (normalized)


2.16636+00 ***  $g_1$ 
1.11151+00 ***  $g_2$ 
3.09364+00 ***  $g_3$ 
1.17352+00 ***  $g_4$ 
3.09364+00 ***  $g_5$ 
1.11151+00 ***  $g_6$ 
2.16636+00 ***  $g_7$ 
} normalized lowpass coefficients

1.00000+00 *** R (normalized)

```

This highpass example is for a balanced structure filter, and the program output is for an unbalanced structure (one side common). To convert the unbalanced structure to the balanced structure, capacitors are placed in each side of the filter, and their equivalent impedance is one-half the unbalanced value (twice the capacity).

Load this program, Program 2-4, to obtain the un-normalized filter:

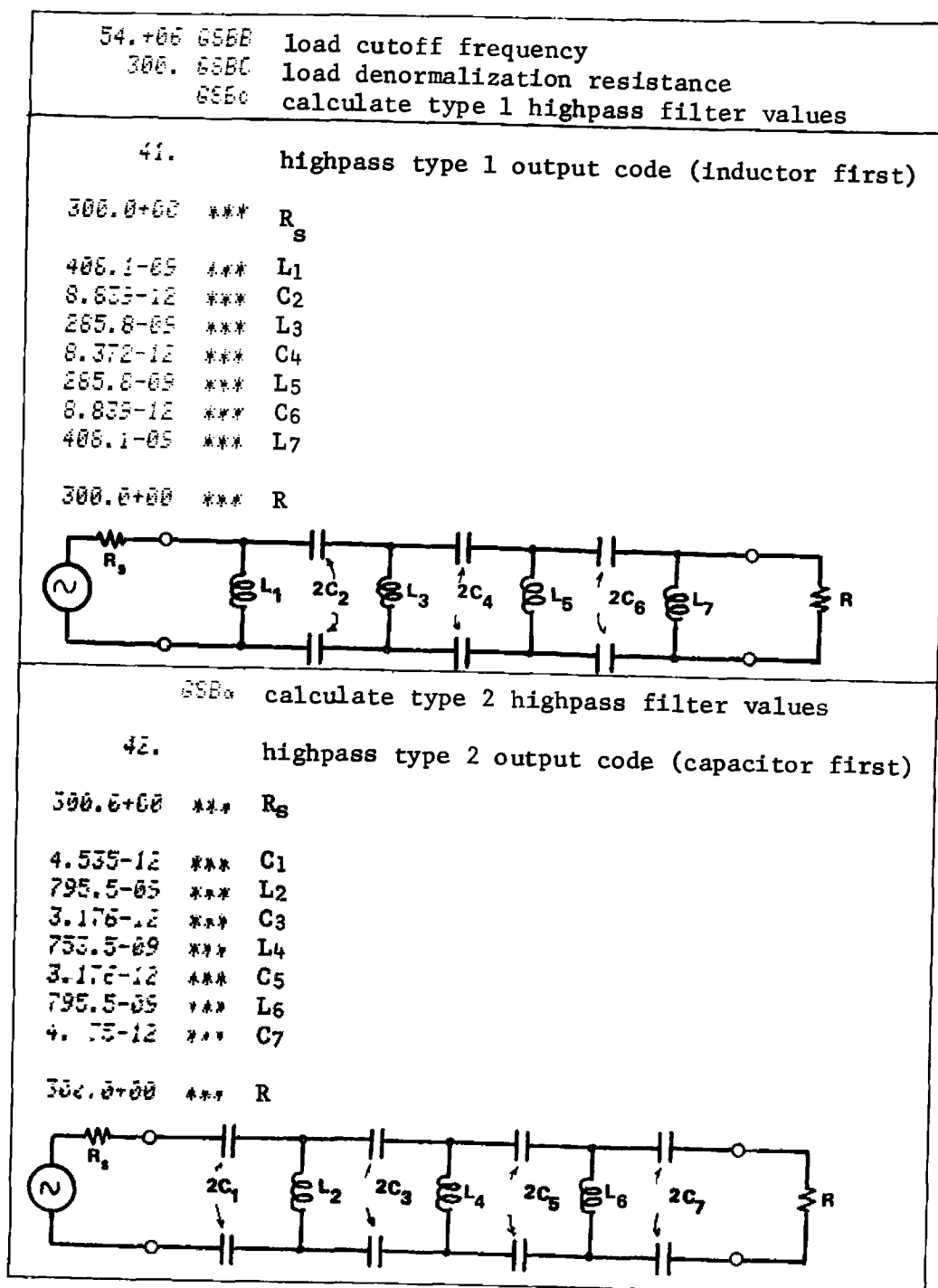

Programs 3-5 and 3-6 can aid in the aircore inductor designs needed here.

Example 2-4.3 Bandstop filter

Consider implementing the filter cited in the previous example as a bandstop filter rather than as a highpass filter. The stopband required is from 26 MHz to 27 MHz. The center frequency of a bandstop (and bandpass) filter is the geometric mean of any two equal attenuation frequencies (this relationship does not hold for narrowband bandpass transformations for frequencies outside the passband). The center frequency of this bandstop filter is then 26.4953 MHz. If the upper -1 dB point is 54 MHz, then the lower -1 dB point is $(26.4953 \text{ MHz})^2 / (54 \text{ MHz}) = 13 \text{ MHz}$. The normalized frequency multiplier, λ , is the ratio between the passband and the stopband, or $\lambda = (54 - 13) / (27 - 26) = 41$. From Program 2-1, the filter order that meets these requirements is 2. Even ordered Chebyshev filters do not have equal termination resistance levels, and this filter is to be placed in a 300 ohm system (equally terminated). To satisfy all requirements including equal termination, a third order bandstop filter will be designed. The HP-97 printout for this filter design follows.

Load Program 2-1 to calculate the minimum filter order required:

```

      GSBK  select Chebyshev
1.00 GSBH  load ApdB
60.00 GSBE  load AsdB
41.00 GSED  load  $\lambda$  and calculate filter order, n
1.86 ***  minimum n to meet requirements (use n = 2 min)

3.00 GSEC  load n desired and calculate  $\lambda$  for AsdB = 60 dB
7.92 ***   $\lambda$ 

      1/x } form 1/ $\lambda$ 
41.00   $\lambda$  }
5.18 ***  stopband bandwidth (MHz)
26.4953 GSED  enter center frequency (MHz) and calculate:
29.21 ***  upper stopband edge (MHz)
24.03 ***  lower stopband edge (MHz)

```

5. G5E4 load filter order
 1. G5E5 load termination resistance ratio desired
 1. G5E0 load Chebyshev passband ripple in dB and start
 1.09487+00 *** λ for 3 dB bandwidth (output)


 1.00000+00 *** R_T (normalized)
 2.02359+00 ***
 994.102-03 *** } normalized lowpass coefficients
 2.02359+00 ***

 1.00000+00 *** R (normalized)

 26.4553+06 G5E4 load filter center frequency
 41.+06 G5E5 load filter bandwidth
 300. G5E0 load de-normalization resistance level
 G5E0 calculate type 1 bandstop

21. type 1 bandstop heading (series tank first)

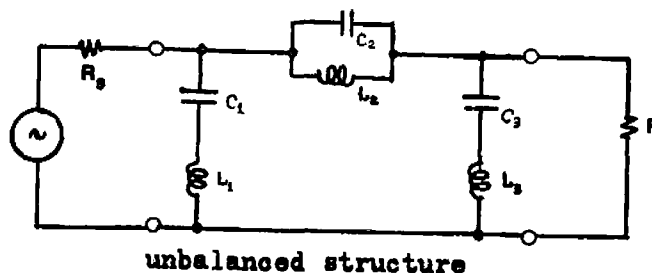
300.0+00 *** R_s
 62.70-12 *** C_1
 575.5-09 *** L_1
 13.02-12 *** C_2
 2.772-06 *** L_2
 62.70-12 *** C_3
 575.5-09 *** L_3
 300.0+00 *** R



G5E0 calculate type 2 bandstop

22. type 2 bandstop heading (parallel tank first)

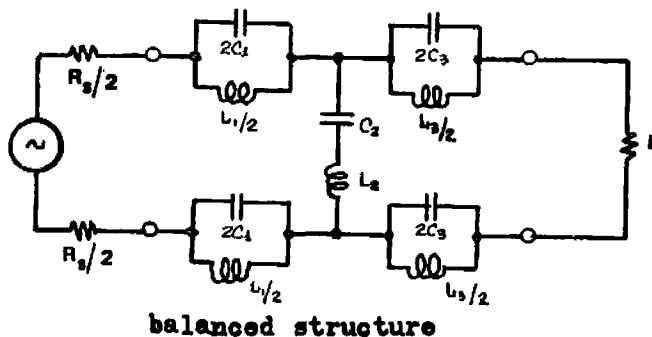300.0+00 *** R_s
 6.394-12 *** C_1
 5.645-06 *** L_1
 30.80-12 *** C_2
 1.171-06 *** L_2
 6.394-12 *** C_3
 5.645-06 *** L_3
 300.0+00 *** R



001	*LBLA	LOAD CENTER FREQUENCY	049	*LBL1	bandstop calculation loop
002	Pi		050	GSB9	increment indices and
003	ENT↑		051	X>Y?	test for loop exit
004	+	$2\pi f_0 \rightarrow R0$	052	GT04	
005	x		053	SPC	
006	ST00		054	RCLi	recall g_k
007	RTN		055	RCL4	recall $R/(\omega_0 \cdot Q_L)$
008	*LBLB	LOAD BANDWIDTH OR CUTOFF FREQ	056	CF0	set print order for type 1
009	Pi		057	F1?	test for type 1 filter
010	ENT↑		058	GT06	
011	+	$2\pi BW \rightarrow R1$	059	CLX	
012	x		060	RCL5	substitute $1/(R \cdot \omega_0 \cdot Q_L)$ in R_x
013	ST01		061	SF0	set print order for type 2
014	RTN		062	*LBL6	
015	*LBLC	LOAD DENORMALIZATION RESIST	063	GSB8	gosub elt calculation & print
016	ST02	$R \rightarrow R2$	064	GSB9	increment indices and
017	RTN		065	X>Y?	test for loop exit
018	*LBLO	BANDSTOP TYPE 1 ROUTINE	066	GT04	
019	SPC		067	SPC	
020	2		068	RCLi	recall g_k
021	1	print heading "21"	069	RCL5	recall $1/(R \cdot \omega_0 \cdot Q_L)$
022	PRTX		070	SF0	set print order for type 1
023	CF1	indicate type 1 topology	071	F1?	test for type 1 filter
024	GT00		072	GT06	
025	*LBLE	BANDSTOP TYPE 2 ROUTINE	073	CLX	
026	SPC		074	RCL4	substitute $R/(\omega_0 \cdot Q_L)$ in R_x
027	2		075	CF0	
028	2	print heading "22"	076	*LBL6	
029	PRTX		077	GSB8	gosub elt calculation & print
030	SF1	indicate type 2 topology	078	GT01	goto loop start
031	*LBLO		079	*LBL8	element calculation & print
032	SF2	calculate and print R_s	080	x	
033	GSB2		081	ST08	form and store $g_k \cdot R_x \rightarrow R8$
034	RCL2	calculate and store:	082	F0?	
035	RCL1		083	PRTX	if flag 0 print R8
036	x		084	RCL0	calculate mating
037	RCL0	$\frac{R \cdot BW}{\omega_0^2} = \frac{R}{\omega_0 \cdot Q_L} \rightarrow R4$	085	X?	resonant element:
038	X?		086	x	
039	÷		087	1/X	$C, L = \frac{1}{\omega_0^2 \cdot (L, C)}$
040	ST04		088	PRTX	
041	RCL2		089	F0?	if flag 0, return to
042	X?	$\frac{1}{R \cdot \omega_0 \cdot Q_L} \rightarrow R5$	090	RTN	main program
043	÷		091	RCL8	recall and print R8
044	ST05		092	PRTX	
045	CLX		093	RTN	return to main program
046	ST07	initialize index registers	094	*LBL9	LOWPASS TYPE 1 ROUTINE
047	9		095	SPC	
048	ST01		096	3	
			097	1	print heading "31"
			098	PRTX	
			099	CF0	indicate lowpass filter
			100	CF1	indicate type 1 filter
			101	GSB7	calculate some constants
			102	GT02	goto output routine

103	*LBL6	LOWPASS TYPE 2 ROUTINE
104	SPC	
105	3	
106	2	print heading "32"
107	PRTX	
108	CF0	indicate lowpass filter
109	SF1	indicate type 2 filter
110	GSB7	compute LP type 1 constants
111	RCL2	
112	X ²	
113	ST=4	change to LP type 2 constants
114	ST×5	
115	GT02	goto output routine
116	*LBL6	HIGHPASS TYPE 2 ROUTINE
117	SPC	
118	4	
119	2	print heading "42"
120	PRTX	
121	SF0	indicate highpass
122	SF1	indicate type 2
123	GSB7	compute LP type 1 constants
124	GT02	goto output routine
125	*LBL6	HIGHPASS TYPE 1 ROUTINE
126	SPC	
127	4	
128	1	print heading "41"
129	PRTX	
130	SF0	indicate highpass
131	CF1	indicate type 1
132	GSB7	calculate LP type 1 constants
133	RCL2	
134	X ²	
135	ST=4	change to HP type 1 constants
136	ST×5	
137	*LBL2	LP & HP output routine
138	SPC	
139	RCL0	recall R _T
140	F1?	
141	1/X	if type 2 filter, form 1/R _T
142	RCL2	
143	X	calculate and print R _g
144	PRTX	
145	F2?	
146	RTN	test for return to bandstop
147	SPC	

148	*LBL3	LP and HP output loop start
149	GSB9	increment indices and
150	X×Y?	test for loop exit
151	GT04	
152	RCL1	recall g _k
153	F0?	
154	1/X	if highpass, form 1/g _k
155	RCL5	
156	X	calculate and print
157	PRTX	first filter element
158	GSB9	increment indices and
159	X×Y?	test for loop exit
160	GT04	
161	RCL1	recall g _k
162	F0?	
163	1/X	if highpass, form 1/g _k
164	RCL4	
165	X	calculate and print
166	PRTX	other type of filter element
167	GT03	goto loop start
168	*LBL4	
169	SPC	recall and print port 2
170	RCL2	termination resistance
171	PRTX	
172	SPC	
173	SPC	
174	RTN	return control to keyboard
175	*LBL7	subroutine to calc LP - 1
176	RCL2	
177	RCL1	calculate and store
178	=	inductor scaling:
179	ST04	R/(2π·BW) → R ₄
180	RCL2	
181	X ²	calculate and store
182	=	capacitor scaling:
183	ST05	1/(2π·BW·R) → R ₅
184	CLX	
185	ST07	
186	9	initialize indices
187	ST01	
188	RTN	
189	*LBL9	incr indices and loop exit
190	EEX	
191	ST+7	
192	ISZ1	
193	RCL6	
194	RCL7	
195	RTN	

LABELS					FLAGS	SET STATUS			
A	B	C	D	E	0	FLAGS		TRIG	DISP
load f ₀	load BW	load R	BS ₁	BS ₂	Highpass				
a LP ₁	b LP ₂	c HP ₁	d HP ₂	e	1 Type 2	ON	OFF	USER'S CHOICE	
0 calculate BS coef	1 BS loop rtn	2 calc R _f	3 LP/HP loop rtn	4 print R	2 lbl 2 return	0	1	DEG	FIX
5	6 local loop destination	7 LP/HP coeffs	8 bandstop output	9 index incr & loop exit test	3	2	2	GRAD	SCI
						3	3	RAD	ENG
									n

HP-67 suggested program changes. A print or R/S routine has not been provided, although register 9 and label "e" could have been used for this purpose. The reason for this omission is to preserve the heading format. Any program statements placed between a numeric entry and a print statement cause the printed format to be in the set status of the program; however, by placing the print statement directly after the numeric entry (see lines 20 through 22), "21" is printed without trailing zeros.

On the HP-67, the "print" statement causes the program halt for 5 seconds and a flashing decimal point. This situation slows program execution and may not be desirable. The HP-67 user may wish to have the program stop at the data output points. To cause the program to stop at these points, change the program as follows: Delete steps 019 - 022, 026 - 029, 095 - 098, 104 - 107, 117 - 120, and 126 - 129. Change the "print" statements to "R/S" statements at the following line numbers: 083, 088, 092, 144, 157, 166, and 171. To restart program execution after a program halt, execute a "R/S" from the keyboard.

Remember, when deleting steps from a program, always work from the back of the program forward. By observing this convention, the line numbers of steps not yet deleted will remain unaltered.

PROGRAM 2-5 NORMALIZED LOWPASS TO BANDPASS FILTER TRANSFORMATIONS,
TYPES 1, 2, 6, AND 7.

Program Description and Equations Used

This program converts normalized lowpass filter element values to a set of four bandpass topologies [16], [21], [56]. The four topologies are shown in Fig. 2-5.1, and the parameter A_{ij} is defined by Eq. (2-5.1). Types 1 and 2 are exact transformations and will transform the lowpass response independent of the loaded filter Q (Eq. (2-4.7)). Types 6 and 7 of this program, and types 8, and 9 of Program 2-6 are narrowband approximations, and only provide accurate transformation results when the loaded Q is greater than 5, and preferably greater than 10.

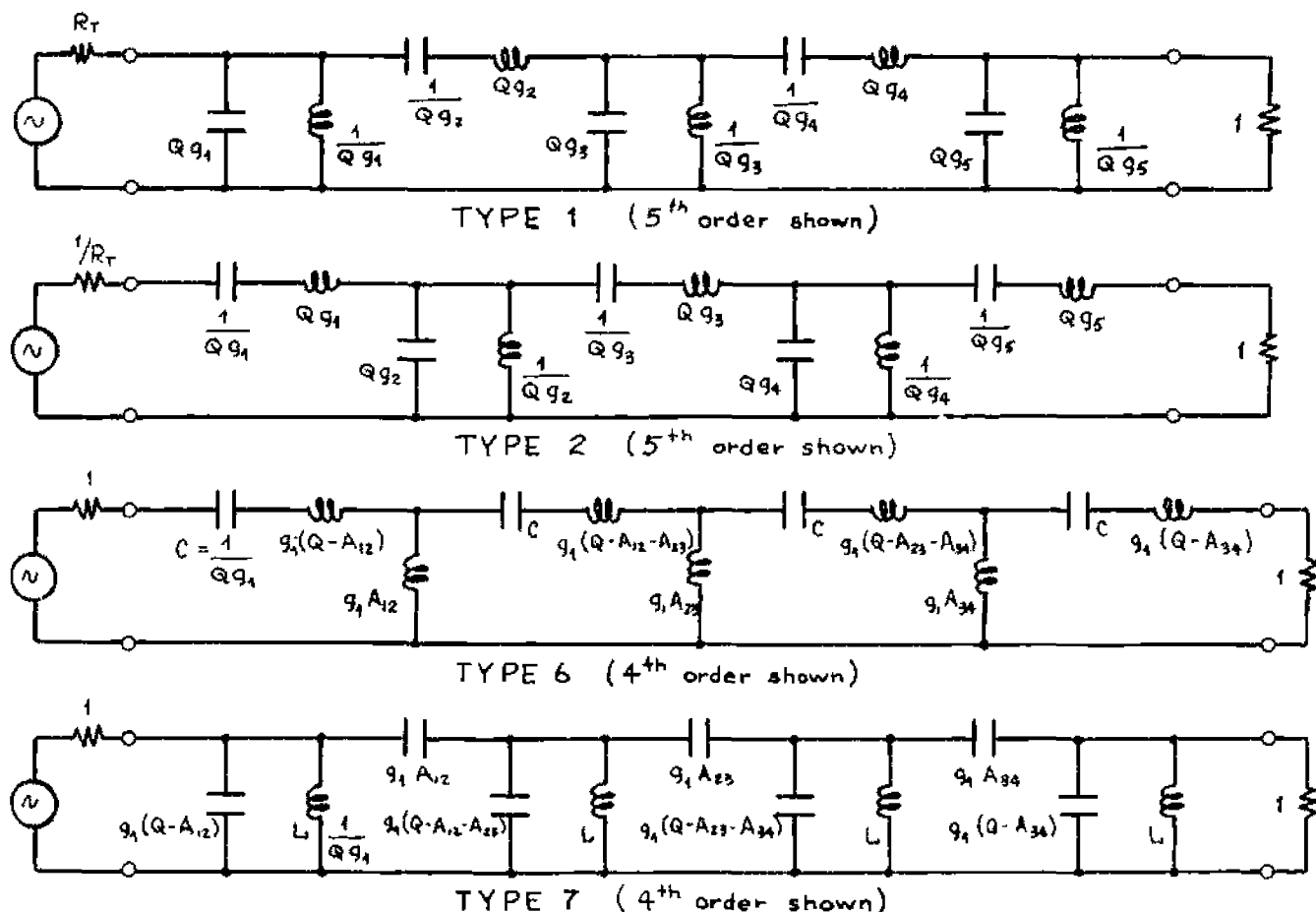


Figure 2-5.1 Bandpass filter topologies for types 1, 2, 6, & 7.

$$A_{ij} = (g_i \cdot g_j)^{-\frac{1}{2}} \quad (2-5.1)$$

Figure 2-5.2 is a reproduction of Table 7.2 in White [56] and is intended as a guide to the best suited filter topology for a particular application. The physical realizability of a filter topology is assigned one of four possible scores based upon element values. These scores are defined as follows:

Readily realizable (R):

$$\begin{aligned} 1 \mu\text{h} &\leq L \leq 1 \text{ h} \\ 5 \text{ pF} &\leq C \leq 1 \mu\text{F} \end{aligned}$$

Practical (P):

$$\begin{aligned} 0.2 \mu\text{h} &\leq L \leq 10 \text{ h} \\ 2 \text{ pF} &\leq C \leq 10 \mu\text{F} \end{aligned}$$

Marginally practical (M):

$$\begin{aligned} 50 \text{ nh} &\leq L \leq 100 \text{ h} \\ 0.5 \text{ pF} &\leq C \leq 500 \mu\text{F} \end{aligned}$$

Impractical (I):

All element values that lie outside the range of marginal i.e.,

$$\begin{aligned} L &< 50 \text{ nh} \\ L &> 100 \text{ h} \\ C &< .5 \text{ pF} \\ C &> 500 \mu\text{F} \end{aligned}$$

The table headings are meant to indicate ranges of loaded Q , filter center frequency, and termination resistance level. These ranges are:

Frequency;

$$\begin{aligned} f_o = 10 \text{ Hz} &\text{ implies: } 3 \text{ Hz} \leq f_o < 30 \text{ Hz} \\ f_o = 100 \text{ Hz} &\text{ implies: } 30 \text{ Hz} \leq f_o < 300 \text{ Hz} \\ f_o = 1 \text{ kHz} &\text{ implies: } 300 \text{ Hz} \leq f_o < 3 \text{ kHz} \\ f_o = 10 \text{ kHz} &\text{ implies } 3 \text{ kHz} \leq f_o < 30 \text{ kHz} \\ f_o = 100 \text{ kHz} &\text{ implies: } 30 \text{ kHz} \leq f_o < 300 \text{ kHz} \\ f_o = 1 \text{ MHz} &\text{ implies: } 300 \text{ kHz} \leq f_o < 3 \text{ MHz} \\ f_o = 10 \text{ MHz} &\text{ implies: } 3 \text{ MHz} \leq f_o < 30 \text{ MHz} \\ f_o = 100 \text{ MHz} &\text{ implies: } 30 \text{ MHz} \leq f_o < 300 \text{ MHz} \end{aligned}$$

At frequencies above 300 MHz, lumped element filters are generally replaced with transmission line type filters.

Loaded Q (Q_L), for bandpass and bandstop,

$$Q_L = 5 \text{ implies: } 3 \leq Q_L < 10$$

$$Q_L = 15 \text{ implies: } 10 \leq Q_L < 30$$

$$Q_L = 50 \text{ implies: } 30 \leq Q_L \leq 100$$

Impedance Level (source and load resistances equal)

$$R = 3 \text{ ohms implies: } 1 \leq R < 10 \text{ (power filters)}$$

$$R = 50 \text{ ohms implies: } 10 \leq R < 150$$

$$R = 500 \text{ ohms implies: } 150 \leq R < 2.5k$$

$$R = 10k \text{ ohms implies: } 2.5k \leq R < 50k$$

Band-Pass Filter Prototype	$f_0 = 1 \text{ kHz}$									$f_0 = 10 \text{ kHz}$								
	$Q_L = 5$			$Q_L = 15$			$Q_L = 50$			$Q_L = 5$			$Q_L = 15$			$Q_L = 50$		
Type	50	500	10K	50	500	10K	50	500	10K	50	500	10K	50	500	10K	50	500	10K
1st	I	P	P	I	I	I	I	I	I	M	R	P	I	M	P	I	M	P
2nd	I	P	P	I	I	I	I	I	I	M	R	P	I	M	P	I	M	P
3rd	I	M	I	I	I	I	I	I	I	M	P	M	I	P	P	I	M	P
4th	I	M	P	I	I	P	I	I	M	M	P	P	I	P	P	I	M	P
5th	P	P	P	P	I	P	P	P	I	R	R	P	R	P	P	R	P	M
6th	P	P	I	P	P	I	P	P	I	R	R	P	R	P	P	R	P	M
7th	I	M	P	I	M	P	I	M	P	M	P	P	I	P	R	I	M	P
8th	I	M	P	I	M	P	I	M	P	M	P	P	P	P	P	P	M	P
9th	I	M	P	I	M	P	I	M	P	M	P	P	P	P	P	P	M	P
10th	M	P	M	P	R	P	P	R	P	P	R	P	R	R	R	R	R	R
11th	M	P	P	M	P	P	M	M	P	P	R	R	P	R	R	M	P	R

Band-Pass Filter Prototype	$f_0 = 100 \text{ kHz}$									$f_0 = 1 \text{ MHz}$								
	$Q_L = 5$			$Q_L = 15$			$Q_L = 50$			$Q_L = 5$			$Q_L = 15$			$Q_L = 50$		
Type	50	500	10K	50	500	10K	50	500	10K	50	500	10K	50	500	10K	50	500	10K
1st	P	R	R	P	P	I	M	M	I	P	R	P	P	P	I	M	P	I
2nd	P	R	R	P	P	I	M	M	I	P	R	P	P	P	I	M	M	I
3rd	P	R	P	P	P	P	M	P	P	R	R	P	R	R	R	M	P	I
4th	P	R	P	P	P	P	M	P	P	R	R	P	R	R	R	M	P	I
5th	P	R	P	P	P	P	M	P	P	R	R	P	R	R	R	M	P	I
6th	R	R	P	R	R	P	R	P	P	R	R	P	R	R	M	R	P	I
7th	P	R	R	P	R	R	M	P	P	R	R	R	P	R	R	M	P	I
8th	P	R	R	P	R	R	M	P	P	R	R	R	P	R	R	M	P	I
9th	P	R	R	P	R	R	M	P	P	R	R	R	P	R	R	M	P	I
10th	R	R	R	R	R	P	R	P	P	R	R	R	P	R	R	M	R	M
11th	R	R	R	R	R	P	R	P	P	R	R	R	P	R	R	M	R	M

Band-Pass Filter Prototype	$f_0 = 10 \text{ MHz}$									$f_0 = 100 \text{ MHz}$								
	$Q_L = 5$			$Q_L = 15$			$Q_L = 50$			$Q_L = 5$			$Q_L = 15$			$Q_L = 50$		
Type	50	500	10K	50	500	10K	50	500	10K	50	500	10K	50	500	10K	50	500	10K
1st	M	P	M	I	P	I	I	I	I	I	I	I	I	I	I	I	I	I
2nd	M	P	M	I	P	I	I	I	I	I	I	I	I	I	I	I	I	I
3rd	P	R	M	R	P	I	I	M	I	I	M	I	I	I	I	I	I	I
4th	M	R	R	I	P	R	I	M	R	I	M	R	I	I	P	I	I	M
5th	P	R	M	M	P	I	P	M	I	M	M	I	I	I	I	M	L	I
6th	R	R	M	P	P	I	P	M	I	P	M	I	M	I	I	M	I	I
7th	M	R	P	I	P	P	I	P	P	I	P	M	I	I	I	M	I	I
8th	R	R	M	R	P	I	P	M	I	P	M	I	P	I	I	M	I	I
9th	M	R	R	I	P	R	I	M	R	I	M	R	I	I	P	I	I	M
10th	P	R	I	P	M	I	P	M	I	P	M	I	M	I	I	M	I	I
11th	M	R	M	M	P	M	I	P	M	I	M	I	I	M	I	I	I	I

Fig. 2-5.2 Physical realizability of bandpass filters.

Courtesy Don White Consultants Inc.

To use the routines for types 6 through 9, the filter must have termination resistances as close to unity as possible. To achieve this result, a desired termination resistance level of 1.0 should be loaded into Program 2-3.

Of the filter types presented both in this program, and the accompanying program (types 1, 2, 6, 7, 8, 9, 10, and 11) only types 1, 2, 10, and 11 are exact transformations of the lowpass characteristic. All the remaining filter types are narrowband approximations, i.e., they will faithfully transform the lowpass characteristics within the passband and within a few octaves of the stopband. Types 6, 7, 8, and 9 do not have equal numbers of transmission zeros at both zero frequency and at infinite frequency. The result of this imbalance is to skew the filter response away from the frequency where the extra zeros exist. Figure 2-5.3 shows this occurrence.


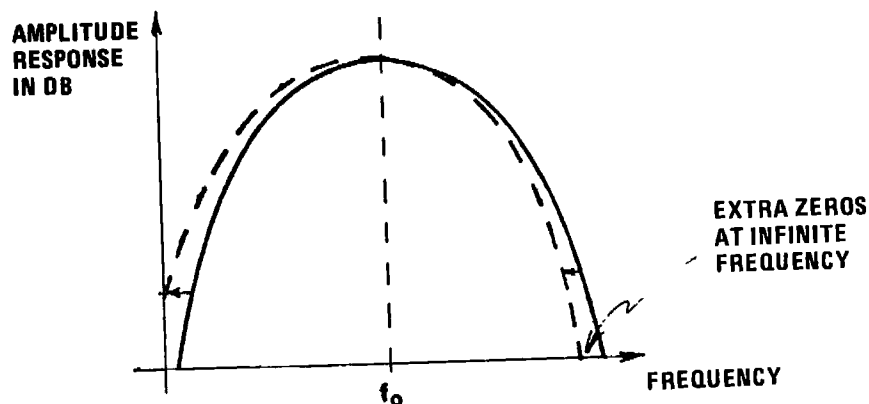


Figure 2-5.3 Bandpass filter response skewing due to extra transmission zeros at infinity.

One should not choose types 1, 2, 10, or 11 automatically. Types 1 and 2 may be difficult to realize in a narrowband application, and types 10 and 11 (also types 6 and 9) contain redundant inductors. Depending upon the frequency range and element values, these redundant inductors can be burdensome. As a guide, filters operating below 1 kHz may best be realized with an active filter (this subject is covered by other programs in this section); between 1 kHz and 100 kHz, the minimum inductor LC design should be considered and compared with active approaches; above 1 MHz the simplest LC topology should be sought to ease the tuning problem.

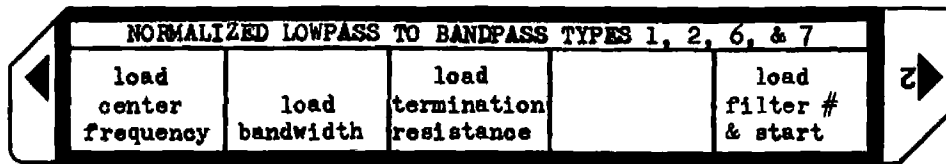

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card			
2	Load center frequency in Hz	f_o	A	ω_o
3	Load bandwidth in Hz	BW	B	Q
4	Load termination resistance in ohms	R	O	R
5	Load filter type number and start	type	E	R
				tank O
				tank L
				cp1g elt*
				tank O
				tank L
				cp1g elt*
				tank O
				tank L
				:
				:
				R _T
6	For another case goto steps 2 through 5 as applicable			

Example 2-5.1 Type 6 filter

A maximally flat passband (Butterworth) bandpass filter is to pass a 500 Hz band of frequencies centered around 10 kHz. In a bandpass (or bandstop) filter, the center frequency is the geometric mean of the upper and lower bandedge frequencies, i.e., $f_o = (9750 \cdot 10250)^{1/2}$, or $f_o = 9996.87$ Hz. The filter should reject by at least 30 dB those frequencies removed from the center frequency by more than 500 Hz. The required filter order is obtained from Program 2-1. Using this program, a minimum filter order of 5 is calculated given $A_{s_{dB}} = 3$, $A_{p_{dB}} = 30$, and $\lambda = 1000/500 = 2$. Program 2-3 is used to obtain the Butterworth normalized coefficients for use by this program.

The proper bandpass topology is selected from the table in Fig. 2-5.2 under the headings: $f_o = 10$ kHz, $Q_L = 10000/500 = 20$ (use $Q_L = 15$ column), and $R = 50$ to find that a type 6 is readily realizable, therefore a type 6 filter will be designed. The HP-97 printout for the above operations is shown below.

Load Program 2-1 to calculate minimum filter order:

```

        GSEF select Butterworth
5.00 GSEF load ApdB
30.00 GSEF load AsdB
2.00 GSEF load λ and calculate n
4.59 *** filter.order, n (output)

5.00 GSEF load integral n and calculate λ
2.00 *** λ for given ApdB and AsdB

2.00 GSEF load λ and calculate AsdB
32.03 *** AsdB

```

Load Program 2-3 to calculate normalized LP Butterworth coeffs:

```

5. GSEF load filter order
1. GSEF load desired termination resistance ratio
GSEF calculate Butterworth coefficients
1.000000+00 *** RT (normalized port 1 termination resistor)

618.034-03 *** g1 }
1.61803+00 *** g2 } normalized lowpass coefficients
2.00000+00 *** g3 }
1.61803+00 *** g4 }
618.034-03 *** g5 }

1.000000+00 *** R (normalized port 2 termination resistor)

```

Example 2-5.1, continued:

Load Program 2-5 (this program) and calculate type 6 elements.

```

9996.87 652A load center frequency
500. 652B load bandwidth
50. 652C load termination resistance
6. 652E load filter type desired and start

50.000+00 *** termination resistance

25.768-09 *** C1
9.3443-03 *** L1

491.97-06 *** L12

25.768-09 *** C2
9.0709-03 *** L2

273.48-06 *** L23

25.768-09 *** C3
9.2894-07 *** L3

273.48-06 *** L34

25.768-09 *** C4
9.0709-03 *** L4

491.97-06 *** L45

25.768-09 *** C5
9.3443-03 *** L5

50.000+00 *** termination resistance

```

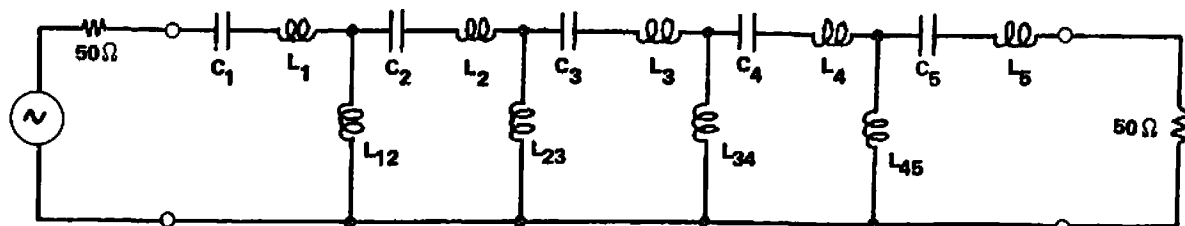


Figure 2-5.4 Type 6 bandpass filter schematic.

Type 6 tuning technique.* After the filter is designed, the inductors fabricated and adjusted, the capacitors obtained, and the filter constructed, the filter must be tuned. For series resonant tanks, such as in this filter and types 8 and 10, tuning is accomplished by decoupling individual tank circuits using open circuits.

Assume the inductors are wound on ferrite pot cores, and are the adjustable elements. Referring to Fig. 2-5.5, to tune L_1 temporarily open the circuit at "B" and tune L for series resonance of the L_1 , L_{12} , C circuit at the center frequency of the filter, 9996.87 Hz in this case.

To tune L_2 , L_{12} , L_{23} , and C, re-establish the connection at "B," and temporarily open the circuit at points "A" and "C." Tune L_2 for series resonance at the center frequency. Continue this procedure of opening adjacent tank circuits and tuning until all series resonant loops have been tuned to the filter center frequency.

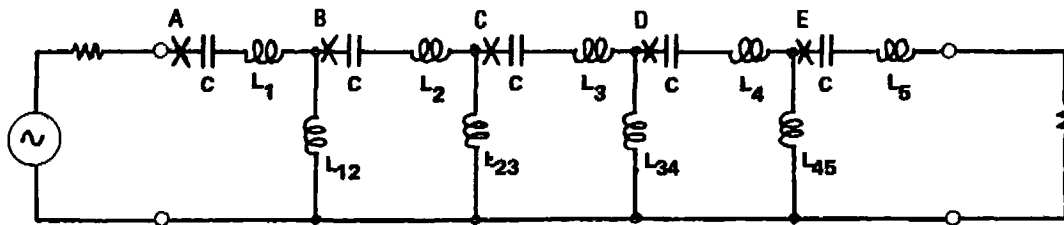


Figure 2-5.5 Type 6 filter showing circuit opens for tuning.

For information on ferrite pot core inductor design, see the Ferroxcube catalog "Linear Ferrite Materials and Components," and use Programs 3-1 and 3-2 to aid in the design of these inductors.

When designing the inductors, the designer must not allow the magnetic core excitation to drive the core near saturation. The voltage across an inductor is "Q" times the voltage across the series LC tank at

*For parallel tank filter tuning procedure, see the example in the type 8, 9, 10, and 11 transformations program.

resonance. With inductor Q's of 100 or better, inductor voltages can be large with respect to the voltage across the filter. The voltage across a filter element at center frequency is approximately

$I_{in} \cdot X_{element}$ where I_{in} is the filter input current and $X_{element}$ is the element reactance.

Program Listing I

001 *LBLA	LOAD CENTER FREQUENCY	049 *LBL0	type 1 calculation start
002 P;		050 *LBL1	type 2 calculation start
003 ENT1	form and store:	051 GSB9	initialize flags & regs
004 +		052 *LBL2	types 1 & 2 loop start
005 *		053 RCL7	
006 ST00	$2\pi f_0 \rightarrow R_0$	054 2	
007 RTN		055 ÷	set flag 2 if branch
008 *LBLB	LOAD BANDWIDTH	056 FRC	number is even where
009 P;		057 X=0?	k is the branch number
010 ENT1	form and store:	058 SF2	
011 +		059 RCL1	
012 *		060 RCL1	form $Q \cdot g_1$
013 RCL0		061 *	
014 XZY	$Q = \frac{2\pi f_0}{2\pi BW} \rightarrow R_1$	062 F2?	if branch even, form $1/Q \cdot g_1$
015 ÷		063 1/X	
016 ST01		064 ST0C	calculate and print
017 RTN		065 F0?	branch capacitor
018 *LBLC	LOAD TERMINATION	066 GSB8	
019 ST02	RESISTANCE	067 F1?	
020 RTN		068 GSB7	
021 *LBLE	LOAD FILTER TYPE (1,2,6,7)	069 RCLC	
022 ST0I		070 F0?	
023 8	generate "ERROR" if other	071 GSB7	calculate and print
024 X<Y?	than filter types 1, 2,	072 F1?	branch inductor
025 GT00	6, or 7 loaded.	073 GSB8	
026 RCL1		074 SPC	
027 3	"ERROR" is generated by	075 DSZ1	
028 X=Y?	calling unused label (a)	076 EEX	increment indices
029 GT00		077 ST+7	
030 RCL1		078 RCL6	
031 4		079 RCL7	test for loop exit
032 X=Y?		080 X<Y?	
033 GT00		081 GT02	
034 RCL1		082 RCLD	
035 5		083 F0?	calculate and print
036 X=Y?		084 1/X	termination resistance
037 GT00		085 RCL2	
038 RCL1	calculate indirect label	086 *	
039 2	corresponding to desired	087 GSB6	
040 ÷	filter type	088 GT06	
041 ST0I			
042 INT			
043 XZI			
044 FRC	set flag 0 if types 1		
045 SF0	or 7 are entered otherwise		
046 X=0?	clear flag 0		
047 CF0			
048 ST0I			

REGISTERS									
0 $2\pi f_0$	1 Q	2 R	3	4 $\frac{1}{\omega_0 R}$ or $\frac{R}{\omega_0}$	5 $\frac{R}{\omega_0}$ or $\frac{1}{\omega_0 R}$	6 n	7 k	8 g_n	9 $A_{i,i+1}$
S0 g_1	S1 g_2	S2 g_3	S3 g_4	S4 g_5	S5 g_6	S6 g_7	S7 g_8	S8 g_9	S9 g_{10}
A g_n	B g_{12}	C types 6 & 7 common element			D R_T	E g_{i+1}	I index		

089 *LBL3	types 6 & 7 start	141 *LBL5	common element print subr
090 GSB9	initialize flags & regs	142 RCLC	
091 RCL7		143 *LBL7	type 6 0 or type 7 L subr
092 STOE	recall and store g_n	144 1/X	
093 ST08		145 RCL5	
094 RCL1		146 x	
095 x	calculate and store $Q \cdot g_n$	147 PRTX	
096 ST0C		148 RTN	
097 *LBL4	types 6 & 7 loop start	149 *LBL8	type 6 L or type 7 0 subr
098 F1?	if type 6 print common	150 RCL4	
099 GSB5	tank capacitor value	151 x	
100 DS2T		152 PRTX	
101 EEX	increment indicies	153 RTN	
102 ST+7		154 *LBL9	initialization subroutine
103 RCL1	recall g_1	155 SPC	
104 RCL6		156 SF1	if flag 0 is set, clear
105 XZY	interchange g_1 and g_{i+1}	157 F0?	flag 1 and vice-versa
106 STOE		158 CF1	
107 x		159 RCL0	if type 6:
108 1/X	calculate $A_{1, i+1}$	160 1/X	$\frac{R}{\omega_0} \rightarrow R_4; \frac{1}{R\omega_0} \rightarrow R_5$
109 1/X		161 ST04	
110 RCL9	interchange	162 ST05	
111 XZY	$A_{1, i+1}$ and $A_{i+1, i+2}$	163 RCL2	if type 7:
112 ST09		164 F1?	$\frac{1}{R\omega_0} \rightarrow R_4; \frac{R}{\omega_0} \rightarrow R_5$
113 +	calculate type 6 tank L	165 1/X	
114 GSB0	or type 7 tank Q	166 ST+4	
115 RCL9		167 STX5	
116 RCL8		168 EEX	initialize k
117 x	calculate coupling element	169 ST07	
118 GSB8		170 CLX	initialize $A_n, n+1$
119 SPC		171 ST09	
120 RCL7		172 RCL6	calculate register index
121 RCL6	test for loop exit	173 9	for g_n
122 XZY?		174 +	
123 GT04		175 ST01	
124 F1?	if type 6 print last tank	176 RCL2	recall termination R
125 GSB5	capacitor	177 *LBL6	print and space subroutine
126 RCL9	calculate type 6 last tank	178 PRTX	
127 GSB0	L_i or type 7 last tank Q	179 *LBL6	space and return subroutine
128 RCL2		180 SPC	
129 GSB6	print termination resistance	181 RTN	
130 GT06			
131 *LBL0	types 6 & 7 common element		
132 RCL8			
133 x	calculate and print type 6		
134 CHS	tank inductor or type 7		
135 RCLC	tank capacitor		
136 +			
137 GSB6			
138 F0?	if type 7 print common tank		
139 GSB5	inductor value		
140 GT06	goto space and return		

LABELS					FLAGS		SET STATUS		
A load f_0	B load BW	C load R	D	E load type	0 type 1 or 7		FLAGS	TRIG	DISP
a	b space & rtn	c	d	e	1 type 2 or 6		ON OFF	USERS CHOICE	
0 type 1 start	1 type 2 start	2 types 1 & 2 loop start	3 types 6 & 7 start	4 types 6 & 7 loop start	2 even branch		0	DEG	FIX
5 print common element	6 prt & space	7 CorL output	8 L or C output	9 initialize	3		1	GRAD	SCI
							2	RAD	ENG
							3		n

HP-67 suggested program changes. The "print" mode of output can be changed to the "R/S" mode by changing like statements at line numbers 147, 152, and 178. The program execution will halt at each data output point and await restart by the user via the "R/S" key.

**PROGRAM 2-6 NORMALIZED LOWPASS TO BANDPASS FILTER TRANSFORMATIONS,
TYPES 8, 9, 10, AND 11.**

Program Description and Equations Used

This program converts normalized lowpass filter element values to a set of four bandpass filter topologies [16], [56]. These four topologies are shown in Fig. 2-6.1 in normalized form (1 ohm, 1 radian/sec center frequency). The parameter A_{ij} is defined by Eq. (2-5.1). Types 8 and 9 are narrowband transformations of types 2 and 1, while types 10 and 11 are exact transformations of types 2 and 1 obtained by applying Norton transformations to the shunt elements of type 2 to form type 10, or to the series elements of type 1 to form type 11. This transformation process is detailed in the equation derivation section following Example 2-6.2. The types 8 and 9 narrowband transformations will only provide accurate results when the loaded Q (ratio of center frequency to bandwidth) is greater than 5 or so. This restriction is not present with types 10 or 11. Because the type 8 or 9 coupling element causes extra zeros of transmission at either dc or infinite frequency, the frequency response will be skewed away from the extra transmission zero frequencies as implied by Fig. 2-5.3. Figure 2-5.2 should be consulted for picking the filter type best suited to the center frequency, loaded Q , and impedance level of the intended application.

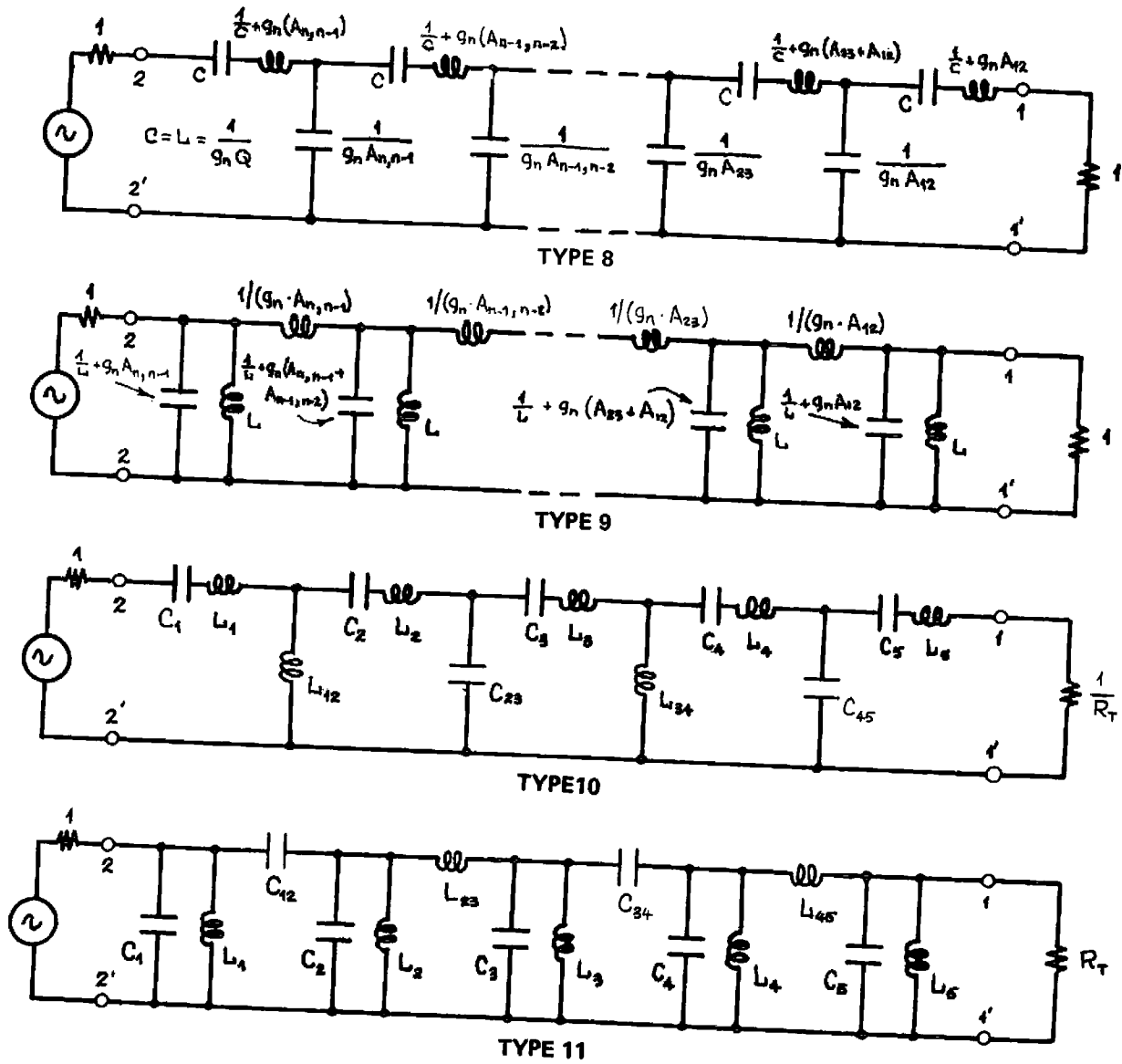


Figure 2-6.1 Normalized bandpass filter topologies for types 8, 9, 10, and 11.

Table 2-6.1 Types 10 and 11 normalized element values.

Type 10 element	Type 11 element	normalized element value
C_k	L_k	$\left(Q \cdot g_1 - \frac{N_{i+2}-1}{Q \cdot g_{i+1}} \right)^{-1}$
L_k	C_k	$Q \cdot g_1 - \frac{N_i - 1}{Q \cdot g_{i-1}}$
$L_{k, k+1}$	$C_{k, k+1}$	$\frac{N_i}{Q \cdot g_{i-1}}$
C_{k+1}	L_{k+1}	$\frac{1}{Q \cdot g_n}$
L_{k+1}	C_{k+1}	$Q \cdot g_n$
$C_{k+1, k+1}$	$L_{k+1, k+2}$	$\frac{Q \cdot g_{i-1}}{N_i}$

$$N_i = \frac{1}{2} \left(1 + \sqrt{1 + 4Q^2 \cdot g_{i-1} \cdot g_n} \right) ; g_{n+1} \equiv 0$$

$$k = 1, 3, 5, \dots, n \quad (n \text{ must be odd})$$

$$i = n - k + 1$$

The reverse ordering of the normalized lowpass coefficients from the element subscripts occurs because the dual form of the normalized lowpass filter is used. The dual is required to place the 1 ohm resistor next to the first shunt capacitor which is required for types 8 and 9 when transforming even ordered filters. Since the same register setup and recall routine is used for types 10 and 11, the dual form is carried over for convenience (it is not required).

Types 10 and 11 can be redrawn to show the ladder structure as T's or pi's of inductors and capacitors as shown in Fig. 2-6.2.

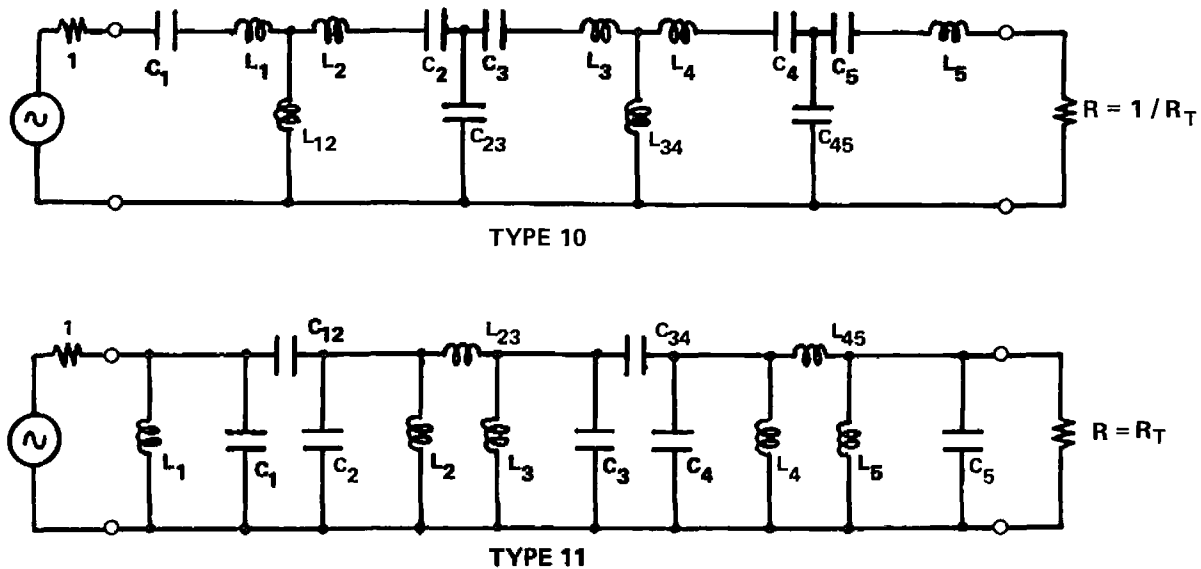


FIGURE 2-6.2 Types 10 and 11 showing T's and pi's of L's and C's.

These pi's and T's of inductors can be replaced with an active realization that contains only op-amps, resistors, and capacitors by using 2 back-to-back generalized impedance converter (GIC) circuits as detailed in Orchard and Sheahan's paper [42], and shown in Figs. 2-6.3 & 4.

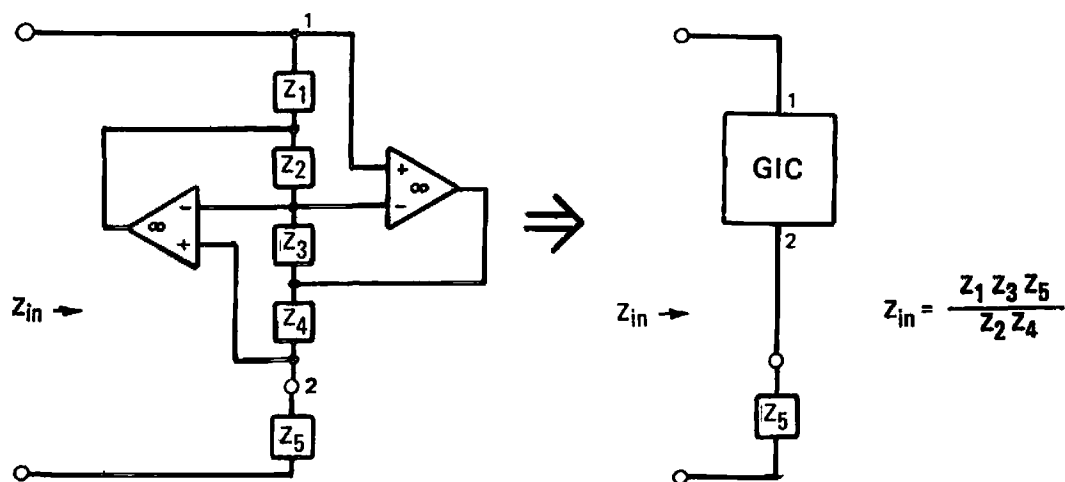


Figure 2-6.3 Antoniou GIC circuit [3].

If Z_1 , Z_2 , Z_3 , and Z_5 are resistors and Z_4 is a capacitor, then,

$$Z_{in} = \frac{R_1 R_3 R_5}{R_2} \cdot sC_4 = sL \quad (2-6.1)$$

Furthermore, if $R_2 = R_3$ (a Q enhancement condition), then,

$$L = R_1 C_4 R_5 \quad (2-6.2)$$

Two GIC circuits with the component selection outlined above can be combined to produce a circuit that simulates a T or pi of inductances. These circuits are shown in Fig. 2-6.4.

Aside from the elimination of inductors, this particular mechanization is very easy to tune. Changing resistor R_1 in the GIC alters the apparent inductance seen at the terminals. The capacitor, C_4 , needs to be stable (e.g., polystyrene or mica) but can have a large initial tolerance which is accommodated during the tuning procedure.

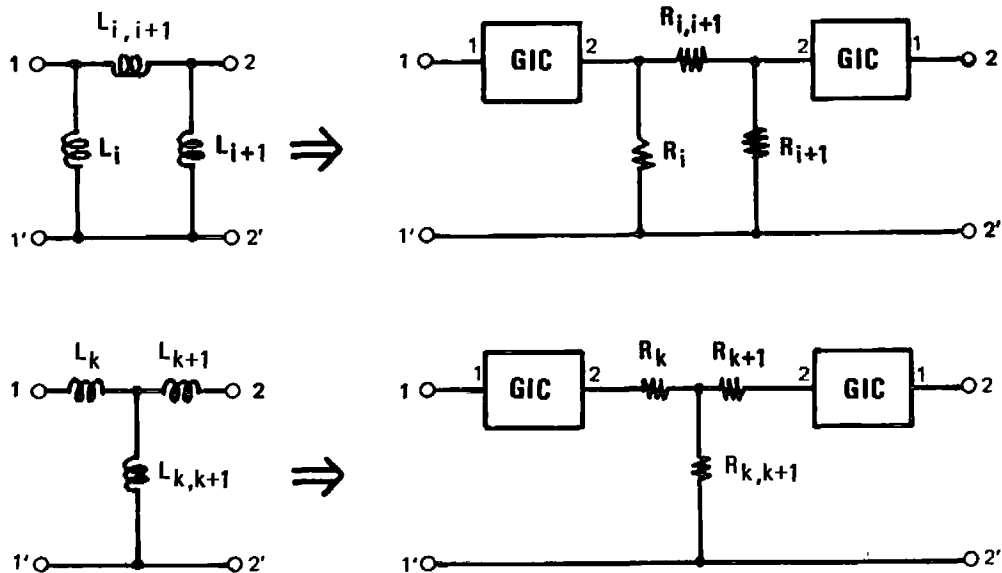


Figure 2-6.4 Pi or T inductance simulation circuits using GIC's.

The diagrams and discussion thus far have used the filters in normalized form, i.e., 1 ohm termination resistor, and 1 radian/second center frequency. The prototype filter is denormalized by

multiplying each normalized inductor by $2\pi f_o/R$, and dividing each normalized capacitor by $2\pi f_o R$, where f_o and R are the desired center frequency and termination resistance level respectively. The program accomplishes this denormalization by calling either subroutine 7 or 8. For types 8 and 10, subroutine 7 denormalizes capacitors and subroutine 8 denormalizes inductors, and the reverse is true for types 9 and 11.

Tuning procedure for types 7, 9, and 11*. After the component values have been calculated, the inductors designed,** fabricated and adjusted to value, and the capacitors selected and padded to the proper value, the filter may be assembled and tuned so it will exhibit the desired response.

Tuning is accomplished by adjusting each of the parallel tank elements. For low frequency filters, the inductor is usually chosen as the adjustable element. At higher frequencies the capacitor is usually chosen as the adjustable element. The resonance of the tank circuit must include the effects of the coupling elements. By temporarily shorting out adjacent tank circuits, the coupling element influence will be included. This tuning procedure is described next.

- 1) Temporarily place a short at location "B" and adjust C_1 (or L_1) to resonate the tank circuit at the center frequency of the filter, f_o . The connection (short) must be low inductance with respect to the other inductances in the circuit.
- 2) Remove the short at "B," and temporarily place shorts at locations "A" and "C." Adjust C_2 (L_2) for tank circuit resonance at the filter center frequency.
- 3) Continue shorting out adjacent tanks with low inductance shorts at locations "B" & "D," "C" & "E," and "D," and adjusting each resulting tank circuit for resonance at the filter center frequency, f_o . These steps will complete the tuning of the filter.

** For more information on inductor design, see the ferromagnetic core and air core inductor design programs contained in another section of this book. Also see the Ferroxcube Inc. publication "Linear Ferrite Materials and Components" for information on ferrite pot core inductor design.

* See program 2-5 for the type 6, 8, and 10 tuning procedure.


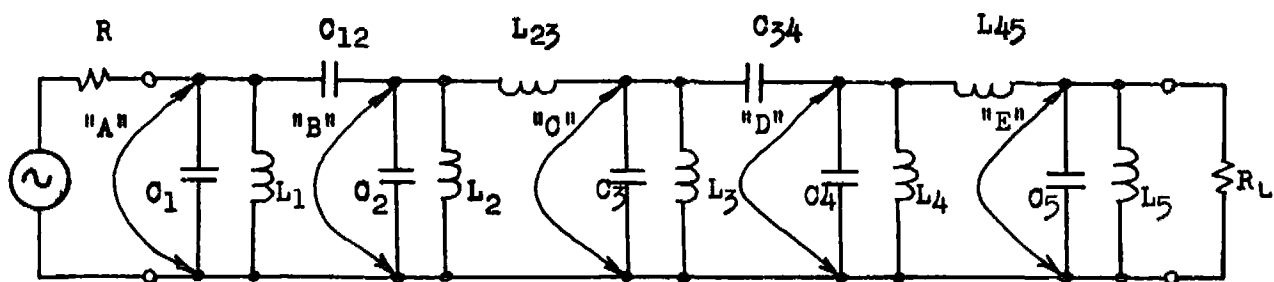


Figure 2-6.5 Circuit shorts for Types 7, 9, and 11 tuning.

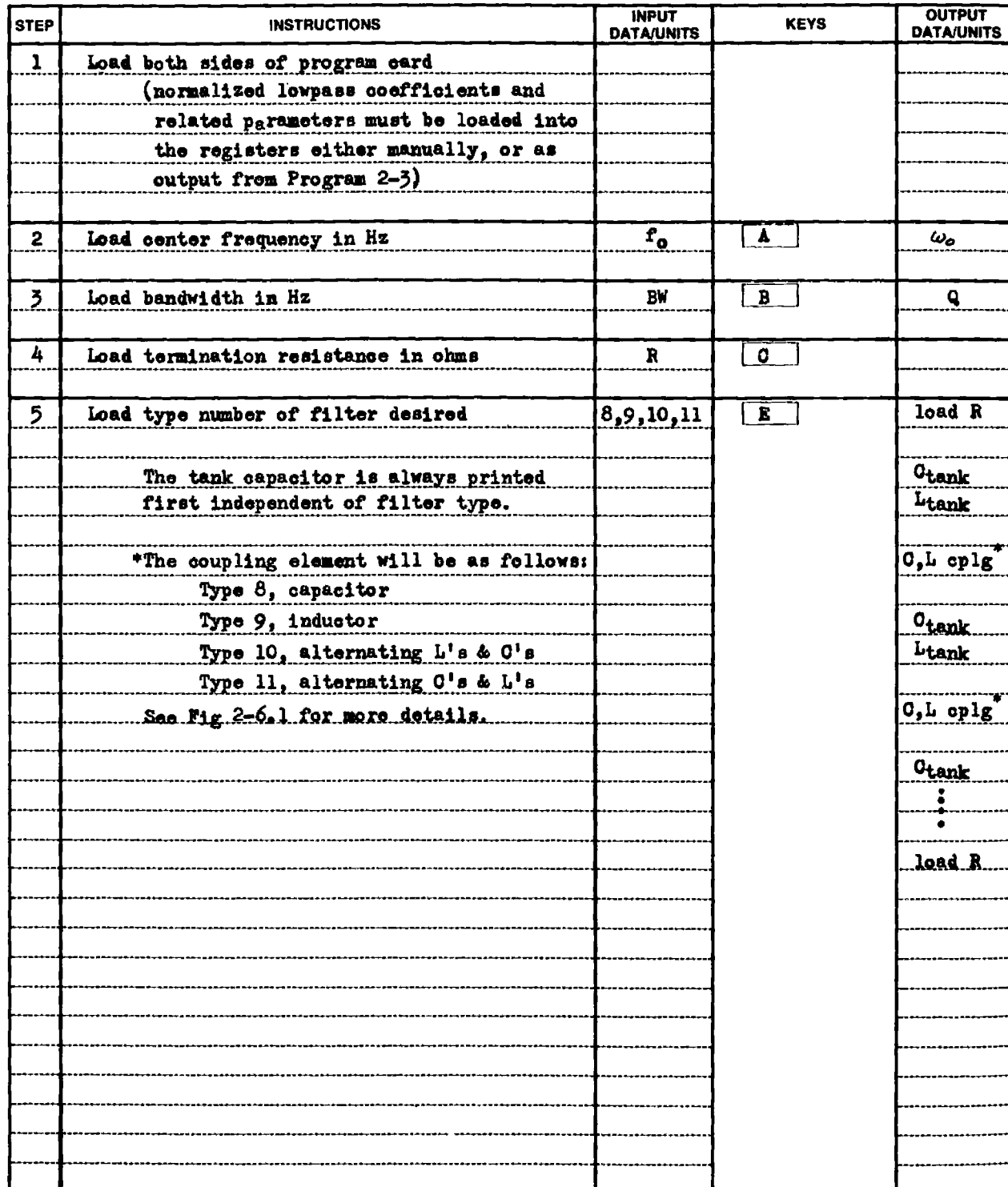

Example 2-6.1 Type 10 Filter Design

A Chebyshev response bandpass filter is required to pass a 20 Hz band of information geometrically centered about 1000 Hz with 0.5 dB ripple or less, and to operate in a 1000 ohm system. The filter stop-bandwidth is 60 Hz, and the filter should reject frequencies lying outside this band by at least 60 dB.

Referring to Fig. 2-5.2 under the headings $f = 1$ kHz, $Q_L = 1000/20 = 50$, and $R = 500$, type 8 is practical, and type 10 is readily realizable. Since active inductor simulation is anticipated, type 10 will be selected.

Program 2-1 is used to calculate the filter order necessary to meet the requirements, and Program 2-3 is used to calculate and store the normalized lowpass coefficients for use by this program. The HP-97 printout for all these programs is shown below.

Load Program 2-1 and calculate required filter order

```

      GSBH select Chebyshev response
    .50 GSBH load ApdB
    60.00 GSBH load AsdB
    3.00 GSBH load  $\lambda$  and calculate minimum filter order
    4.51 *** n, the minimum filter order (output)

    5.00 GSBH load integral filter order and calculate  $\lambda$ 
    2.51 ***  $\lambda$  to meet ApdB and AsdB given n = 5

    3.00 GSBH load  $\lambda$  required and calculate actual AsdB
    61.48 *** AsdB for n = 5 and  $\lambda = 3$ 

```

Load Program 2-3 and calculate Chebyshev LP normalized coefficients

```

    5. GSBH load required filter order
    1. GSBH load desired termination resistance ratio
    .5 GSBH load Chebyshev passband ripple and start
    1.05926+00 *** normalized -3dB frequency (output)

    1.00000+00 ***  $R_T$  (normalized port 1 termination resistance)

    1.70577+00 *** g1
    1.22963+00 *** g2
    2.54083+00 *** g3
    1.22963+00 *** g4
    1.70577+00 *** g5

    1.00000+00 *** R (normalized port 2 termination resistance)

```

Example 2-6.1 (continued)

Load program 2-6 and calculate type 10 filter elements

1000. GSBA load center frequency
 20. GSBB load bandwidth
 1000. GSBC load termination resistor
 10. GSBE select filter type and start

1.00000+03 *** R
 1.86608-09 *** C1
 13.3879+00 *** L1
 188.752-03 *** L12
 1.86608-09 *** C2
 13.5741+00 *** L2
 134.199-09 *** C23
 1.26442-09 *** C3
 20.0331+00 *** L3
 188.752-03 *** L34
 1.86608-09 *** C4
 13.5741+00 *** L4
 134.199-09 *** C45
 1.89203-05 *** C5
 13.5741+00 *** L5
 1.00000+03 *** R_T

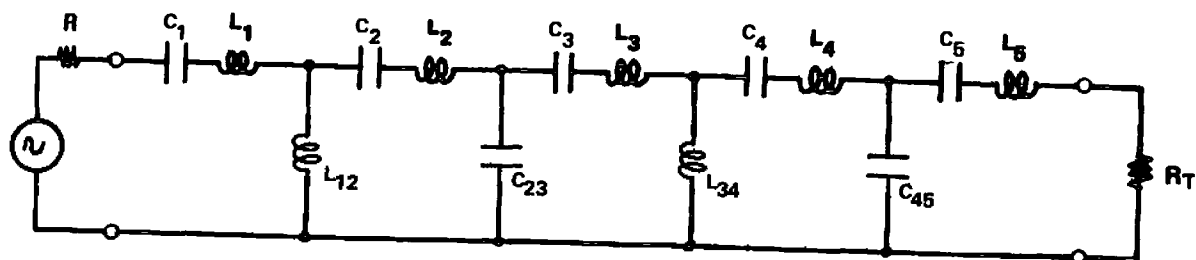


Figure 2-6.6 Type 10 bandpass filter schematic.

Example 2-6.2 Singly terminated type 10 filter design

Because the type 10 filter is an exact bandpass transformation of the lowpass prototype (as is the type 11), the terminating resistances need not be equal. This example will show the synthesis of a singly terminated type 10 filter, i.e., R_T is allowed to approach infinite resistance. The equally terminated filter case is the least sensitive to component value changes. When the filter is singly terminated, the operating Q's of the tank circuits become higher as the open (or shorted) end of the filter is approached. This means that the changes in tank Q's will have a greater effect on the overall operating Q of the tank in the filter, and hence, the filter response. The HP-97 printout for the singly terminated type 10 filter follows. Refer to Fig. 2-6.6 for the filter schematic.

Load Program 2-3

```

      5. GSBA      load n
    1.+05 GSBB      load  $R_T$  ratio
      .5 GSBD      load Chebyshev ripple
1.05926+00 ***       $\omega_{-3dB}$  (output)

100.000+03 ***       $R_T$ 

1.53866+00 ***      g1
1.64272+00 ***      g2
1.81407+00 ***      g3
1.42917+00 ***      g4
852.839-03 ***      g5

1.00000+00 ***      R

```

Load Program 2-6

1000. GSBA	load f_o
20. GSBB	load bandwidth
1000. GSBL	load termination R
10. GSBE	select type & start
1.00000+03 ***	R
3.73236-09 ***	C ₁
6.66484+00 ***	L ₁
124.064-03 ***	L ₁₂
3.73236-09 ***	C ₂
6.78668+00 ***	L ₂
204.171-09 ***	C ₂₃
1.76961-09 ***	C ₃
14.3222+00 ***	L ₃
115.645-03 ***	L ₃₄
3.73236-09 ***	C ₄
6.78668+00 ***	L ₄
219.028-09 ***	C ₄₅
2.08814-09 ***	C ₅
12.2443+00 ***	L ₅
10.0000-03 ***	R _T (short circuit)

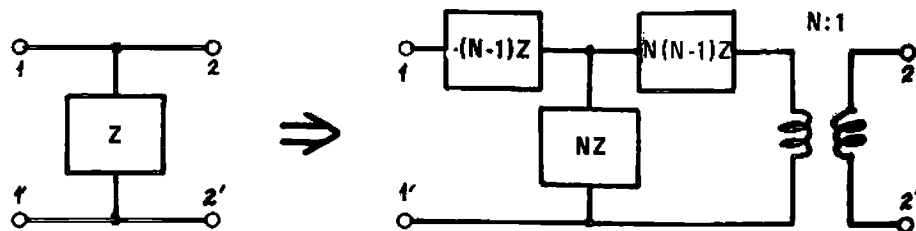
Derivation of types 10 and 11 transformations

Figure 2-6.7 Norton's second transformation.

Figure 2-6.7 shows one form of Norton's second transformation [39]. This transformation changes a single shunt impedance into a T of impedances, one of which is negative, plus an ideal transformer with turns ratio N . Figure 2-6.8 shows how a parallel resonant tank circuit can be changed into a section of a type 10 bandpass filter structure.

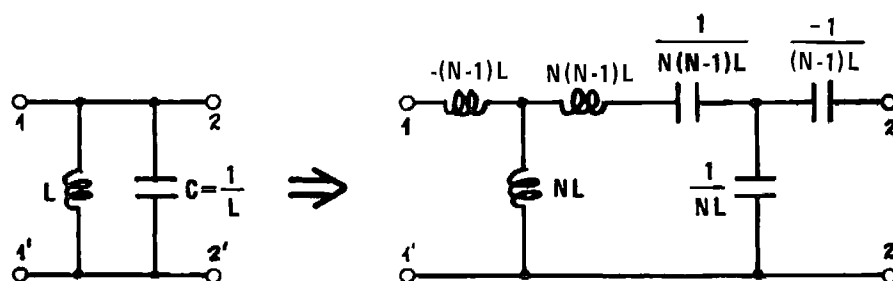


Figure 2-6.8 Norton's second transformation applied to a parallel LC tank circuit.

In Fig. 2-6.8, Norton's transformation has been applied back-to-back, i.e., the 2-2' terminals of the Norton transformation of the inductor have been connected to the 2-2' terminals of the Norton transformation of the capacitor. The same transformer ratio, N , is used for both transformations, therefore, the two ideal transformers are back-to-back providing an overall transformer ratio of unity and can be eliminated.

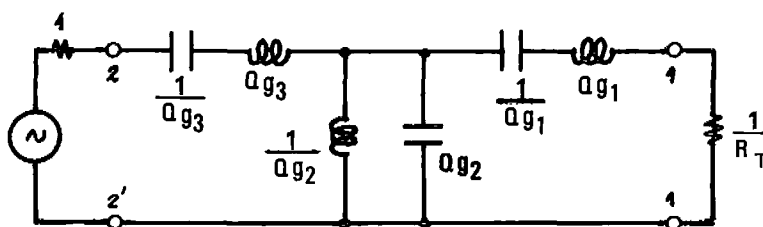


Figure 2-6.9 Type 2 normalized bandpass filter obtained from lowpass prototype (note port ordering).

Figure 2-6.9 shows a type 2 normalized bandpass filter obtained from the transformation of a lowpass prototype. The dual lowpass form is used (see Fig. 2-3.1 lower) and is scaled to a cutoff frequency of $1/Q$ (Q is the ratio of the filter center frequency to bandwidth); each frequency scaled series lowpass inductor is series resonated with a capacitor at $\omega = 1$, and each shunt scaled lowpass capacitor is parallel resonated with an inductor at $\omega = 1$. Next, the circuit of Fig. 2-6.8 is substituted for the parallel resonant tank, and the negative elements in the series arms combined with the positive series elements of Fig. 2-6.9. The results of this process yield the topology shown in Fig. 2-6.10. Higher ordered (odd order) filters are obtained by repeated application of this procedure.

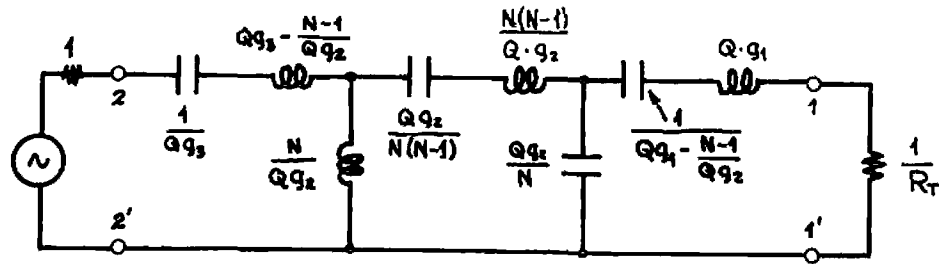


Figure 2-6.10 Type 10 normalized bandpass filter resulting from transformation.

The type 11 bandpass filter is shown in Fig. 2-6.1 and is the dual of the type 10 structure. Type 11 can be derived in a manner similar to the type 10 procedure by applying Norton's first transformation to a type 1 normalized bandpass filter. Norton's first transformation is shown in Fig. 2-8.1. Since type 11 is the dual of type 10 it can be more directly derived from the type 10 structure itself as shown by Fig. 2-6.1 and Table 2-6.1.

The value for N_1 given in Table 2-6.1 is derived by making the transformed tank capacitor (inductor) value the same as the first ladder tank capacitor (inductor) for type 10 (11), i.e.,

$$\frac{1}{Q \cdot g_n} = \frac{Q \cdot g_1 - 1}{N_1 \cdot (N_1 - 1)} \quad (2-6.3)$$

Solving for N_1 yields:

$$N_1 = \frac{1}{2} \left(1 + \sqrt{1 + 4Q^2 \cdot g_{1-1} \cdot g_n} \right) \quad (2-6.4)$$

Program Listing I

LOAD CENTER FREQUENCY									
001	*LBL4								
002	F1								
003	ENT1								
004	+	form and store $2\pi f_0 \rightarrow R_0$							
005	x								
006	STO0								
007	RTN								
LOAD FILTER BANDWIDTH									
008	*LBL5								
009	F1								
010	ENT1								
011	+								
012	x	form and store:							
013	RCL0								
014	XZY	$Q_L = \frac{2\pi f_0}{2\pi BW} \rightarrow R_1$							
015	=								
016	STO1								
017	RTN								
LOAD TERMINATION RESISTANCE									
018	*LBL6								
019	STO2								
020	RTN								
LOAD FILTER TYPE AND START									
021	*LBL7								
022	2								
023	=	calculate starting label							
024	STO1	index							
025	INT								
026	4								
027	-								
028	X<0?	generate "ERROR" if filter							
029	GT00	type is less than 8							
030	XZ1	store label index							
031	SF0								
032	FRC								
033	X=0?	set flag 0 if order is odd							
034	CF0								
035	GT01	goto starting label							
036	*LBL8	type 8 and 9 routine							
037	GSB9	initialize registers							
038	RCL1	recall and store g_1 for							
039	STOE	dual filter topology							
040	STO8								
041	RCL1	calculate and store common							
042	x	element value reciprocal							
043	STOC								
044	CLX	initialize $A_{01} = 0$							
045	STO9								
046	*LBL2	types 8 & 9 loop start							
047	F1?	print type 9 tank							
048	GSB5	capacitor							
049	DSZ1								
050	EEX	increment indices							
051	ST+7								
052	RCL1	recall g_{i+1}							
053	RCL5								
054	XZY	recall g_1 and store g_{i+1}							
055	STOE								
calculate $A_{i, i+1}$									
056	x								
057	JX	calculate $A_{i, i+1}$							
058	1/X								
059	RCL9								
060	XZY	interchange $A_{i-1, i}$ & $A_{i, i+1}$							
061	STO9								
062	+	form $A_{i-1, i} \rightarrow A_{i, i+1}$ and							
063	GSB0	output related element							
064	RCL9								
065	RCL8	calculate and output							
066	x	coupling element							
067	GSB7								
068	SPC								
069	RCL7								
070	RCL6	test for loop exit							
071	XZY?								
072	GT02								
073	F1?	output type 9 tank							
074	GSB5	capacitor							
075	RCL9	output rest of last							
076	GSB0	tank circuit							
077	RCL2								
078	GSB6	recall and print terminating							
079	GT06	resistance value							
080	*LBL0	types 8 & 9 output routine							
081	RCL8								
082	x	output type 8 tank							
083	RCLC	capacitor, or type 9							
084	+	tank inductor							
085	GSB8								
086	F0?	output type 8 tank							
087	GSB5	inductor							
088	GT06								
089	*LBL1	types 10 & 11 routine start							
090	GSB9	initialize registers							
091	*LBL3	types 10 & 11 loop start							
092	RCL9	$Q \cdot g_{i+1}$							
093	RCL1	$i = n, n-2, \dots, 1$							
094	RCL1	$Q \cdot g_i$							
095	x								
096	STO9								
097	XZY								
098	RCL5	$N_{i+2} \quad (N_{n+2} \equiv 1)$							
099	EEX								
100	-								
101	XZY								
102	=								
103	-								
104	STO3	$Q \cdot g_i - \frac{N_{i+2}-1}{Q \cdot g_{i+1}}$							
105	F3?	if first time through loop,							
106	STOC	store value of first L or C							
107	F1?	output type 11 tank							
108	GSB7	capacitor							
109	2								
110	ST+7	increment index, k							
REGISTERS									
0	$2\pi f_0$	1	Q_L	2	R	3	scratch	4	$\frac{1}{\omega_0 R}, \frac{1}{\omega_0}$
5	R	6	n	7	k	8	scratch	9	scratch
10	g_1	11	g_2	12	g_3	13	g_4	14	g_5
15	g_6	16	g_7	17	g_8	18	g_9	19	g_{10}
20	g_{11}	21	g_{12}	22	common element	23	R_T	24	N, g_{i-1}
25		26		27		28		29	index

Program Listing II

111	RCL6		166	RCL3	output type 10
112	RCL7	test for loop exit	167	F0?	tank inductor
113	X>Y?		168	GSB7	
114	GT00		169	SPC	calculate and print
115	RCL9	calculate and store	170	RCL2	termination resistance
116	DSZ1	transformer ratio for	171	RCLD	
117	RCLi	Norton transformation:	172	F1?	
118	RCL1		173	1/X	
119	X		174	X	
120	ST09		175	GSB6	
121	4	$N_i = \frac{1}{2}(1 + \sqrt{1 + 4Q^2 q_n \cdot q_{i-1}})$	176	GT06	
122	X		177	*LBL5	common element output subr
123	RCLC		178	RCLC	recall common element
124	X		179	*LBL7	L/C (odd/even) output subr
125	EEX		180	1/X	
126	+		181	RCL5	
127	JX		182	X	
128	EEX		183	PRTX	
129	+		184	RTN	
130	2		185	*LBL8	G/L (odd/even) output subr
131	=		186	RCL4	
132	ST0E		187	X	
133	EEX	calculate and print tank	188	PRTX	
134	-	inductor for type 10 or	189	RTN	
135	RCL9	tank capacitor for type 11	190	*LBL9	initialization subroutine
136	=		191	SPC	
137	-		192	SF1	
138	GSB8		193	F0?	flag 1 flag 0
139	RCL3	print type 11 tank inductor	194	CF1	
140	F0?		195	SF3	
141	GSB7		196	RCL0	
142	SPC		197	1/X	setup denormalization
143	RCLC		198	ST04	constants for L's and C's
144	RCL9	calculate and print	199	ST05	(register order changed
145	=	coupling element, L for	200	RCL2	depending upon filter type
146	ST08	type 10 or C for type 11	201	F1?	being odd or even)
147	GSB8		202	1/X	
148	SPC		203	ST=4	
149	RCLC	print type 10	204	STX5	
150	F1?	tank capacitor	205	EEX	
151	GSB7	print type 10 tank	206	ST07	initialize registers
152	RCLC	inductor, or print type 11	207	ST09	
153	GSB8	tank capacitor	208	ST0E	
154	RCLC		209	RCL6	
155	F0?	print type 11	210	9	initialize normalized LP
156	GSB7	tank inductor	211	+	coef recall index register
157	SPC		212	ST01	
158	RCL8	calculate and print	213	RCL2	recall termination R
159	GSB7	coupling element, C for	214	*LBL6	print and space subroutine
160	SPC	type 10 or L for type 11	215	PRTX	
161	DSZ1	decrement index and	216	*LBL6	space and return subroutine
162	GT03	return to loop start	217	SPC	
163	*LBL0	last tank output	218	RTN	
164	RCL9	C for type 10, or			
165	GSB8	L for type 11			

LABELS					FLAGS	SET STATUS		
A load f ₀	B Load BW	C load R	D	E Load type	0 type 9 or 11	FLAGS TRIG DISP		
a	b space & rtn	c	d	e	1 type 8 or 10	ON OFF	DEG	FIX
0 types 8 & 9 start	1 types 10 & 11 start	2 types 8 & 9 loop start	3 types 10 & 11 loop start	4	2	0 <input type="checkbox"/>	GRAD	SCI
5 print common elt.	6 print, spc, return	7 print Cor L	8 print L or C	9 initialize	3 first time thru loop	1 <input type="checkbox"/>	RAD	ENG <input type="checkbox"/>
						2 <input type="checkbox"/>		n 5
						3 <input type="checkbox"/>		

HP-67 suggested program changes. To change from the "print" to "R/S" mode for program output, make the respective change at the following line numbers: 183, 188, and 217. The program will now stop at output points and await restart via the "R/S" command from the keyboard.

PROGRAM 2-7 WYE-DELTA TRANSFORMATIONS FOR R, L, OR C.

Program Description and Equations Used

This program performs the Y- Δ transformation for groups of three resistors, capacitors, or inductors. These transformations find use whenever awkward or physically impractical element values result from electrical network design. The resistive transformation is often used with operational amplifier summing network design to keep the resistor values low. The inductive and capacitive transformations can be of assistance in filter design.

The Y- Δ transformations for one-of-a-kind elements are summarized below:

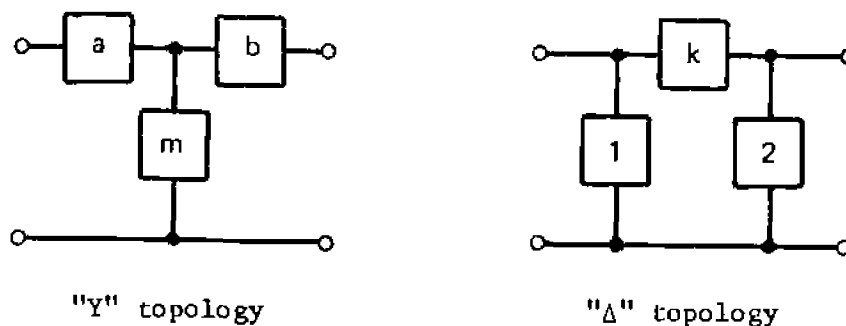


Figure 2-7.1 "Y" and "Δ" topology definitions.

For capacitors as network elements:

Y \rightarrow Δ

$$\begin{aligned} C_1 &= C_a \cdot C_m / \Sigma C \\ C_2 &= C_b \cdot C_m / \Sigma C \\ C_k &= C_a \cdot C_b / \Sigma C \\ \Sigma C &= C_a + C_b + C_m \end{aligned}$$

$\Delta \rightarrow Y$

$$\begin{aligned} C_a &= \Sigma CC / C_2 \\ C_b &= \Sigma CC / C_1 \\ C_m &= \Sigma CC / C_k \\ \Sigma CC &= C_1 C_2 + C_2 C_k + C_1 C_k \end{aligned}$$

For inductors or resistors as network elements (read L's as R's):

Y→Δ

Δ→Y

$$L_1 = \Sigma LL / L_b$$

$$L_2 = \Sigma LL / L_a$$

$$L_k = \Sigma LL / L_m$$

$$\Sigma LL = L_a L_b + L_a L_m + L_b L_m$$


$$L_a = L_1 \cdot L_k / \Sigma L$$

$$L_b = L_2 \cdot L_k / \Sigma L$$

$$L_m = L_1 \cdot L_2 / \Sigma L$$

$$\Sigma L = L_1 + L_2 + L_k$$

User Instructions

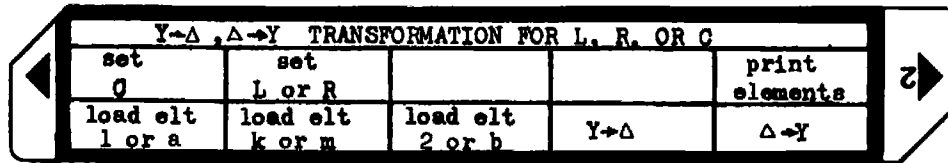

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load program card (one sided card)			
2	Select element type: if capacitors if inductors, or resistors		<div>f</div> <div>A</div> <div>f</div> <div>B</div>	
3	Load element values Load element 1 or a Load element k or m Load element 2 or b		<div>A</div> <div>B</div> <div>Q</div>	
4	Select transformation type: Y→Δ transformation		<div>D</div>	element a element m element b $\Sigma a, m, b$ element 1 element k element 2 $\Sigma 1, k, 2$
	Δ→Y transformation		<div>E</div>	element 1 element k element 2 $\Sigma 1, k, 2$ element a element m element b $\Sigma a, m, b$
5	To print presently stored elements		<div>f</div> <div>E</div>	elt 1, a elt k, m elt 2, b Σ elts.

Example 2-7.1

Convert the Y network of Fig. 2-7.2 into an equivalent Δ network. Compute the total capacitance both before and after the transformation.

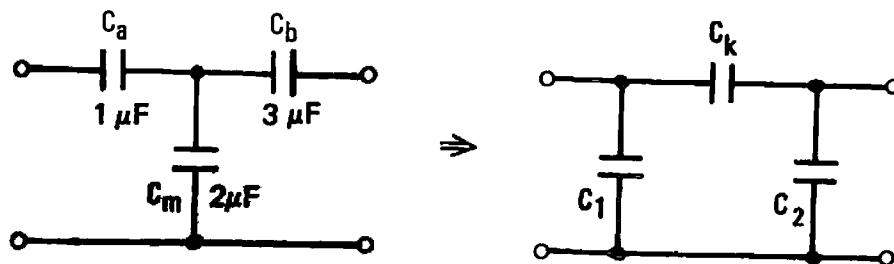


Figure 2-7.2 Capacitor networks for Example 2-7.1.

HP-97 printout

```

1.000-06 *** Ca
3.000-06 *** Cm
2.000-06 *** Cb
          *** } load capacitor values
          GSB0 select capacitors
          GSB0 perform Y→Δ transformation

1.000-06 *** Ca
2.000-06 *** Cm
3.000-06 *** Cb
6.000-06 *** ΣC's } before transformation

333.3-05 *** C1
500.0-05 *** Ck
1.000-06 *** C2
1.833-06 *** ΣC's } after transformation
  
```

As a result of the transformation, the total capacity has been reduced by 69.4%.

Example 2-7.2

A top coupled parallel resonant bandpass filter of the type 7 topology has been designed with the element values shown in Fig. 2-7.3. The 1 picofarad coupling capacitor is a problem since it is the same relative value as the parasitic (stray) capacities of the printed circuit board. By converting from a Δ capacitor configuration to a Y configuration, the minimum filter capacity is 202 pF as seen in Fig. 2-7.4, and the parasitic capacities of the printed circuit board are easily managed.

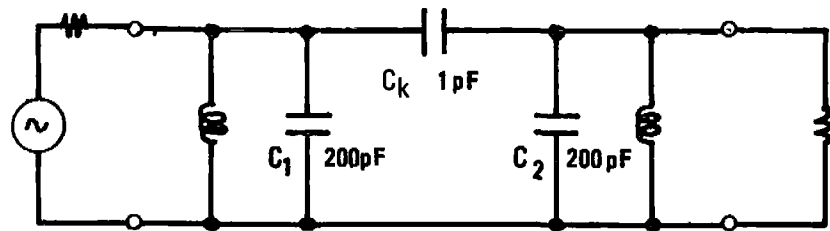


Figure 2-7.3 Type 7 filter design.

HP-97 printout for $\Delta \rightarrow Y$ transformation:


```

200.-12 GSB C1 }
      GSB C2 } load capacitor values
      .-12 GSB Ck }
      GSB select capacitors
      GSB start  $\Delta \rightarrow Y$  transformation

200.0-12 *** C1 }
1.000-12 *** Ck } summary before
200.0-12 *** C2 } transformation
401.0-12 *** total capacity }

202.0-12 *** Ca }
40.40-09 *** Cm } summary after
202.0-12 *** Cb } transformation
40.80-09 *** total capacity }

```

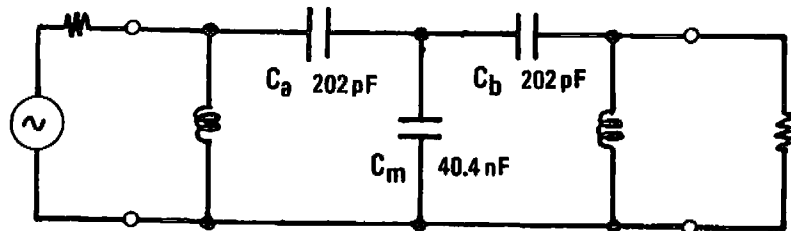Figure 2-7.4 Network after $\Delta \rightarrow Y$ transformation.

PROGRAM 2-8 NORTON TRANSFORMATIONS.

Program Description and Equations Used

Two network equivalence transformations developed by Edward L. Norton are shown below. They can be extremely useful for modifying network element values or topology.

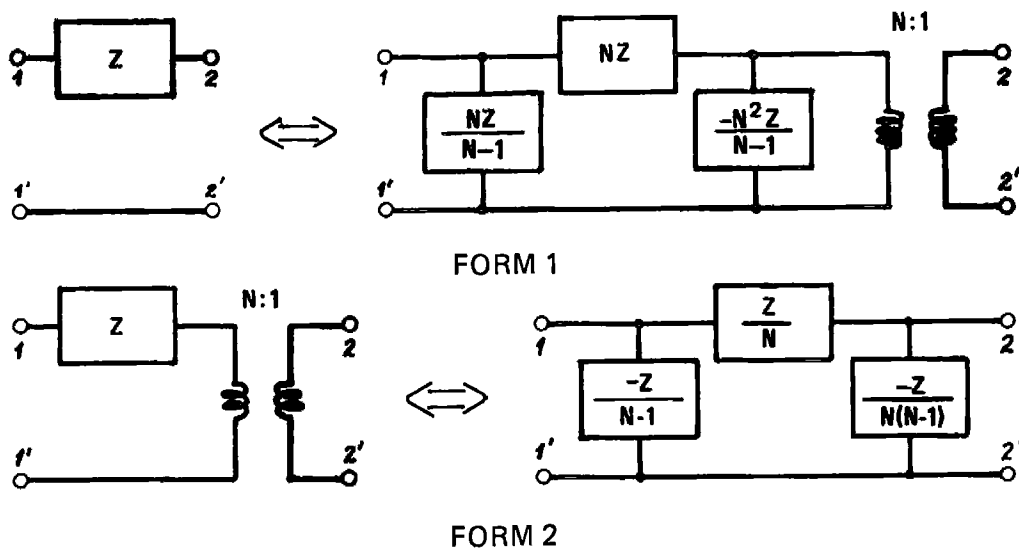


Figure 2-8.1 Two forms of Norton's first transformation.

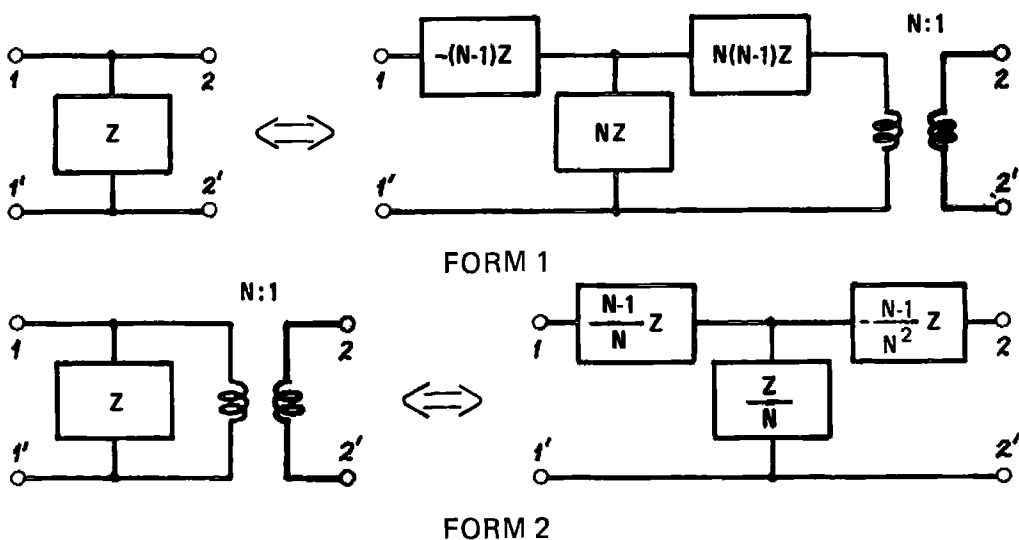


Figure 2-8.2 Two forms of Norton's second transformation.

Figure 2-8.1 shows two forms of Norton's first transformation, and Fig. 2-8.2 shows two forms of Norton's second transformation. The transformed network always contains a negative element, which is combined with a positive element not involved in the transformation. N must be chosen so this combination results in a zero or positive element value if the element is to be realized passively (there are active circuits which can simulate negative elements). When N is chosen so the negative and positive elements annihilate one-another, the overall network topology changes. This technique can be used to reverse an "L" network as shown in Fig. 2-8.3

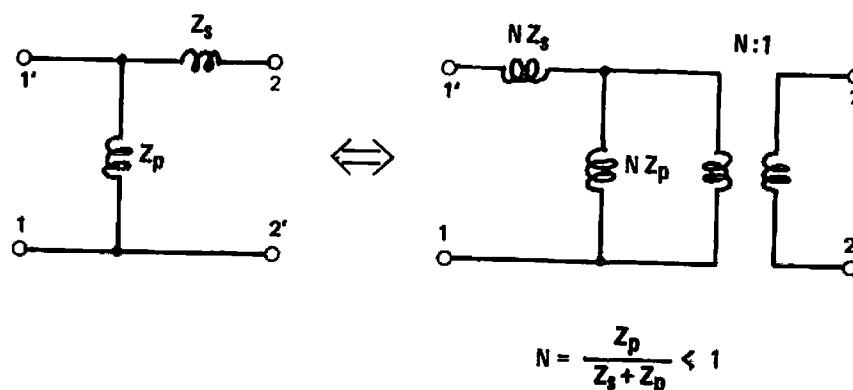


Figure 2-8.3 Norton transformation applied to an "L" network.

Chapter 10 of Zverev [58] has many example of the application of Norton's transformations. Some insight into the power of Norton's transformations is related in the article "Reminiscences" by W.R. Bennett in CAS-24 no. 12 (Dec. 1977). Dr. Bennett recollects that Ed Norton could efficiently furnish a network to give a prescribed loss characteristic with the minimum number of elements by using only a very ordinary sliderule, his intuition, and his transformations.

This HP-67/97 program will transform either capacitors or inductors and resistors. Because the impedance of a capacitor is inversely proportional to the capacitance, multiplying an impedance by N has the effect of dividing the capacitance by N . Figure 2-8.4 shows form 1 of Norton's first transformation when the element being transformed is a capacitor.

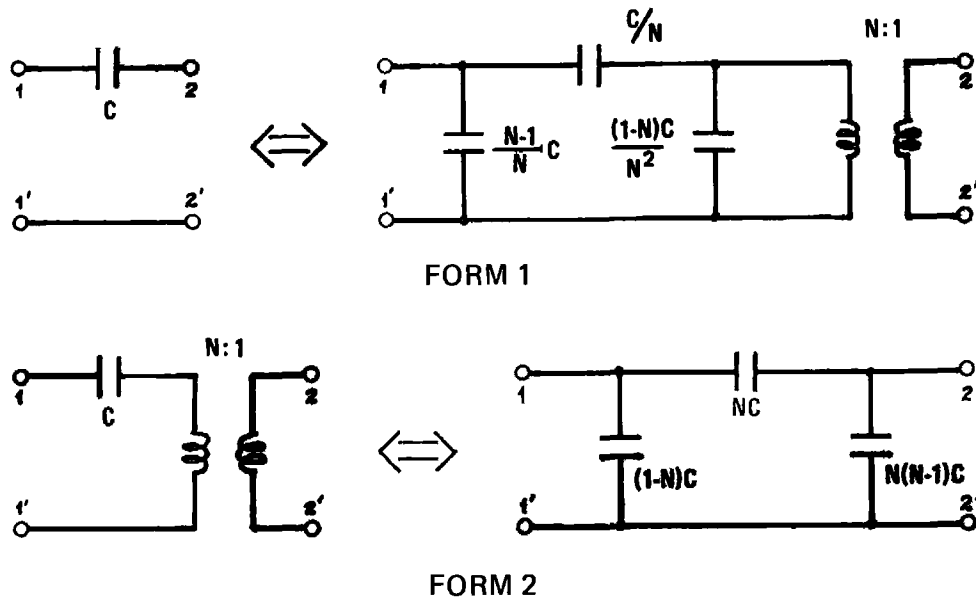


Figure 2-8.4 Norton's first transformation for capacitors.

The same reciprocal relations hold for Norton's second transformation as applied to capacitor networks.

User Instructions

NORTON TRANSFORMATIONS				
load C	OR	load L or R	load N	calculate 1st xfm forms
				calculate 2nd xfm forms

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load program card			
2	If a capacitor network is being transformed, load capacitor value	C	A	
	OR			
	If an inductor or resistor network is being transformed, load L or R value	L, R	B	
3	Load ideal transformer ratio desired	N	C	
4	To calculate both forms of Norton's first transformation		D	shunt elt
			form one	series elt
				shunt elt
				space
				xfmr ratio
				space
				space
			form two	shunt elt
				series elt
				shunt elt
5	To calculate both forms of Norton's second transformation		E	series elt
			form one	shunt elt
				series elt
				space
				xfmr ratio
				space
				space
			form two	series elt
				shunt elt
				series elt

Example 2-8.1

An impedance stepdown of 3:1 is required at the output of the bandpass filter shown in Fig. 2-8.5. A transformer could be used to provide this function. Instead, use Norton's first transformation to provide the impedance stepdown without a transformer.

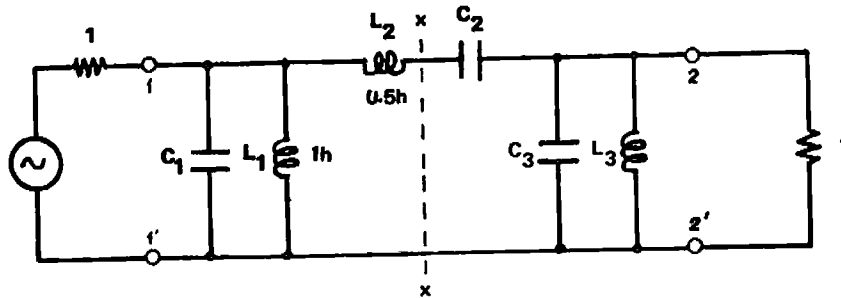


Figure 2-8.5 Bandpass filter network for Ex. 2-8.1.

A hypothetical $\sqrt{3}:1$ turns ratio transformer is inserted at $x-x$, and all network elements to the right scaled down in impedance by a factor of 3 as shown in Fig. 2-8.6.

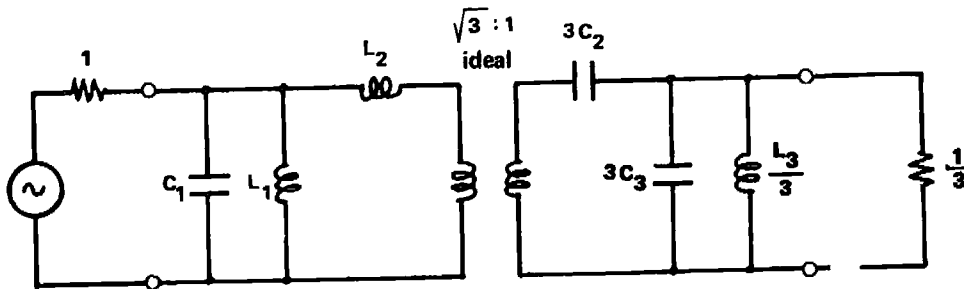


Figure 2-8.6 Network of Fig. 2-8.5 after insertion of hypothetical transformer.

Form 2 of Norton's first transformation is applied to L_2 and the transformer as shown in Fig. 2-8.7. The resulting negative shunt inductor is combined with L_1 as shown in Fig. 2-8.8.

HP-97 printout for Norton's first transformation

.5 655E L₂

$$\left. \begin{array}{l} \bar{c}_1 \quad \sqrt{\lambda} \\ 655E \end{array} \right\} N$$

655E calculate Norton's first transformation

$$\left. \begin{array}{lll} 1.183+20 & *** & L_a \\ 656.0-03 & *** & L_b \\ -2.045+00 & *** & L_c \\ 1.771+00 & *** & \text{transformer ratio} \end{array} \right\} \text{form 1}$$

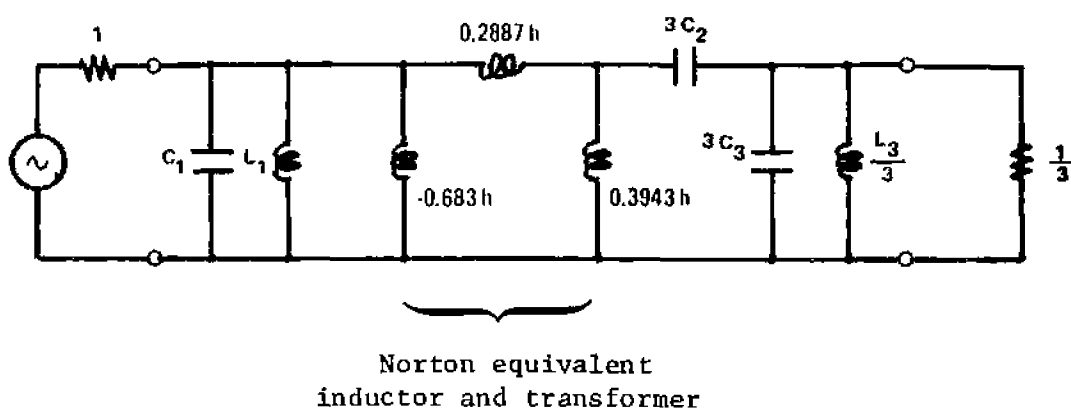
$$\left. \begin{array}{lll} -683.0-03 & *** & L_a \\ 336.7-03 & *** & L_b \\ 354.3-03 & *** & L_c \end{array} \right\} \text{form 2}$$


Figure 2-8.7 Network of Fig. 2-8.6 with form 2 of Norton's first transformation applied.

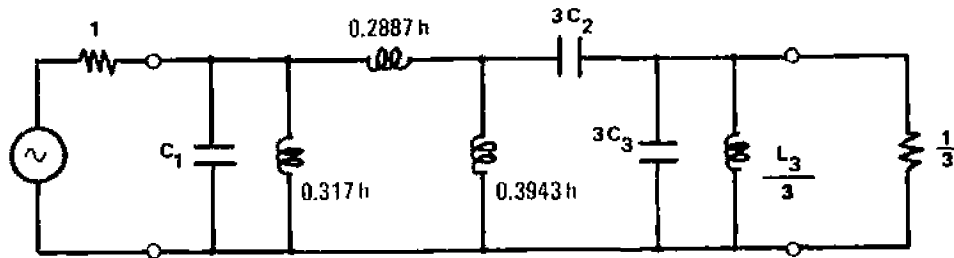


Figure 2-8.8 Final network with all negative elements absorbed.

Program Listing I

001 *LFL4	LOAD C	053 *LBLE	CALCULATE SECOND TRANSFORM
002 SFB	indicate capacitor entry	054 SPC	
003 1/X	form and store reciprocal	055 RCL0	
004 ST02	of entry	056 RCL1	form 1 series element
005 1 Y	restore entry	057 EEX	calculation
006 RTN		058 -	
007 *LBLE	LOAD L OR R	059 x	
008 CFB	indicate L or R entry	060 ST02	
009 ST00	store entry	061 CHS	
010 RTN		062 GSB0	
011 *LBLE	LOAD N	063 RCL0	
012 ST01		064 RCL1	form 1 shunt element
013 PTN		065 x	calculation
014 *LBLE	CALCULATE FIRST TRANSFORM	066 GSB0	
015 SPC		067 RCL2	
016 RCL1		068 RCL1	form 1 series element
017 RCL1	form 1 shunt element	069 x	calculation
018 EEX	calculation	070 GSB0	
019 -		071 SPC	
020 ÷		072 RCL1	recall and print ideal
021 RCL0		073 PRTX	transformer turns ratio
022 x		074 SPC	
023 ST02		075 SPC	
024 GSB0		076 RCL1	
025 RCL0		077 EEX	
026 RCL1	form 1 series element	078 -	form 2 series element
027 x	calculation	079 RCL1	calculation
028 GSB0		080 ÷	
029 RCL2		081 RCL0	
030 RCL1	form 1 shunt element	082 x	
031 x	calculation	083 ST02	
032 CHS		084 GSB0	
033 GSB0		085 RCL0	
034 SPC		086 RCL1	form 2 shunt element
035 RCL1	recall and print transformer	087 ÷	calculation
036 PRTX	turns ratio	088 GSB0	
037 SPC		089 RCL2	
038 SPC		090 CHS	
039 RCL0		091 *LBL1	
040 RCL1	form 2 shunt element	092 RCL1	form 2 series element
041 EEX	calculation	093 ÷	calculation
042 -		094 GSB0	
043 ÷		095 SPC	
044 ST02		096 SPC	
045 CHS		097 RTN	
046 GSB0		098 *LBL0	output subroutine
047 RCL0		099 F0?	
048 RCL1	form 2 series element	100 1/X	
049 ÷	calculation	101 PRTX	
050 GSB0		102 RTN	
051 RCL2	form 2 shunt element		
052 ST01	calculation		

REGISTERS

0 1 C or L	1 N	2 scratch	3	4	5	6	7	8	9
S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
A	B	C	D	E	I				

LABELS						FLAGS	SET STATUS		
A load C	B load L	C load N	D calc type 1	E calc type 2	F capacitor		ON OFF	USER'S CHOICE	DISP
a	b	c	d	e	f		0 ■	DEG FIX	
output subr.	1	2	3	4	5		1	GRAD SCI	
	6	7	8	9	10		2	RAD ENG	n _____
							3		

PROGRAM 2-9 BUTTERWORTH AND CHEBYSHEV ACTIVE LOWPASS FILTER DESIGN AND POLE LOCATIONS.

Program Description and Equations Used

This program calculates the pole locations and Sallen and Key topology element values for un-normalized Butterworth or Chebyshev all pole lowpass filter approximations.

The program is designed to allow the use of capacitors with specified values as might result from the actual capacity measurement of a selected capacitor. The design process starts by assuming that all resistors are equal to the design resistance level, and the capacitor values are calculated to meet the filter requirements. The user may select new capacitor values near the original values, and the program will calculate new resistor values to meet the filter requirements. These resistor values can generally be selected from the nearest standard 0.1% resistor values.

The normalized pole locations of a Butterworth lowpass filter lie on a circle of unit radius as shown by Fig. 2-2.1 with the generalized pole locations given by Eqs. (2-2.12) and (2-2.13). The normalized pole locations for a Chebyshev lowpass filter lie on an ellipse as shown by Fig. 2-2.3 with the generalized pole locations given by Eqs. (2-2.15), (2-2.16), (2-2.17), and (2-2.18).

Each complex conjugate pole pair can be expressed in either the cartesian (real and imaginary parts) or the polar (magnitude and angle) co-ordinate systems. A variation on the polar system allows the pole pair to be defined in terms of the natural frequency (polar radius), ω_n , and "Q," or quality factor. The relationship between these co-ordinate systems is shown in Fig. 2-9.1, and described by Eqs. (2-9.1) through (2-9.3).

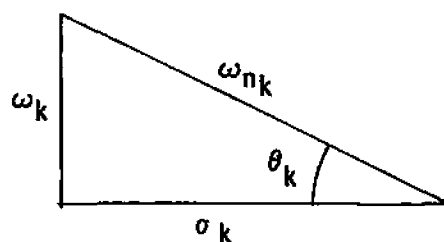


Figure 2-9.1 Co-ordinate system relationships.

$$\omega_{n_k}^2 = \sigma_k^2 + \omega_k^2 \quad (2-9.1)$$

$$\theta_k = \tan^{-1} \left(\frac{\omega_k}{\sigma_k} \right) \quad (2-9.2)$$

$$Q_k = \frac{1}{2 \cos \theta_k} = \frac{\omega_{n_k}}{2\sigma_k} \quad (2-9.3)$$

The element values for the Sallen and Key type active resonator are easily expressed in terms of ω_n and Q as follows:

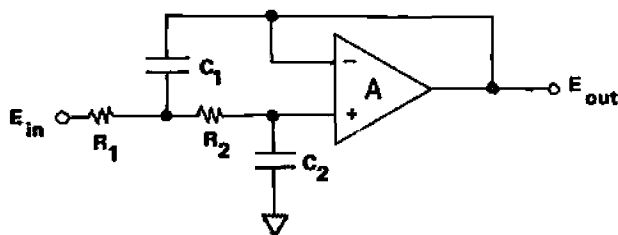


Figure 2-9.2 Sallen and Key active lowpass filter topology.

$$C_1 = \frac{Q(R_1 + R_2)}{\omega_n R_1 R_2} \quad \Bigg| \quad = \quad \frac{2Q}{\omega_n R} \quad (2-9.4)$$

$$C_2 = \frac{1}{\omega_n Q (R_1 + R_2)} \quad \Bigg| \quad = \quad \frac{C_1}{4Q^2} \quad (2-9.5)$$

$$R_1 = R_2 = R$$

The Sallen and Key resonator topology is chosen over other types because of the low parameter sensitivities to element changes. This type of filter synthesis is called the cascade method. Each pole pair is synthesized by an isolated op-amp resonator circuit. The entire filter is formed from a cascade of these resonator circuits. With each pole pair being independent, the overall filter sensitivities to component value changes are higher than an equivalent LC filter. See reference [49] (page 314) for more details.

If higher order filters are required (n greater than 9 or so), either the leapfrog (Szentirmai) topology using Deliyannis resonators [48], [20] or Cauer-Chebyshev filters using biquadratic sections [35] should be considered.

If the two capacitors in the Sallen and Key circuit are specified, then the following equations express the resistor values.

$$R_1 = \frac{1 + \sqrt{1 - 4Q^2 C_2 / C_1}}{2Q\omega_n C_2} \quad (2-9.6)$$

$$R_2 = \frac{1}{\omega_n^2 C_1 C_2 R_1} \quad (2-9.7)$$

To ensure the quantity under the radical is positive in the equation for R_1 , C_2 should be selected to be a lower value, and C_1 a higher value than given by Eqs. (2-9.4) and (2-9.5).

If the filter order is odd, then a real pole exists. A third order op-amp resonator circuit may be used to produce both the real pole and a complex conjugate pair. The lowest Q pole pair is selected for realization by this circuit to minimize sensitivities, and to keep the element value spread within bounds. The third order section topology is

shown in Fig. 2-9.3.

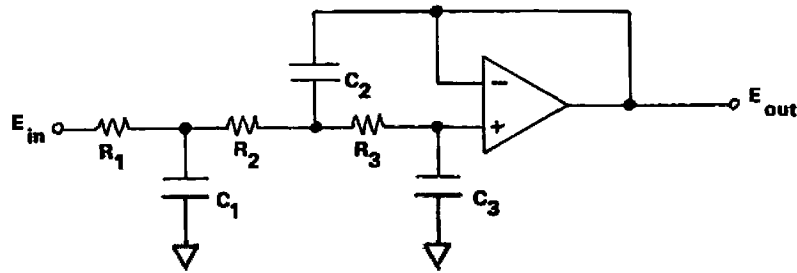


Figure 2-9.3 Third order op-amp resonator circuit.

$$\frac{E_{out}}{E_{in}} = \frac{1}{D(s)} \quad (2-9.8)$$

where

$$D(s) = s^3 C_1 C_2 C_3 R_1 R_2 R_3 + s^2 C_3 \{ C_1 R_1 (R_2 + R_3) + C_2 R_3 (R_1 + R_2) \} + s \{ C_1 R_1 + C_3 (R_1 + R_2 + R_3) \} + 1$$

$$\frac{E_{out}}{E_{in}} = \frac{1}{Cs^3 + Bs^2 + As + 1} = \frac{1}{\frac{s^2}{\omega_n^2} + \frac{s}{\omega_n Q} + 1} \cdot \frac{1}{\tau s + 1} \quad (2-9.9)$$

$$\text{for } R_1 = R_2 = R_3 = 1 \quad (2-9.10)$$

$$A = C_1 + 3C_3 = \tau + \frac{1}{\omega_n Q} \quad (2-9.11)$$

$$B = 2C_3(C_1 + C_2) = \frac{\tau}{\omega_n Q} + \frac{1}{\omega_n^2} \quad (2-9.12)$$

$$C_1 = C_1 C_2 C_3 = \frac{\tau}{\omega_n^2} \quad (2-9.13)$$

The equations for A, B, and C represent three equations in three unknowns, C_1 , C_2 , and C_3 . By algebraic manipulation, a cubic equation in C_1 alone may be obtained.

$$C_1^3 - C_1^2 (A) + C_1 \left(\frac{3}{2} B\right) - 3C = 0 \quad (2-9.14)$$

A Newton-Raphson iterative solution is used to find the real root of this equation (there will be at least one). Once C_1 is found, the remaining two capacitors are found as follows:

$$C_3 = \frac{A - C_1}{3} \quad (2-9.15)$$

$$C_2 = \frac{C}{C_1 C_3} \quad (2-9.16)$$

If the three capacitors are specified, then the transmission function (Eq. (2-9.9)) may be used to obtain three equations in terms of the three unknown resistors. Equating like powers of s , as before, these equations result:

$$A = C_1 R_1 + C_3 (R_1 + R_2 + R_3) = \tau + \frac{1}{\omega_n Q} \quad (2-9.17)$$

$$B = C_3 \{C_1 R_1 (R_2 + R_3) + C_2 R_3 (R_1 + R_2)\} = \frac{\tau}{\omega_n Q} + \frac{1}{\omega_n^2} \quad (2-9.18)$$

$$C = C_1 C_2 C_3 R_1 R_2 R_3 = \frac{\tau}{\omega_n^2} \quad (2-9.19)$$

By algebraic manipulation, R_2 may be eliminated leaving two equations in two unknowns, R_3 as a cubic function of R_1 alone, and a quadratic equation in R_1 with R_3 as a parameter. The quadratic formula is used to reduce the second equation to R as a function of R_1 alone. These two non-linear equations in two unknowns are solved using an iterative method given in an unpublished paper by Robert Esperti of Delco Electronics.

$$R_3 = \frac{1}{R_1^2 C_2 C_3} \left\{ R_1^2 (C_1 (C_1 + C_3)) + R_1^2 (A C_1) + R_1 (B) + \frac{C}{C_1} \right\} \quad (2-9.20)$$

$$R_1 = \frac{-b}{2a} + \sqrt{\left(\frac{b}{2a}\right)^2 - \frac{c}{a}} \quad (2-9.21)$$

$$\frac{-b}{2a} = \frac{A - C_3 R_3}{2(C_1 + C_3)} ; \quad \frac{c}{a} = \frac{C}{(C_1 + C_3) \cdot C_1 C_2 R_3} \quad (2-9.22)$$

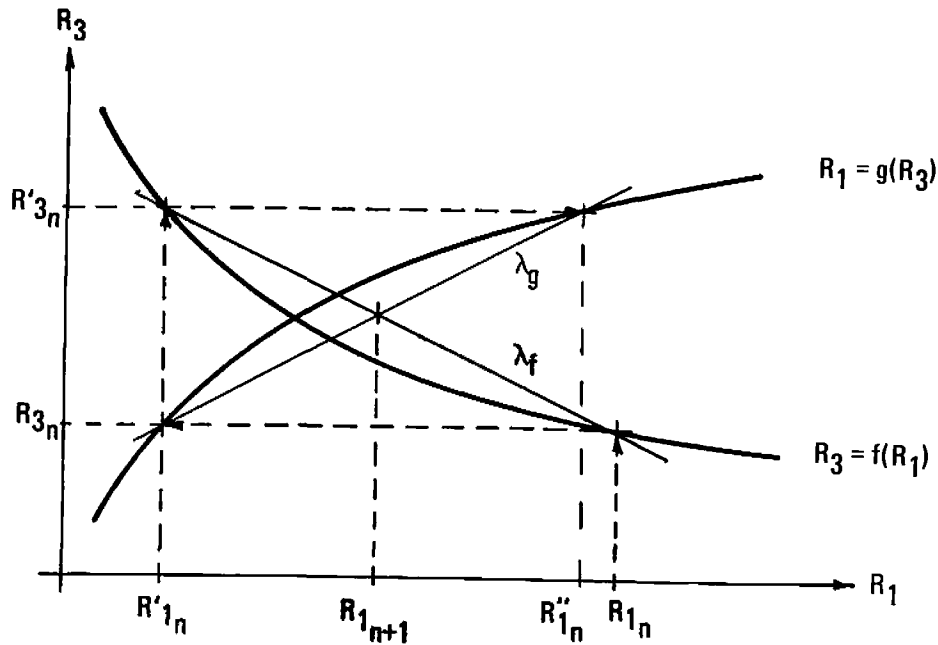


Figure 2-9.4 Esperti's iterative method.

Referring to Fig. 2-9.4, an initial guess for R_1 is made. The corresponding value for R_3 is calculated using $R_3 = f(R_1)$. The corresponding value for R_1 (say R'_1) is calculated using the above value for R_3 in $R'_1 = g(R_3)$. Using $R_3 = f(R'_1)$, a second value of R_3 is calculated; this value of R_3 is designated R'_3 . Finally, a second value of R_1 is calculated using $R_1 = g(R'_3)$; this value of R_1 is designated R''_1 . Straight lines designated λ_f and λ_g are drawn as shown. The intersection of these two lines defines the next guess for R_1 . The iteration is halted when the new and old values for R_1 agree within $10^{-6}\%$. The convergence of this method is quite fast with four iterations generally providing the above accuracy. Furthermore, the method will converge when direct substitution type iteration proves to be divergent.

The above procedure may be done algebraically to yield a recursion relationship as shown below:

$$R_{1n+1} = R_{1n} + \frac{g(f(R_{1n})) - R_{1n}}{1 - \frac{g(f(g(f(R_{1n})))) - g(f(R_{1n}))}{g(f(R_{1n})) - R_{1n}}} \quad (2-9.23)$$

The recursion relationship may be further reduced to an algorithm that can be used to program the HP-97. This algorithm is shown below:

$$R'_{1n} = g(f(R_{1n})) \quad (2-9.24)$$

$$R''_{1n} = g(f(R'_{1n})) \quad (2-9.25)$$

$$\delta = R'_{1n} - R_{1n} \quad (2-9.26)$$

$$\delta' = R''_{1n} - R'_{1n} \quad (2-9.27)$$

$$\epsilon = \frac{\delta}{1 - \delta'/\delta} \quad (2-9.28)$$

$$R_{1n+1} = R_{1n} + \epsilon \quad (2-9.29)$$

$$\text{Terminate if } \left| \frac{\epsilon}{R_{1n+1}} \right| \leq 10^{-8} \quad (2-9.30)$$


Each time through the $R'_{1n} = g(f(R_{1n}))$ calculation, the value of R_3 is stored in a scratchpad register. After the iteration loop termination, values for R_1 and R_3 will be at hand. The following formula relates R_2 to these resistors and the other known quantities:

$$R_2 = \frac{C}{C_1 C_2 C_3 R_1 R_3} \quad (2-8.31)$$

To simplify the initial guess for R_1 and to keep the range of numbers within bounds, the selected values for the capacitors are normalized to 1 ohm, 1 radian/second values for use by the program. After the corresponding normalized resistors are calculated, the resistance values are de-normalized before output.

User Instructions

BUTTERWORTH & CHEBYSHEV ACTIVE LP FILTER DESIGN & POLES				
$O_1: n \uparrow \epsilon_{dB}$			enter f_{-dB} & start	
$B_1: n$	$B_1: -\epsilon_{dB}$	R	enter f_{-3dB} & start	enter $O_1 \uparrow O_2$

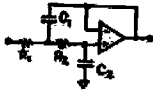STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card # 1			
2	If Chebyshev: enter filter order enter passband ripple go to step 4	n ϵ_{dB}	ENT f A	
3	If Butterworth: enter filter order if bandedge is defined by other than the $-3dB$ point, enter the dB down defining the bandedge	n $-\epsilon_{dB}$	A B	
4	Enter the design resistance level	R, Ω	0	
5	If bandedge is $-3dB$ point, enter f_{-3dB} & start	f_{-3dB}, Hz	D	If Cheb f_{-dB} see below for rest
6	If bandedge is $-\epsilon_{dB}$ point, enter $f_{-\epsilon_{dB}}$ & start The data is for the second order filter section, and alternate capacitor values entered in next step are also for the second order section. The third order section (for odd filter order) is output last and is described on the next page.	$f_{-\epsilon_{dB}}, Hz$	f D 	If Buttw f_{-3dB} space ω_n Q $C_{1,F}$ $C_{2,F}$ stop
7	If alternate capacitor values are desired, enter C'_1 (to skip this step, press "E" without numeric entry) enter C'_2 After the second resistor value output, the program execution will automatically return to step six until all second order sections have been outputted. If the filter is odd order, the display will flash to indicate the reading of the second card is required.	C'_1, F C'_2, F	ENT E	third order section output ω_n Q σ flashing display R_1, Ω R_2, Ω

Example 2-9.1

A 1 dB ripple Chebyshev lowpass active filter must pass all frequencies between dc and 1000 Hz within 3 dB, and must reject all frequencies higher than 2000 Hz by more than 60 dB. Program 2-1 may be used to determine the necessary filter order. This program calculates a minimum filter order of 6.19, which is rounded to the next highest integer, 7. A 7th order, 1 dB ripple Chebyshev lowpass filter that is 3 dB down at 1000 Hz, will be 1 dB down at 983.1 Hz and 69.4 dB down at 2000 Hz ($\lambda = 2000/983.1 = 2.035$).

This program (Program 2-9) is used to calculate the element values for a 7th order, 1 dB ripple, 1000 Hz -3 dB cutoff frequency Chebyshev filter. A design resistance level of 10000 ohms is chosen which will make the capacitor values around $1/(2\pi fR) = 0.016 \mu\text{F}$.

PROGRAM INPUT

```

      7. ENT↑  n
      1. GSBa  εdB

    10000. GSEC  design resistance level

      1000. GSBD  -3dB frequency
    983.1+00 ***  -1dB frequency (output)

```

PROGRAM OUTPUT

section one

```

    6.154+03 ***  ωna
    10.90+00 ***  Qa
    354.2-05 ***  C1a
    745.5-12 ***  C2a
      .47-06 ENT↑  C1a
      750.-12 GSBE C2a } alternate values
    14.83+03 ***  R1a
    5.052+03 ***  R2

```

section two

```

    4.993+03 ***  ωnb
    3.156+00 ***  Qb
    126.4-09 ***  C1b
    3.173-09 ***  C2b
      .22-06 ENT↑  C1b
      3.-09 GSBE C2b } alternate values
    17.72+03 ***  R1b
    3.429+03 ***  R2b

```

section three

```

    2.965+03 ***  ωn } of second order pair
    1.297+00 ***  Q }
    1.269+03 ***  σ, real pole location
    85.66-05 ***  C1c
    163.9-09 ***  C2c
    6.385-09 ***  C3c
      .1-06 ENT↑  C1c
      .22-06 ENT↑  C2c } alternate values
      6.2-09 GSBE C3c
    9.800+03 ***  R1c
    6.113+03 ***  R2c
    12.62+03 ***  R3c

```

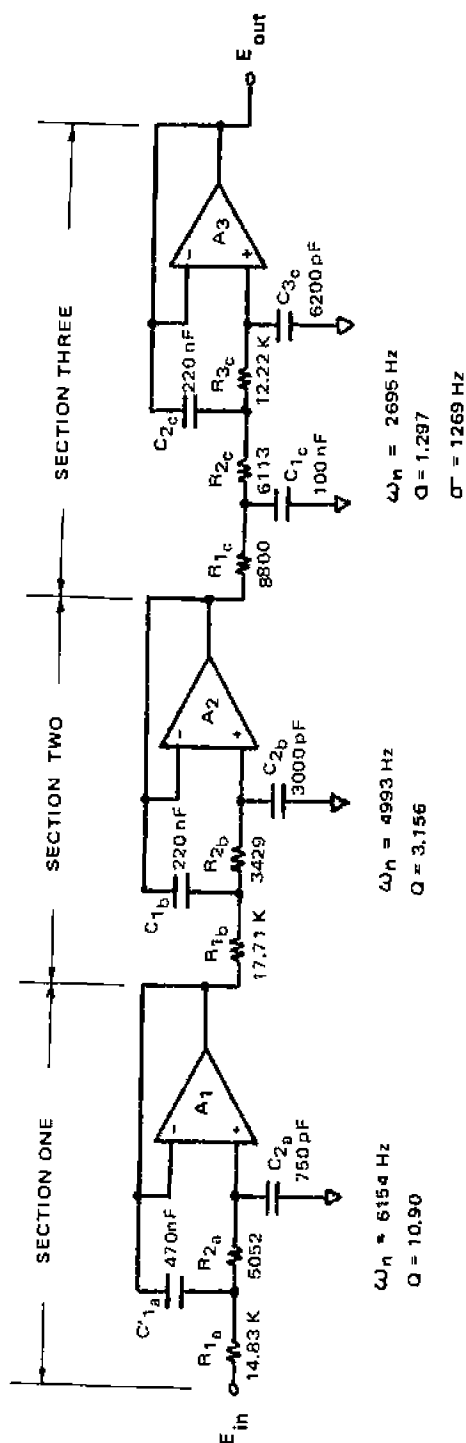


Figure 2-9.5 Overall active filter schematic:

7th order Chebyshev lowpass

1 dB passband ripple

-3 dB at 1000 Hz

-69.4 dB at 2000 Hz

Note:

This ordering of the filter sections will result in the lowest output noise assuming the resistance levels in the resonator sections are low enough so the op-amp voltage noise dominates (see Program 1-6). Because the highest Q resonator is first, it will be prone to overload at frequencies near the resonant peak. For filters operating at higher signal levels where self noise is not a concern, the ordering of the sections should be reversed with the lowest Q section placed first.

Example 2-9.2

An active Butterworth lowpass filter must pass all frequencies between dc and 1000 Hz within 1 dB, and must reject all frequencies higher than 3000 Hz by at least 60 dB. Program 2-1 may be used to determine the minimum filter order. This program calculates a minimum filter order of 6.90, which is rounded to 7, the next highest integer. This filter will be 60.9 dB down at 3000 Hz ($\lambda = 3000/1000 = 3$).

This program (Program 2-9) is used to find the element values for a 7th order, 1000 Hz -1 dB cutoff, Butterworth lowpass active filter. A design resistance level of 10000 ohms will keep the capacitor values centered around $1/(2\pi fR) = 0.016 \mu\text{F}$.

PROGRAM INPUT

```

7. GSE+ n
1. GSEB  $\epsilon_{dB}$ 
10000. GSB C R, design resist level
1000. GSE $\sigma$  f- $\epsilon_{dB}$ 
1.101+03 *** f-3dB (output)

```

PROGRAM OUTPUT

section one

```

6.920+03 ***  $\omega$ 
2.247+00 ***  $Q^n$ 
64.34-09 ***  $C_1$ 
3.215-09 ***  $C_2$ 
68.-03 ENT1  $C'_1$  } alternate values
3000.-12 GSEB  $C'_2$  }
14.26+03 ***  $R_1$ 
7.180+03 ***  $R_2$ 

```

section two

```

6.920+03 ***  $\omega$ 
801.5-02 ***  $Q^n$ 
23.18-09 ***  $C_1$ 
9.010-09 ***  $C_2$ 
24.-09 ENT1  $C'_1$  } alternate values
8200.-12 GSEE  $C'_2$  }
14.61+03 ***  $R_1$ 
7.164+03 ***  $R_2$ 

```

section three

```

6.920+03 ***  $\omega$  } of second order pair
555.6-03 ***  $Q^n$  }
6.920+03 ***  $\sigma$  }
19.32-09 ***  $C_1$  }
22.14-09 ***  $C_2$  }
7.058-09 ***  $C_3$  }
32.-09 ENT1  $C'_1$  } alternate values
22.-09 ENT1  $C'_2$  }
6300.-12 GSEB  $C'_3$  }
9.172+03 ***  $R_1$ 
7.675+03 ***  $R_2$ 
13.63+03 ***  $R_3$ 

```

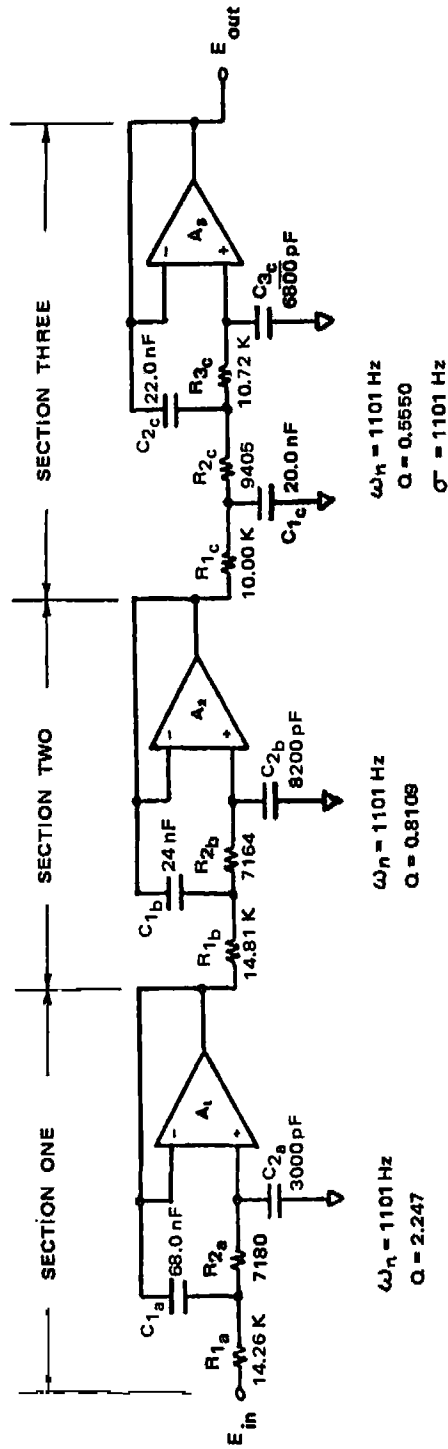


Figure 2-8.6 Overall active filter schematic:
 7th order Butterworth lowpass filter
 -1 dB @ 1000 Hz
 -3 dB @ 1101 Hz
 -60.9 dB @ 2000 Hz

Program Listing I

001 *LBLA BUTTERWORTH; LOAD n	056 ENT↑
002 SF1 indicate Butterworth	057 +
003 EEX setup registers;	058 1/X
004 STOB f-3dB/f-εdB = 1	059 CHS
005 STOD cosh a = 1	060 YX
006 STOE sinh a = 1	061 STOB
007 R↓ recover n	062 GT05 goto data entry flag clear
008 GT08 goto filter order entry subr.	063 *LBLC LOAD OPERATING RESISTANCE
009 *LBLA CHEBYSHEV; LOAD n fεdB	064 ST06 LEVEL
010 STOB fεdB	065 GT05 goto data entry flag clear
011 R↓ recover filter order, n	066 *LBLD LOAD f-3dB & START
012 CF1 indicate Chebyshev	067 F1?
013 GSB8 gosub filter_order_entry_subr	068 GT07 jump, if Butterworth
014 RCLB	069 ST09
015 EEX	070 RCL5
016 1 calculate;	071 ENT↑
017 ÷	072 X²
018 10× $\epsilon = \sqrt{10^{0.1\epsilon_{dB}} - 1}$	073 EEX
019 EEX	074 -
020 -	075 JX
021 JX	076 + for Chebyshev, calculate
022 1/X	077 RCLA
023 ST05	078 1/X $f_{-3dB} = \frac{f_{-3dB}}{\cosh\left[\frac{1}{n} \cosh^{-1}\left(\frac{1}{\epsilon}\right)\right]}$
024 ENT↑	079 YX
025 X²	080 ENT↑
026 EEX calculate and store;	081 1/X
027 +	082 +
028 JX $a = \frac{1}{n} \sinh^{-1}\left(\frac{1}{\epsilon}\right) \rightarrow R2$	083 ÷
029 +	084 ENT↑
030 RCLA	085 +
031 1/X	086 SF3 set data entry flag
032 YX	087 PRTX print f-εdB
033 ST02	088 *LBLJ LOAD f-εdB AND START
034 ENT↑	089 F1?
035 1/X	090 RCLB
036 - calculate and store;	091 F1?
037 2	092 x
038 ÷ sinh a → R _E	093 F1?
039 STOE	094 PRTX
040 RCL2	095 *LBL7
041 ENT↑	096 P;
042 1/X calculate and store;	097 ENT↑
043 +	098 +
044 2 cosh a → R _D	099 x if flag 3, 2πf → R3
045 ÷	100 F3?
046 STOD	101 ST03
047 GT05 go to data entry flag clear	102 EEX
048 *LBLB LOAD -ε _{dB} FOR BUTTERWORTH	103 ST00 setup for next loop
049 EEX if bandedge is not defined	104 SPC
050 1 by -3dB point	105 *LBL1 second order filter loop
051 ÷ calculate and store;	106 SPC
052 10×	107 RCL0
053 EEX $\frac{f_{-3dB}}{f_{-εdB}} = \left[10^{0.1\epsilon_{dB}} - 1\right]^{\frac{1}{2n}} \rightarrow R_B$	108 RCL1
054 -	109 x
055 RCLA	110 EEX

REGISTERS									
0 2k - 1	1 2Q	2 a or ω _n	3 ω _{-3dB}	4 0 ₁	5 1/ε	6 R	7 ω _k	8 σ _k	9 scratch
S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
A filter order, n	B ε _{dB} , 1, or f _{-3dB} /f _{-εdB}	C 0 ₂	D cosh a or 1	E sinh a or 1	F π/(2n)				

Program Listing II

111	→R		167	EEX	R ₁ calculation (continued)
112	RCLD	calculate pole positions:	168	+	
113	x		169	↖X	
114	STO7	$\sigma_k = (\sinh a)(\sin \frac{2k-1}{2n} \pi)$	170	EEX	
115	XZY		171	+	
116	RCLD	$\omega_k = (\cosh a)(\cos \frac{2k-1}{2n} \pi)$	172	RCL1	
117	x		173	÷	
118	STO8		174	RCL2	
119	→P		175	÷	
120	RCL3		176	RCL9	
121	x	calculate ω_{n_k} and Q_k	177	÷	
122	PRTX		178	PRTX	
123	STO2	$\omega_{n_k}^2 = \sigma_k^2 + \omega_k^2$	179	RCL4	
124	XZY		180	x	R ₂ calculation:
125	COS	$Q_k = 1/(2 \cos(\tan^{-1} \frac{\omega_k}{\sigma_k}))$	181	RCL9	
126	1/X		182	x	
127	STO1		183	RCL2	$R_2 = 1/(\omega_n^2 \cdot C_1' \cdot C_2' \cdot R_1)$
128	2		184	XZ	
129	÷		185	x	
130	PRTX		186	1/X	
131	LSTX	increment k by 2	187	PRTX	
132	ST+0		188	*LBL4	
133	F0?	jump if n is even	189	RCL0	test for loop exit
134	GT03		190	RCLA	
135	RCL0		191	XZY?	
136	EEX	odd order filter:	192	GT01	
137	+	test for last section	193	SPC	space paper upon loop exit
138	RCLA	(3rd order section)	194	SPC	
139	XZY?		195	RTN	
140	GT02		196	*LBL2	calculate real 3rd order pole
141	*LBL3	calculate C_1 for 2nd order	197	RCLD	
142	RCL1		198	RCL3	
143	RCL2		199	x	
144	÷	$C_1 = \frac{2Q}{\omega_n \cdot R}$	200	PRTX	
145	RCL6		201	*LBL0	wait loop for 2nd card read
146	÷		202	PSE	
147	PRTX		203	GT00	
148	ENT↑	save C_1 in stack	204	*LBL8	filter order entry subr
149	ENT↑		205	STO4	
150	RCL1	calculate C_2 for 2nd order	206	2	
151	XZ		207	÷	
152	÷	$C_2 = \frac{C_1}{4 \cdot Q^2}$	208	ENT↑	set flag 0 if n is even
153	PRTX		209	INT	
154	RTN		210	CF0	
155	*LBL5	LOAD ALT CAPACITOR VALUES	211	X=Y?	
156	F3?		212	SF0	
157	F3?	if numeric entry, store,	213	Pi	
158	GT04	otherwise jump	214	RCLA	calculate and store:
159	STO9		215	ENT↑	$\pi/(2n) \rightarrow R_1$
160	XZY	calculate R_1 :	216	+	
161	STO4		217	÷	
162	÷		218	STO1	
163	RCL1	$R_1 = \frac{1 + \sqrt{1 - 4Q^2 \cdot C_2' / C_1'}}{2 \cdot Q \cdot \omega_n \cdot C_2'}$	219	*LBL5	data entry flag clear subr
164	XZ		220	CF3	
165	x		221	RTN	
166	CHS				

LABELS					FLAGS	SET STATUS				
A load n ↑ dB	B load R	C $\frac{1}{R} = 3dB$ & go	D $\frac{1}{R} = 4dB$ & go	E load C_1 & C_2	0 n even	FLAGS		TRIG	DISP	
a capacitor entry tog	b	c	d	e	1 set for Buttr	ON OFF				
0 2nd card read loop	1 n & Q calculation	2 odd order output	3 even ord output	4 loop exit test	2	0 <input type="checkbox"/>	DEG	SCI		
5 clr data entry flag	6	7	8	9	3 data entry	1 <input type="checkbox"/>	GRAD	ENG		
						2 <input type="checkbox"/>	RAD			
						3 <input type="checkbox"/>			n 3	

Program Listing I

001	RCL7	ω_k	for 3rd order section	056	ST00		
002	RCL8	σ_k		057	CLX	calculate $f'(C_1)$ as	
003	RCL6	R		058	3		
004	P=S			059	x	$f'(C_1) = 3C_1^2 - 2AC_1 + \frac{3B}{2}$	
005	SF2			060	RCLA		
006	ST06	store denormalization R		061	2		
007	R↓			062	x		
008	ST00	calculate and store;		063	-		
009	→P			064	x		
010	X ²	$\omega_{nk}^2 = \omega_k^2 \sigma_k^2$		065	RCL4		
011	ST01			066	+		
012	2	$2\sigma_k = \frac{\omega_n}{Q}$		067	ST=0	form and store;	
013	ST×0			068	RCL0	$C_{1n+1} = C_{1n} - \frac{f(C_{1n})}{f'(C_{1n})}$	
014	RCL5	calculate and store;		069	ST-3		
015	RCL1			070	RCL3	iterate again if	
016	x	$C = \frac{\tau}{\omega_n^2}$		071	÷		
017	1/X			072	ABS	$\left \frac{f(C_{1n})}{f'(C_{1n})} \right \geq 10^{-8}$	
018	STOC			073	RCL9		
019	ST05			074	X≠Y?		
020	RCL5	calculate and store;		075	GT00		
021	RCL0			076	RCLA	calculate and store;	
022	+	$B = \frac{\tau}{\omega_n Q} + \frac{1}{\omega_n^2}$ as		077	RCL3		
023	x			078	-		
024	ST08	$(\frac{\tau}{\omega_n^2})(\frac{1}{\tau} + \frac{\omega_n}{Q})$		079	3	$C_3 = \frac{A - C_1}{3}$	
025	ST04			080	÷		
026	RCL5	calculate and store;		081	ST04		
027	RCL0			082	RCL3	calculate;	
028	x	$A = \tau + \frac{1}{\omega_n Q}$ as		083	x		
029	RCL1			084	RCLC	$C_2 = \frac{C}{C_1 \cdot C_3}$	
030	+			085	X≠Y		
031	RCLC	$(\frac{\tau}{\omega_n^2})(\omega_n^2 + \frac{\omega_n}{Q})$		086	÷		
032	x			087	RCL4	order C_1 , C_2 , and C_3 in	
033	ST0A			088	X≠Y	the stack	
034	3	use register arithmetic		089	RCL3		
035	ST×4	to form and store;		090	GSB9	restore P S order	
036	ST×5	$3B/2$, and $3C$		091	GSB1	denormalize and print	
037	2			092	GSB1	capacitors	
038	ST÷4			093	*LBL1		
039	ST03	initialize registers for		094	RCL3	capacitor denormalization	
040	EEX	Newton-Raphson iteration		095	÷		
041	CHS			096	RCL6	$C_{den} = C_{nor}/(\omega_{edB} \cdot R)$	
042	8			097	÷		
043	ST09			098	PRTX		
044	*LBL0	Newton-Raphson routine to		099	R↓		
045	RCL3	find the real 3rd order		100	RTN		
046	RCL3	root of $f(C_1) = 0$		101	*LBL5	LOAD ALTERNATE CAPACITOR	
047	RCL3			102	GSB9	VALUES FOR C_1 , C_2 , & C_3	
048	RCLA			103	RCL3		
049	-	calculate $f(C_1)$ as:		104	P=S		
050	x			105	SF2	initialize registers	
051	RCL4	$f(C_1) = C_1^3 - AC_1^2 + \frac{3B}{2}C_1 - 3C$		106	R↓		
052	+			107	ST02	store C_1 , C_2 , & C_3	
053	x			108	R↓		
054	RCL5			109	ST01		
055	-			110	R↓		

REGISTERS									
0	2k-1	1	2	3	4	5	6	7	8
				ω_{-3dB}		$1/\epsilon$	R	ω_k	σ_k
S0	$C_1, \frac{\omega_n}{Q}$	S1	C_2, ω_n^2	S2	C_3	S3	R_1	S4	$R_1, \frac{3B}{2}$
						S5	$R_1, 3C$	S6	R
A	$A = \tau + \frac{1}{\omega_n Q}$	B	$B = \frac{\tau}{\omega_n Q} + \frac{1}{\omega_n^2}$	C	$C = \frac{\tau}{\omega_n^2}$	D	cosh a	E	sinh a
								I	$C/(C_1 \cdot C_2)$

HP-67 suggested program changes. Program space does not allow the addition of a print, R/S toggle and associated output routine. If the HP-67 user would like the program to stop instead of halting for 5 seconds (print command) change the "print" statements to "R/S" at the following line numbers: (program 1); 122, 130, 147, 153, 178, 187, and 200; (program 2); 098, 165, 167, and 169. To resume program execution with the above changes, execute a "R/S" command from the keyboard after each data output point.

PROGRAM 2-10 BUTTERWORTH AND CHEBYSHEV ACTIVE HIGHPASS FILTER DESIGN AND POLE LOCATIONS.

Program Description and Equations Used

This program calculates the normalized pole locations and provides element values for the un-normalized, unity gain Sallen and Key type second and third order highpass active resonator circuit. Higher order filters are formed by cascading second order sections, and one third order section if the filter order is odd. The program uses either the Butterworth (maximally flat) or Chebyshev (equiripple passband) all pole filter descriptions.

The program is designed to allow the use of specified capacitor values such as would result from the actual measurement of a standard value capacitor. The corresponding resistor values are calculated for each section. The nearest 1% standard value precision resistor will generally suffice for the calculated value.

The design process starts by finding the normalized lowpass pole locations for the desired filter type. If the passband cutoff frequency is different from the conventional definition of the bandedge, a scaling of the normalized cutoff frequency is done. The Butterworth amplitude response is 3 dB down at the passband edge, while the Chebyshev amplitude response is ϵ dB down at the passband edge, where ϵ dB is the passband ripple in dB. The scaling factor is K , and the normalized filter cutoff frequency is denoted by ω_n .

The normalized and scaled lowpass pole locations are sequentially found as complex conjugate pairs, and, if the filter order is odd, the real pole location. The lowpass, unity-gain, Sallen and Key, normalized active filter circuit element values may be found in terms of these pole locations. The element values of the highpass normalized active resonator may be found from the normalized lowpass structure. The normalized lowpass structure is transformed to the normalized highpass structure by replacing each lowpass resistor with a capacitor and vice versa.

The normalized highpass element values are the reciprocals of the corresponding converted lowpass element, i.e., a 2 farad capacitor becomes a $\frac{1}{2}$ ohm resistor. This conversion is equivalent to replacing s by $1/s$ in the lowpass transfer function equation. The un-normalized highpass equation is found by replacing s by ω_c/s , where $\omega_c = 2\pi f_c$, and f_c is the highpass cutoff frequency in hertz.

Each complex conjugate pole pair can be expressed in either the cartesian (real and imaginary parts) or the polar (magnitude and angle) co-ordinate system. A variation on the polar system allows the pole pair to be defined in terms of the natural frequency, ω_n , and "Q" or quality factor. The relationships between these co-ordinate systems is shown in Fig. 2-9.1 The Butterworth and Chebyshev pole locations are given in Program 2-2. By putting all the foregoing concepts together, the denormalized highpass element values can be expressed in terms of ω_n and Q with the second order circuit topology as shown in Fig. 2-10.1.

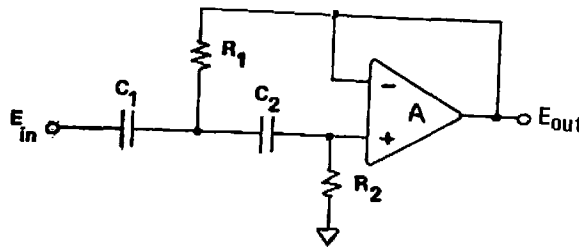


Figure 2-10.1 Highpass Sallen and Key circuit.

$$R_1 = \frac{\omega_n / \omega_c}{Q(C_1 + C_2)} \quad (2-10.1)$$

$$R_2 = \frac{(\omega_n / \omega_c)^2}{R_1 \cdot C_1 \cdot C_2} \quad (2-10.2)$$

The Sallen and Key unity-gain op-amp resonator is chosen over other types because of its low component count and low parameter sensitivities to element value changes (see [19]). High Q realizations are difficult with this resonator type since the resistor value spread is $4Q^2$ when the capacitor values are equal, however, this constraint is not a problem here since the pole Q's are rarely greater than 10.

High pole Q 's occur with higher order filters (n greater than 9 or so). In these cases, the Szentirmai leapfrog topology [48], should be given consideration, or else an elliptic response lower order filter might meet the amplitude response requirements (the phase response will be less linear however).

All operational amplifiers have bandwidth limitations, i.e., the $\mu A-741$ has unity open loop gain at 500 kHz typically. When the operating frequency range of the active filter contains frequencies that approach 1% of the op-amp unity gain crossover frequency (500 kHz for the $\mu A-741$), then the contribution of the operational amplifier compensation pole and lower open loop gain must be considered. Program 1-3 can be used to calculate the pole location shifts. Positive and negative feedback resonators of the Deliyannis type can accommodate the op-amp compensation pole and open loop gain characteristic (see [19]).

If the filter order is odd, then a real pole exists. A third order op-amp active resonator circuit may be used to produce both the real pole and a complex conjugate pair. The lowest Q pole pair is chosen for realization by this circuit to keep the element value spread within bounds, and also to minimize sensitivities. The third order active high-pass topology is shown in Fig. 2-10.2.

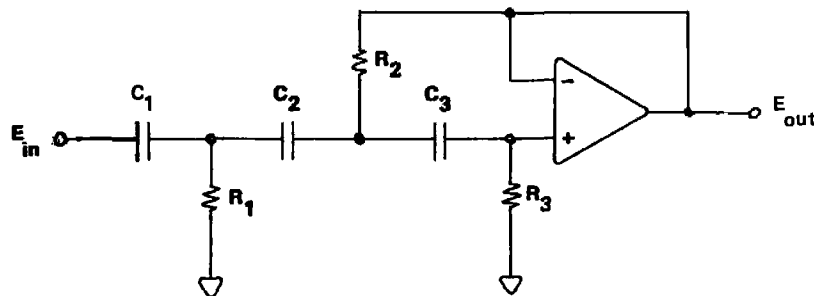


Figure 2-10.2 Third order highpass active filter section.

The transfer function in terms of the R's and C's assuming an ideal operational amplifier is:

$$\frac{E_{out}}{E_{in}} = \frac{s^3 R_1 R_2 R_3 C_1 C_2 C_3}{D(s)} \quad (2-10.3)$$

where

$$D(s) = s^3 R_1 R_2 R_3 C_1 C_2 C_3 + s^2 R_2 \{R_3 C_2 C_3 + R_1 \Sigma CC\} \\ + s \{R_1 (C_1 + C_2) + R_2 (C_2 + C_3)\} + 1$$

and

$$\Sigma CC = C_1 C_2 + C_2 C_3 + C_1 C_3 \quad (2-10.4)$$

The resistor values may be obtained from the capacitor values and the pole locations by the simultaneous solution of three equations in three unknowns. These three equations are generated by equating like powers of s between the desired transfer function as expressed with the pole locations and the above transfer function. The desired transfer function in terms of the complex conjugate pole pair as expressed through ω_n and Q , and the real pole location, $1/\tau$, is:

$$\frac{E_{out}}{E_{in}} = \frac{s^3 \left(\frac{1}{\omega_c \tau} \right) \cdot \left(\frac{\omega_n}{\omega_c} \right)^2}{\left\{ \frac{s}{\omega_c \tau} + 1 \right\} \left\{ s^2 \left(\frac{\omega_n}{\omega_c} \right)^2 + s \left(\frac{1}{Q} \right) \left(\frac{\omega_n}{\omega_c} \right) + 1 \right\}} \quad (2-10.5)$$

or, in descending powers of s :

$$\frac{E_{out}}{E_{in}} = \frac{s^3 \left(\frac{\omega_n}{\omega_c} \right)^2 \cdot \left(\frac{1}{\omega_c \tau} \right)}{s^3 \left(\frac{\omega_n}{\omega_c} \right)^2 \left(\frac{1}{\omega_c \tau} \right) + s^2 \left(\frac{\omega_n}{\omega_c} \right)^2 \left(1 + \frac{1}{\omega_n Q \tau} \right) + s \left(\frac{\omega_n}{\omega_c} \right) \left(\frac{1}{Q} + \frac{1}{\omega_n \tau} \right) + 1} \quad (2-10.6)$$

The resulting three equations in three unknowns are:

$$R_1 R_2 R_3 C_1 C_2 C_3 = \left(\frac{\omega_n}{\omega_c} \right)^2 \left(\frac{1}{\omega_c \tau} \right) \quad (2-10.7)$$

$$R_2 (R_3 C_2 C_3 + R_1 \Sigma CC) = \left(\frac{\omega_n}{\omega_c} \right)^2 \left(1 + \frac{1}{\omega_n Q \tau} \right) \quad (2-10.8)$$

$$R_1 (C_1 + C_2) + R_2 (C_2 + C_3) = \left(\frac{\omega_n}{\omega_c} \right) \left(\frac{1}{Q} + \frac{1}{\omega_n \tau} \right) \quad (2-10.9)$$

After algebraic manipulation, a cubic equation in R_1 alone is obtained:

$$R_1^3 K_3 + R_1^2 K_2 - R_1 K_1 + K_0 = 0 \quad (2-10.10)$$

where the constants K_3 , K_2 , K_1 , and K_0 are defined by:

$$K_3 = - (C_1 + C_2) (C_1 \Sigma CC) \quad (2-10.11)$$

$$K_2 = \left(\frac{1}{Q} + \frac{1}{\omega_n \tau} \right) (C_1 \Sigma CC) \left(\frac{\omega_n}{\omega_c} \right) \quad (2-10.12)$$

$$K_1 = \left(1 + \frac{1}{\omega_n Q \tau} \right) (C_1 (C_2 + C_3)) \left(\frac{\omega_n}{\omega_c} \right)^2 \quad (2-10.13)$$

$$K_0 = (C_2 + C_3) \left(\frac{1}{\omega_c \tau} \right) \left(\frac{\omega_n}{\omega_c} \right)^2 \quad (2-10.14)$$

The program uses a Newton-Raphson iterative solution to find the real root of Eq. (2-10.10) for R_1 (there will be at least one real root). The details of the Newton-Raphson technique are shown in Program 1-5.

Once R_1 has been obtained, the values for R_2 and R_3 are obtained using the following equations:

$$R_2 = \left(\frac{1}{C_2 + C_3} \right) \left\{ \frac{\omega_n}{\omega_c} \left(\frac{1}{Q} + \frac{1}{\omega_n \tau} \right) - R_1 (C_1 + C_2) \right\} \quad (2-10.15)$$


$$R_3 = \left(\frac{\omega_n}{\omega_c} \right)^2 \left(\frac{1}{\omega_c \tau} \right) \left(\frac{1}{R_1 R_2 C_1 C_2 C_3} \right) \quad (2-10.16)$$

User Instructions

BUTTERWORTH AND CHEBYSHEV ACTIVE HIGHPASS FILTERS				
C: $n \leq \epsilon$ dB			load $f - \epsilon$ dB & start	
B: n	B: ϵ dB	R	load $f - 3$ dB & start	load C_1, C_2

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Read both sides of program card one			
2	If Chebyshev response is desired: a) Load filter order b) Load passband ripple in dB c) go to step 4	n ϵ dB	ENT ↑ f A	
3	If Butterworth response is desired: Load filter order If the passband edge is defined at other than the -3 dB point, enter the bandedge attenuation in dB (attenuation is expressed as a positive number)	n ϵ dB	A B	
4	Load operating resistance level *** The calculated resistor values will usually be within a decade of this value.	R	0	
5	If the passband edge is defined by the -3 dB amplitude response point, enter $f - 3$ dB *** *The Chebyshev bandedge is usually defined by the $-\epsilon$ dB point since the passband response oscillates within a band ϵ dB wide. If a Chebyshev response has been selected, the frequency where the amplitude response exits the ϵ dB ripple band will be printed. go to step 7 (read step 6 commentary)	$f - 3$ dB	D	$f - \epsilon$ dB* See step 6 continuation on next page for rest of output.
6	If the passband edge is defined by the $-\epsilon$ dB point, enter $f - \epsilon$ dB *** **If Butterworth response has been selected, the frequency where the response is 3 dB down will be printed.	$f - \epsilon$ dB	f D	$f - 3$ dB**

User Instructions

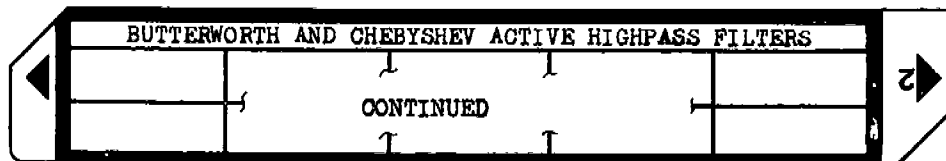

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
6	<p>The design capacitance value is outputted.*** If this value is unacceptable from a circuit or practicality point of view, alter the design resistance level accordingly using key "C", then recalculate the design capacitance level using key "D". The design cutoff frequency need not be re-entered even though the original frequency entry was via keys "f", "D".</p> <p>When an acceptable design capacitance level has been found, continue program output by using "R/S".</p>	new R	<div>C</div> <div>D</div> <div>R/S</div>	C_{design} new C_{des} ω_{n1} Q_1 stop
7	<p>Enter capacitor values to be used in this second order filter section***</p> <p>Keep entering capacitor values for succeeding sections until all second order sections have been defined.</p> <p>If an odd order filter is being designed, the last printout will be a set of three numbers, and the display will flash to indicate that the loading of the second card is required. It is not necessary to stop the program, just insert the second card into the card reader and read both sides.</p> <p>After the second card reading is complete, load the three capacitor values to be used with this third order filter section using key "E".</p> <p>*** The unit of resistance is ohms, capacitance is farads, and frequency is hertz.</p>	C_1 C_2 C_{12} C_{22} : : : C_{1n} C_{2n}	<div>ENT ↑</div> <div>E</div> <div>ENT ↑</div> <div>E</div>	R_1 R_2 space n_2 Q_2 stop R_{12} : : : : R_{2n} odd order filter: last sect ω_n Q $1/\tau$ flashing display R_1 R_2 R_3

Example 2-10.1

A fifth order, $\frac{1}{2}$ dB passband ripple Chebyshev active highpass filter is to have 3 dB or less attenuation at 10 Hz. A National Semiconductor type LF-156 bi-fet operational amplifier is chosen as the active element in the filter.

Design an active filter to meet these specifications and choose the operating resistance level to achieve the lowest capacitance values in the filter without affecting the dc drift characteristics of the operational amplifier by more than 10%. The operating temperature range is -25°C to $+85^{\circ}\text{C}$.

From the LF-156 data sheet, the maximum input bias current occurs at the highest operating temperature, $+85^{\circ}\text{C}$, and is approximately 1 nA. The typical input offset voltage is 3 millivolts. The resistance level that will generate 0.3 millivolts with 1 nA flowing is:

$$R = (3 \times 10^{-4} \text{ V}) / (1 \times 10^{-9} \text{ A}) = 300 \text{ k}\Omega$$

The filter is then designed with this value in mind as the largest resistance value which has an effect on the dc output of the last filter stage. Being a highpass filter, each stage of the filter blocks the dc voltage present from the preceding stage.


The filter design will be done twice, once with 300 k Ω as the design resistance level to determine the value of R_2 in the last (third order) section. The operating resistance level is then scaled to cause the highest resistance value (R_2) to be 300 k Ω . The HP-97 printout for these operations is shown on the next page.

In the second run of the program, the design capacitance level is 0.1749 μF . The nearest larger standard capacitor value is 0.22 μF . The filter will require five capacitors, therefore, five 0.22 μF mylar capacitors were drawn from stock, and their capacities measured. The measured values were: .2236 μF , .2014 μF , .1965 μF , .2173 μF , and 0.2542 μF . The filter resistances are designed around these capacitor values.

Example 2-10.1 printout

FIRST PROGRAM RUN			SECOND PROGRAM RUN		
LOAD FIRST PROGRAM CARD			LOAD FIRST PROGRAM CARD		
5. ENT↑	load filter order		5. ENT↑		
.5 GSB _a	load passband ripple		.5 GSB _a		
300000. GSB _C	load design resist		90.99+03 GSB _C	load new design resistance level	
10. GSB _D	load -3dB frequency		10. GSB _D		
10.59+00 ***	-1dB frequency (o/p)		10.59+00 ***		
53.05-05 ***	design capacitance level (output)		174.9-09 ***	new design capacitor value (output)	
R/S	continue execution		R/S		
960.8-33 ***	ω_n first section		960.8-03 ***	ω_n	
4.545+00 ***	Q		4.545+00 ***	Q	
53.05-09 ENT↑	enter first section design capacitance		.2236-06 ENT↑	O ₁ first section selected caps	
GSBE			.2014-06 GSB _E	O ₂	
31.71+03 ***	R ₁ first section		7.916+03 ***	R ₁ first section	
2.620+06 ***	R ₂ resistor values		655.9+07 ***	R ₂ resistor values	
651.9-03 ***	ω_n		651.9-03 ***	ω_n	
1.178+00 ***	Q second section		1.178+00 ***	Q second section	
342.1-03 ***	1/τ		342.1-03 ***	1/τ	
	LOAD SECOND CARD			LOAD SECOND CARD	
53.05-09 ENT↑			.1965-06 ENT↑	O ₁	} second section input (third order filter)
ENT↑	enter design cap		.2173-06 ENT↑	O ₂	
GSBE			.2542-06 GSB _E	O ₃	
90.47+07 ***	R ₁	} second section resistor values	24.17+03 ***	R ₁	} second section resistor values
43.86-03 ***	R ₂		9.014+03 ***	R ₂	
989.1+03 ***	R ₃		247.8+03 ***	R ₃	
989.1+03 ENT↑					
300.+03 =	scale design resistance level				
1 *					
303.3-03 ***	to make R ₃ become				
300000.	300 kΩ				
90.99+03 ***					

FINAL SCHEMATIC

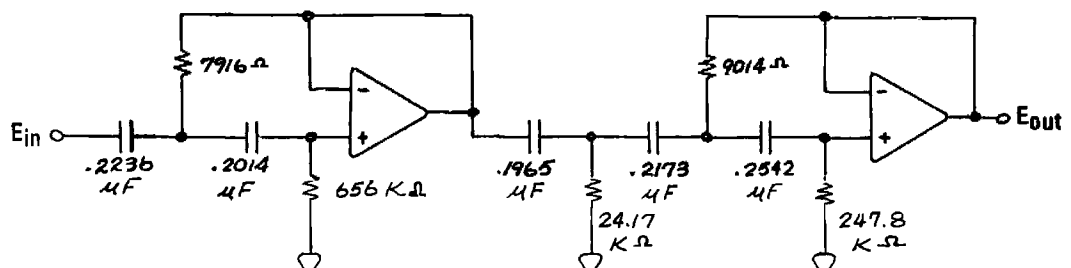

Program Listing I

001	*LBLA	BUTTERWORTH: LOAD n	056	Y*
002	SF1	indicate Butterworth	057	ENT↑
003	EEX	setup registers:	058	1/X
004	STOB	f-3dB/f-εdB = 1	059	+
005	STOD	cosh a = 1	060	÷
006	STOE	sinh a = 1	061	STOB
007	GSE5		062	GT06
008	GT06		063	*LBLB
009	*LBLA	CHEBYSHEV: LOAD n, εdB	064	EEX
010	CF1	indicate Chebyshev	065	1
011	STOB	store εdB	066	÷
012	GSE5	gosub input routine	067	10*
013	RCLB	calculate:	068	EEX
014	EEX		069	-
015	1	$\epsilon = (10^{0.1\epsilon\text{dB}} - 1)^{\frac{1}{2}}$	070	RCLA
016	÷		071	1/X
017	10*		072	Y*
018	EEX		073	JX
019	-		074	1/X
020	JX		075	STOB
021	1/X		076	GT06
022	STO5	store 1/ε → R5	077	*LBLC
023	ENT↑	calculate and store:	078	STO6
024	X²		079	GT06
025	EEX		080	*LBLD
026	+		081	STOC
027	JX	$a = \frac{1}{n} \sinh^{-1}(\frac{1}{\epsilon}) \rightarrow R2$	082	F1?
028	+		083	GT00
029	RCLA		084	RCLB
030	1/X		085	STO3
031	Y*		086	÷
032	STO2		087	F3?
033	ENT↑	calculate and store:	088	GSE4
034	1/X		089	RCLC
035	-	sinh a → RE	090	*LBLD
036	2		091	STOC
037	÷		092	RCLB
038	STOE		093	F1?
039	RCL2	calculate and store:	094	STO3
040	ENT↑		095	÷
041	1/X		096	F1?
042	+	cosh a → RD	097	PRTX
043	2		098	*LBL0
044	÷		099	SPC
045	STOD		100	CF2
046	LSTX	calculate and store:	101	RCLC
047	RCL5		102	ENT↑
048	ENT↑		103	+
049	X²		104	Pi
050	EEX	$\frac{f-\epsilon\text{dB}}{f-3\text{dB}} = \cosh(\frac{1}{n} \cosh^{-1}(\frac{1}{\epsilon}))$	105	x
051	-		106	F3?
052	JX		107	STO5
053	+		108	RCL5
054	RCLA		109	RCL6
055	1/X		110	x
056	Y*			
057	ENT↑			
058	1/X			
059	+			
060	÷			
061	STOB			
062	GT06			
063	*LBLB	LOAD εdB for Butterworth		
064	EEX	calculate and store:		
065	1			
066	÷			
067	10*			
068	EEX			
069	-	$\frac{f-3\text{dB}}{f-\epsilon\text{dB}} = \left[10^{0.1\epsilon\text{dB}} - 1\right]^{\frac{1}{2n}}$		
070	RCLA			
071	1/X			
072	Y*			
073	JX			
074	1/X			
075	STOB			
076	GT06			
077	*LBLC	LOAD OPERATING RESISTANCE		
078	STO6	LEVEL		
079	GT06			
080	*LBLD	LOAD f-3dB and START		
081	STOC	temporarily store f-3dB		
082	F1?	jump if Butterworth		
083	GT00			
084	RCLB	recall Cheb denorm ratio		
085	STO3			
086	÷	form -εdB frequency		
087	F3?	print f-εdB if data entered		
088	GSE4			
089	RCLC	recall f-3dB		
090	*LBLD	LOAD f-εdB and START		
091	STOC	temporarily store frequency		
092	RCLB	recall Buttr denorm ratio		
093	F1?	if Buttr, store ratio		
094	STO3			
095	÷			
096	F1?	if Butterworth, calculate		
097	PRTX	and print f-3dB		
098	*LBL0			
099	SPC			
100	CF2			
101	RCLC			
102	ENT↑	if flag 3, 2πf _c → R5		
103	+			
104	Pi			
105	x			
106	F3?			
107	STO5			
108	RCL5			
109	RCL6	calculate and print		
110	x	nominal capacitor value		

REGISTERS

0	2k-1	1	Q	2	a or ω _n	3	K	4	0 ₁	5	ω _c , 1/ε	6	R	7	ω _r /ω _c	8		9	C ₂
S0		S1		S2		S3		S4		S5		S6		S7		S8		S9	
A filter order, n		B ε _{dB} , 1, f-3dB, f-εdB		C cutoff frequency		D cosh a or 1		E sinh a or 1		F $\frac{\pi}{2n}$									

Program Listing II

111	1/X	print design capacitance	166	RCL4	calculate and print R ₂
112	PRTX		167	X	
113	SPC	stop program execution and	168	RCL9	
114	R/S	await operator decision	169	X	$R_2 = \frac{(\omega_n/\omega_c)^2}{R_1 \cdot C_1 \cdot C_2}$
115	EEX	setup for next loop	170	RCL7	
116	STO0		171	X ²	
117	*LBL1	second order filter loop	172	X ² Y	
118	SPC		173	÷	
119	RCL0	calculate normalized	174	PRTX	
120	RCL1	pole locations:	175	RCL0	
121	X		176	RCLA	test for loop exit
122	EEX		177	X>Y?	
123	→R	$\sigma_k = (\sinh a)(\sin((2k-1)\frac{\pi}{2n}))$	178	STO1	
124	RCLD		179	SPC	loop exit
125	X	$\omega_k = (\cosh a)(\cos((2k-1)\frac{\pi}{2n}))$	180	SPC	
126	X ² Y		181	RTN	
127	RCL5		182	*LBL2	3rd order filter section
128	X		183	RCL5	calculate and print
129	→P	calculate ω_{n_k} and Q_k , scale	184	RCL3	real 3rd order pole location
130	RCL3	ω_{n_k} for proper normalized	185	X	
131	X	bandedge	186	PRTX	
132	PRTX		187	SPC	
133	STO2	$\omega_{n_k} = [\omega_k^2 + \sigma_k^2]^{\frac{1}{2}} \cdot (K)$	188	*LBL3	wait loop for second
134	X ² Y		189	SF2	card read
135	COS		190	PSE	
136	ENT↑	$Q_k = \frac{1}{2 \cos(\tan^{-1} \frac{\omega_k}{\sigma_k})}$	191	GT03	
137	+		192	*LBL4	print and set flag 3
138	1/X		193	PRTX	
139	STO1		194	SF3	
140	PRTX		195	RTN	
141	2	increment 2k by 2	196	*LBL5	entry subroutine
142	ST+0		197	R↓	recover and store n
143	F0?	if even order filter, rtn	198	STOA	
144	RTN	and await capacitor values	199	2	
145	RCL0	odd order filter:	200	÷	set flag 0 if n is even
146	RCLA	jump if last section	201	FRC	
147	X ² Y?		202	CF0	
148	GT02		203	X=0?	
149	RTN	await capacitor values	204	SF0	
150	*LBL5	LOAD CAPACITOR VALUES	205	P↑	
151	F2?	reject input if 3rd order	206	RCLA	calculate and store:
152	GT03	section has been outputted	207	ENT↑	
153	STO9	store C ₂	208	+	$\frac{\pi}{2n} \rightarrow RI$
154	X ² Y		209	÷	
155	STO4	store C ₁	210	STO1	
156	+	calculate and print R ₁	211	EEX	
157	RCL1		212	STO3	ω_n initialization
158	X	$R_1 = \frac{\omega_n/\omega_c}{Q(C_1 + C_2)}$	213	RTN	
159	RCL2		214	*LBL6	exit routine,
160	RCL5		215	SPC	clear flag 3 and space
161	÷		216	CF3	
162	STO7		217	RTN	
163	X ² Y				
164	÷				
165	PRTX				

LABELS				FLAGS	SET STATUS		
A Buttr load n	B Buttr load n dB	C LOAD R	D LOAD R-3dB & START	0 n even	FLAGS		DISP
a Cheb load n dB	b	c	d LOAD R-3dB & START	1 Buttr	ON OFF	TRIG	
0 2nf calc	1 2nd order filter loop	2 3rd order filter lp	3	4 print & set flag 3	2 go to wait loop	DEG	FIX
5 entry subroutine	6 exit subroutine	7	8	9	3 data in	GRAD	SCI
						RAD	ENG
							n_3

NOTE TRIG MODE

Program Listing I

001	R/S	cancel pause after card read	044	x	
002	*LBLE	LOAD 01+02+03 and START	045	RCL4	
003	SPC		046	+	form $C_1(\frac{1}{\tau Q} + \omega_n)$
004	GSEB9	test for PzS	047	RCL1	
005	PzS	execute and signal PzS	048	x	
006	SF2		049	RCL2	
007	ST03	store 03	050	RCL3	form and store 02 + 03
008	R↓	store 02	051	+	
009	ST02		052	ST0A	
010	R↓	store 01	053	x	
011	ST01		054	RCL4	form and store:
012	RCL2	calculate and store:	055	x	
013	x		056	RCL1	$K_1 = \frac{\omega_n}{\omega_c^2}(\frac{1}{\tau Q} + \omega_n)C_1(C_2+03)$
014	RCL2		057	x²	
015	RCL3	$01 \cdot \Sigma 00 \rightarrow R7$	058	÷	
016	x		059	ST0B	
017	+		060	RCL4	
018	RCL3		061	RCL1	
019	RCL1		062	÷	form and store:
020	x		063	x²	
021	+		064	RCL1	
022	RCL1		065	÷	$K_0 = (\frac{\omega_n^2}{\tau})(02 + 03)(\frac{1}{\omega_c^3})$
023	x		066	RCL5	
024	ST07		067	x	
025	GSEB9	PzS and reset flag 2	068	RCLA	
026	RCL5	obtain and store ω_0	069	x	
027	ST01		070	ST0A	
028	RCL5		071	RCL5	
029	RCL3	calculate $1/\tau$	072	RCL4	
030	x		073	RCL6	
031	RCL1	recall: Q	074	x	form and store:
032	RCL2	ω_n	075	+	
033	RCL6	R	076	RCL7	
034	PzS	execute and signal PzS	077	x	$K_2 = (\frac{1}{\tau} + \frac{\omega_n}{Q})(01 \Sigma 00) \frac{1}{\omega_c}$
035	SF2		078	RCL1	
036	ST00	store R	079	÷	
037	R↓	store ω_n	080	ST0C	
038	ST04		081	RCL1	
039	R↓		082	RCL2	form and store:
040	1/X	form and store $1/Q$	083	+	
041	ST06		084	RCL7	
042	x²Y		085	x	
043	ST05	store $1/\tau$	086	CHS	$K_3 = -(01 + 02)(01 \Sigma 00)$
			087	ST0D	
			088	RCL0	
			089	EEX	form and store $10^{-8} \cdot R$
			090	8	for iteration loop
			091	÷	exit test
			092	ST09	

REGISTERS									
0	1	2	3	4	5	6	7	8	9
S0 R1	S1 01	S2 02	S3 03	S4 ω_n	S5 $1/\tau$	S6 $1/Q$	S7 $01 \cdot \Sigma 00$	S8 f/f'	S9 $10^{-8} \cdot R$
A K_0	B $-K_1$	C K_2	D K_3	E $\sinh a$ or 1	F ω_c				

Program Listing II

<pre> 093 *LBL0 Newton-Raphson loop for R1 094 RCL0 095 RCL0 096 RCL0 097 RCLD form and store: 098 x 099 RCLC f(R1) = K3R1^3 + K2R1^2 + K1R1 + K0 100 + 101 x 102 RCLB 103 - 104 x 105 RCL0 106 + 107 ST08 108 CLX 109 + 110 + form: 111 + 112 RCLD f'(R1) = 3K3R1^2 + 2K2R1 + K1 113 x 114 RCLC 115 ENT↑ 116 + 117 + 118 x 119 RCLB 120 - 121 ST08 form -ΔR1 = f(R1)/f'(R1) 122 RCLB form R1n+1 = R1n + ΔR1 123 ST-0 124 ABS 125 RCL9 iterate again if 126 X<Y? ΔR1 ≥ 10^-6 · R1 127 GT00 </pre>					<pre> 128 RCL0 129 PRTX recall and print R1 130 RCL5 131 RCL4 132 RCL6 calculate and print R2 133 x 134 + 135 RCL1 136 ÷ 137 RCL1 138 RCL2 139 + 140 RCL0 141 x 142 - 143 RCL2 144 RCL3 145 + 146 ÷ 147 PRTX 148 RCL0 149 x 150 RCL1 151 x 152 RCL2 153 x 154 RCL3 155 x 156 1/X 157 RCL4 158 RCL1 159 ÷ 160 X^2 161 x 162 RCL1 163 ÷ 164 RCL5 165 x 166 PRTX 167 SPC 168 *LBL9 169 F2? 170 P≠S if flag 2, execute P≠S 171 RTN </pre>				
					$R_2 = \frac{\frac{1}{\omega_c} \left(\frac{1}{\tau} + \frac{\omega_0}{Q} \right) - R_1 (C_1 + C_2)}{C_2 + C_3}$				
					$R_3 = \left(\frac{1}{\omega_c^2} \right) \frac{\omega_n^2 / \tau}{R_1 R_2 C_1 C_2 C_3}$				
LABELS					FLAGS	SET STATUS			
A	B	C	D	E load capacitors	0	FLAGS		TRIG	DISP
a	b	c	d	e	1	ON OFF			
0 Newton-Raphson	1	2	3	4	2 P≠S	0		DEG	FIX
5	6	7	8	9 P≠S	3	1		GRAD	SCI
						2	■	RAD	ENG ■
						3			n_3

**PROGRAM 2-11 DELIYANNIS POSITIVE AND NEGATIVE FEEDBACK ACTIVE
RESONATOR DESIGN (USED FOR ACTIVE BANDPASS FILTERS).**

Program Description and Equations Used

Active filter resonators are constrained by component value ranges (10 ohms to 10 megohms, 100 pF to 10 μ F), operational amplifier gain-bandwidth limitations, and overall circuit sensitivities. The Deliyannis resonator circuit allows high Q realizations and also compensates for the finite gain and bandwidth of the operational amplifier [20].

This resonator synthesizes a second order pole pair of given ω_n and Q. The natural frequency, ω_n , and the quality factor, Q, are provided as outputs from the active Butterworth and Chebyshev filter programs contained in this section.

This resonator type has the ability to synthesize a resonator with infinite Q. The infinite Q resonator is used in the interior stages of the Szentirmai leapfrog filter topology [48]. The leapfrog active filter is a direct simulation of a passive LC filter, and generally has the same low sensitivity characteristics of the LC topology. When narrow-band active filters are required, the leapfrog topology will be one of the viable candidates for filter realization (also see the GIC realization in Program 2-6).

The circuit for the Deliyannis second order bandpass circuit is shown in Fig. 2-11.1.

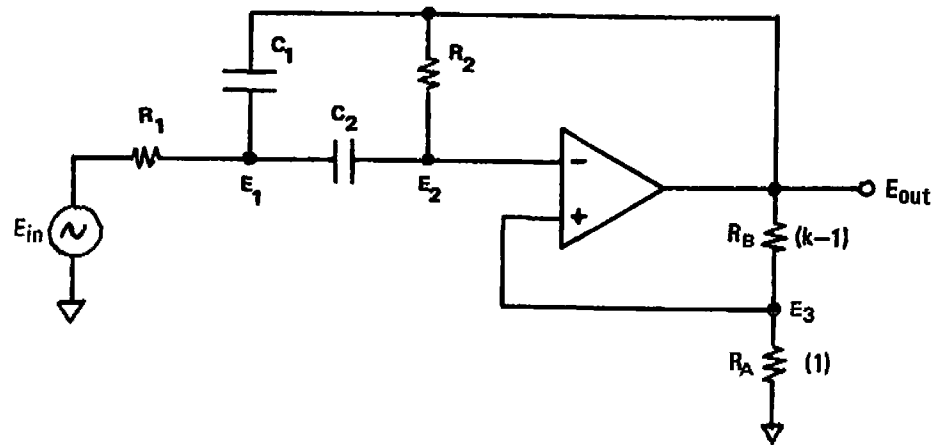


Figure 2-11.1 Deliyannis bandpass resonator circuit.

The transmission function is obtained using nodal analysis. In matrix form, the nodal equations are:

$$E_{out} = A(s)[E_3 - E_2], \text{ (op-amp transmission fcn)} \quad (2-11.1)$$

$$\begin{bmatrix} \left\{ \frac{1}{R_1} + s(C_1 + C_2) \right\} & \{ -sC_2 \} \\ \{ -sC_2 \} & \left\{ \frac{1}{R_2} + sC_2 \right\} \end{bmatrix} \cdot \begin{bmatrix} E_1 \\ E_2 \end{bmatrix} = \begin{bmatrix} \frac{1}{R_1} & sC_1 \\ 0 & \frac{1}{R_2} \end{bmatrix} \cdot \begin{bmatrix} E_{in} \\ E_{out} \end{bmatrix} \quad (2-11.2)$$

where

$$E_3 = E_{out}/k \quad (2-11.3)$$

Solving for E_2 from Eqs. (2-11.1) and (2-11.3):

$$E_2 = E_{out} \left[\frac{1}{k} - \frac{1}{A(s)} \right] \quad (2-11.4)$$

The transmission function is first obtained for the general case using $A(s)$, then more specifically using $A(s) = A_0/(\tau s)$. The passive sensitivities may be obtained from the general solution, and the active sensitivities obtained from the specific solution, $A(s) = A_0/(\tau s)$.

The matrix equation is rewritten to bring $1/k - 1/A(s)$ inside the coefficient matrix, and to bring all dependent variables to the right

hand side of the equation:

$$\begin{bmatrix} \left\{ \frac{1}{R_1} + s(C_1 + C_2) \right\} & \left\{ -s \left[C_1 - C_2 \left(\frac{1}{k} - \frac{1}{A(s)} \right) \right] \right\} \\ \left\{ -sC \right\} & \left\{ \left(\frac{1}{R_2} \right) \left(\frac{1}{k} - \frac{1}{A(s)} - 1 \right) + sC_2 \left(\frac{1}{k} - \frac{1}{A(s)} \right) \right\} \end{bmatrix} \cdot \begin{bmatrix} E_1 \\ E_{out} \end{bmatrix} = \begin{bmatrix} \frac{1}{R_1} \\ 0 \end{bmatrix} \cdot E_{in} \quad (2-11.5)$$

Cramer's rule is used to find the expression for E_{out}/E_{in} , the filter transmission function.

$$\frac{E_{out}}{E_{in}} = \frac{-\frac{s}{R_1 C_1 \left(1 + \frac{1}{A(s)} - \frac{1}{k} \right)}}{s^2 + s \left\{ \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} + \frac{1}{R_1 C_1} \cdot \frac{\frac{1}{A(s)} - \frac{1}{k}}{1 + \frac{1}{A(s)} - \frac{1}{k}} \right\} + \frac{1}{R_1 R_2 C_1 C_2}} \quad (2-11.6)$$

The passive sensitivities may be evaluated assuming the op-amp to be ideal, i.e., the open loop gain is allowed to approach infinity. In this situation, the transmission function becomes:

$$\frac{E_{out}}{E_{in}} = \frac{-\frac{ks}{R_1 C_1 (k-1)}}{s^2 + s \left\{ \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} - \frac{1}{(k-1) R_1 C_1} \right\} + \frac{1}{R_1 R_2 C_1 C_2}} \quad (2-11.7)$$

The coefficients of the denominator of this equation may be compared with the like coefficients in the standard second order form to derive expressions for ω_n and Q . The standard second order form of the transmission function is:

$$\frac{E_{out}}{E_{in}} = \frac{ks}{s^2 + \frac{\omega_n}{Q} s + \omega_n^2} \quad (2-11.8)$$

The following expressions for ω_n , Q , and K are obtained:

$$K = - \frac{k}{R_1 C_1 (k-1)} \quad (2-11.9)$$

$$\omega_n = (R_1 R_2 C_1 C_2)^{-\frac{1}{2}} \quad (2-11.10)$$

$$Q = \frac{\sqrt{\frac{R_2}{R_1}}}{\sqrt{\frac{C_2}{C_1}} + \sqrt{\frac{C_1}{C_2}} - \frac{1}{k-1} - \frac{R_2}{R_1} \cdot \sqrt{\frac{C_2}{C_1}}} \quad (2-11.11)$$

Let $\mu = R_2/R_1$, and $\delta = C_2/C_1$, then:

$$Q = \frac{\sqrt{\mu\delta}}{\delta + 1 - \mu\delta/(k-1)} \quad (2-11.12)$$

The denominator of Eq. (2-11.12) can be made arbitrarily small by proper choice of μ . The denominator can be made to vanish completely causing Q to become infinite, thus generating the infinite Q resonator required for the interior stages of the leapfrog filter topology.

Sensitivities are a way of expressing how much a given parameter, say Q , is affected by a change in one of the circuit elements. The general convention is to express sensitivities as a demensionless number formed from the ratio of individual percentage changes:

$$S_R^Q = \lim_{\Delta R \rightarrow 0} \frac{\Delta Q/Q}{\Delta R/R} = \frac{R}{Q} \cdot \frac{\partial Q}{\partial R} \quad (2-11.13)$$

Applying this definition to the expressions for ω_n , Q , and K , the following passive sensitivities result:

$$S_{R_1, R_2, C_1, C_2}^{\omega_n} = -\frac{1}{2} \quad (2-11.14)$$

$$S_{R_1}^Q = -S_{R_2}^Q = -\frac{1}{2} - Q \frac{\sqrt{\mu\delta}}{k-1} \quad (2-11.15)$$

$$S_{C_1}^Q = -S_{C_2}^Q = -\frac{1}{2} + Q\sqrt{\mu\delta} \left(\frac{1}{\mu} - \frac{1}{k-1} \right) \quad (2-11.16)$$

$$S_{R_B}^Q = -S_{R_A}^Q = Q \frac{\sqrt{\mu\delta}}{k-1} \quad (2-11.17)$$

$$s_{R_1}^K, C_2 = -1 \quad (2-11.18)$$

$$s_{R_A}^K = -s_{R_B}^K = 1/k \quad (2-11.19)$$

The break frequency of the open loop transmission function of most operational amplifiers is around 10 Hz, and the gain-bandwidth product (GBP) is about 10^6 Hz thus, the finite gain characteristics of the op-amp begin to affect the active filter response when kilohertz frequencies are involved. In this frequency range, the operational amplifier transmission function, $A(s) = A_0/(1 + \tau s)$, may be approximated by $A(s) = A_0/\tau s$. With this approximation, the active filter transmission function becomes:

$$\frac{E_{out}}{E_{in}} = \frac{-\frac{s}{(R_1 C_1)(1 + \tau s/A_0 - 1/k)}}{s^2 + s \left\{ \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} + \frac{1}{R_1 C_1} \cdot \frac{\tau s/A_0 - 1/k}{1 + \tau s/A_0 - 1/k} \right\} + \frac{1}{R_1 R_2 C_1 C_2}} \quad (2-11.20)$$

This expression is expanded, and like powers of s collected to form the final expression for the active filter transmission function:

$$\frac{E_{out}}{E_{in}} = \frac{s \frac{-k}{R_1 C_1}}{D(s)} \quad (2-11.21)$$

where

$$D(s) = s^3 \frac{k\tau}{A_0} + s^2 \left\{ k-1 + \frac{k\tau}{A_0} \left(\frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} + \frac{1}{R_1 C_1} \right) \right\} + s \left\{ (k-1) \left(\frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} \right) - \frac{1}{R_1 C_1} + \frac{\tau k}{A_0 R_1 R_2 C_1 C_2} \right\} + \frac{k-1}{R_1 R_2 C_1 C_2}$$

The denominator is factored into a single pole and a complex conjugate pair:

$$\frac{E_{out}}{E_{in}} = \frac{H \cdot \frac{s}{\omega_n Q}}{\left(\frac{s}{\sigma} + 1 \right) \left(\frac{s^2}{\omega_n^2} + \frac{s}{\omega_n Q} + 1 \right)} \quad (2-11.22)$$

The natural frequency, ω_n , and the quality factor, Q , are derived by equating like powers of s between Eqs. (2-11.21) and (2-11.22):

$$\omega_n = \frac{1}{R_1 R_2 C_1 C_2} \cdot \sqrt{1 - \frac{\tau k^2}{A_o(k-1) R_1 C_1}} \quad (2-11.23)$$

$$BW = \frac{\omega_n}{Q} = \left\{ \frac{1}{R_2 C_1} + \frac{1^*}{R_2 C_2} + \frac{1}{R_1 C_1 (k-1)} \right\} \left\{ 1 - \frac{\tau k^2}{A_o(k-1) R_1 R_2} \right\} \quad (2-11.24)$$

From these equations, the active sensitivities are derived:

$$S_{A/\tau}^{\omega_n} = S_{A/\tau}^Q = \frac{1}{2} \cdot \frac{\omega_n}{A_o} \cdot \left(\frac{k}{k-1} \right)^2 \cdot \sqrt{\mu \delta} \quad (2-11.25)$$

$$\text{where } \mu = R_2/R_1 \quad (2-11.26)$$

$$\text{and } \delta = C_2/C_1 \quad (2-11.27)$$

as defined previously. The objective is to choose μ or δ to strike a happy medium between the active and the passive sensitivities (see [19], p. 319).

The Designers Guide to Active Filters [26], has the set of equations that generate the element values for this positive and negative feedback biquad. The point is made that by choosing $\delta < 1$ some of the active sensitivities may be reduced at the expense of resistor value spread (μ increases).

Equations (2-11.28) through (2-11.42) are used by the HP-67/97 program. The equation solution starts with a choice for the capacitor ratio, δ , and positive feedback ratio, k , and the operational amplifier dc gain, A_o , and gain bandwidth product, GBP. The resonant frequency is f_o and $p = 1/k$ ($f_a = 1/(2\pi\tau)$).

$$\Omega = f_a/f_o = \text{GBP}/(f_o A_o) \quad (2-11.28)$$

$$\gamma = A_o \Omega = \text{GBP}/f_o \quad (2-11.29)$$

$$d = 1/Q \quad (2-11.30)$$

$$\beta = \Omega - p\gamma = \left(1 - \frac{A_o}{k}\right) \quad (2-11.31)$$

$$m = \gamma + \beta = \Omega \left\{ 1 + A_o \left(1 - \frac{1}{k} \right) \right\} \quad (2-11.32)$$

$$a_2 = (\delta + 1) \{ m(m-d) + 1 \} \quad (2-11.33)$$

$$a_1 = \delta m - (\delta + 1) \beta - (m-d)(md-1) \quad (2-11.34)$$

$$a_0 = m(\beta - d) + 1 \quad (2-11.35)$$

$$\left. \begin{array}{l} C_1 = 1 \\ C_2 = \delta \end{array} \right\} \text{normalized values} \quad (2-11.36)$$

The quadratic equation is used to find the positive real root (R_1) of:

$$a_2 R_1^2 + a_1 R_1 + a_0 = 0 \quad (2-11.38)$$

i.e.,

$$R_1 = \frac{-a_1}{2a_2} + \sqrt{\left(\frac{a_1}{2a_2} \right)^2 - \frac{a_0}{a_2}} \quad (2-11.39)$$

then

$$R_2 = \frac{m(\delta + 1) R_1 - (dm-1)}{(R_1 - \beta) \delta} \quad (2-11.40)$$

H is the gain of the filter at resonance:

$$H = \frac{-R_2 \cdot \delta \cdot Q}{1 - \frac{1}{k} + \frac{1}{A_o}} \quad (2-11.41)$$

A parasitic pole also exists. The location of this pole is at $-\sigma$, where:

$$\sigma = \frac{m}{\delta R_1 R_2} \quad (2-11.42)$$

The normalized transmission function with the above element values becomes:

$$G(s) = \frac{E_{out}}{E_{in}} = \frac{\frac{H}{Q} s}{\left(s^2 + \frac{s}{Q} + 1 \right) \left(\frac{s}{\sigma} + 1 \right)} \quad (2-11.43)$$

The design of this filter type is somewhat cut and try if low sensitivities are to be achieved. The program is written to take the desired resonant frequency, the operational amplifier parameters, the capacitor ratio, one capacitor value, and the positive feedback ratio, and provides the remaining element values.

Because the resonator design exhibits a gain, H , at resonance, the input resistor, R_1 , may be split into two resistors to provide a Thevenin equivalent circuit with gain $H_{\text{desired}}/H = 1/H'$ and impedance R_1 . This equivalent circuit is shown in Fig. 2-11.2.

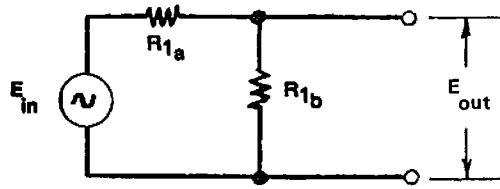


Figure 2-11.2 Equivalent input resistor network.

$$E_{out}/E_{in} = 1/H' = R_{1b}/(R_{1a} + R_{1b}) \quad (2-11.44)$$

$$R_{\text{equiv}} = (R_{1a} \cdot R_{1b})/(R_{1a} + R_{1b}) = R_1 \quad (2-11.45)$$

Equation (2-11.44) is solved for $R_{1a} + R_{1b}$, and substituted into Eq. (2-11.45) to yield an expression for R_{1a} :

$$R_{1a} = H' \cdot R_1 \quad (2-11.46)$$

Substituting Eq. (2-11.46) into Eq. (2-11.44) yields an expression for R_{1b} :

$$R_{1b} = R_{1a}/(H'-1) \quad (2-11.47)$$

Equations (2-11.46) and (2-11.47) are used by the program to split the input resistor and provide the desired resonator gain at the resonant frequency.

User Instructions

DELIYANNIS POSITIVE AND NEGATIVE FEEDBACK RESONATOR				
resistance level	δ	H_{desired}		
Q	p	op-amp gain-BW	op-amp dc gain	load f & start

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card			
2	Load Q, the quality factor	Q	A	
3	Load p, the positive feedback ratio ($p = 1/k$)	p	B	
4	Load R, the operating resistance level	R, Ω	f A	
5	Load δ , the ratio of C2 to C1 (Eq. (2-10.27))	δ	f B	
6	Load desired gain at resonance	H_{desired}	f C	
7	Load op-amp gain-bandwidth product	GBP, Hz	C	
8	Load op-amp dc gain	A_0	D	
9	Load resonant frequency desired and start	f_0 , Hz		<div> R_1 R_2 H σ R_B </div> <div> R_1 R_2 C_1 C_2 R_{1a} R_{1b} </div> <div> $S_{R_1, R_2, C_1, C_2}^{\omega_n}$ $S_{R_1, R_2}^{\sigma} - S_{R_2}^{\sigma}$ $S_{R_1, R_2}^{\sigma} - S_{R_2}^{\sigma}$ $S_{C_1, C_2}^{\sigma} - S_{C_2}^{\sigma}$ $S_{A_0}^{\omega_n} - S_{A_0}^{\sigma}$ </div>
	<p>note:</p> <p>Flag 3 is tested on all input routines to determine whether input or output of the respective parameter is desired. If an input key ("A" - "D" and "a" - "c") is keyed without numeric entry, or following the clear key (e), the presently stored parameter will be displayed.</p>			
10	Go back and change any parameters in any order, and rerun program. The center frequency need not be reloaded unless it is being changed.			

Example 2-11.1

A second order Deliyannis resonator is to be designed using a type 741 operational amplifier. The operational amplifier characteristics and resonator specifications are:

Center frequency:	1000 Hz
Q:	100
gain at resonance:	1.0
capacitor ratio:	1.0
p, positive fdbk ratio:	0.04
resistance level:	10000 Ω
op-amp gain-bandwidth:	500000 Hz
op-amp dc gain:	100000

Find the element values and calculate the sensitivities for this design. Investigate the effect of different values of positive feed-back on the component value spread and sensitivities. The HP-97 print-out for this problem is shown on the next page, and the schematic is shown in Fig. 2-11.3.

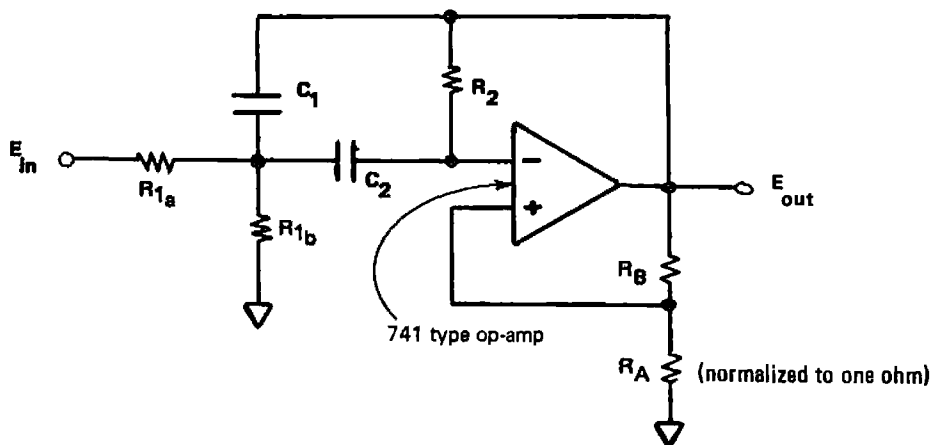


Figure 2-11.3 Deliyannis resonator schematic.

HP-97 printout for Example 2-11.1

```

100. GSBA load Q
10000. GSBA load denormalization resistance level, R
.04 GSBE load positive feedback ratio, p
1. GSBB load capacitor ratio, S
1. GSBC load gain desired at resonance, Hdesired
500000. GSBC load op-amp GBP
100000. GSBD load op-amp dc gain, A0
1000. GSBE load f0 and start

145.776-03 *** R1
6.75947+00 *** R2
-704.104+00 *** H
487.151+00 *** σ
24.0000+00 *** RB (RA = 1)
    } normalized values
    } (C1 = 1)

10.0000+03 *** R1
463.707+03 *** R2
2.32001-09 *** C1
2.32001-09 *** C2
    } denormalized values

7.04104+06 *** R1A
10.0142+03 *** R1B
    Thevenin equivalent input resistor pair

-500.000-03 ***  $S_{R_1, R_2, C_1, C_2}^{\omega_h}$ 
28.3733+00 ***  $S_{R_1}^Q, -S_{R_2}^Q$ 
-28.8733+00 ***  $S_{R_1}^Q, -S_{R_2}^Q$ 
-14.1882+00 ***  $S_{C_1}^Q, -S_{C_2}^Q$ 
7.38889-03 ***  $S_{A/\tau}^Q, -S_{A/\tau}^{\omega_h}$ 
    
```

The following printouts have all parameters the same except the positive feedback ratio, p. Notice passive sensitivities increase and active decrease.

1.-09 GSBE p		.004 GSBE p		.4 GSBE p	
GSBE		GSBE		GSBE	
3.79141-03 ***		46.3615-03 ***		577.077-03 ***	
172.670+00 ***		20.6707+00 ***		1.71635+00 ***	
-17.2668+03 ***		-2.07535+03 ***		-286.053+00 ***	
763.761+00 ***		519.661+00 ***		302.893+00 ***	
1.00000+09 ***		249.000+00 ***		1.50000+00 ***	
10.0000+03 ***		10.0000+03 ***		10.0000+03 ***	
455.423+06 ***		4.45860+06 ***		29.7421+03 ***	
60.3422-12 ***		737.866-12 ***		9.18446-09 ***	
60.3422-12 ***		737.866-12 ***		9.18446-09 ***	
172.668+06 ***		20.7535+06 ***		2.86053+06 ***	
10.0006+03 ***		10.0048+03 ***		10.0351+03 ***	
-500.000-03 ***		-500.000-03 ***		-500.000-03 ***	
21.3406-06 ***		8.48008+00 ***		114.973+00 ***	
-500.021-03 ***		-8.98008+00 ***		-115.473+00 ***	
-31.4320-03 ***		-4.24420+00 ***		-57.4880+00 ***	
213.406-03 ***		21.2853-03 ***		4.79053-03 ***	

Program Listing I

001	*LBLA	LOAD Q	056	+	
002	1/X		057	STOD	
003	STO0	store d = 1/Q	058	RCL2	
004	GT00		059	RCLC	
005	*LBLA	LOAD DENORMALIZATION	060	x	
006	ST08	RESISTANCE LEVEL	061	RCL9	$a_1 = \delta m - (\delta + 1)\beta - (m - d)(dm - 1)$
007	GT00		062	RCLB	
008	*LBLB	LOAD p	063	x	
009	ST01		064	-	
010	GT00		065	RCLC	
011	*LBLK	LOAD C_1/C_2 RATIO	066	RCL0	
012	ST02		067	x	
013	GT00		068	EEX	$dm - 1 \rightarrow R_1$
014	*LBLC	LOAD OP-AMP GBP	069	-	
015	ST03		070	STOI	
016	GT00		071	RCLC	
017	*LBLC	LOAD $H_{desired}$	072	x	
018	PZS		073	-	
019	ST00		074	2	$\frac{a_1}{2} \rightarrow R_6$
020	PZS		075	=	
021	GT00		076	STO6	
022	*LBLO	LOAD OP-AMP A_0	077	RCL0	
023	ST04		078	RCLB	
024	*LBL0	clear flag 3 subroutine	079	-	
025	CF3		080	RCLC	$a_0 = m(\beta - d) + 1$
026	RTN		081	x	
027	*LBLE	LOAD f_0 AND START ANALYSIS	082	EEX	
028	F3?	store f_0 if entered	083	-	
029	ST05	from keyboard	084	RCLD	
030	SPC		085	ST÷6	
031	RCL3		086	÷	
032	RCL5	$\gamma = \frac{A_0}{f_0} \rightarrow R_A$	087	RCL6	
033	÷		088	X²	
034	STO8		089	+	$R_1 = \sqrt{\left(\frac{a_1}{2a_2}\right)^2 - \frac{a_0}{a_2}} - \frac{a_1}{2a_2}$
035	RCL4		090	JX	
036	÷		091	RCL6	
037	RCLA		092	-	
038	RCL1	$\beta = \frac{\gamma}{A_0} - \frac{\gamma}{k} \rightarrow R_B$	093	STOD	
039	x		094	PRTX	
040	-		095	RCLC	
041	STO8		096	RCL9	
042	RCLA		097	x	
043	+	$m = \gamma + \beta$	098	x	
044	STOC		099	RCLI	
045	RCL2		100	-	
046	EEX		101	RCLD	$R_2 = \frac{m(\delta + 1)R_1 - (dm - 1)}{(R_1 - \beta)\delta}$
047	+	$\delta + 1 \rightarrow R_9$	102	RCLB	
048	STO9		103	-	
049	x	$m(\delta + 1)$	104	÷	
050	RCLC		105	RCL2	
051	RCL0		106	÷	
052	-	$m - d \rightarrow R_E$	107	STOE	
053	STOE		108	PRTX	
054	x		109	RCL2	
055	RCL9	$a_2 = (\delta + 1)\{m(m - d) + 1\} \rightarrow R_D$	110	x	

REGISTERS									
0	$d = \frac{1}{Q}$	1	$p = \frac{1}{k}$	2	$\delta = \frac{C_2}{C_1}$	3	op-amp GBP	4	op-amp dc gain, A_0
5	f_0	6	H , or a_1/a_2	7	$R_2\delta$, or μ	8	resistance level	9	$\delta + 1$, or $Q/\mu\delta$
S0	$H_{desired}$	S1		S2		S3		S4	
A	γ	B	β	C	m or $\epsilon = \frac{1}{k-1}$	D	a_2 , or R_1	E	$m - d$, or R_2
								F	$dm - 1$, or -0.5

[illegible]

PROGRAM 2-12 ELLIPTIC FILTER ORDER AND LOSS POLE LOCATIONS.

Program Description and Equations Used

This program finds the lowest elliptic (also called Cauer-Chebyshev) lowpass filter order that will meet the requirements for A_{\max} , A_{\min} , f_{\max} , and f_{\min} . These parameters are defined with the aid of Fig. 2-12.1.

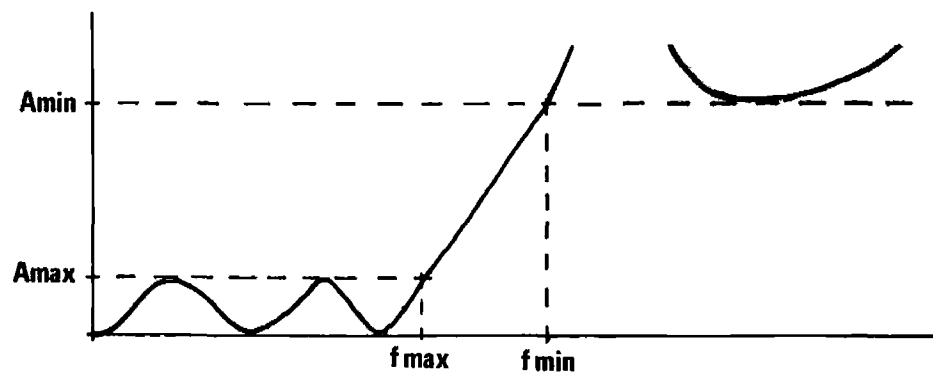


Figure 2-12.1 Elliptic filter loss function, where:

- A_{\max} : maximum passband ripple in dB
- A_{\min} : minimum stopband attenuation in dB
- f_{\max} : maximum passband frequency (passband edge)
- f_{\min} : minimum frequency where A_{\min} is achieved.

The program also calculates the attenuation pole frequencies. From these frequencies the filter response at any frequency outside the passband may be determined by using the Z transformation. This transformation technique is described in the next program, and also in chapter 8 of Daniels' book [17]. The analog Z transformation should not be confused with the digital z transformation.

The elliptic filter response is not monotonic in the stopband as can be seen in Fig. 2-12.1. This stopband response is the characteristic difference between the Chebyshev and elliptic filter responses. Both filter types have equiripple behavior in the passband, but Chebyshev

(and Butterworth) filters have all attenuation poles located at infinite frequency, while elliptic filters have finite attenuation poles. Because of these finite attenuation poles, the elliptic filter has a sharper transition from passband to stopband for a given filter order.

The elliptic response also has its drawbacks. As the transition band becomes sharper (the filter more selective) the transfer function phase angle changes more rapidly with frequency, and so the group delay becomes peaked near the passband edge frequency. Uniform group delay is required for filters that must process pulses without exhibiting ringing amplitude responses; thus, the transmission function of the elliptic filter tends toward the optimum only from the point of view of the attenuation requirement.

If the LC filter is being designed as a basis for an active filter design such as the leapfrog topology, or an elliptic response is being contemplated for active simulation by cascaded active resonators, the elliptic filter transmission zero (attenuation pole) simulation will require a biquadratic resonator circuit. The designer should always compare the sensitivities of the elliptic active filter circuit versus the sensitivities of a higher order all-pole active design which meets the overall same specifications. In general, as the active resonator circuit becomes more complicated, or the operating gain-bandwidth requirements approach the op-amp gain-bandwidth, the circuit sensitivities become worse, and the final filter design may not meet the specification requirements when component drift due to temperature and aging is considered.

The following formulas are discussed in detail in the equation derivation section and the results brought forward. The loss function, L , is defined by Eq. (2-12.1) (refer to Fig. 2-12.1).

$$L^2 = \frac{10^{0.1 A_{\min}} - 1}{10^{0.1 A_{\max}} - 1} \quad (2-12.1)$$

Furthermore, x_L is the ratio of the lowpass stopband edge frequency to the lowpass passband edge frequency (refer to Fig. 2-12.1):

$$x_L = \frac{f_{\max}}{f_{\min}} \quad (2-12.2)$$

The minimum elliptic filter order that will meet the requirements for A_{\max} , A_{\min} , f_{\max} , and f_{\min} is calculated from Eq. (2-12.28).

$$n = \frac{K(x_L^{-1}) \cdot K'(L^{-1})}{K'(x_L^{-1}) \cdot K(L^{-1})} \quad (2-12.30)$$

where $K(\)$ is the complete elliptic integral of the first kind, and $K'(\)$ is the complementary complete elliptic integral of the first kind. These functions are defined by Eqs. (2-12.11) through (2-12.14) and are calculated by a truncated infinite series as given by Eqs. (2-12.18) through (2-12.21).

The loss poles of the elliptic filter transfer function are given by Eqs. (2-12.31) and (2-12.32).

$$x_v = \frac{x_L}{x_{zv}} \quad (2-12.31)$$

where

$$x_{zv} = \begin{cases} \operatorname{sn} \left\{ \frac{2v}{n} K(x_L^{-1}), x_L^{-1} \right\} & n \text{ odd} \\ \operatorname{sn} \left\{ \frac{2v-1}{n} K(x_L^{-1}), x_L^{-1} \right\} & n \text{ even} \end{cases} \quad (2-12.32)$$

The elliptic sine is evaluated by means of a Fourier series given by Eqs. (2-12.24) and (2-12.25).

The even ordered elliptic filters have a stopband loss that approaches a constant, finite value as the frequency approaches infinity, i.e., the even ordered elliptic filter does not have a loss pole at infinite frequency. The lossless LC synthesis of such a filter cannot be done without the use of mutual inductive coupling between the filter sections. On the other hand, active filter realizations can be done without the loss pole locations being a constraint.

A special form of the Möbius transformation (a bilinear change of variables) may be applied to the even ordered elliptic loss pole frequencies to move the highest frequency loss pole to infinity and thereby allow LC synthesis without mutual inductance. The even ordered elliptic filter element value tables in Zverev [58], already have this transformation applied, hence $x_L^{-1} = \sin \theta$ only for odd order filters (θ is the tabulated modular angle).

The general form of the Möbius transformation is:

$$s^2 = \left(\frac{\Omega_C^2 - \Omega_B^2}{\Omega_B^2 - \Omega_0^2} \right) \Omega_B^2 \cdot \left(\frac{s^2 + \Omega_0^2}{s^2 + \Omega_C^2} \right) \quad (2-12.3)$$

This transformation converts frequencies as follows:

- 1) $S = j \Omega_0$ to $s = 0$
- 2) $S = j \Omega_B$ to $s = j \Omega_B$ (no change in passband edge)
- 3) $S = j \Omega_C$ to $s = \infty$

It is not desired to transform the dc, or zero frequency, location in the lowpass filter, hence, $\Omega_0 = 0$; furthermore, the loss poles lie directly on the $j\omega$ axis so the transformation need only apply to $s = j\omega$, thus Eq. (2-12.3) becomes:

$$\omega^2 = \left(\Omega_C^2 - \Omega_B^2 \right) \frac{\Omega^2}{\Omega_C^2 - \Omega^2} \quad (2-12.4)$$

The program calculates and prints (displays) the original even-ordered pole locations as calculated from Eq. (2-12.32) applies Eq. (2-12.4), and prints and stores the transformed pole locations. For odd-ordered filters, the program calculates, prints, and stores the finite loss pole locations from Eq. (2-12.32) without transformation. In both the even and odd cases, the loss pole frequencies are stored in normalized form ($\Omega=1$), but are denormalized for printout or display.

The normalized loss pole frequencies are used by the next program in this section to calculate the filter attenuation at any frequency within the passband or the stopband by using the Z transform.

User Instructions

ELLIPTIC FILTER ORDER AND LOSS POLE LOCATIONS				
Amin	fmin	change n		
Amax	fmax	compute n	compute loss poles	

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of magnetic card			
2	Load maximum passband ripple in dB	Amax	A	
3	Load minimum stopband loss in dB	Amin	f A	
4	Load passband cutoff frequency	fmax	B	
5	Load minimum stopband loss frequency	fmin	f B	
6	Calculate filter order to meet requirements		C	n n*
	<p>*The first n will be the result of the calculations and will generally not be an integer. The second n is the next highest integer, and is the stored value. Both values are given so the designer can get a feeling for the design margin. If the two values are close, the next higher filter order might be considered.</p> <p>If the program stops displaying "Error", the input data for Amax and Amin are too far apart (.005dB and 100dB for example) and calculations for $K(L^{-1})$ exceed the precision capability of the HP-97. The filter order may be obtained from the Kawakami OC nomograph [54], [58], and the program restarted with step 7. Step 8 will still run correctly.</p>			
7	To change filter order (integers only)	n	f C	
8	To calculate loss poles (frequencies of maximum attenuation)		D	f ₁ f ₂ : f _{n/2} ** space f ₁ ' *** f ₂ ' : f' _{(n-1)/2}
	<p>**The number of loss poles will be the integral part of n/2, i.e., a fifth order filter will have two loss poles.</p> <p>***If n is even, the Möbius transformation is done to ensure a loss pole at infinity. The primed frequencies (f') are the Möbius transformed frequencies. The highest original loss frequency has been transformed to infinite frequency, and is not printed out, i.e., a sixth order filter only has two transformed loss frequencies printed out. The original frequency, f_{n/2}, is the transformed fmin frequency.</p>			

Example 2-12.1

Compute the filter order and loss pole locations for an elliptic filter to meet the following specifications.

$$A_{\max} = .28 \text{ dB } (\rho = 25\%, A_{\max} = -10 \log(1-\rho^2))$$

$$A_{\min} = 63 \text{ dB}$$

$$f_{\max} = 1000 \text{ Hz}$$

$$f_{\min} = 2000 \text{ Hz}$$

HP-97 input/output

```

      .28 GSBF  load Amax
     63.00 GSBF  load Amin
    1000.00 GSBF  load fmax
    2000.00 GSBF  load fmin
      GSBG      calculate minimum filter order

     4.97 ***   actual calculated filter order, n
     5.00 ***   nearest integral value for n to meet specs

      GSBG      calculate loss pole locations
    3250.804880 ***
    2089.246505 ***

```

These results may be checked by comparing them to the 30° modular angle filter design shown in the "Catalog of Normalized Lowpass Models" on page 220 of Zverev [58].

Example 2-12.2

Compute the minimum filter order and loss pole locations for an elliptic filter which meets the following specifications:

$$A_{\max} = .1773 \text{ dB } (\rho = 20\%, A_{\max} = -10 \log(1-\rho^2))$$

$$A_{\min} = 78 \text{ dB}$$

$$f_{\max} = 1000 \text{ Hz}$$

$$f_{\min} = 2000 \text{ Hz}$$

```

.1773 GSBa load Amax
78.00 GSBa load Amin
1000.00 GSEF load fmax
2000.00 GSEb load fmin
        GSEC calculate minimum filter order

5.96 *** actual calculated filter order, n
6.00 *** nearest integral n to meet specs

        GSED calculate loss pole locations:
7235.802719 *** }
2732.053511 *** } untransformed loss poles
2061.105330 *** }
                    also represents transformed fmin

2922.132266 *** }
2129.548771 *** } transformed loss pole locations
    
```

Derivation of Equations Used

The elliptic response is governed by the Chebyshev rational function, which is a ratio of polynomials. The development of the Chebyshev rational function in terms of elliptic functions is beyond the scope of this discussion. This development is discussed in Chapter 5 of Daniels' book [17]. A few highlights of the Chebyshev rational function and elliptic functions will be used to show the development of the equations used by this program.

The Chebyshev response becomes the elliptic response when the Chebyshev polynomial, $T_n(x)$, is replaced by the Chebyshev rational function, $R_n(x,L)$, in the filter transfer function (Feldtkeller equation).

$$|H(j\omega)|^2 = 1 + |K(j\omega)|^2 \quad (2-12.5)$$

$$\text{for Chebyshev response, } |K(j\omega)|^2 = \epsilon^2 \cdot T_n^2(x) \quad (2-12.6)$$

$$\text{for elliptic response, } |K(j\omega)|^2 = \epsilon^2 \cdot R_n^2(x, L) \quad (2-12.7)$$

Hence, the elliptic attenuation function is:

$$A(\omega)_{dB} = 20 \cdot \log |H(j\omega)| \quad (2-12.8)$$

$$= 10 \cdot \log \left\{ 1 + \epsilon^2 \cdot R_n^2(x, L) \right\} ;$$

$$\text{where } x = \omega/\omega_{max} = f/f_{max} \quad (2-12.9)$$

The Chebyshev rational function, $R_n(x, L)$, has the following properties (also see Fig. 2-11.2).

- 1) R_n is odd when n is odd and vice versa.
- 2) All the zeros of R_n lie within the interval $-1 < x < 1$, while all the poles lie outside this interval.
- 3) $R_n(x, L)$, like $T_n(x)$, oscillates between ± 1 for $-1 < x < 1$. This interval defines the passband.
- 4) $R_n(1, L) = +1$ (passband edge).
- 5) $|R_n| > L$ (oscillates outside of L) for $|x| > x_L$, where x_L is defined as the first value of x where $R_n(x, L) = L$, and hence, A_{min} is achieved (defines stopband).

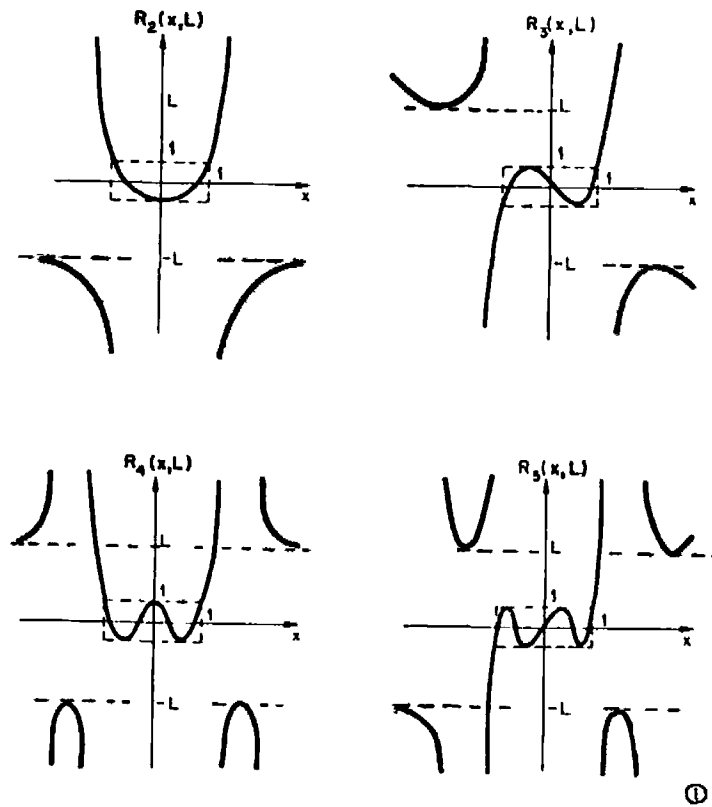


Figure 2-11.2 Chebyshev rational functions for $n = 2$ to 5.

By using Eq. (2-12.8) and condition 5, an expression for L can be found in terms of the filter parameters A_{\min} and ϵ .

$$L^2 = \frac{10^{0.1A_{\min}} - 1}{\epsilon^2} \quad (2-12.10)$$

Since $A(\omega) = A_{\max}$ at the passband edge, f_{\max} , condition 4 and Eq. (2-12.8) can be used to find an expression for ϵ .

$$\epsilon^2 = 10^{0.1A_{\max}} - 1 \quad (2-12.11)$$

Not surprisingly, this is the same expression as is used in the Chebyshev case, and for the same reasons (condition 3).

By putting Eqs. (2-12.10) and (2-12.11) together, the expression for L is obtained:

$$L^2 = \frac{10^{0.1A_{\min}} - 1}{10^{0.1A_{\max}} - 1} \quad (2-12.12)$$

ELLIPTIC FUNCTIONS

There are three kinds of elliptic integrals (see Abramowitz and Stegun, [1]). Only the elliptic integral of the first kind is needed for elliptic filters. The elliptic integral of the first kind is defined by the following equation:


$$u(\phi, k) = \int_0^{\phi} \frac{dx}{(1 - k^2 \sin^2 x)^{1/2}} \quad (2-12.13)$$

The two variables, ϕ and k , are called the amplitude and modulus respectively. Some elliptic function tables [1], and some elliptic filter tables [58], are parametric in terms of the modular angle, θ , instead of the modulus, k . The modular angle is defined by:

$$k = \sin \theta \quad (2-12.14)$$


The complete elliptic integral of the first kind results when ϕ , the limit of integration, is taken as $\pi/2$ radians. This value, $u(\pi/2, k)$ is defined as $K(k)$.

Figure 2-12.3 shows $u(\phi, k)$ parametric with the modular angle, θ . $u(\phi, k)$ has been normalized with respect to $K(k)$. Figure 2-12.4 shows the complete elliptic integral, $K(k)$ by itself.

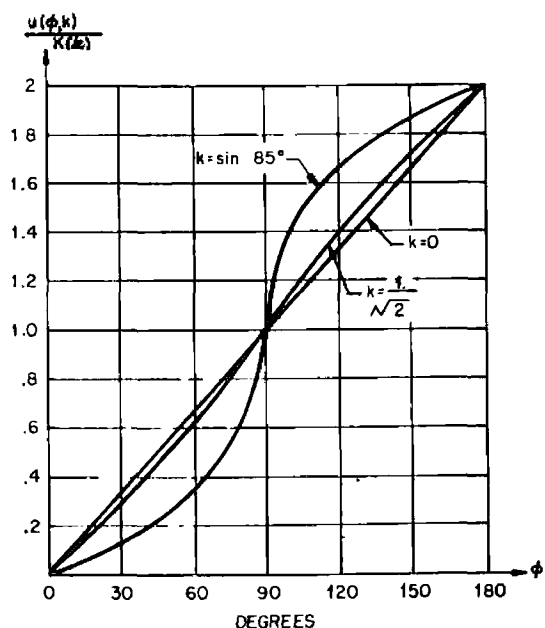

②

Figure 2-12.3 Elliptic integral.

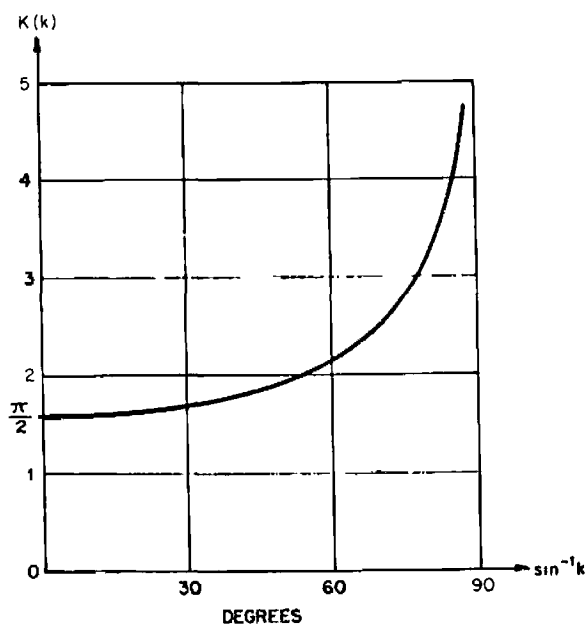

③

Figure 2-12.4 Complete elliptic integral.

The complementary modulus is defined in terms of the modulus, k , or the modular angle, θ , as:

$$k' = (1 - k^2)^{\frac{1}{2}} = \cos \theta \quad (2-12.13)$$

The complementary complete elliptic integral is defined in terms of the complementary modulus:

$$K'(k) = K(k') = u(\pi/2, k') \quad (2-12.16)$$

The elliptic sine is an elliptic function, and is defined in a somewhat reverse manner from the elliptic integral:

$$u(\phi, k) = \int_0^{\phi} (1 - k^2 \sin^2(x))^{-\frac{1}{2}} dx \quad (2-12.17)$$

$$\text{sn}(u, k) = \sin \phi \quad (\text{elliptic sine}) \quad (2-12.18)$$

$$\text{cn}(u, k) = \cos \phi \quad (\text{elliptic cosine}) \quad (2-12.19)$$

The definition is "reverse" since the limit of integration, ϕ , must be found to yield the "input," $u(\phi, k)$ and k . Figure 2-12.5 shows the elliptic sine and elliptic cosine functions.

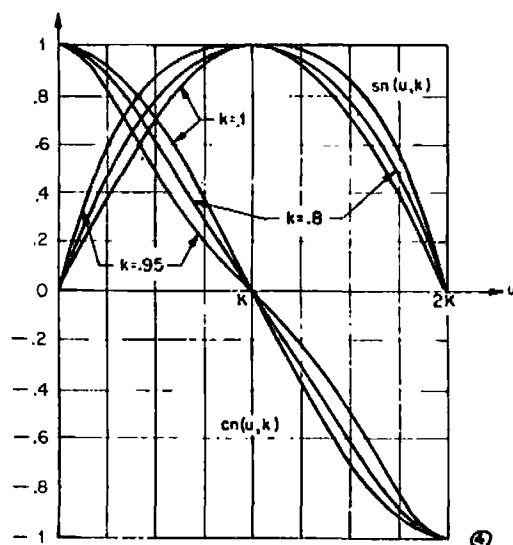


Figure 2-12.5 Elliptic sine and cosine functions.

CREDITS: 1, 2, 3, & 4: Reproduced from "Approximation Methods for Electronic Filter Design," by R.W. Daniels, copyright, © 1974, by Bell Telephone Labs, Inc., used with permission of McGraw-Hill Book Company, Inc., New York, N.Y.

Luckily, there are rapidly converging series expansions for both $K(k)$ and $\text{sn}(u, k)$, [12], and the programmable calculator can be used to perform the iterative calculations. These series expansions are:

Complete elliptic integral

$$K(k) = \frac{\pi}{2} \prod_{m=0}^{\infty} (1 + k_{m+1}^2) ; \quad (2-12.20)$$

where

$$k_{m+1} = (1 - k_m^2) / (1 + k_m^2) \quad (2-12.21)$$

$$k_m' = (1 - k_m^2)^{1/2}, \text{ (complementary modulus)} \quad (2-12.22)$$

$$k_0 \equiv k \quad (2-12.23)$$

The terms of the infinite product expansion rapidly converge toward unity. The series is terminated when $k_m < 10^{-9}$. This accuracy is generally achieved in four iterations or less.

Elliptic sine

The elliptic sine is calculated from the following Fourier series:

$$s_n(u, k) = \frac{2\pi}{K(k) \cdot k} \sum_{m=0}^{\infty} \left\{ \frac{q^{m+1/2}}{1 - q^{2m+1}} \right\} \cdot \sin \left((2m+1) \frac{\pi u}{2K(k)} \right) \quad (2-12.24)$$

where q is Jacobi's nome (also called modular elliptic function):

$$q = e^{-\frac{\pi K'(k)}{K(k)}} \quad (2-12.25)$$

The series is terminated when $(q^{m+1/2}) / (1 - q^{2m+1}) < 10^{-9} q$

This particular algorithm for the elliptic sine is only one of many which can be used to calculate the function. For sharp cutoff filters, the convergence is slow; however, of all the algorithms researched by the author, the Fourier series method could be coded to fit into the HP-97 program memory and still leave enough room for the coding needed for the rest of the program.

If more registers were available, the descending Landen transformation method could have been combined with the calculation of $K(k)$ to simultaneously yield $K(k)$ and $\text{sn}(u, k)$ as outlined in Skwirzynski and Zdunek's article [46]. If more program space were available, the

elliptic sine could be calculated from the ratios of sums of hyperbolic sines and cosines as recommended by Orchard [41]. Also, if more program space were available, the calculation of the transmission zeros could be done directly from adaptations of the elliptic sine as represented by infinite products of hyperbolic tangents given by Amstutz [2] or as interpreted by Geffe [27]. Darlington's algorithm [18] is used in Program 2-15, and is a concise method for calculating the transmission zeros and poles when the filter order is odd.

Filter order calculation: Just as the trigonometric sine is periodic, so is the elliptic sine, although the elliptic sine is doubly periodic with a real period of $4 \cdot K(k)$, and an imaginary period of $2 \cdot K'(k)$. The Chebyshev rational function, $R(x, L)$ may be expressed in terms of the complete elliptic integral and the elliptic sine. By relating the real and imaginary periods of the elliptic sine function to the real and imaginary periods of the Chebyshev rational function, two equations in two unknowns, C and n , may be formulated. These equations are:

Chebyshev rational function and elliptic functions

$$R_n(x, L) = \begin{cases} \operatorname{sn}(uL/C, L^{-1}) & n \text{ odd} \\ \operatorname{sn}(uL/C + (-1)^{\frac{n}{2}} \cdot K(L^{-1}), L^{-1}) & n \text{ even} \end{cases} \quad (2-12.26)$$

where C is a constant, and u is the solution to:

$$x = \operatorname{sn}(x_L^{-1} \cdot u, x_L^{-1}) \quad (2-12.27)$$

Simultaneous equations in C and n :

$$x_L^{-1} \cdot K(x_L^{-1}) = n \cdot C \cdot L^{-1} \cdot K(L^{-1}) \quad (\text{real periods}) \quad (2-12.28)$$

$$x_L^{-1} \cdot K'(x_L^{-1}) = C \cdot L^{-1} \cdot K'(L^{-1}) \quad (\text{imaginary periods}) \quad (2-12.29)$$

Eliminating C by simultaneous solution of Eqs. (2-12.28) and (2-12.29) results in the following expression for the filter order, n :

$$n = \frac{K(x_L^{-1}) \cdot K'(L^{-1})}{K'(x_L^{-1}) \cdot K(L^{-1})} \quad (2-12.30)$$

where x_L^{-1} is defined by Eq. (2-12.2) and L^{-1} by Eq. (2-12.18):

$$x_L^{-1} = (f_{\max})/(f_{\min})$$

$$L^{-1} = \left\{ \frac{10^{0.1A_{\max}} - 1}{10^{0.1A_{\min}} - 1} \right\}^{1/2}$$

The loss poles of the elliptic filter transfer function, Eq. (2-12.5), are given by:

$$x_v = \frac{x_L}{x_{zv}} \quad (2-12.31)$$

where:

$$x_{zv} = \left\{ \begin{array}{ll} \operatorname{sn} \left(\frac{2v}{n} K(x_L^{-1}), x_L^{-1} \right) & n \text{ odd} \\ \operatorname{sn} \left(\frac{(2v-1)}{n} K(x_L^{-1}), x_L^{-1} \right) & n \text{ even} \end{array} \right\}_{v=1, 2, \dots, n} \quad (2-12.32)$$

In Eq. (2-12.22) k becomes x_L^{-1} for the above elliptic sine computation, hence:

$$x_v = \frac{K(x_L^{-1})}{2\pi\sum} \quad (2-12.33)$$

where \sum is the term summation in Eq. (2-12.24).

0	1	2	3	4	5	6	7	8	9
Amax	Amin	fmax	fmin	n	scratch	index, ν	$K(x_L^{-1})$	$K'(x_L^{-1})$	x_L^{-1}
$S_0 (\pi\nu)/n$	$S_1 2m+1$	$S_2 \frac{q^{m+1/2}}{1-q^{2m+1}}$	$S_3 \Sigma$						
loss pole storage				loss pole storage registers					
A				B		C		D	
loss pole storage				10^{-10}		NINF (used by next program)		storage reg. index	

Program Listing II

113	GT01		169	X≠Y?	test for loop exit
114	RCL3	recall summation & compute sn:	170	GT02	
115	PzS		171	DSZ1	restore highest reg. index
116	ENT↑		172	2	NINF = 2 for transformed
117	+	$\frac{sn(x, x_L^{-1})}{x_L} = \frac{2\pi \sum}{K(x_L^{-1})}$	173	ST00	even ordered filters
118	Pi		174	*LBL3	
119	x		175	DSP2	set original display format
120	RCL7		176	SPC	
121	=		177	RTN	return control to keyboard
122	1/X	compute and store normalized	178	*LBL4	compute K(k)
123	ISZ1	loss pole locations	179	X²	
124	ST01		180	CHS	form complementary modulus:
125	RCL2	denormalize and print loss	181	EEX	
126	x	pole locations	182	+	$k' = \sqrt{1 - k^2}$
127	PRTX		183	JX	
128	EEX		184	*LBL5	compute K'(k)
129	ST+6	increment register index	185	ST05	store argument, k
130	RCL6		186	Pi	initialize product register
131	ENT↑	test for loop exit:	187	2	
132	+	loop if n > 2v	188	=	
133	RCL4		189	ST06	
134	X>Y?		190	*LBL6	complete elliptic integral
135	GT00		191	EEX	
136	SPC		192	RCL5	
137	F0?	jump if n is odd	193	X²	
138	GT03		194	-	$K(x) = \frac{\pi}{2} \prod_{m=0}^{\infty} (1 + k_m)$
139	1	initialize index register	195	JX	
140	4	and store highest register	196	EEX	
141	XZ1	number for later exit test	197	XZV	$k_{m-1} = \frac{1 - k_m}{1 + k_m}$
142	ST0E		198	-	
143	RCL1	recall Ω_c	199	LSTX	
144	X²	store Ω_c^2	200	EEX	$k_1' = \sqrt{1 - k_1^2}$
145	ST05		201	+	
146	*LBL2	Möbius transformation loop	202	=	
147	ISZ1	calculate Möbius transform	203	ST05	
148	RCL1	for even ordered lowpass:	204	EEX	
149	X²		205	+	
150	RCL5		206	ST+6	
151	LSTX		207	RCL5	
152	X²		208	EEX	
153	-		209	CHS	test for loop exit:
154	=	$\omega^2 \cdot (\Omega_c^2 - 1) \frac{\Omega^2}{\Omega_c^2 - \Omega^2}$	210	1	loop if $k_m > 10^{-10}$
155	RCL5		211	0	
156	EEX		212	ST0C	
157	-		213	X≠Y?	
158	x		214	GT06	
159	ABS		215	RCL6	recall K(k)
160	JX		216	RTN	return to main program
161	DSZ1		217	*LBL7	subroutine to compute:
162	ST01	store normalized & xmed	218	EEX	
163	ISZ1	loss pole location	219	1	$10^{0.1A} - 1$
164	RCL2	denormalize and print loss	220	=	
165	x	pole location	221	10*	
166	PRTX		222	EEX	
167	RCL1		223	-	
168	RCL5		224	RTN	

LABELS					FLAGS	SET STATUS		
A load Amax	B load fmax	C calc n	D calc loss poles	E	0 n odd	FLAGS	TRIG	DISP
a load Amin	b load fmin	c enter n	d	e	1	ON OFF	DEG	FIX
0 sn(u,k)	1 sn loop start	2 Möbius transform	3 jump test	4 K(k)	2	1	GRAD	SCI
5 K'(k)	6 K'(k) loop	7 conversions	8	9	3	2	RAD	ENG
		subroutine				3		n 2

PROGRAM 2-13 RESPONSE OF A FILTER WITH CHEBYSHEV PASSBAND AND ARBITRARY STOPBAND LOSS POLES.

Program Description and Equations Used

This program will calculate the passband and stopband attenuation of lowpass, highpass, bandpass, and bandstop filters having Chebyshev (equi-ripple) passbands and arbitrary stopband loss pole locations. The elliptic filter is a special case of this filter class in that the loss pole locations are chosen to provide equi-ripple stopband behavior.

Bandpass and bandstop filters are assumed to be the classic transformations of the lowpass structure, i.e., equal numbers of attenuation poles on either side of the passband, and geometrical symmetry of those poles about the center frequency. The program is designed to take either stored normalized lowpass loss pole frequencies provided by Program 2-12, or to accept normalized lowpass loss pole frequencies, number of poles at infinite frequency, and passband ripple as provided by the user.

This program is adapted from an unpublished HP-67/97 elliptic stopband attenuation program written by Philip R. Geffe. The basis of the program is the Z transformation, and the associated loss function, $L(Z)$. This function allows the calculation of the stopband attenuation of equi-ripple passband elliptic filters from a knowledge of the loss pole frequencies only [17]. The transformed variable, Z , is defined by:

$$Z^2 = (s^2 + \omega_B^2) / (s^2 + \omega_A^2) \quad (2-13.1)$$

This function spreads the passband ($s = j\omega_A$ to $j\omega_B$) over the entire imaginary Z axis, and spreads the stopbands along the real Z axis. Although use of the Z transform allows greater numerical accuracy due to the spreading out of the passband poles, the prime reason for its use in this program is the mathematical expressions for elliptic filters are simpler in the Z domain than in the s domain.

Given a filter with equiripple passband extending from ω_A to ω_B , having NZ attenuation poles at the origin, N finite loss poles, and $NINF$

attenuation poles at infinite frequency, the loss function in terms of Z is:

$$L(Z) = \left\{ \frac{Z + \omega_B/\omega_A}{Z - \omega_B/\omega_A} \right\}^{\frac{NZ}{2}} \left\{ \frac{Z + 1}{Z - 1} \right\}^{\frac{NINF}{2}} \prod_{i=1}^N \frac{Z + z_i}{Z - z_i} \quad (2-13.2)$$

If $L(Z)$ represents a normalized lowpass filter, then $\omega_A = 0$, $\omega_B = 1$, and $NZ = 0$. Letting $s = j\Omega$, Z and $L(Z)$ become:

$$Z = (1 - 1/\Omega^2)^{1/2} \quad (2-13.3)$$

$$L(Z) = \left\{ \frac{Z + 1}{Z - 1} \right\}^{\frac{NINF}{2}} \prod_{i=1}^N \frac{Z + z_i}{Z - z_i} \quad (2-13.4)$$

The attenuation function, $A(\Omega)$, is defined in terms of the loss function, $L(Z)$, as follows:

$$A(\Omega) = 10 \cdot \log \left\{ 1 + \frac{\epsilon^2}{4} \left(L(Z) + \frac{(-1)^{NINF}}{L(Z)} \right)^2 \right\} \quad (2-13.5)$$

$$\epsilon^2 = 10^{0.1A_{\max}} - 1 \quad (2-13.6)$$

In the stopband, the attenuation function may be simplified:

$$A(\Omega) = 10 \log \left[1 + \frac{\epsilon^2}{4} \left\{ |L(Z)| + 1/|L(Z)| \right\}^2 \right] \quad (2-13.7)$$

The filter passband ripple (A_{\max}) may sometimes be expressed in terms of a reflection coefficient, ρ . The relationship between these quantities is:

$$A_{\max} = -10 \log (1 - \rho^2) \quad (2-13.8)$$

Within the normalized lowpass passband ($\Omega < 1$), Z becomes purely imaginary. Equation (2-13.4) may be rewritten in exponential form to eliminate the need for complex arithmetic:

$$L(Z) = e^{jB} \quad (2-13.9)$$

where

$$B = \frac{NINF}{2} \tan^{-1} \left\{ \frac{-2|Z|}{|Z|^2 - 1} \right\} + \sum_{i=1}^N \tan^{-1} \left\{ \frac{-2|Z|z_i}{|Z|^2 - z_i^2} \right\} \quad (2-13.10)$$

substituting Eq. (2-13.9) into (2-13.5) yields:

$$A(\Omega) = 10 \log (1 + \epsilon^2 \cos^2 B) \text{ for NINF even,} \quad (2-13.11)$$

and

$$A(\Omega) = 10 \log (1 + \epsilon^2 \sin^2 B) \text{ for NINF odd.} \quad (2-13.12)$$

The program uses Eqs. (2-13.3) through (2-13.12) to find the filter loss at any frequency. Two ancillary relations are used to convert unnormalized bandpass or bandstop frequencies to the normalized lowpass frequency, Ω . Lowpass and highpass filters are only special cases of bandpass and bandstop filters respectively, in that the center frequency is zero. These two ancillary equations are:

Bandpass to normalized lowpass

$$\Omega_{BP} = \frac{1}{BW} \left\{ f - \frac{f_o^2}{f} \right\} \quad (2-13.13)$$

where

BW = bandwidth

f_o = center frequency

Bandstop to normalized lowpass

$$\Omega_{BS} = 1/\Omega_{BP} \quad (2-13.14)$$


Equation (2-13.4) will predict the stopband attenuation for even ordered elliptic filters of Cauer types A and B (the Möbius transformation - see previous program for description). The type A, even-ordered filter has no attenuation poles at infinite frequency, and can only be realized with mutual inductive coupling between filter sections, while the Möbius transformed pole locations (type B) can be realized with a ladder structure containing only L's and C's. The even ordered type B ladder structure possesses a double pole of attenuation at infinite frequency.

Equation (2-13.4) will not work with the pole locations resulting from a transformation to Cauer type C filters (equal resistive termination for even-ordered elliptic filters), i.e., one must use types A and B only. See Saal and Ulbrich [45] for details.

User Instructions

CHEBYSHEV PASSBAND - ARBITRARY STOPBAND RESPONSE				
load p_1	load NINF	load + ρ or $-A_{max}$		
bandpass: f_0 BW	bandstop: f_0 BW	load f_{st} f_{sp} Δf	start sweep	calculate $f \rightarrow A(f)$

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of magnetic card			
2	If this program is being used concurrently with Program 2-11, the loss poles, A_{max} , and NINF are already stored by that program. Go to step 6 and continue.			
3	Load normalized loss pole frequencies	setup P_1 P_2 \vdots P_n	f A R/S R/S \vdots R/S	
4	Load number of loss poles at infinite frequency	NINF	f B	
5	Load either the reflection coefficient or the passband ripple in dB (related quantities). The program differentiates the quantities by sign. Both quantities are normally positive			
	Reflection coefficient	ρ	f 0	A_{max}
	or			
	Passband ripple in dB (note sign)	$-A_{max}$	f 0	A_{max}
6	Select filter type:			
	Bandpass or Lowpass:	f_0	ENT↑	
	The lowpass filter is a special case of the bandpass filter in that the center frequency is zero. The bandwidth is the lowpass cutoff frequency.	BW	A	
	Bandstop or Highpass:	f_0	ENT↑	
	The highpass filter is a special case of the bandstop filter in that the center frequency is zero. The bandwidth is the highpass cutoff frequency.	BW	B	

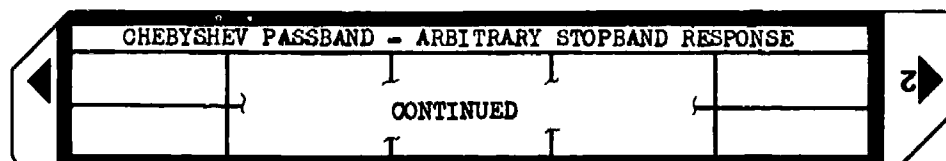

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
7	Load denormalized stopband frequency and calculate stopband attenuation	f	E	A(f)
8	If a sweep of frequencies is desired: a) Load sweep parameters The frequency increment is either an additive delta, or a multiplicative delta depending upon lin/log sweep. If linear sweep is desired, then the increment should be entered as a negative quantity, i.e., for 100 Hz linear steps, the increment should be entered as -100. Whether the increment is linear or logarithmic, the sweep will be always in the direction of increasing frequency.	f _{start} f _{stop} f _{incr}	ENT↑ ENT↑ 0	
	b) Start sweep		D	f A(f) space f A(f) : .
9	Go back to any step desired, modify, and rerun program			

Example 2-13.1

An elliptic bandpass filter is required to pass frequencies between 5 kHz and 15 kHz with 0.0436 dB ripple or less (10% reflection coefficient), and reject frequencies lying outside a 4.1 kHz to 19 kHz band by at least 60 dB. Find the minimum filter order that will satisfy these requirements, and predict the stopband response.

The center frequency is the geometric mean of the upper and lower passband edge frequencies. Likewise, the stopband edge frequencies must be geometrically symmetrical about the center frequency. In this example, the above frequencies do not satisfy this requirement, hence, the narrowest stopband with geometric symmetry must be defined. The filter center frequency is calculated from the passband edge frequencies:

$$f_o = (5000 \cdot 15000)^{\frac{1}{2}} = 8660.25 \text{ Hz}$$

The narrowest stopband may be found by calculating the geometrical mating frequencies to the given stopband frequencies, and taking the narrowest set:

$$f_u = f_o^2 / 4100 = 18292.68 \text{ Hz}$$

$$f_L = f_o^2 / 19000 = 3947.37 \text{ Hz}$$

The narrowest stopband is 4100 Hz to 18292.68 Hz for a stopband width of 14192.68 Hz.

The stopband and passband data are loaded into Program 2-12 to find the minimum filter order and loss pole locations. Because bandpass data was loaded, the loss pole frequencies that are output represent loss pole bandwidths, or the separation of loss pole frequencies in the upper and lower stopbands that are geometrically related to the filter center frequency. To convert these bandwidths into loss pole frequencies, the subprogram contained in Program 2-1 can be used. These equivalent bandpass loss pole frequencies are not necessary for proper operation of this program, but are calculated for information only. They can also be useful when tuning the final filter. All normalized loss pole information is automatically stored by Program 2-12 for use by this program.

Example 2-13.1 continued

Load Program 2-12 and calculate filter order and loss poles.

```
.0436 GSBA load Amax
60.00 GSBA load Amin
10000.00 GSBE load fmax (passband bandwidth)
14192.68 GSBk load fmin (stopband minimum bandwidth)
```

GSBC calculate minimum filter order

```
6.72 ***
```

```
7.00 *** minimum integral filter order, n
```

GSBD calculate loss pole bandwidths

```
28.69564+03 *** loss pole bandwidth #1
```

```
17.08915+03 *** loss pole bandwidth #2
```

```
14.44925+03 *** loss pole bandwidth #3
```

Load Program 2-1 to calculate loss pole locations from loss pole bandwidths.

```
28695.64 ENT+ load loss pole bandwidth #1
```

```
8660.25 GSBA load f0
```

```
31106.65 *** upper BP loss pole frequency #1
```

```
2411.05 *** lower BP loss pole frequency #1
```

```
17089.19 ENT+ load loss pole bandwidth #2
```

```
8660.25 GSBA load f0
```

```
20710.53 *** upper BP loss pole frequency #2
```

```
3621.34 *** lower BP loss pole frequency #2
```

```
14449.25 ENT+ load loss pole bandwidth #3
```

```
8660.25 GSBA load f0
```

```
18502.71 *** upper BP loss pole frequency #3
```

```
4053.46 *** lower BP loss pole frequency #3
```

Load this program (Program 2-13) and calculate filter response.

```
8660.25 ENT+ load f0
```

```
10000.00 GSBA load passband width and select bandpass
```

```
2000.00 ENT+ load f-start
```

```
5000.00 ENT+ load f-stop
```

```
-200.00 GSBC load f-increment (a negative value
means linear sweep increments)
```

```
GSBD start sweep:
```

the output is on the next page.

(sweep step size changes were made between output segments)

PROGRAM OUTPUT FOR EXAMPLE 2-13.1						
LOWER STOPBAND		PASSBAND			UPPER STOPBAND	
2000.00 f		5000.0000	10000.0000	f	15000.00	30000.00 f
68.02 A(f) dB		0.0436	0.0434	A(f)	0.04	79.85 A(f)
2200.00		5500.0000	10500.0000		16000.00	31000.00
73.03		0.0020	0.0342		12.98	100.57
2400.00		6000.0000	11000.0000		17000.00	32000.00
98.12		0.0389	0.0115		31.72	82.55
2600.00		6500.0000	11500.0000		18000.00	33000.00
73.25		0.0002	0.0000		52.97	76.47
2800.00		7000.0000	12000.0000		19000.00	34000.00
67.19		0.0248	0.0144		64.35	73.25
3000.00		7500.0000	12500.0000		20000.00	35000.00
64.45		0.0434	0.0389		68.65	71.15
3200.00		8000.0000	13000.0000		21000.00	36000.00
63.90		0.0234	0.0385		77.55	69.63
3400.00		8500.0000	13500.0000		22000.00	37000.00
66.45		0.0016	0.0082		66.70	68.49
3600.00		9000.0000	14000.0000		23000.00	38000.00
84.71		0.0065	0.0090		64.24	67.60
3800.00		9500.0000	14500.0000		24000.00	39000.00
66.03		0.0293	0.0430		63.83	66.89
4000.00			15000.0000		25000.00	40000.00
67.53			0.0436		64.45	66.31
4200.00					26000.00	41000.00
49.19					65.75	65.84
4400.00		NOTE: The display was changed manually to DSP4 for the passband printout, then changed back to DSP2 for the upper stopband output.			27000.00	42000.00
32.55					67.65	65.45
4600.00					28000.00	43000.00
18.89					70.25	65.13
4800.00					29000.00	44000.00
5.63					73.91	64.66
5000.00						45000.00
0.04						64.64

Example 2-13.2

Compute the minimum stopband attenuation of an eleventh order, 20% reflection coefficient, 75 degree modular angle elliptic filter (see p. 326 of Saal and Ulbrich [45]).

Load Program 2-12 and calculate filter order and loss pole locations.

```

1.00 ENT1
.20 X2
-
LOS
10.00 /
CHS
3.1772877 ***

```

} calculate $A_{max} = 10 \log (1 - \rho^2)$

```

GSEH load Amax
100.00 GSEb load dummy Amin large enough to cause "error" halt
1.00 GSEB load normalized passband edge
75.00 D=K
SIN
1/X
1.035276 ***
GSEb load normalized stopband edge

```

} calculate stopband edge from modular angle

```

GSEC start filter order calculation (computes K(k))
ERROR program halt since  $L^{-1}$  is too small

```

ii. GSEc load desired filter order

```

GSEb output loss pole locations and store for next program
2.292241158 ***
1.744326902 ***
1.126546299 ***
1.05117641 ***
1.037519314 ***

```

Load this program (Program 2-13) and calculate filter response.

```

0.000 ENT1 load filter center frequency (lowpass)
1.000 GSEH load bandwidth (normalized for this example)
1.000 GSEb load number of poles at infinity

```

} calculate normalized stopband edge frequency

```

75.000 SIN
1/X
GSEB calculate stopband loss at this frequency
60.006 *** minimum stopband loss in dB (Amin defined at fmin)

```

Program Listing I

001 *LBL0	SETUP LOSS POLE ENTRY	057 *LBL1	
002 1		058 RCL2	
003 3	initialize index register	059 RCL0	test for loop exit
004 ST01		060 PZS	
005 SF2	indicate initialization reqd	061 X<Y?	
006 *LBL0		062 GT0D	
007 R/S	enter normalized loss pole	063 RTN	
008 ISZ1		064 *LBL1	LOAD f, calculate A(f)
009 ST01		065 ST06	temporarily store f
010 GT00		066 F2?	if first time through here,
011 *LBL6	LOAD NINF, the number of	067 GSB8	goto initialization routine
012 ST0D	lowpass loss poles at	068 RCL6	
013 GT06	infinite frequency	069 RCL8	calculate:
014 *LBL6	LOAD P or -Amax	070 RCL6	
015 X<0?	if negative entry, jump	071 ÷	$\Omega = \frac{1}{BW} \left[f - \frac{f_0^2}{f} \right]$
016 GT01		072 -	
017 X2	calculate:	073 ABS	
018 CHS	Amax = 10log (1 - p ²)	074 RCL9	
019 GSB7		075 ÷	
020 *LBL1		076 X=0?	$\Omega = 0$ escape
021 ABS	store Amax	077 RTN	
022 ST00		078 F0?	if bandstop, form inverse
023 GT06	goto space and return	079 1/X	
024 *LBLA	LOAD f ₀ & BW for bandpass	080 EEX	test for passband ($\Omega < 1$)
025 CF0	indicate bandpass	081 CF3	
026 GT01		082 X>Y?	set flag 3 if passband
027 *LBLB	LOAD f ₀ & BW for bandstop	083 SF3	
028 SF0	indicate bandstop	084 XZV	
029 *LBL1	store BW (bandwidth)	085 X2	
030 ST09		086 1/X	form and store:
031 R4		087 -	
032 X2	form and store f ₀ ²	088 ABS	$ Z = \left(\left 1 - \frac{1}{\Omega} \right \right)^{\frac{1}{2}}$
033 ST08		089 JX	
034 GT06	goto space and return	090 ST06	
035 *LBLC	LOAD f-start, f-stop, Δf	091 F3?	jump if in passband
036 PZS	store f-increment (Δf)	092 GT03	
037 ST01		093 EEX	stopband attenuation,
038 R4	store f-stop	094 +	form and store:
039 ST02		095 RCL6	
040 R4	store f-start	096 EEX	$\left[\frac{Z + 1}{Z - 1} \right]^{NINF/2}$
041 ST00		097 -	
042 PZS	restore register order	098 ÷	
043 GT06	goto space and return	099 ABS	
044 *LBLD	START SWEEP	100 RCLD	
045 PZS		101 YX	beginning of L(Z) calc
046 RCL0	recall and print	102 JX	
047 PZS	present frequency	103 ST05	
048 PRTX		104 RCL7	initialize index register
049 GSBE	calculate and print A(f)	105 ST01	
050 PZS	recall frequency increment	106 *LBL2	L(Z) calculation loop
051 RCL1		107 ISZ1	
052 X<0?		108 RCL6	calculate $\frac{Z + Z_1}{Z - Z_1}$
053 ST-0	if increment negative,	109 RCLi	
054 X<0?	use additive delta	110 +	
055 GT01		111 RCL6	
056 STX0	if plus, use product delta	112 RCLi	

REGISTERS

0 Amax	1 e ² /4	2	3	4	5 L	6 scratch	7 "13"	8 f ₀ ²	9 BW
S0 present freq	S1 freq incr	S2 stop freq	S3	S4	S5	S6	S7	S8	S9
				loss pole storage registers					
A ← loss pole storage →		C 10 ⁻⁹		D NINF		E I _{max}		I storage register index	

169	EEX		
170	→R	form $\sin \beta$, and $\cos \beta$	
171	F1?	recall $\sin \beta \rightarrow R_x$ if NINF odd	
172	X≠Y		
173	ENT↑	prepare to double R_x	
174	*LBL5	Output routine; form	
175	+	$\epsilon^2/4 (L+1/L)^2$ if stopband	
176	X ²		
177	RCL1	$\epsilon^2 \frac{\sin^2 \beta}{\cos^2 \beta}$ if passband	
178	x		
179	GSB7	calculate and print	
180	RND	$10 \log(1 + R_x)$	
181	PRTX		
182	*LBL6	space and return subroutine	
183	SPC		
184	RTN		
185	*LBL7	subroutine to calculate:	
186	EEX		
187	+	$10 \log(1 + (\cdot))$	
188	LOG		
189	EEX		
190	1		
191	x		
192	RTN		
193	*LBL8	initialization routine	
194	RCL1	store highest loss pole	
195	STOE	register number	
196	RCL0		
197	EEX	calculate and store:	
198	1		
199	÷		
200	10 ^x	$\frac{\epsilon^2}{4} = \frac{10^{0.1A_{\max}} - 1}{4}$	
201	EEX		
202	-		
203	4		
204	÷		
205	STO1		
206	1	store index register	
207	3	initialization, and	
208	STO7	initialize index register	
209	STO1		
210	*LBL9	loss pole Z transform loop	
211	ISZ1	increment index register	
212	EEX	calculate and store:	
213	RCLi		
214	X ²	$Z_1 = (1 - 1/(p_1)^2)^{\frac{1}{2}}$	
215	1/X	where p_i are the normalized	
216	-	loss pole frequencies	
217	√X		
218	STO1		
219	RCL1	test for loop exit	
220	RCL6		
221	X≠Y?		
222	GT09		
223	RTN	return to main program	

167 GT04		168 RCL5 recall 0		LABELS		FLAGS		SET STATUS							
A BANDPASS		B BANDSTOP		C START SWEEP		D f → A(f)		0 bandstop		FLAGS		TRIG		DISP	
f ₀ BW		f ₀ BW		f ₀ BW		f ₀ BW		1 NINF odd		ON OFF		DEG		FIX	
a loss pole		b load		c load		d		2 init		0		1		2	
entry		NINF		por-Amaz		3 passband		4 L(Z) pass		1		2		3	
0 loss pole		1 local lb1		2 L(Z) stop		3 passband		4 L(Z) band		2		3		4	
ent loop		1 local lb1		2 L(Z) band		3 passband		4 L(Z) band		3		4		5	
5 output		6 space &		7 A(f)		8 init		9 loss pole		3		4		5	
routine		return		A(f)		init		Z xfms		4		5		6	

PROGRAM 2-14 POLE AND ZERO LOCATIONS OF A FILTER WITH CHEBYSHEV PASSBAND AND ARBITRARY STOPBAND LOSS POLE LOCATIONS.

Program Description and Equations Used

This program calculates the complex zero locations of the filter transfer function, $H(s) = E_{in}/E_{out}$, from the loss pole frequencies (frequencies of infinite attenuation). The zero locations are also called the natural modes of $H(s)$. The pole locations of $H(s)$, are the loss pole frequencies and lie on the $j\omega$ axis. The transmission function, $T(s)$, is the reciprocal of the filter transfer function, and may be more familiar to some readers. When active elliptic filters are being designed [35], one approach is to divide the transmission function into bi-quadratic factors with each factor (second order pole pair, and second order zero pair) being synthesized with a separate active network [38].

The loss pole frequencies can be supplied by the user in the case of arbitrary stopband, equiripple passband filters, or can be generated by Program 2-12 for elliptic filters (equiripple stopband and passband).

This program works in the Z-domain to spread out the pole and zero frequencies, and enhance the numerical accuracy of the final output. The s-domain frequencies are Z transformed using Eq. (2-14.1), which is the normalized lowpass form of the more generalized Z transform.

$$Z^2 = 1 + \frac{1}{s^2} \bigg|_{s=j\omega} = 1 - \frac{1}{\omega^2} \quad (2-14.1)$$

The filter transfer function is a rational function, i.e., it is a ratio of polynomials:

$$H(s) = \frac{e(s)}{q(s)} \quad (2-14.2)$$

This transfer function is related to the filter characteristic function, $K(s)$, by the Feldtkeller equation:

$$H(s)H(-s) = 1 + K(s)K(-s) \quad (2-14.3)$$

where the characteristic function has been defined in terms of the Chebyshev rational function, $R(x, L)$, by Eq. (2-12.3), and also is a ratio of polynomials:

$$K(s) = \frac{f(s)}{q(s)} \quad (2-14.4)$$

Expanding the Feldtkeller equation to remove the denominator polynomial, $q(s)$, yields:

$$e(s)e(-s) = q(s)q(-s) + f(s)f(-s) \quad (2-14.5)$$

If the normalized lowpass Z transformation of these s -domain polynomials are defined by:

$$F(Z) \Leftrightarrow f(s)/s^m \quad (2-14.6)$$

$$Q(Z) \Leftrightarrow q(s)/s^m \quad (2-14.7)$$

where

$$m = N_{INF} + N \quad (2-14.8)$$

$$N_{INF} = \text{number of attenuation poles at } \infty \quad (2-14.9)$$

$$N = \text{number of finite loss pole freqs} \quad (2-14.10)$$

then the Z transform equivalent of Eq. (2-14.5) becomes:

$$E(Z)E^*(Z) = Q^2(Z) + F^2(Z) \quad (2-14.11)$$

where

$$E(Z) \Leftrightarrow e(s)/s^m \quad (2-14.11a)$$

$$E^*(Z) \Leftrightarrow e(-s)/s^m \quad (2-14.11b)$$

The derivation of $Q^2(Z)$ and $F^2(Z)$ in terms of the Z transformed loss pole frequencies, Z_1 , is done later and the results brought forward:

$$Q^2(Z) = (1-Z^2)^{N_{INF}} \prod_{i=1}^N (Z^2 - Z_1^2)^2 \quad (2-14.12)$$

$$F^2(Z) = \epsilon^2 (E_v A(Z))^2 \quad (2-14.13)$$

$$A(Z) = (Z + 1)^{N_{INF}} \prod_{i=1}^N (Z + Z_1)^2 \quad (2-14.14)$$

The program Z transforms the loss pole frequencies using Eq. (2-14.1) then forms $E(Z)E^*(Z)$ using Eqs. (2-14.11), (2-14.12), (2-14.13), and (2-14.14). The roots of $E(Z)E^*(Z)$ are found using the secant iteration method (described later), and exist as quads, i.e.:

$$(Z+\sigma+j\omega)(Z+\sigma-j\omega)(Z-\sigma+j\omega)(Z-\sigma-j\omega) = Z^4 + pZ^2 + q \quad (2-14.15)$$

Equation (2-14.1) may be used in reverse to convert Eq. (2-14.15) to the s -domain equivalent. The right half s plane (RHP) poles are assigned to $e(-s)$, and the LHP poles assigned to $e(s)$. These LHP poles represent the natural modes of the filter, and may be defined by a natural frequency, ω_n , and a quality factor, Q :

$$\omega_n = (1 + p + q)^{\frac{1}{2}} \quad (2-14.16)$$

$$Q = \left[2 \left\{ 1 - \left(1 + \frac{p}{2} \right) (1 + p + q) \right\} \right]^{\frac{1}{2}} \quad (2-14.17)$$

The natural frequency and Q represent the program output.

User Instructions

CARD # 1, CARD # 2

TRANSFER FUNCTION ZEROS FROM LOSS POLE LOCATIONS				
				START

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
	NOTE: This program takes loss pole frequencies stored in registers S4 through S8. Program 2-11 automatically stores the loss pole frequencies in these registers. If the loss pole frequencies are provided by the user, they should be loaded before proceeding.			
1	Load both sides of program card one			
2	Start program execution		E	flashing display
3	Insert second card into card reader, this card will be read by the program at the appropriate time. If the card is not inserted, the display will flash when the second card is to be read.			
4	Read both sides of second program card The program execution will automatically resume. If the first program is halted (R/S key) when the display flashes, the second program execution may be resumed by depressing key "E" after the second card loading.			ω_{nN} Q_N space ω_{nN-1} Q_{N-1} \vdots \vdots ω_{n1} Q_1 space σ_o (if odd)

Example 2-14.1

Find the natural modes for the elliptic filter given in Example 2-12.2.

Load Program 2-11 and calculate loss pole frequencies.

```

1.00 ENT1
.20 X2
-
LOG
10.00 X
CHS
DSP6
0.177288 ***
DSP2
GSBA
78.00 GSBA
1.00 GSBB
2.00 GSBB
GSBC
5.90 ***
6.00 ***
GSBD
7.235803+00 ***
2.732051+00 ***
2.061105+00 ***
2.922132+00 ***
2.129549+00 ***

```

} convert 20% reflection coefficient into
 passband ripple in dB using:
 $A_{p\text{dB}} = -10\log(1-\rho^2)$
 } $A_{p\text{dB}}$, passband ripple in dB
 } load stopband attenuation reqd, $A_{s\text{dB}}$
 } load normalized cutoff frequency
 } load normalized minimum stopband frequency
 } calculate minimum filter order
 } calculated filter order
 } nearest integral filter order
 } calculate loss pole frequencies
 } untransformed even order
 } loss pole frequencies
 } Möbius transformed loss pole frequencies

Load this program (Program 2-14) and calculate the natural modes.

```

GSBE start E(Z)E*(Z) calculation
0.83278696 ***
1.57099957 ***
1.03809259 ***
5.89989183 ***
0.50679327 ***
0.62665941 ***

```

$\left. \begin{matrix} \omega_{n_1} \\ Q_1 \\ \omega_{n_2} \\ Q_2 \\ \omega_{n_3} \\ Q_3 \end{matrix} \right\}$ complex zero locations describing
 natural modes

The complex zero locations may be converted from the ω_n and Q description to real and imaginary parts to enable checking results against elliptic filter tables (see p. 248 of Zverev [58]). Equations (2-9.1), (2-9.2), and (2-9.3) are used for the conversion.

1.57099957	ENT↑	load Q_1 and calculate θ_1
	+	
	1/X	
	COS ⁻¹	
71.44174416	***	θ_1 (degrees)
.83278696	→R	load ω_{n1} and calculate real and imag parts
0.26505003	***	σ_1
	X↑↑	
0.78948249	***	ω_1
<hr/>		
5.89989189	ENT↑	load Q_2 and calculate θ_2
	+	
	1/X	
	COS ⁻¹	
85.13850531	***	θ_2 (degrees)
1.03809259	→R	load ω_{n2} and calculate real and imag parts
0.08797556	***	σ_2
	X↑↑	
1.03435603	***	ω_2
<hr/>		
.62665941	ENT↑	load Q_3 and calculate θ_3
	-	
	1/X	
	COS ⁻¹	
37.07171837	***	θ_3 (degrees)
.50079327	→R	load ω_{n3} and calculate real and imag parts
0.39957373	***	σ_3
	X↑↑	
0.30188530	***	ω_3

Derivation of Equations Used

The characteristic function, $K(s)$, is a ratio of polynomials as indicated by Eqs. (2-14.4) and (2-12.3). The denominator of this function is already known in terms of the loss pole frequencies. In low-pass form, this polynomial is:

$$q(s) = \prod_{i=1}^N (s^2 + \omega_i^2) \quad (2-14.18)$$

$H(s)$, the filter transfer function, is described in terms of the polynomials of the characteristic function by Eqs. (2-14.2) and (2-14.5). Since $H(s)$ describes a realizable transfer function, the zeros of $H(s)$ must lie in the LHP. With this condition in mind, the LHP zeros of $e(s)$ $e(-s)$ are assigned to $e(s)$ and the RHP zeros assigned to $e(-s)$. This root splitting brings us to the concept of a quad. Assume that $e(s)$ is represented by complex conjugate root pairs and a real root if $e(s)$ is odd, i.e.,

$$e(s) = (s + \sigma_o) \prod_{i=1}^N \{s^2 + s(2\sigma_i) + \sigma_i^2 + \omega_i^2\} \quad (2-14.19)$$

Then the right half s -plane roots are represented by $e(-s)$:

$$e(-s) = (-s + \sigma_o) \prod_{i=1}^N \{s^2 - s(2\sigma_i) + \sigma_i^2 + \omega_i^2\} \quad (2-14.20)$$

hence:

$$e(s) e(-s) = (-s^2 + \sigma_o^2) \prod_{i=1}^N \{s^4 + s^2 2(\omega_i^2 - \sigma_i^2) + (\omega_i^2 + \sigma_i^2)^2\} \quad (2-14.21)$$

This concept is illustrated in Fig. 2-14.1.

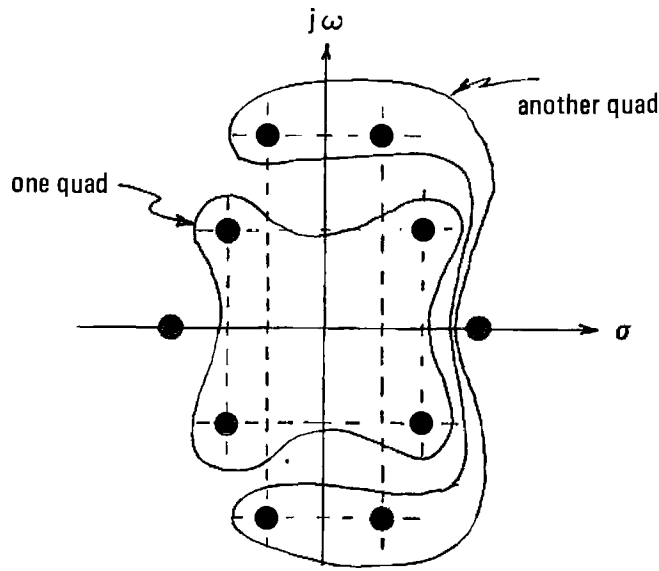


Figure 2-14.1 Concept of a quad.

The importance of this concept is once one root of $e(s) e(-s)$ is found, three other roots of the quad are also defined, and may be removed to reduce the order of $e(s) e(-s)$ by four.

The Characteristic Function in Terms of the Transformed Variable

The actual finding of the polynomials of $H(s)$ is done in the Z -plane rather than the s -plane for two reasons: 1) The solution is numerically more accurate because the roots are spread out and the small difference between big numbers problem is much reduced. 2) The expressions for $F^2(Z)$ and $Q^2(Z)$ are much simpler in terms of the transformed loss pole frequencies than are $f^2(s)$ and $q^2(s)$ in terms of the actual loss pole frequencies, ω_i . These transformations are defined as follows:

$$F(Z) \Leftrightarrow \frac{f(s)}{(s^2 + \omega_a^2)^{m/2}} \quad (2-14.22)$$

$$Q(Z) \Leftrightarrow \frac{q(s)}{(s^2 + \omega_a^2)^{m/2}} \quad (2-14.23)$$

where

$$Z^2 = \frac{s^2 + \omega_b^2}{s^2 + \omega_a^2} \quad (2-14.24)$$

and

$$m = N_{ZERO} + N_{INF} + N \quad (2-14.25)$$

$$N_{ZERO} = \text{number of attenuation poles at dc} \quad (2-14.26) \\ (\text{equals zero for lowpass filters})$$

$$N_{INF} = \text{number of attenuation poles at infinity} \quad (2-14.9)$$

$$N = \text{number of finite loss pole frequencies} \quad (2-14.10)$$

In the normalized lowpass case, the lower bandedge transformation frequency, ω_a is dc ($\omega_a = 0$), and the upper bandedge transformation frequency, ω_b , is unity. Under these conditions the Z transformation becomes:

$$F(Z) \Leftrightarrow \frac{f(s)}{s^m} \quad (2-14.6)$$

$$Q(Z) \Leftrightarrow \frac{q(s)}{s^m} \quad (2-14.7)$$

with

$$Z^2 = 1 + 1/s^2, \text{ or for } s = j\omega, Z^2 = 1 - 1/\omega^2$$

The lowpass form of $q(s)$ is given by Eq. (2-14.18):

$$q(s) = \prod_{i=1}^N (s^2 + \omega_i^2)$$

The Z transformed equivalent is:

$$Q(Z) \Leftrightarrow \frac{1}{s^m} \prod_{i=1}^N (s^2 + \omega_i^2) \quad (2-14.27)$$

$$= \frac{1}{s^{N_{INF}}} \prod_{i=1}^N \left(\frac{s^2 + \omega_i^2}{s^2} \right) \quad (2-14.28)$$

The filter poles can be found from the zeros of the attenuation function, Eq. (2-13.5), i.e.,

$$1 + \frac{\epsilon^2}{4} \left\{ L(Z) + \frac{(-1)^{NINF}}{L(Z)} \right\}^2 = 0 \quad (2-14.29)$$

where $L(Z)$ is defined by Eq. (2-13.4):

$$L(Z) = \left\{ \frac{Z+1}{Z-1} \right\}^{\frac{NINF}{2}} \cdot \prod_{i=1}^N \frac{Z + Z_i}{Z - Z_i} \quad (2-13.4)$$

then $Q(Z)$, as defined by Eq. (2-14.28), is the common denominator for Eq. (2-14.29). The quantity inside the brackets of Eq. (2-14.29) can be written in terms of $Q(Z)$ and $A(Z)$ (Eq. (2-14.14)) as follows:

$$L(Z) + \frac{(-1)^{NINF}}{L(Z)} = \frac{A(Z) + (-1)^{NINF} \cdot A(-Z)}{Q(Z)} \quad (2-14.30)$$

Fortunately, the sign of $(-1)^{NINF}$ causes the numerator to be an even polynomial in Z as is required for the resulting polynomials of the Chebyshev rational function to be Hurwitz.

Thus, the equation whose zeros are to be found is:

$$1 + \frac{\epsilon^2}{4} \left\{ \frac{A(Z) + (-1)^{NINF} \cdot A(-Z)}{Q(Z)} \right\}^2 = 0 \quad (2-14.31)$$

Because of the even numerator polynomial, Eq. (2-14.31) becomes:

$$1 + \frac{\epsilon^2}{4} \left\{ \frac{2 \cdot \text{Ev} (A(Z))}{Q(Z)} \right\}^2 = 0 \quad (2-14.32)$$

Cancelling out constants and placing the entire expression over a common denominator yields:

$$Q^2(Z) + \epsilon^2 \left\{ \text{Ev} A(Z) \right\}^2 = 0 \quad (2-14.33)$$

Substituting $F(Z)$ from Eq. (2-14.13) results the desired expression for the transfer function zeros:

$$Q^2(Z) + F^2(Z) = 0 \quad (2-14.34)$$

Secant iteration method

The secant iterative method finds the values for the variable, x , where the function $f(x) = 0$ (zeros of x). It is similar to the

Newton-Raphson method except the derivative of the function is numerically approximated from the present and past values of $f(x)$:

$$x_{i+1} = x_i - f(x_i) \left\{ \frac{x_i - x_{i-1}}{f(x_i) - f(x_{i-1})} \right\} \quad (2-14.35)$$

where x_i is the present estimate for the variable.

The iteration is continued until the correction term magnitude becomes smaller than a given error radius. For this program, that error radius is chosen to be 10^{-9} .

Two values for x are needed to start the secant iteration, a past value and a present value. In this program, the past value is chosen as 0 and the present value as 1460° . As the iteration starts, the method may not converge, but may get sent far away from the desired solution. This can happen if the present and past estimates lie on opposite sides of a saddle (see Fig. 2-14.3). To help force convergence, the magnitude of the correction radius is limited to 0.1. When the iteration starts, the estimates have a random nature, but can't get far away from the origin. As a zero is approached, the method rapidly converges.

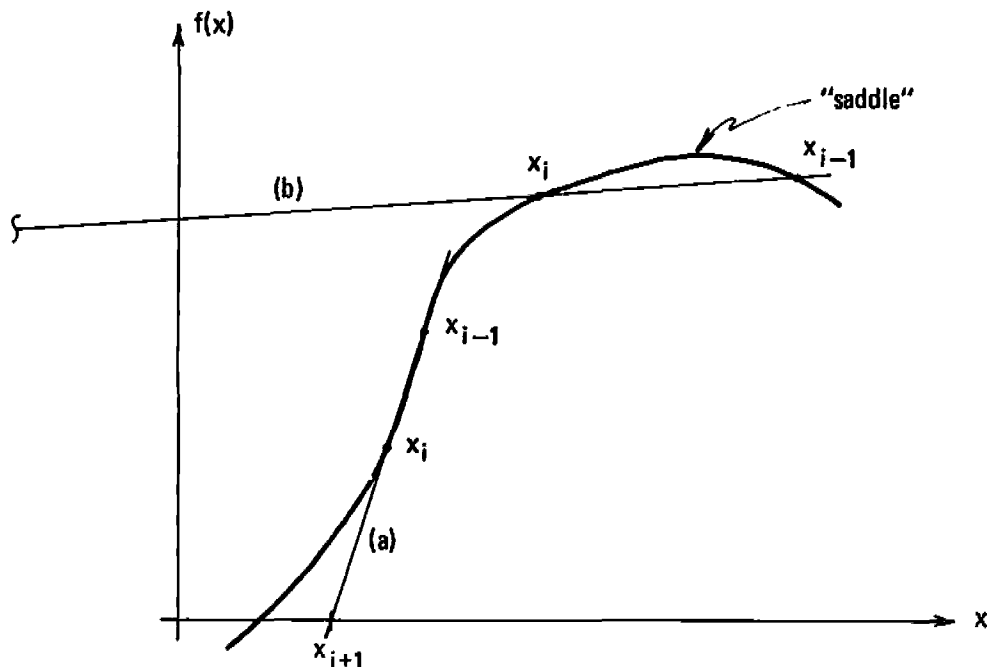


Figure 2-14.3 Secant method, two cases a) normal convergence, and b) divergence caused by the presence of a "saddle" in the function.

Figure 2-14.3 shows a two dimensional representation of the method, but in the present instance, the application is three dimensional because of the complex nature of the variable. As each complex zero is found, three others are defined automatically because of the quadrangle symmetry (quads) in the zeros of the filter transfer function (see Fig. 2-14.1), thus the order of the equation may be reduced by four through polynomial division. If the filter order is odd, a real zero exists in the transfer function. After all quads have been removed from the transfer function, the remainder will be the real zero. This technique is used herein, zeros are removed from $E(Z)E^*(Z)$ until a second order polynomial or less remains. If the filter order is even, no remainder exists, but if the filter order is odd, the second order remainder represents the LHP and RHP parts of the real zero. The RHP zero is discarded since it belongs to $H(-s)$, and the LHP zero location is transformed back to the s -domain for output.

Program Listing I

ALGORITHM TO FORM $E(Z)E^*(Z)$
FROM $F^2(Z) + Q^2(Z)$

001 *LBL1	START	057 RCLP	
002 RCL1	store index number of	058 X#Y?	test for loop exit
003 STOB	highest register w/ coeffs	059 GT01	
004 RCL0		060 CLX	start A(Z) calculation
005 EEX		061 STOA	
006 1	calculate ϵ^2	062 3	initialize index register
007 =		063 STOI	
008 10*	$\epsilon^2 = 10^{0.1\epsilon dB} - 1$	064 P*S	place $Q^2(Z)$ in secondary regs
009 EEX		065 EEX	initialize polynomial
010 -		066 STOB	product registers
011 RCLD		067 RCLB	
012 +	store NINF + ϵ^2	068 EEX	reduce highest loss pole
013 STOD		069 1	register number by 10 to
014 1		070 -	reflect P*S of registers
015 3	initialize index register	071 STOB	
016 STOI		072 *LBL2	A(Z) calculation loop start
017 *LBL0	Z transform loss pole freqs	073 ISZI	
018 ISZI		074 RCL1	$A(Z) = (Z+1)^{NINF} \prod_{i=1}^N (Z+Z_i)^2$
019 EEX		075 JX	$Z_i \rightarrow R_c$
020 RCL1		076 STOC	
021 X2	$Z_1^2 = 1 - 1/\omega_i^2$	077 GSB9	multiply existing polynomial
022 1/X		078 GSB9	product by $(Z + Z_1)^2$
023 -		079 RCL1	
024 STOI		080 RCLB	test for loop exit
025 RCL1		081 X#Y?	
026 RCLB	test for loop exit	082 GT02	
027 X#Y?		083 EEX	setup to form $(Z+1)^{NINF}$
028 GT00		084 STOC	
029 RCLD	set flag 2 if NINF = 2	085 GSB9	multiply existing polynomial
030 INT		086 F0?	by $(Z+1)^{NINF}$, (NINF = 1 or 2)
031 2		087 GSB9	
032 CF0		088 EEX	calculate highest register
033 X=Y?		089 RCLB	number containing polynomial
034 SF0		090 RCLB	coefficients:
035 EEX	start $Q^2(Z)$ calculation:	091 +	
036 STOA		092 5	
037 CHS		093 +	$2B + 10 + F0 \rightarrow RB$
038 STOC	form and store $(1 - Z^2)^{NINF}$	094 F0?	
039 F0?	for NINF = 1 or 2	095 +	
040 CHS		096 STOB	
041 STOI		097 STOI	initialize index register
042 CHS		098 *LBL3	
043 STOB		099 ISZI	clear registers not contain-
044 F0?		100 CLX	ing polynomial coefficients
045 GSB9		101 STOI	
046 1		102 P*S	
047 3	initialize index register	103 STOI	
048 STOI		104 P*S	
049 *LBL1	$Q^2(Z)$ calculation loop	105 RCL1	
050 ISZI		106 1	
051 RCL1		107 9	test for loop exit
052 CHS		108 X#Y?	
053 STOC	$Q^2(Z) = (1 - Z^2)^{NINF} \prod_{i=1}^N (Z^2 - Z_i^2)^2$	109 GT03	
054 GSB9		110 RCL0	form $(Ev A(Z))^2$:
055 GSB9	$-Z_i^2 \rightarrow R_c$	111 RCL2	
056 RCL1		112 x	

REGISTERS									
⁰ Q ₀ , A ₀ , A ₀	¹ Q ₁ , A ₁ , A ₂	² Q ₂ , A ₂ , A ₄	³ Q ₃ , A ₃ , A ₆	⁴ Q ₄ , A ₄ , A ₈	⁵ Q ₅ , A ₅ , A ₁₀	⁶ Q ₆ , A ₆ , A ₁₂	⁷ Q ₇ , A ₇ , A ₁₄	⁸ Q ₈ , A ₈ , A ₁₆	⁹ Q ₉ , A ₉ , A ₁₈
^{S0} Q ₀ , F ₀	^{S1} Q ₁ , F ₁	^{S2} Q ₂ , F ₂	^{S3} Q ₃ , F ₃	^{S4} Q ₄ , F ₄ , Z ₁	^{S5} Q ₅ , F ₅ , Z ₂	^{S6} Q ₆ , F ₆ , Z ₃	^{S7} Q ₇ , F ₇ , Z ₄	^{S8} Q ₈ , F ₈	^{S9} Q ₉ , F ₉
^A Q & F index	^B highest reg. number used	^C Z ₁ ²	^D $\epsilon^2 + NINF$	^E Z index	^I index				

Program Listing II

113	ST01	$A_2' = 2A_0A_2$	169	9	initialize index register
114	ST+1		170	ST01	
115	RCL0		171	*LBL4	
116	RCL6	(NOTE: the primed coefs	172	DSZI	form $E(Z)E^*(Z)$
117	x	represent the coefs of	173	SF2	
118	RCL2	$A^2(Z)$. After this part	174	RCLi	$E(Z)E^*(Z) = Q^2(Z) + F^2(Z)$
119	RCL4	of the program is done	175	P+S	
120	x	the coefficients of	176	ST+i	
121	+	$A^2(Z)$ have replaced the	177	P+S	
122	ST03	coefficients of $A(Z)$.)	178	FZ?	test for loop exit
123	ST+3	$A_6' = 2(A_0A_6 + A_2A_4)$	179	GT04	
124	RCL2		180	*LBL5	
125	RCL8		181	PSE	wait loop for 2nd card read
126	x		182	GT05	
127	RCL4	$A_{10}' = 2(A_2A_8 + A_4A_6)$	183	*LBL7	$A^2(Z)$ calculation subr
128	RCL6		184	RCLi	forms:
129	x		185	ST+i	
130	+		186	R↓	$R(1)^2 + 2(Rx)$, and returns
131	ST05		187	ST+i	
132	ST+5		188	ST+i	$R(1) \rightarrow Rx$
133	RCL6		189	R↑	
134	RCL8		190	DSZI	
135	x	$A_{14}' = 2A_6A_8$	191	DSZI	
136	ST07		192	RTN	
137	ST+7		193	RTN	
138	6	initialize index register	194	*LBL9	polynomial multiplication
139	ST01		195	SF2	flag 2 indicates 1st time
140	RCL8	$A_{16}' = A_8^2$	196	RCLA	initialize index register
141	STx8		197	XZ1	with Q or F index
142	RCL4		198	STOE	save existing index
143	x	$A_{12}' = A_6^2 + 2A_4A_8$	199	*LBL8	polynomial mult loop
144	GSB7		200	RCLi	
145	RCL2		201	ISZI	
146	x		202	RCLC	$a_{k+1} = C \cdot a_{k+1} + a_k$
147	RCL8		203	FZ?	$C = 0$ for $k = n$
148	JX	$A_8' = A_4^2 + 2(A_2A_6 + A_0A_8)$	204	CLX	
149	RCL0		205	STx;	
150	x		206	R↓	
151	+		207	ST+i	
152	GSB7		208	CF1	decrement I register, and
153	RCL0		209	DSZI	set flag 1 if $I \neq 0$
154	x	$A_4' = A_2^2 + 2A_0A_4$	210	SF1	
155	GSB7		211	DSZI	decrement I register
156	RCL0	$A_0' = A_0^2$	212	F1?	
157	STx0		213	GT08	test for loop exit
158	RCLD	recall ϵ^2	214	RCLC	finish poly multiplication
159	FRC		215	STx0	$a_0 = C \cdot a_0$
160	STx0		216	RCLC	restore pre-existing index
161	STx1	form $F^2(Z) = \epsilon^2(Ev(A(Z)))^2$	217	ST01	
162	STx2		218	RCLA	increment F or Q index
163	STx3		219	EEX	
164	STx4		220	+	
165	STx5		221	ST0A	
166	STx6		222	RTN	return to main program
167	STx7				
168	STx8				

LABELS					FLAGS	SET STATUS		
A	B	C	D	E START	0 NINF = 2	FLAGS	TRIG	DISP
a	b	c	d	e	1	ON OFF		
0 Z_1 calo	1 $Q^2(Z)$	2 $A(Z)$	3 clear unused reg	4 $E(Z)E^*(Z)$	2 $I = 0$	0 <input type="checkbox"/>	DEG	FIX <input type="checkbox"/>
5 wait loop	6	7 $F^2(Z)$ subr	8 poly multiply	9 poly multiply	3	1 <input type="checkbox"/>	GRAD	
						2 <input type="checkbox"/>	RAD	n 2
						3 <input type="checkbox"/>		

Program Listing I

SECANT ITERATION TO FIND
ROOTS OF $E(Z)E^*(Z)$

001	*LBLE	START SECANT ITERATION	056	RCLD	continue complex multiply
002	EEX		057	X	
003	CHS	set correction radius for	058	-	$(a + jb)(\text{Re}(Z^2) + j\text{Im}(Z^2)) =$
004	9	loop exit	059	RCL6	$a \cdot \text{Re}(Z^2) - b \cdot \text{Im}(Z^2) +$
005	STOE		060	RCLD	$j(a \cdot \text{Im}(Z^2) + b \cdot \text{Re}(Z^2))$
006	*LBLE	secant outer loop start	061	X	
007	CLX		062	RCL7	
008	STO0	set $Z_0 = 0 + j0$	063	RCLC	
009	STO1		064	X	
010	STO5		065	+	
011	PZS		066	STO7	
012	RCL0	set $F(Z_0) = E_0 + j0$	067	RJ	
013	PZS		068	STO6	
014	STO4		069	STO1	
015	6	set $Z_1 = 1 \angle 60^\circ$	070	*LBL2	form Z estimate correction:
016	0		071	RCL7	
017	ENT↑		072	RCL6	
018	EEX		073	→P	
019	→R		074	STO8	$\Delta Z_k = F(Z_k) \left[\frac{Z_k - Z_{k-1}}{F(Z_k) - F(Z_{k-1})} \right]$
020	STO2		075	XZY	
021	XZY		076	STO9	
022	STO3		077	RCL3	
023	*LBL0	prepare for polynomial	078	RCL1	
024	RCL2	evaluation;	079	-	
025	RCL3		080	RCL2	
026	X	form $Z^2 = (\sigma - j\omega)^2$;	081	RCL0	
027	ENT↑		082	-	
028	+		083	→P	
029	STO0	$\text{Im}(Z^2) = 2\sigma\omega \rightarrow R_D \rightarrow R_7$	084	STX8	
030	STO7		085	XZY	
031	RCL2		086	ST+9	
032	X ²		087	RCL7	
033	RCL3	$\text{Re}(Z^2) = \sigma^2 - \omega^2 \rightarrow R_0 \rightarrow R_6$	088	RCL5	
034	X ²		089	-	
035	-		090	RCL6	
036	STOC		091	RCL4	
037	STO6		092	-	
038	RCLB	set index to highest register	093	→P	
039	STO1	number that has coefficients	094	X=0?	escape if $F(Z_k) - F(Z_{k-1}) = 0$
040	RCL7	start polynomial evaluation	095	STO3	
041	STX6	by forming $E_{2n} \cdot Z^2$	096	ST=8	finish ΔZ_k calculation
042	STX7		097	XZY	
043	*LBL1	polynomial eval loop start,	098	ST-9	
044	DSZ1	decrement register index	099	RCL7	shift register contents,
045	RCL7	recall E_{2k}	100	STO5	Z_k becomes Z_{k-1} , and
046	ST+6	add to calculation real part	101	RCL6	$F(Z_k)$ becomes $F(Z_{k-1})$ for
047	RCL1		102	STO4	the next iteration
048	EEX	test for loop exit	103	RCL3	
049	1		104	STO1	
050	X=Y?		105	RCL2	
051	STO2		106	STO0	
052	RCL6	perform complex multiply	107	RCL8	recall $ \Delta Z_k $
053	RCLC	by Z^2 on the ongoing	108	.	limit $ \Delta Z_k $ to 0.1 to help
054	X	calculation	109	1	ensure convergence
055	RCL7		110	XZY?	

REGISTERS									
0	Re Z_{k-1}	1	Im Z_{k-1}	2	Re Z_k	3	Im Z_k	4	Re $F(Z_{k-1})$
5	Im $F(Z_{k-1})$	6	Re $F(Z_k)$	7	Im $F(Z_k)$	8	scratch	9	scratch
S0	E_0	S1	E_2	S2	E_4	S3	E_6	S4	E_8
S5	E_{10}	S6	E_{12}	S7	E_{14}	S8	E_{16}	S9	E_{18}
A	B highest register #			C	Re(Z_k^2)		D	Im(Z_k^2)	
							E	error radius for loop exit	
								I index	

PROGRAM 2-15 DARLINGTON'S ELLIPTIC FILTER ALGORITHMS.

Program Description and Equations Used

This program calculates the normalized transmission function pole and zero locations, and minimum stopband rejection for odd order elliptic filters. The program is based on Professor Sidney Darlington's paper which describes simple elliptic filter algorithms using transformations on elliptic sines and their moduli [18], and his unpublished HP-65 program on the same subject.

The output data is normalized to the passband cutoff frequency (f_p), however, the algorithm is normalized to the geometric mean of the passband and stopband edge frequencies as shown by Fig. 2-15.1.

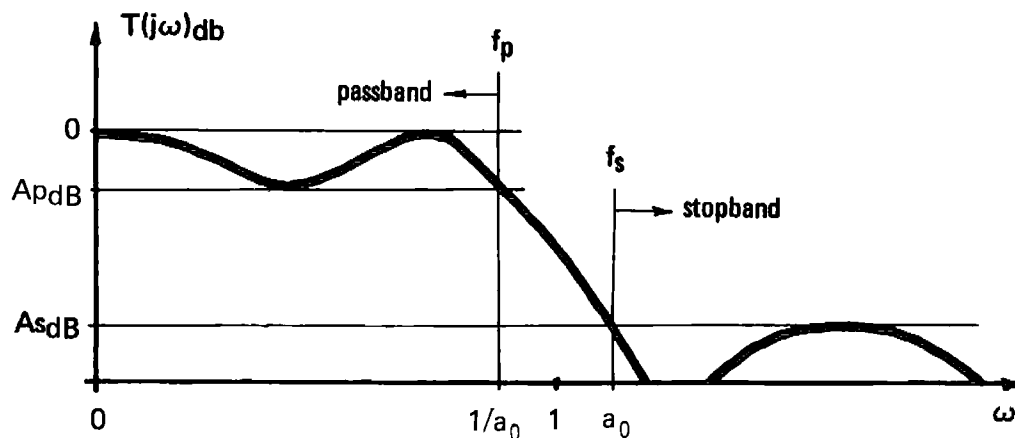


Figure 2-15.1 Definition of elliptic filter terms.

Thus, the transition ratio, λ , becomes:

$$\lambda = \frac{f_s}{f_p} = \frac{a_0}{1/a_0} = a_0^2 \quad (2-15.1)$$

or

$$a_0 = \sqrt{\lambda} \quad (2-15.2)$$

The filter transmission function, $T(s)$, is the reciprocal of the filter transfer function, $H(s)$, which is related to the filter characteristic function, $K(s)$, through the Feldtkeller equation:

$$|T(j\omega)|^2 = \frac{\text{power out}}{\text{power in}} = \left| \frac{1}{H(j\omega)} \right|^2 = \frac{1}{1 + \epsilon^2 |K(j\omega)|^2} \quad (2-15.3)$$

where the characteristic function is the Chebyshev rational function described in Program 2-12. Darlington's algorithms are a very elegant way of approximating the Chebyshev rational function using simple recursive relationships. These relationships can also be used to find the LHP poles and zeros of:

$$T(s)T(-s) = \frac{1}{1 + \epsilon^2 K(s)K(-s)} \quad (2-15.4)$$

Normalized transmission zero frequencies. If Y_0 represents geometrically normalized frequency (Fig. 2-15.1) and Y_{0k} ($k = 1, 2, \dots, \frac{n-1}{2}$) represents the normalized transmission zero frequencies where n is the filter order, then the characteristic function for odd order, equi-ripple passband, lowpass filters is given by:

$$|K(Y_0)|^2 = |J_0 \cdot F_0(Y_0)|^2 \quad (2-15.5)$$

where J_0 is a constant and

$$F_0(Y_0) = Y_0 \prod_{k=1}^{(n-1)/2} \frac{1 - Y_{0k}^2 Y_0^2}{Y_0^2 - Y_{0k}^2} \quad (2-15.6)$$

For the elliptic filter case (equal ripple passband and stopband):

$$\epsilon^2 = 10^{0.1A_{p\text{dB}}} - 1 \quad (2-15.7)$$

$$J_0 = F_0(a_0) \quad (2-15.8)$$

$$F_0\left(\frac{1}{Y_0}\right) = \frac{1}{F_0(Y_0)} \quad (2-15.9)$$

These quantities and Y_{0k} may be found through recursive use of a variable transformation which spreads out the transition interval.

$$\text{Let } a_{k+1} = a_k^2 + \sqrt{a_k^4 - 1} \quad (2-15.10)$$

then, given a_0 as defined by Eq. (2-15.2), find and store a_1 , a_2 , a_3 , and a_4 . Four applications of the recursion formula will provide precision which will be calculator limited rather than algorithm limited (see p. 37 of [18]).

Let h represent the index for the transmission zero frequencies; $h = 1, 2, \dots, (n-1)/2$, then let

$$Y_{4h} = \frac{a_4}{\cos\{(2h-1)(90/n)\}} \quad (2-15.11)$$

and recursively calculate:

$$Y_{(k-1)h} = \frac{1}{2a_k} (Y_{kh} - 1/Y_{kh}) \quad (2-15.12)$$

$$k = 4, 3, 2, 1$$

The transmission zero frequencies normalized with respect to the pass-band edge are:

$$a_0 \cdot Y_{0h} \quad (2-15.13)$$

Minimum stopband rejection. The minimum stopband rejection for elliptic filters first occurs at the stopband frequency edge (geometrically normalized frequency a_0) and may be found from J_0 and Eqs. (2-15.4), (2-15.5), and (2-15.8), i.e.:

$$As_{dB} = 10 \log (1 + e^{2J_0^2 J_0^2}) \quad (2-15.14)$$

J_0 is found from another recursion relationship; let

$$J_4 \cong 2^{n-1}, \quad a_4^n = \frac{(2 \cdot a_4)^n}{2} \quad (2-15.15)$$

then recursively calculate and store J_k 's using:

$$J_{k-1} = \frac{1}{2} \sqrt{(J_k - 1/J_k)} \quad (2-15.16)$$

$$k = 4, 3, 2, 1$$

Transmission function pole locations. Let s_{oh} represent the complex pole location, and let

$$J_o \cdot s_{oo} = 1/\varepsilon \quad (2-15.17)$$

Then recursively calculate:

$$s_{(k+1)o} = J_k \cdot s_{ko} + \sqrt{(J_k \cdot s_{ko})^2 + 1} \quad (2-15.18)$$

$k = 0, 1, 2$

As the index increases, the terms $J_k \cdot s_{ko}$ become numerically very large since the J_k 's increase nearly geometrically for J_k large. To avoid numeric overflow (10^{99}) use:

$$s_{4o} \approx 2 \cdot J_3 \cdot s_{3o} \quad (2-15.19)$$

Calculate and store:

$$s_{5o} = \left\{ \frac{J_4}{s_{4o}} + \sqrt{\left(\frac{J_4}{s_{4o}} \right)^2 + 1} \right\}^{\frac{1}{n}} \quad (2-15.20)$$

To calculate the pole locations, let:

$$s_{5h} = s_{5o} \cdot e^{jh(\pi/n)} \quad (2-15.21)$$

$h = 0, 1, 2, \dots, (n-1)/2$

Using complex arithmetic, recursively calculate:

$$s_{(k-1)h} = \frac{1}{2 \cdot a_{k-1}} (s_{kh}^{-1} / s_{kh}) \quad (2-15.22)$$

$k = 5, 4, 3, 2, 1$

The pole locations normalized to the passband edge are given by:

$$s_{oh} \cdot a_o \quad (2-15.23)$$

The subroutine that calculates Eq. (2-15.22) may seem obscure to some readers. The particular coding that is used minimizes the amount of data that must undergo polar-to-rectangular and rectangular-to-polar conversions, and hence, maximizes the numerical accuracy of the routine. The normal format for the pole locations is polar as given by Eq. (2-15.21). In general, let:

$$s_{kh} = \rho_{kh} \cdot e^{j\beta_{kh}} \quad (2-15.24)$$

In rectangular format, Eq. (2-15.24) becomes:

$$s_{kh} = \rho_{kh} \cos \beta_{kh} + j \rho_{kh} \sin \beta_{kh} \quad (2-15.25)$$

For the reciprocal case, let:

$$\frac{1}{s_{kh}} = \frac{1}{\rho_{kh}} e^{-j\beta_{kh}} \quad (2-15.26)$$

which using rectangular format becomes:

$$\frac{1}{s_{kh}} = \frac{1}{\rho_{kh}} \cos \beta_{kh} - j \frac{1}{\rho_{kh}} \sin \beta_{kh} \quad (2-15.27)$$

hence,


$$s_{kh} - \frac{1}{s_{kh}} = \left(\rho_{kh} + \frac{1}{\rho_{kh}} \right) \cos \beta_{kh} + j \left(\rho_{kh} - \frac{1}{\rho_{kh}} \right) \sin \beta_{kh} \quad (2-15.28)$$

or,

$$s_{kh} - \frac{1}{s_{kh}} = \left(1 + \frac{1}{\rho_{kh}^2} \right) \rho_{kh} \cos \beta_{kh} + j \left(1 - \frac{1}{\rho_{kh}^2} \right) \rho_{kh} \sin \beta_{kh} \quad (2-15.29)$$

In Eq. (2-15.29), the terms $\rho_{kh} \cos \beta_{kh}$ and $\rho_{kh} \sin \beta_{kh}$ are the output components of a polar-to-rectangular conversion, and ρ_{kh} is saved in the last x register, and has not undergone any conversion. The stack is used to hold the intermediate parts of Eq. (2-15.29). A rectangular-to-polar conversion then completes the subroutine.

User Instructions

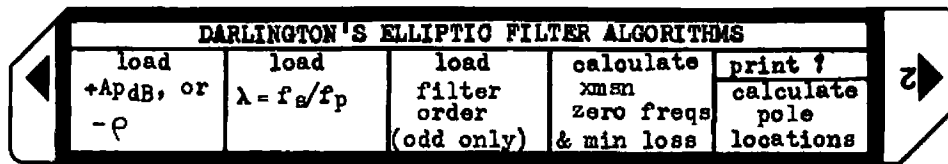

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card			
2	Select print or R/S option (toggle)		<div>f E</div> <div>f E</div> <div>f E</div>	0 (R/S) 1 (print) 0 (R/S) :
3	Load passband ripple in dB or reflection coefficient	ApdB P	<div>A</div> <div>chs A</div>	ϵ^2 ϵ^2
4	Load stopband to passband frequency ratio	λ	B	
5	Load filter order (must be odd)	n	0	
6	Calculate normalized transmission zero frequencies and minimum stopband loss		<div></div> <div>D</div>	Ω_1 Ω_2 : Ω_{n-1} $A_{s\text{dB}}$
7	Calculate real and imaginary parts of normalized transmission function poles		E	Re s_{o1} Im s_{o1} Re s_{o2} Im s_{o2} : : Re s_{on} Im s_{on}

Example 2-15.1

Find the transmission function poles and zeros for a 9th order, elliptic filter having a 85° modular angle, and 50% reflection coefficient. Also calculate the minimum stopband attenuation in dB. Compare the results to the output of Program 2-11.

PROGRAM 2-15 INPUT	PROGRAM 2-15 OUTPUT
<pre> -1.5 GSBA load - ρ 85. SIN calculate 1% and load λ 1.003819836+00 *** GSBE 9. GSBC load n, the filter order </pre>	<pre> GSBD calc xmsn 0's 1.004553794+00 *** z₁ 1.014264420+00 *** z₂ 1.071140576+00 *** z₃ 1.449931830+00 *** z₄ 33.62429965+00 *** As_{dB} min GSBE calc xmsn fcn poles 372.8205714-03 *** Re p₀ 0.000000000+00 *** Im p₀ 182.7207935-03 *** Re p₁ 739.3062101-03 *** Im p₁ 41.73031846-03 *** Re p₂ 351.6234634-03 *** Im p₂ 7.869871962-03 *** Re p₃ 992.6118076-03 *** Im p₃ 1.191142421-02 *** Re p₄ 999.9098960-03 *** Im p₄ </pre>

Load Program 2-12 and calculate transmission zeros (loss poles) for the same conditions.

PROGRAM 2-12 INPUT	PROGRAM 2-12 OUTPUT
1. ENT1 .5 X ² - calculate LOG and load 10. x Ap _{dB} for CHS 50% refl 1.249387366+00 *** coef GSB _A	GSB _C calculate filter order 8.352734615+00 *** calc order 9.000000000+00 *** integral order to meet specs
30. GSB _A load As _{dB} 1. GSB _B load f _p	GSB _D calculate xmsn zero freq's 1.449931802+00 *** z ₄ 1.071140568+00 *** z ₃ 1.014284418+00 *** z ₂ 1.004553794+00 *** z ₁
65. SIN calculate and 1/X load f _s for 1.003815838+00 *** 85° modular GSB _k angle	

Comparing these results to those obtained from Program 2-15, differences exist in the 9th and 10th places sometimes. It is the author's opinion that the output from Program 2-12 is accurate to 2 parts in 10¹⁰, since the elliptic sine algorithm and complete elliptic integral algorithm have been checked against the elliptic function tables in Abramowitz and Stegun [1] and disagree by at most one in the least significant digit of the HP-97 output (see Program 5-1 for details).

001	*LBLA	LOAD ApdB or - ρ	053	*LBL1	
002	X<0?	test for - ρ	054	GSB8	$Y_{k-nh} = \frac{1}{2a_k} (Y_{kn} - \frac{1}{Y_{kn}})$
003	GTOa		055	RCLi	$k = 4, 3, 2$
004	EEX	calculate and store;	056	÷	
005	1		057	DSZ1	test for loop exit
006	÷	$\epsilon^2 = 10^{0.1 \text{ ApdB}} - 1$	058	GTO1	
007	10*		059	GSB8	$Y_0 a_0 = \text{xmsn zero freq}$
008	EEX		060	GSBd	print xmsn zero freq
009	-		061	2	
010	STOA		062	ST+9	increment 2h-1
011	GTO9		063	RCL9	
012	*LBLc		064	RCLC	test for loop exit
013	X²	calculate and store;	065	X>Y?	
014	CHS		066	GTO0	
015	EEX		067	GSB9	space if flag 1 is set
016	+		068	EEX	initialize k-1
017	1/X	$\epsilon^2 = \frac{1}{1-\rho^2} - 1$	069	STOI	
018	EEX		070	RCL4	calculate and store;
019	-		071	ENT↑	
020	STOA		072	+	$J_4 \approx \frac{(2a_4)^n}{2}$
021	GTO9		073	RCLC	
022	*LBLB	LOAD λ, the stopband to	074	Y*	
023	STOB	passband frequency ratio	075	2	
024	GTO9		076	÷	
025	*BLBC	LOAD n, the filter order	077	PzS	
026	STOC	(must be odd)	078	STO0	
027	GTO9		079	CF0	indicate full subr
028	*LBLD	CALL. xmsn zeros & AsdB	080	GSB8	
029	9	calculate and store;	081	GSB8	$J_{k-1} = \sqrt{\frac{1}{2} (J_k - \frac{1}{J_k})}$
030	0		082	GSB8	$k = 4, 3, 2, 1$
031	RCLC	$\frac{90}{n} \rightarrow R_E$	083	GSB8	
032	÷		084	PzS	calculate and print;
033	STOE		085	X²	
034	EEX		086	X²	
035	STOI	initialize k+1, 2h-1	087	RCLA	
036	STO9		088	x	
037	RCLB	$a_0 = \sqrt{f_s/f_p}$	089	EEX	$A_{\text{dBS}} = 10 \log(1 + \epsilon^2 J_0^4)$
038	1X		090	+	
039	GSB7		091	LOG	
040	GSB7	$a_{k+1} = a_k^2 + \sqrt{a_k^4 - 1}$	092	1	
041	GSB7	$k = 0, 1, 2, 3$	093	0	
042	GSB7		094	x	
043	*LBL0		095	PRTX	
044	3	initialize k-1	096	GTO9	goto space and return subr
045	STOI		097	*LBL7	subroutine to calculate;
046	RCL4	calculate;	098	X²	
047	RCL9		099	ENT↑	
048	RCLC	$Y_{4h} = \frac{a_4}{\cos \{(2h-1) \frac{90}{n}\}}$	100	X²	
049	x		101	EEX	
050	COS	$h = 1, 2, \dots, \frac{n-1}{2}$	102	-	
051	÷		103	JX	$a_{k+1} = a_k^2 + \sqrt{a_k^4 - 1}$
052	SF0	indicate early subr exit	104	+	
			105	STOI	
			106	ISZ1	
			107	RTN	

108	*LBL8	subroutine to calculate:	165	2	increment 2h
109	ENT↑		166	ST+2	
110	1/X		167	PCLE	
111	+	$u_{k-1} \cdot c_{k-1} = \frac{1}{2} (u_k + \frac{1}{u_k})$	168	RCLE	test for loop exit
112	2		169	X*Y	
113	÷		170	STC4	
114	F0?	test for early exit	171	*LBL9	space and return subr
115	RTN		172	F1?	space if flag 1 is set
116	JX		173	SFC	
117	STOI		174	RTN	
118	ISZ1	$J_{k-1} = \sqrt{\frac{1}{2} (J_k - \frac{1}{J_k})}$	175	STC5	R/S lookup
119	RTN		176	*LBL5	subroutine to calculate
120	*LBL5	CALCULATE POLE LOCATIONS	177	AF	using complex arithmetic:
121	3		178	LST4	
122	STOI	initialize 3-k	179	1	
123	RCLA		180	1.2	
124	JX	$J_0 s_{00} = \frac{1}{\epsilon}$	181	EEA	
125	1/X		182	-	
126	P+S		183	-	
127	*LBL2	calculate:	184	LST4	$s_{k-1} \cdot a_{k-1} = \frac{1}{2} (s_k - \frac{1}{s_k})$
128	GSB6	$s_{(k+1)0} = J_k s_{k0} + \sqrt{J_k^2 s_{k0}^2 + 1}$	185	2	
129	RCL1		186	+	
130	x	k = 0, 1, 2,	187	F1	
131	DSZ1	test for loop exit	188	x	
132	GT02		189	X*Y	
133	ENT↑	to avoid overflow, use:	190	AF	
134	+	$s_{40} \approx 2 J_3 s_{30}$	191	2	
135	RCL1	calculate and store:	192	÷	
136	P+S		193	RTN	
137	X*Y		194	*LBL5	subroutine to calculate:
138	=	$s_{50} = \left\{ \frac{J_4}{s_{40}} + \sqrt{\left(\frac{J_4}{s_{40}} \right)^2 + 1} \right\}^{\frac{1}{n}}$	195	ENT↑	
139	GSB6		196	X*	
140	RCLC		197	EEA	$s_{(k+1)0} = J_k s_{k0} + \sqrt{(J_k s_{k0})^2 + 1}$
141	1/X		198	+	
142	YX		199	JX	
143	STOD		200	+	
144	CLX	initialize 2h	201	RTN	
145	STO9		202	*LBL6	print or R/S subroutine
146	*LBL4	pole location calc loop	203	F1?	
147	4		204	PRTX	print and return if flag 1
148	STOI	initialize k-1	205	F1?	is set, otherwise
149	RCL9	calc	206	RTN	
150	RCLC	$s_{5h} = s_{50} e^{j h \frac{\pi}{n}}$	207	R/E	stop program execution
151	x		208	RTN	
152	RCLD	$h = 0, 1, 2, \dots, \frac{n-1}{2}$	209	*LBL5	PRINT-R/S TOGGLE
153	*LBL3		210	CF1	clear flag 1 and place
154	GSB5	$s_{(k-1)h} = \frac{1}{2 a_{k-1}} (s_{kh} - \frac{1}{s_{kh}})$	211	CLX	a zero in the display
155	RCL1		212	RTN	
156	÷	k = 5, 4, 3, 2	213	*LBL5	
157	DSZ1	test for loop exit	214	SF1	set flag 1 and place
158	GT03		215	EEA	a one in the display
159	GSB5	finish pole location	216	RTN	
160	→R	calculation and print			
161	GSB6	pole locations			
162	X*Y				
163	GSB6				
164	GSB5				

Part 3

ELECTROMAGNETIC COMPONENT DESIGN

PROGRAM 3-1 FERROMAGNETIC CORE INDUCTOR DESIGN – MAGNETICS.

Program Description and Equations Used

This program calculates the various parameters relating to inductor or transformer design on closed magnetic cores. Given the core relative permeability (μ), the core length (ℓ_c), the core area (A), the air gap (ℓ_{air}), the required inductance (L), the dc current (I_{dc}), the applied ac voltage (E), and the excitation frequency (f), the program will calculate the number of turns required (N), the core H (oersteds) and B (gauss) resulting from the dc excitation, the ac excitation, and the total from both excitations. The dimensions of the core and air-gap can be entered in either centimeter or inch units. Program 3-2 will calculate the wire size and winding resistance given the window area and mean turn length. The program will also calculate the coil inductance if the number of turns, the core permeability and dimensions, and the air gap dimensions are given.

If the inductance in millihenries per 1000 turns is given (the A_L value) along with the core dimensions and permeability, the effective air gap will be calculated and stored in place of the given air gap. The inductance or turns, and core excitation will then be calculated on the basis of the calculated air gap.

The magnetic equations used are:

$$H = \frac{0.4 \mu N I}{\ell_c + \mu_c \ell_{air}} \quad (3-1.1)$$

$$E = 10^{-8} \cdot N \frac{d\phi}{dt} = 10^{-8} N A \frac{dB}{dt} \quad (3-1.2)$$

where I is the current in the coil. Equation (3-1.2) can be rearranged to yield B, the core flux density:

$$B = \frac{10^8}{N A} \int E \cdot dt \quad (3-1.3)$$

If $E = \sqrt{2} \cdot E_{\text{rms}} \cdot \sin(2\pi ft)$ is the sinewave excitation, then:

$$B_{\text{peak}} = \frac{10^8 \cdot E_{\text{rms}}}{\sqrt{2} \pi A N f} \quad (3-1.4)$$

If E is a symmetrical squarewave with voltage E_{pk} as shown by Fig. 3-1.1, then:

$$B_{\text{peak}} = \frac{10^8 E_{\text{pk}}}{4 A N f} \quad (3-1.5)$$

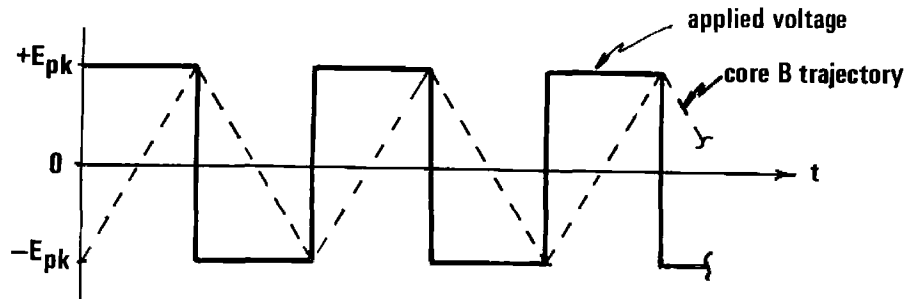


Figure 3-1.1 Square wave coil excitation and magnetic flux density trajectory.

Remembering the differential relationship between current and voltage in an inductor, $E = L(dI/dt)$, an expression can be derived relating the inductance, L , to the magnetic circuit quantities:

$$B = \mu H \quad (3-1.6)$$

From Eqs. (3-1.2) and (3-1.6):

$$E = 10^{-8} N A \mu \frac{dH}{dt} \quad (3-1.7)$$

From Eq. (3-1.1):

$$\frac{dH}{dt} = \frac{0.4 \pi N}{\ell_c + \mu \ell_{\text{air}}} \cdot \frac{dI}{dt} \quad (3-1.8)$$

Combining Eqs. (3-1.7) and (3-1.8) yields the inductance expression:

$$E = \frac{0.4 \pi N^2 A \cdot 10^{-8}}{\ell_c + \mu \ell_{\text{air}}} \cdot \frac{dI}{dt} \quad (3-1.9)$$

hence

$$L = \frac{0.4 \pi N^2 \mu A \cdot 10^{-8}}{\ell_c + \mu \ell_{\text{air}}} \quad (3-1.10)$$

This equation may be rearranged to yield the equivalent air gap if the inductance per turn squared and core dimensions are known:

$$\ell_{\text{air}} = \frac{0.4\pi N^2 A \cdot 10^{-8}}{L} - \frac{\ell_c}{\mu}, \text{ cm} \quad (3-1.11)$$

Generally the inductance index in millihenries per 1000 turns is provided by the core manufacturer:

$$L^* = \text{millihenries per 1000 turns} \quad (3-1.12)$$

hence,

$$\ell_{\text{air}} = \frac{4\pi A}{L^*} - \frac{\ell_c}{\mu} \text{ cm} \quad (3-1.13)$$

Equation (3-1.10) can be rearranged to yield an expression for N, the number of turns, required to achieve a given inductance, L:

$$N = \left\{ L \frac{(\ell_c + \mu \ell_{\text{air}}) \cdot 10^8}{0.4 \pi \mu A} \right\}^{1/2} \quad (3-1.14)$$

The program uses these equations as follows: Labels "A," "a," "B," and "b" are used to load and store the core parameters. The actual stored parameters are in centimeters, and entries with inch units (Labels "A" and "B") are converted before storage. Label "C" uses Eq. (3-1.14) to calculate N given L. Label "c" uses Eq. (3-1.10) to calculate L given N. Label "d" uses Eq. (3-1.13) to calculate the equivalent air gap given the inductance index, L*. The new air gap dimension replaces the presently stored air gap dimension. Label "D" uses Eq. (3-1.1) to calculate the dc magnetizing force, H, given the dc current through the core. Since the number of turns are required for this calculation, the use of "C" or "c" must precede the use of "D." The dc flux density, B_{dc} , is calculated using Eq. (3-1.6). Label "E" uses Eq. (3-1.4) to calculate the peak core flux density given the ac coil excitation. The flux in the core will vary sinusoidally with sinusoidal excitation. The peak ac magnetizing force is calculated using Eq. (3-1.6). The peak ac and dc core magnetic parameters are added together and printed to provide the peak excitation in the core. The peak excitation should be kept below the magnetic saturation level of the core material for linear operation. Label "e" uses Eq. (3-1.5) to calculate peak core flux density from squarewave coil excitation, and provides a summary as above.


User Instructions

INDUCTOR DESIGN - MAGNETICS				
$\mu \uparrow l_c \uparrow A_c$ cm	l_{air} cm	$N \rightarrow L$	$L^*, \frac{mh}{1000T}$	$E_{pk} \uparrow fHz$ H, B_{ac}, pk
$\mu \uparrow l_c \uparrow A_c$ inches	l_{air} inches	$L \rightarrow N$	$I_{dc} \rightarrow H, B_{dc}$	$E_{rms} \uparrow fHz$ H, B_{ac}, pk

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of magnetic card			
2	Load magnetic core parameters			
	a) for dimensions in inches			
	i) relative permeability of core	μ	ENT ↑	
	ii) effective core length	l_c	ENT ↑	
	iii) effective core cross-sectional area	A_c	A	μ
	b) for dimensions in centimeters			
	i) relative permeability of core	μ	ENT ↑	
	ii) effective core length	l_c	ENT ↑	
	iii) effective core cross-sectional area	A_c	f A	μ
3	Load air gap length (if L^* is to be used, skip this step)			
	a) for dimensions in inches	l_{air}	B	l_{air}, cm
	b) for dimensions in centimeters	l_{air}	f B	l_{air}, cm
4	Load L^* (mh/1000T) if air gap is unknown	L^*	f D	l_{air}, cm
5	To calculate the number of turns to achieve a given inductance	L, h	G	N
6	To calculate the inductance given the number of turns	N	f G	L, h
7	Load dc coil current	I_{dc}	D	H_{dc}, Oe B_{dc}, G
8	If sinewave ac coil excitation is present			
	a) load the rms voltage	E_{rms}, V	ENT ↑	
	b) load the frequency	f, Hz	E	H_{ac}, pk, Oe H_{dc}, Oe H_{total}, Oe B_{ac}, pk, G B_{dc}, G B_{total}, G

INDUCTOR DESIGN - MAGNETICS				
		CONTINUED		

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
9	If square-wave coil excitation is present a) load the peak voltage (see Fig. 3-1.1) b) load the frequency	E_{pk} f , Hz	ENT ↑ f E	$H_{ac\ pk}$, Oe H_{dc} , Oe H_{total} , Oe $B_{ac\ pk}$, G B_{dc} , G B_{total} , G
10	To obtain the wire size and winding resistance for the above winding, load Program 3-2.			

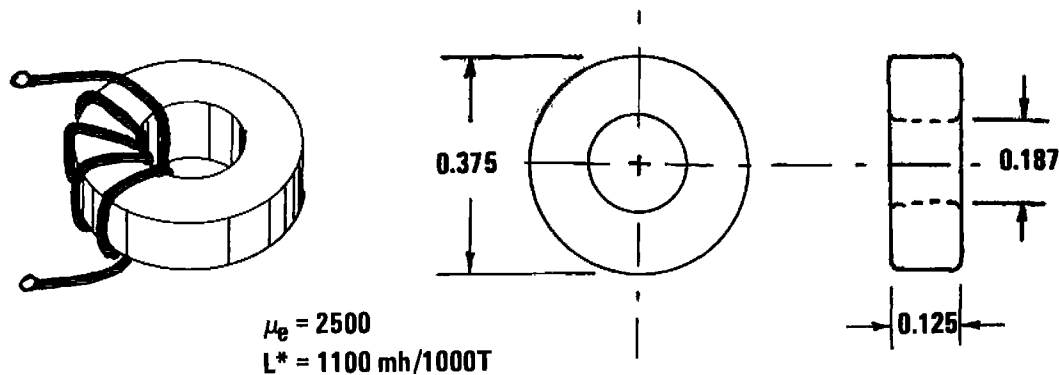Example 3-1.1

Design an inductor to have an inductance of 20 millihenries using the above core (a Ferroxcube 266CT1253B7). The operating frequency is 10 kHz, and the applied ac voltage is 1 Vrms sinewave. There will be 1 mA of dc flowing in the winding.

The core physical constants are needed first:

$$\begin{aligned}
 A &= (.125)(.375 - .187)/2 = 11.8 \times 10^{-3} \text{ inches}^2 \\
 \ell_c &= \pi(.375 + .187)/2 = .883 \text{ inches (mfr says .852 in)} \\
 \ell_{\text{air}}^c &= 0 \text{ (no air gap)}
 \end{aligned}$$

These dimensions along with $\mu_e = 2500$ are loaded using the A & B keys.

```

2500. ENT+  μe
.852 ENT+  ℓc, inches
11.8-03 GSE+ A, inches²

0. GSE+  ℓair

1100. GSE+  L* (mh/1000T)
4.062-05 *** ℓair    calculated, cm

.020 GSE+  L required, h
134.8+00 *** N calculated (use 135T)


1.-03 GSED  Idc, amps
77.93-03 *** Hdc, oersteds
134.8+00 *** Bdc, gauss

1. ENT+  Vrms
10000. GSE+  freq, Hz, sinewave
87.71-03 *** Hac peak, oersteds
77.93-03 *** Hdc      "
165.6-03 *** H total  "

219.3+00 *** Bac peak, gauss
134.8+00 *** Bdc      "
414.1+00 *** B total  "

```

Since the core saturates at around 2500 gauss, and this design only excites the core to 414 gauss peak, the design appears adequate from a magnetics standpoint.

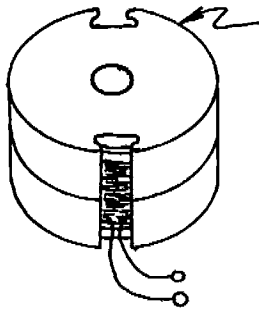Example 3-1.2

Ferrite pot core: Ferroxcube 2213C A400 3B7

ℓ = 3.15 cm
 A^c = 0.635 cm²
 μ_e = 1845
 L^* = 400 mh/1000T
 B_{max} < 2000 gauss for stable inductance

This pot core is to be used in a tank circuit of a class A tuned amplifier operating at 50 kHz. The dc current is 30 mA, and the applied ac voltage is 10 Vrms. The required inductance is 40 mh (the resonating capacitor is 253 pF). Calculate the effective air gap, the number of turns required, the dc and ac core excitation, and the peak flux density. The following HP-97 printout shows the data entry and calculated parameter output.

```

1845. ENT+   $\mu_e$ 
 3.15 ENT+   $\ell^e$ , centimeters
.635 GSB:    $A^c$ , cm2

400. GSBd   $L^*$  (mh/1000T)
18.24-03 ***  $\ell_{air}$  calculated

.040 GSBd  L required, h
316.2+00 *** N calculated (use 316)

.030 GSEt  Idc, amps
323.9-03 *** Hdc, oersteds
597.6+00 *** Bdc, gauss

10. ENT+   Vrms
50000. GSEE Freq, Hz, sinewave
12.15-03 *** Hac peak, oersteds
323.9-03 *** Hdc, "
336.1-03 *** H total, "

22.42+00 *** Bac peak, gauss
597.6+00 *** Bdc, "
620.0+00 *** B total, "
  
```

A printout of the registers reveals this stored information:

```

PREC
1.845+03 0
3.150+00 1  $\ell$  cm
.635-03 2  $A^c$ , cm2
18.24-03 3  $\ell_{air}$ , cm
316.2+00 4 N, turns
50.00+03 5 freq, Hz
323.9-03 6 Hdc, Oe
597.6+00 7 Bdc, gauss
0.000+00 8
22.42+00 9 Bac pk, gauss
10.00+00 A Vac, volts
30.00-03 B Idc, amps
4.000+06 C  $L \times 10^8$ 
400.0+00 D  $L^*$ , mh/1000T
0.000+00 E
0.000+00 I
  
```

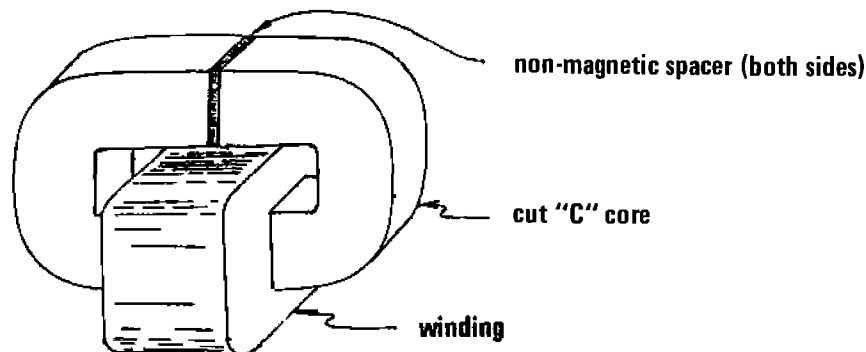
Example 3-1.3

Figure 3-1.2 Inductor on cut C-core.

An inductor to carry dc is needed for the power separation assembly at the end of a coax cable. One ampere dc must flow through the inductor without forcing the B-H loop into a nonlinear region. The inductance needed is 1 henry. Ac signals of 10 Vrms across a frequency band covering 10 Hz to 1000 Hz will be applied in addition to the dc current. A tentative selection is a cut "C" core (see Fig. 3-1.2) with dimensions $A_c = 1.0 \text{ in}^2$, $\ell_c = 6 \text{ inches}$, and $\mu = 1000$ (silicon transformer steel). To ensure linear inductance, the peak flux level in the core should not exceed 10000 gauss.

1000. ENT1	μ		
6. ENT1	ℓ_c , inches		
1. G5EA	A_c , inches ²		
.002 G5EE	ℓ_{air} , inches (.031 each side)		
1. G5EC	L, h, required		
1.460+03 ***	N, # turns calc		
1. G5ED	Idc, amps		
10.62+00 ***	Hdc, oersteds		
10.62+03 ***	Bdc, gauss		
10. ENT7	Vrms		
10. G5EE	freq, Hz, sinewave		
2.390+00 ***	Hac peak, oersteds		
10.62+00 ***	Hdc, "		
13.01+00 ***	H total, "		
2.390+03 ***	Bac peak, gauss		
10.62+03 ***	Bdc, "		
13.01+03 ***	B total, "		
B total exceeds 10000 gauss, use a thicker spacer (larger air gap).			
.125 G5EE	new air gap, inches (0.625" each side)		
G5EC	recalculate N		
2.026+03 ***	N, # turns		
G5ED	recalc, H, Bdc		
7.651+00 ***	Hdc, oersteds		
7.651+03 ***	Bdc, gauss		
G5EE	recalc H, Bac, etc.		
1.722+00 ***	Hac peak, oersteds		
7.651+00 ***	Hdc, "		
9.373+00 ***	H total, "		
1.722+03 ***	Bac peak, gauss		
7.651+03 ***	Bdc, "		
9.373+03 ***	B total, "		
B total is less than 10000 gauss, magnetic design is complete.			

REGISTERS									
0	1	2	3	4	5	6	7	8	9
μ	l_c	A_c	l_{air}	N	f	H_{dc}	B_{dc}		$B_{ac, pk}$
S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
A	B	C	D	E	F	G	H	I	J
V_{ac}	I_{dc}	$L \times 10^8$	L^*	10^8				2.54	

Program Listing II

NOTE FLAG SET STATUS

096 *LBL5	LOAD E_{rms} , fHz; CALC H, B	150 *LBL5	initialization subroutine
097 F3?		151 EEX	
098 F3?	jump if no numeric entry	152 8	generate and store 10^8
099 GT01		153 STOE	
100 ST05	store frequency	154 R↓	recover x register
101 XZY		155 2	
102 ST0A	store rms voltage	156 .	
103 *LBL1	setup for B_{peak} calculation	157 5	generate and store 2.54
104 RCLA		158 4	
105 2		159 ST01	
106 JX	$k = \sqrt{2} \pi$	160 R↓	recover x register
107 Pi		161 RTN	return to main program
108 x		162 *LBL6	common magnetics subroutine
109 GT02	goto B calculation	163 RCL3	
110 *LBL6	LOAD E_{pk} , fHz; calc H, B	164 RCL0	
111 F3?		165 x	calculate:
112 F3?	jump if no numeric entry	166 RCL1	
113 GT01		167 +	$\frac{L_c + \mu L_{air}}{0.4 \pi}$
114 ST05	store frequency	168 Pi	
115 XZY		169 ÷	
116 ST0A	store peak voltage	170 .	
117 *LBL1	setup for B calculation	171 4	
118 RCLA		172 ÷	
119 4	$k = 4$	173 RTN	return to main program
120 *LBL2	common B calculation routine		
121 ÷			
122 RCL5			
123 ÷			
124 RCL2			
125 ÷	$B_{peak} = \frac{10^8 \cdot E}{k ANf}$		
126 RCL4			
127 ÷			
128 RCL6			
129 x			
130 ST09	store B_{ac} , pk		
131 RCL0	calculate and print H_{ac} , pk		
132 ÷	$H = B/\mu$		
133 PRTX			
134 RCL6	recall and print H_{dc}		
135 PRTX			
136 +			
137 PRTX	calc and print H_{total}		
138 SPC			
139 RCL9	recall and print B_{ac} , pk		
140 PRTX			
141 RCL7	recall and print B_{dc}		
142 PRTX			
143 +	calculate B_{total}		
144 *LBL3	print and space subroutine		
145 PRTX			
146 *LBL4	space and OF3 subroutine		
147 SPC			
148 CF3			
149 RTN			

NOTE:

To change from the "print" mode to the "R/S" mode for output, change the "print" statements to "R/S" statements at the following line numbers: 075, 133, 135, 137, 140, 142, and 145.

NOTE FLAG SET STATUS

LABELS				FLAGS	SET STATUS		
A $\mu t L_c \uparrow A_c [m]$	B $l_{air} [m]$	C $L \rightarrow N$	D $I_{dc} \rightarrow H_{dc}, B_{dc}$	E $V_{rms} f_{Hz} \rightarrow H_{pk}, B_{pk}$	0	TRIG	
a $\mu t L_c \uparrow A_c [cm]$	b $l_{air} [cm]$	c $N \rightarrow L$	d load L^*	e $V_{pk} \uparrow f_{Hz} \rightarrow H_{pk}, B_{pk}$	1	ON OFF	DISP
0 loop c destination	1 ac flux output routine	2 ac flux output routine	3 print, space, CF3, rtn	4 space CF3, rtn	2 store constants	0	DEG
5 initialize constants	6 $L_c + \mu L_{air}$ 0.4π	7	8	9	3 data entry	1	GRAD
						2	RAD
						3	FIX
							SCI
							ENG
							n. 3

PROGRAM 3-2 FERROMAGNETIC CORE INDUCTOR DESIGN – WIRE SIZE.

Program Description and Equations Used

This program is a companion program to Program 3-1. Given the window area and the number of turns (stored by companion program), this program will calculate the wire size with heavy insulation (class 2) that will fill the window area. If the length of the mean turn is known, the program will also calculate the winding resistance.

The program is also designed to provide information on the wire diameter over class 2 insulation and wire resistance in ohms/inch given the wire size in AWG. The program will also calculate the AWG given the wire diameter over class 2 insulation.

The operation of the program centers around the logarithmic relationship between AWG and the wire cross-sectional area. This logarithmic relationship is:

$$AWG = \frac{1}{b} \ln \frac{\text{diameter in inches}}{a} \quad (3-2.1)$$

$$\begin{array}{lcl} \text{where } a' = 0.3245574964 & \left. \begin{array}{l} \\ b' = -.1159489227 \end{array} \right\} & \text{bare wire} \\ a = 0.3137250775 & \left. \begin{array}{l} \\ b = -.1097881513 \end{array} \right\} & \text{wire with class 2} \\ & & \text{insulation} \end{array}$$

If the total area for a winding of N turns is known, then the area for one turn may be calculated. If the wire is assumed to just fit inside a square with the wire diameter tangent to the sides of the square, then the waste space due to wire stacking can be accommodated (see Fig. 3-6.2). The wire diameter becomes the square root of the square's area. The program uses this algorithm. Once the wire diameter is found, the AWG can be calculated using the logarithmic relationships. The constants for heavy insulation are used. The AWG that is used and is output is the upward rounded value of $(1.5 + \text{calculated AWG})$.

The wire resistance per unit length is inversely proportional to

the copper cross-section, hence, the wire size in AWG also bears a logarithmic relationship to the wire resistance. When the wire resistance is desired as a function of the wire AWG, the relationship becomes exponential:

$$R/\ell \text{ (ohms/inch)} = c \cdot e^{(d \cdot \text{AWG})} \quad (3-2.2)$$

$$\text{where } \left. \begin{array}{l} c = 8.371747114 \times 10^{-6} \\ d = -.2317635483 \end{array} \right\} \begin{array}{l} \text{annealed} \\ \text{copper wire} \end{array}$$

This exponential relationship is used in conjunction with the mean turn length and the number of turns to calculate the total resistance of the winding. The window area and mean turn length may be entered in either units of inches or centimeters. Centimeter dimensions are converted to inch dimensions before storage within the program.

If the AWG is known and the overall wire diameter including the heavy insulation is desired, Eq. (3-2.1) can be rearranged to yield:

$$\text{diameter in inches} = a \cdot e^{(b \cdot \text{AWG})} \quad (3-2.3)$$

This equation is evaluated under label e.

[illegible]

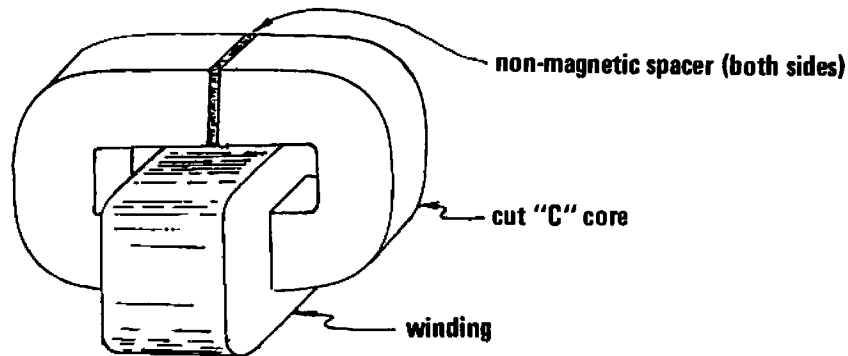
Example 3-2.1

Figure 3-2.1 Inductor on cut C-core.

The inductor in Fig. 3-2.1 was designed to carry dc in Example 3-1.3. If the winding window area is 2 square inches, and the mean turn length is 6 inches, what wire size will fill the winding window, and what will be the total winding resistance?

```

2.  GSEH  window area in square inches
6.  GSEB  mean turn length in inches
    GSEI  start wire size calculation
22. ***  wire size in AWG

    GSED  start winding resistance calculation
16.67+00 ***  winding resistance in ohms

```

Program Listing I

001 *LBL6	LOAD WINDOW AREA IN cm ²	057 *LBL4	print, spe, & eng3 subr
002 F0?	test for initialization	058 PRTX	
003 GSB2		059 SPC	
004 RCL1		060 ENG	
005 X ²	convert area to inches ²	061 DSP3	
006 ÷		062 RTN	
007 *LBL4	LOAD WINDOW AREA IN in ²	063 *LBL5	AWG to ohms/inch subroutine
008 STOA	store window area	064 GSB0	interchange registers
009 F0?	test for initialization	065 RCL3	
010 GSB2		066 X	use Eq. (3-2.2) for
011 RTN	return control to keyboard	067 e ^x	conversion
012 *LBL6	LOAD MEAN TURN LENGTH IN cm	068 RCL2	
013 F0?	test for initialization	069 X	
014 GSB2		070 GT01	test for register interch
015 RCL1	convert length to inches	071 *LBL6	wire diameter to AWG subr
016 ÷		072 GSB0	interchange registers
017 *LBL8	LOAD MEAN TURN LENGTH IN in	073 RCL0	
018 STOC	store mean turn length	074 ÷	use Eq. (3-2.1) for
019 F0?	test for initialization	075 LN	conversion
020 GSB2		076 RCL1	
021 RTN	return control to keyboard	077 ÷	
022 *LBL6	LOAD NUMBER OF TURNS CHANGE	078 .	
023 STOA	store new number of turns	079 5	
024 RTN		080 +	
025 *LBLC	CALCULATE WIRE AWG	081 FIX	
026 RCLA	calculate wire diameter:	082 DSP0	
027 RCL4	$d = \sqrt{\frac{A_{window}}{n}}$	083 RND	
028 ÷		084 GT01	interchange registers
029 JX		085 *LBL0	register interchange subr
030 GSB6	calculate AWG from wire diam	086 F0?	test for initialization
031 EEX	using Eq. (3-2.1)	087 GSB2	
032 +		088 P+S	
033 STOB		089 SF2	
034 GT04	goto print, space & dsp subr	090 RTN	
035 *LBLD	CALCULATE WINDING RESISTANCE		
036 RCL6	use Eq. (3-2.2) to calc		
037 GSB5	ohms/inch		
038 RCLC			
039 X	multiply by total winding		
040 RCL4	length to get total		
041 X	resistance		
042 GT04	print resistance		
043 *LBLD	CONVERT AWG TO OHMS/INCH		
044 GSB5	perform conversion		
045 GT04	print result		
046 *LBL6	CONVERT WIRE DIAMETER TO AWG		
047 GSB6	perform conversion		
048 GT04	print result		
049 *LBLF	CONVERT AWG TO WIRE DIAMETER		
050 GSB0	interchange registers		
051 RCL1			
052 X	use Eq. (3-2.3) for		
053 e ^x	conversion		
054 RCL0			
055 X			
056 GSB1	interchange registers		

NOTE:

To change from the "print" to "R/S" mode for output, change the "print" statement at line 058 to a "R/S" statement.

REGISTERS									
0	1	2	3	4	5	6	7	8	9
S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
.3137250775	-1.1097881513	8.971747114	.231765483						
A	B	C	D	E	F	G	H	I	J
Window Area, in ²	AWG	Mean Turn, in							2.54

091	*LBL2	initialization subroutine	141	CLX	
092	ENG	set engr 3 format	142	.	
093	DSP3		143	2	
094	F2?	test if P2S needed	144	3	
095	P2S		145	1	
096	P2S	execute and note P2S	146	7	
097	SF2		147	6	.231765483 → S3
098	CF0	indicate initialization done	148	3	
099	.		149	5	
100	3		150	4	
101	1		151	8	
102	3		152	3	
103	7		153	ST03	
104	2	.3137250775 → S0	154	CLX	
105	5		155	2	
106	0		156	.	2.54 → RI
107	7		157	5	
108	7		158	4	
109	5		159	ST01	
110	ST00		160	R4	restore x register
111	CLX		161	*LBL1	subroutine to interchange
112	.		162	F2?	registers if flag 2 is set
113	1		163	P2S	
114	0		164	RTN	
115	9				
116	7				
117	8				
118	8	-.1097881513 → S1			
119	1				
120	5				
121	1				
122	3				
123	CHS				
124	ST01				
125	CLX				
126	8				
127	.				
128	3				
129	7				
130	1				
131	7				
132	4	8.371747114 x 10 ⁻⁶ → S2			
133	7				
134	1				
135	1				
136	4				
137	EEX				
138	CHS				
139	6				
140	ST02				

NOTE FLAG SET STATUS

LABELS					FLAGS	SET STATUS			
A load window area in in ²	B load mean turn in inches	C calculate AWG	D calculate winding R	E AWG → wire diam	0 store constants	FLAGS		TRIG	DISP
a load window area in cm ²	b load mean turn in cm	c	d	e wire diam → AWG	1	ON	OFF	DEG	FIX
0 P2S SF2	1 P2S if F2	2 Constant storage	3	4 Print & space	2 P2S used	1		GRAD	SCI
5 AWG → Ω/in	6 wire diam → AWG	7	8	9	3	2		RAD	ENG
						3			n

PROGRAM 3-3 TRANSFORMER LEAKAGE INDUCTANCE AND WINDING CAPACITANCES.

Program Description and Equations Used

This program will calculate the leakage inductance and winding capacitances of a two winding transformer. Both the interwinding capacitance and winding self-capacitances are calculated. The output for both the leakage inductance and winding capacitances are reflected to the primary winding.

Leakage inductance. The total magnetic flux in a transformer is composed of the mutual flux and the leakage flux. The mutual flux follows the core path and links both primary and secondary windings, and results in the mutual, or open-circuit inductance of the transformer. The leakage flux is the relatively small flux which originates in the primary winding and does not link the secondary winding, or vice-versa, and results in the leakage inductance. The leakage flux will be less as the primary and secondary windings are interleaved up to the limit imposed by the space occupied by the insulation between windings. To a degree, the interleaving process is self-defeating, as too much interleaving generates much nonconductive space, and most of the leakage flux flows therein.

Of the many formulas that have been derived for the calculation of leakage inductance, the one by Fortescue [25] is generally accurate and errs, if at all, on the conservative side:

$$L_{\text{leak}} = 10.6 \times 10^{-9} \frac{N^2 \cdot MT(2nc + a)}{n^2 b} \quad (3-3.1)$$

where

L_{leak} = leakage inductance in henries, referred to the winding having N turns (the primary in this program)

MT = mean-turn length in inches for the whole coil (both windings)

n = number of dielectrics between windings

- a = winding buildup in inches
 b = winding traverse in inches
 c = dielectric thickness between windings in inches

Interleaving provides the greatest reduction in leakage inductance when the dielectric height, c , is small compared to the window height. When nc is comparable to the window height, the leakage inductance does not decrease substantially as the number of interleaves, n , is increased. The lowest leakage inductance will be obtained with a transformer having a small number of turns, a short mean turn length, and a low, wide winding window.

The term " a " in Eq. (3-3.1) refers to the total winding buildup composed of the primary buildup, the secondary buildup, and the insulation layers buildup. If a_p represents the buildup of all the primary interleaves, and a_s represents the buildup of all the secondary interleaves, then:

$$2nc + a = 3nc + a_p + a_s \quad (3-3.2)$$

The basis for Eq. (3-3.2) may be seen from Fig. 3-3.1.

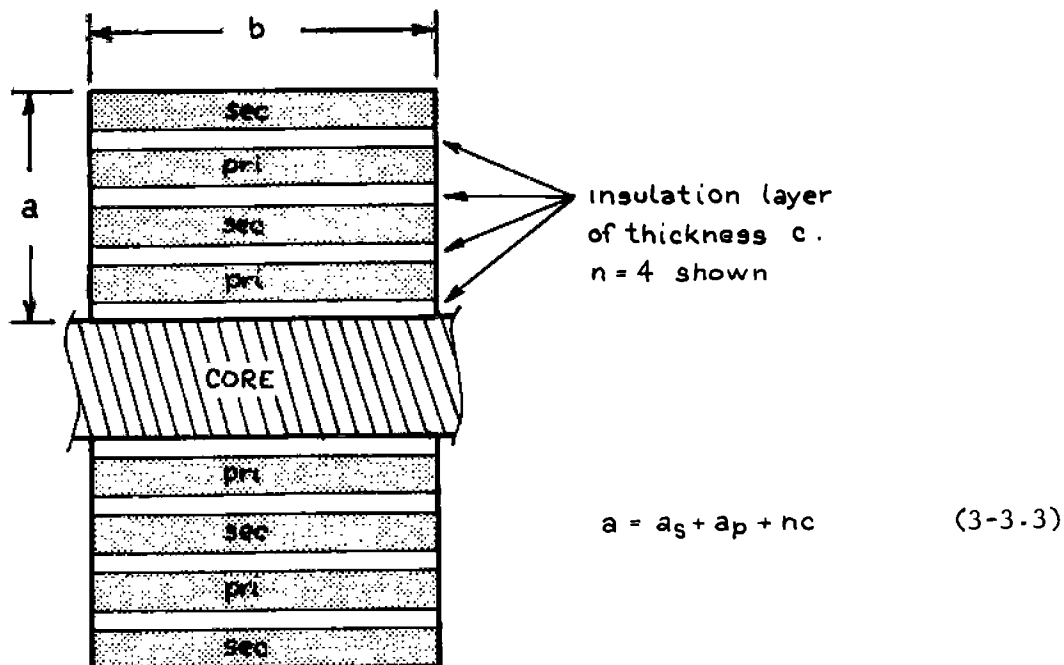


Figure 3-3.1 Cross-section of transformer winding on a core leg.

Interwinding capacitance. The interwinding capacitance is the primary-secondary capacitance. This capacitance is calculated by considering

the primary and secondary windings as single conducting sheets separated by the dielectric formed by the insulating layer and wire insulation. The capacitance of two flat plates separated by a dielectric is:

$$C = .225 \times 10^{-12} \epsilon \frac{A}{t} \quad (3-3.4)$$

where

ϵ is the relative dielectric constant of the dielectric

A is the area of one plate in inches²

t is the dielectric thickness in inches

For the transformer

$$A = n \cdot MT \cdot b \quad (3-3.5)$$

and

$$t = c + t_{\text{primary wire insulation}} + t_{\text{secondary wire insulation}} \quad (3-3.6)$$

The wire insulation thickness for heavy insulation (heavy formvar, etc.) can be obtained from the wire AWG. The AWG is obtained from the wire diameter over class 2 insulation by using Eq. (3-2.1), where the wire diameter is calculated by assuming the wire plus insulation just fits in a box as shown by Fig. 3-6.2. The wire diameter over the insulation then becomes:

$$t_{\text{wire, primary}} = \sqrt{\frac{a \cdot b}{N_p}} \quad (3-3.7)$$

and

$$t_{\text{wire, secondary}} = \sqrt{\frac{a \cdot b}{N_s}} \quad (3-3.8)$$

The diameter of the bare wire is obtained from AWG by using Eq. (3-2.3). Hence, the thickness of the wire insulation is:

$$t_{\text{wire insulation}} = \frac{1}{2} (t_{\text{wire + insulation}} - t_{\text{wire}}) \quad (3-3.9)$$

The wire insulation thickness calculations are performed in the subroutine under label 6 in the HP-67/97 program.

Winding self-capacitance. In a multilayer winding, the voltage between layers is zero at one end of the layer, and $2E/N_L$ at the other where

E is the total winding voltage, and N_L is the number of layers. This voltage gradient model serves as the basis for the total winding capacity as given by Reuben Lee [36].

$$C_i = 1.333 \frac{C_{Li}}{N_{Li}} \left\{ 1 - \frac{1}{N_{Li}} \right\} \quad (3-3.10)$$

$i = \text{pri or sec}$

C_{Li} is the layer-to-layer capacitance, and is found from Eq. (3-3.4) where

$$A = MT \cdot b \quad (3-3.11)$$

and

$$t = t_d + 2t_{\text{wire insulation}} \quad (3-3.12)$$

The basis of Eqs. (3-3.11) and (3-3.12) are shown by Fig. 3-3.2.

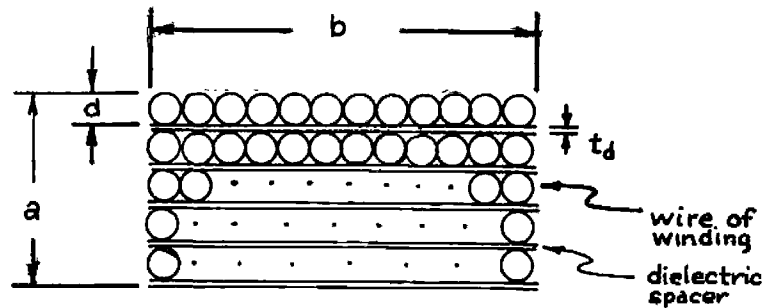


Figure 3-3.2 Cross-section of a winding showing dimensioning.

The number of layers is needed for Eq. (3-3.10) and is found from the number of turns, the interwinding dielectric thickness, and the winding dimensions. The wire cross-sectional area (per Fig. 3-6.2) and the dielectric cross-sectional area must equal the total area available for that winding, i.e.,

$$N_L (d + t_d) = a \quad (3-3.13)$$

$$\text{volume} = a \cdot b = \underbrace{N_L \cdot t_d \cdot b}_{\text{spacer volume}} + \underbrace{N \cdot d^2}_{\text{wire volume}} \quad (3-3.14)$$

Substituting Eq. (3-3.13) into (3-3.14) and solving for N_L yields:

$$N_{L_i} = \frac{N_i d_i}{b_i} \quad (3-3.15)$$

where d is the quadratic solution to:

$$N_i d_i^2 + (N_i t_{d_i}) d_i - a_i b_i = 0 \quad (3-3.16)$$

$i = \text{pri or sec}$

The program calculates the secondary winding capacity and reflects it to the primary winding:

$$C_{\text{sec}} @ \text{ primary} = C_{\text{sec}} \cdot \left(\frac{N_s}{N_p} \right)^2 \quad (3-3.17)$$

The total winding capacity seen at the primary is the sum of the reflected secondary winding capacitance, and the primary winding capacitance.

User Instructions

TRANSFORMER LEAKAGE L AND WINDING C				
winding traverse	$N_p \uparrow N_s$	# of dielectrics	print?	Calculate Leakage C _{winding} C _{interwinding}
pri buildup \uparrow sec buildup	average mean turn length	$t_{dp} \uparrow t_{ds} \uparrow t_d$	$\epsilon_{pri} \uparrow \epsilon_{sec} \uparrow \epsilon_{sp}$	

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card (note flag status)			
2	Load both sides of data card			
3	Select print or R/S option using toggle		<div>f</div> <div>D</div> <div>f</div> <div>D</div> <div>f</div> <div>D</div>	0, R/S 1, print 0, R/S :
4	Load winding traverse in inches	b, in	<div>f</div> <div>A</div>	
5	Load winding buildup in inches: a) primary buildup b) secondary buildup	a_p , in a_s , in	<div>ENT \uparrow</div> <div>A</div>	
6	Load number of turns: a) primary turns	N_p	<div>ENT \uparrow</div> <div>f</div> <div>B</div>	
7	load average mean-turn length for the whole transformer winding in inches	MT, in	<div>B</div>	
8	load the number of dielectrics	n	<div>f</div> <div>0</div>	
9	load dielectric thickness in inches: a) primary interwinding dielectric b) secondary interwinding dielectric c) primary-secondary dielectric	t_{dp} , in t_{ds} , in t_d , in	<div>ENT \uparrow</div> <div>ENT \uparrow</div> <div>0</div>	
10	Load relative dielectric constants: a) average for primary interwinding dielectric and wire insulation b) average for secondary interwinding dielectric and wire insulation c) primary-secondary spacer	ϵ_{pri} ϵ_{sec} ϵ_{sp}	<div>ENT \uparrow</div> <div>ENT \uparrow</div> <div>D</div>	

Example 3-3.1

Find the primary leakage inductance and winding capacitances of a transformer having the following specifications:

traverse: 2"
 number of pri-sec dielectrics: 4 (3 interleaves)
 dielectric thickness: 0.050"
 pri-sec insulator dielectric constant: 10
 mean turn length for whole transformer: 5"

Primary

number of turns: 100
 buildup: 0.25"
 interwinding dielectric thickness: 0.002"
 average interwinding dielectric and wire insulation
 dielectric constant: 10

Secondary

number of turns: 1000
 buildup: 0.3"
 interwinding dielectric thickness: 0
 average interwinding dielectric and wire insulation
 dielectric constant: 5

HP printout for Example 3-3.1

```

      2. GSB0 winding traverse

      .25 ENT1 primary winding buildup
      .3 GSEA secondary winding buildup

    100. ENT1 primary winding turns
    1000. GSB6 secondary winding turns

      5. GSB8 mean turn length for whole transformer

      4. GSBc number of pri-sec dielectrics

    .002 ENT1 primary interwinding dielectric thickness
      0. ENT1 secondary interwinding dielectric thickness
    .05 GSBc pri-sec dielectric thickness

    10. ENT1 average primary dielectric constant
      5. ENT1 average secondary dielectric constant
    10. GSB0 pri-sec dielectric, dielectric constant

      GSBF calculate L's and C's
    19.05-06 *** primary leakage inductance, henrys

    24.00+00 *** secondary wire AWG
    24.49+00 *** number of secondary layers
    23.19-09 *** secondary interwinding C seen @ primary, F

    14.00+00 *** primary wire AWG
    6.972+00 *** number of primary layers
    678.8-12 *** primary interwinding capacity, F
    23.87-09 *** total interwinding capacity @ primary, F

    1.699-09 *** pri-sec winding capacity, F

```

Data Review printout for Example 3-3.1

```

      GSBa
2.000+00 *** traverse

      GSBd
300.0-03 *** secondary winding buildup
250.0-03 *** primary winding buildup

      GSBb
1.000+03 *** secondary turns
100.0+00 *** primary turns

      GSB8
5.000+00 *** mean turn length

      GSBc
4.000+00 *** number of dielectrics

      GSBf
50.00-03 *** primary-sec dielectric thickness
0.000+00 *** secondary interwinding dielectric thickness
2.000-03 *** primary interwinding dielectric thickness

      GSB0
10.00+00 *** pri-sec dielectric, dielectric constant
5.000+00 *** secondary average dielectric constant
10.00+00 *** primary average dielectric constant

```

Program Listing I

001 *LBLA	I/O PRIMARY & SEC BUILDUP	057 GT08	
002 EEV		058 *LBL2	
003 GSB0		059 CF0	
004 0		060 CLX	
005 GT01		061 GT08	
006 *LBL6	I/O WINDING TRAVERSE (b)	062 *LBLE	CALCULATE L's & C's
007 2		063 PZS	calculate leakage inductance
008 GT01		064 RCL4	
009 *LBLE	I/O AVERAGE MEAN TURN (MT)	065 PZS	
010 3		066 RCL4	
011 GT01		067 RCL9	
012 *LBL6	I/O PRIMARY AND SEC TURNS	068 =	
013 5		069 XZ	
014 GSB0		070 X	
015 4		071 RCL3	
016 GT01		072 X	
017 *LBLC	I/O DIELECTRIC THICKNESSES	073 RCL9	
018 8		074 RCL8	
019 GSB0	I/O pri-sec spacer thickness	075 X	
020 7		076 3	
021 GSB0	I/O secondary intrawinding dielectric thickness	077 X	
022 6		078 RCL0	
023 GT01	I/O primary intrawinding dielectric thickness	079 +	
024 *LBLC	I/O NUMBER OF DIELECTRICS	080 RCL1	
025 9		081 +	
026 GT01		082 X	
027 *LBLC	I/O DIELECTRIC CONSTANTS	083 RCL2	
028 1		084 ÷	
029 2		085 GSB3	
030 GSB0	I/O dielectric constant of pri-sec spacer	086 RCL1	calculate and store
031 1		087 RCL2	2-wire, secondary
032 1		088 X	
033 GSB0	I/O secondary insulation dielectric constant	089 RCL5	
034 EEV		090 =	
035 1		091 RCL7	
036 *LBLC	I/O primary insulation dielectric constant	092 GSB6	
037 GSB0	subroutine to I/O last item	093 ST08	
038 GT0P		094 R1	recover d/b
039 *LBLC	main I/O subroutine	095 RCL5	recall H _a
040 ST01	store index	096 GSB5	calc secondary capacitance:
041 R1	recover entry	097 PZS	
042 F3P		098 RCL1	
043 SF1	if flag 3, set flag 1	099 PZS	
044 F1P		100 RCL8	
045 ST01	if flag 1, store entry	101 RCL7	
046 F1P		102 +	
047 R1	if flag 1, recover previous entry	103 GSB4	
048 F1P		104 X	
049 RTN	if flag 1, return	105 RCL5	reflect secondary capacitance to primary:
050 RCL1		106 RCL4	
051 GT07	recall and print item	107 =	
052 *LBLC	PRINT-R/S TOGGLE	108 XZ	
053 CF0		109 X	
054 GT02		110 ST0C	
055 SF0		111 GSB3	
056 EEV		112 RCL0	

0 a _p , pri buildup	1 secondary buildup	2 b, winding traverse	3 MT, mean turn length	4 N _p	5 N _s	6 t _{o pri}	7 t _{o sec}	8 C, t _{o spacer}	9 n, the # of dielectrics
S0 E _{pri}	S1 E _{sec}	S2 E _{spacer}	S3 225 × 10 ⁻¹⁵	S4 10.6 × 10 ⁻⁹	S5 K ₁ = 3137250775	S6 K ₁ = 3245574964	S7 K ₂ = -1097881513	S8 K ₂ = -0.1159489227	S9
A 2x primary wire insulation thickness	B 2x secondary wire insulation thickness	C C _{sec} , or d _{sec}	D	E 1.33333...	F	G	H	I index or scratchpad	

Program Listing II

NOTE FLAG SET STATUS

113 RCL2	calculate and store 2. wire, primary	168 EE ²								
114 Y		169 X ²								
115 RCL4		170 -								
116 ÷		171 -								
117 RCL6		172 RCL6								
118 GSB6		173 X								
119 STOA		174 RTN								
120 R+ calc primary capacitance	175 *LBL6 wire AWG and insulation thk.									
121 RCL4	176 2	calculate wire diameter:								
122 GSB5	177 ÷									
123 P ₂ S	178 STOI									
124 RCL0	179 X ²									
125 P ₂ S	180 +									
126 RCLA	181 JX									
127 RCL6	182 RCL1									
128 +	183 -									
129 GSB4	184 STOI									
130 X	185 RCL2	calculate d/b								
131 GSB7	186 ÷									
132 RCL0 calculate and print:	187 RCL1	calculate insulation thick.								
133 + C _{pri} - N ² .C _{sec}	188 RCL1	calculate wire AWG								
134 GSB3	189 P ₂ S									
135 RCL9 calculate interwinding cap.:	190 RCL5	k ₁								
136 P ₂ S	191 ÷									
137 RCL2	192 LN									
138 P ₂ S	193 RCL7	k ₂								
139 X	194 ÷									
140 RCLA	195 ENT↑									
141 RCL8	196 ENT↑									
142 +	197 EE ²	calculate and print								
143 2	198 +	integral wire size								
144 ÷	199 INT									
145 RCL8	200 GSB7									
146 +	201 R+	calculate bare wire								
147 GSB4	202 RCL8	diameter from AWG								
148 *LBL3 print or R/S subroutine	203 Y									
149 GSB7	204 e ^X									
150 GT08	205 RCL6									
151 *LBL4 capacity subroutine	206 P ₂ S									
152 ÷	207 X									
153 RCL3 MT	208 -	calculate 2. wire insulation								
154 X	209 RTN									
155 RCL2 b	210 *LBL7 print or R/S subroutine									
156 X	211 F0?									
157 P ₂ S	212 PRTX									
158 RCL3 .225 x 10 ⁻¹²	213 F0?									
159 P ₂ S	214 RTN									
160 X	215 R/S									
161 RTN	216 RTN									
162 *LBL5 intrawinding capacity subr	217 *LBL8 space and clear flag 3 subr									
163 X	218 F0?									
164 GSB7 calc and print # of layers	219 SPC									
165 1/X	220 CF1									
166 ENT↑ calculate winding capacity	221 CF3									
167 ENT↑ term:	222 RTN									
	223 GT08									
LABELS		FLAGS	SET STATUS							
A I/O of pri & sec buildup	B I/O of mean turn length	C I/O of dielectric thick	D I/O of relative dielectric const	E calculate L & C's	0 print	FLAGS			TRIG	DISP
a I/O winding traverse	b I/O turns N _p , N _s	c I/O of # of dielectrics	d print or R/S toggle	e	1 input	ON OFF				
0. I/O subroutine	1. I/O subroutine	2 print or R/S toggle	3 print or R/S and space	4 capacitance subroutine	2	0 ■		DEG		FIX
5 winding C subroutine	6 wire diameter subroutine	7 print or R/S subroutine	8 space & CF1, 3 subr	9	3 input	1 ■		GRAD		SCI
						2 ■		RAD		ENG ■
						3 ■				n 3

PROGRAM 3-4 STRAIGHT WIRE AND LOOP WIRE INDUCTANCE.

Program Description and Equations Used

This program calculates the inductance of straight wire lengths and single square wire loops. The permeability of the wire is taken into account only for the inductance calculation, but not for skin depth; therefore, the inductance calculated is the low frequency inductance.

The calculation of wire inductance can be an important design parameter in some instances. For example, the bonding wire inductance of high speed, wideband hybrid integrated circuits affects circuit performance. Wire self-inductance is also important in the design of high frequency (1000 Hz), high power (megawatt) power conversion equipment such as SCR inverters, choppers, cycloconverters, and phase delay rectifiers.

The inductance of a straight wire increases with permeability and length, and decreases with increasing diameter. The combined effect of permeability, length, and diameter is not described simply, but can be easily solved with a scientific calculator. For example, the inductance of copper wire is strongly influenced by diameter while the inductance of a high permeability wire such as permalloy is relatively unaffected by diameter.

The formulas used herein come from Grover [30], and can also be found in Terman [52]. Two basic formulas are used, one for straight wire, and another for wire loops. These formulas are algebraically manipulated to obtain expressions for each of the four variables; wire diameter (d), wire length (ℓ), relative permeability (μ), and inductance in μh (L). The program works in the units of centimeters, but the user may input data in either inch or centimeter units.

Figure 3-4.1 shows the definitions of the wire terms.

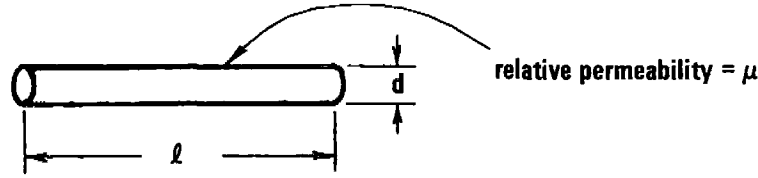


Figure 3-4.1 Straight wire terms.

The formulas for the straight wire case are:

$$L = (2 \times 10^{-3}) \ell \left\{ \ln \left(\frac{4\ell}{d} \right) + \frac{\mu}{4} - 1 \right\}, \mu h \quad (3-4.1)$$

$$d = \frac{4\ell}{e^{(L/(2\ell \times 10^{-3}) - \mu/4 + 1)}} \quad (3-4.2)$$

$$\mu = 4 \left\{ \frac{L}{2\ell \times 10^{-3}} + 1 - \ln \left(\frac{4\ell}{d} \right) \right\} \quad (3-4.3)$$

To obtain the wire length, a Newton-Raphson iterative solution is employed (see Program 1-3 for details), because the equation for ℓ has a logarithm containing ℓ .

$$\ell = \frac{L}{(2 \times 10^{-3}) \left\{ \ln \left(\frac{4\ell}{d} \right) + \frac{\mu}{4} - 1 \right\}} \quad (3-4.4)$$

The Newton-Raphson solution finds where a function is zero, therefore, let:

$$f(\ell) = \ell - \frac{L}{(2 \times 10^{-3}) \left\{ \ln \left(\frac{4\ell}{d} \right) + \frac{\mu}{4} - 1 \right\}} = 0 \quad (3-4.5)$$

and

$$f'(\ell) = \frac{df(\ell)}{d\ell} = 1 + \frac{L}{(2 \times 10^{-3}) \ell \left\{ \ln \left(\frac{4\ell}{d} \right) + \frac{\mu}{4} - 1 \right\}} \quad (3-4.6)$$

The initial guess for ℓ is 1, and the ℓ value for each succeeding iteration is given by:

$$\ell_{i+1} = \ell_i - \frac{f(\ell_i)}{f'(\ell_i)} \quad (3-4.7)$$

The iteration is terminated when:

$$\left| \ell_{i+1} - \ell_i \right| < 10^{-6} \quad (3-4.8)$$

Figure 3-4.2 shows the definitions of the loop wire terms.

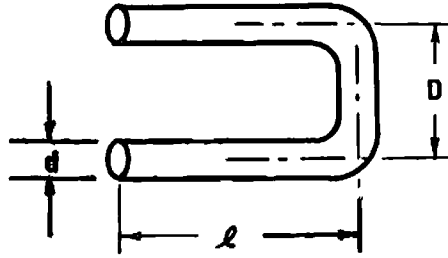


Figure 3-4.2 Loop wire terms.

The formulas for the loop wire case are:

$$L = (4 \times 10^{-3} \ell) \left\{ \ln\left(\frac{2D}{d}\right) + \frac{\mu}{4} - \frac{D}{\ell} \right\}, \mu h \quad (3-4.9)$$

$$d = \frac{2D}{e^{(L/(4 \times 10^{-3} \ell) - \mu/4 + D/\ell)}} \quad (3-4.10)$$

$$\ell = \frac{\frac{L}{4 \times 10^{-3}} + D}{\ln\left(\frac{2D}{d}\right) + \frac{\mu}{4}} \quad (3-4.11)$$

$$\mu = 4 \left\{ \frac{L}{4 \times 10^{-3} \ell} + \frac{D}{\ell} - \ln\left(\frac{2D}{d}\right) \right\} \quad (3-4.12)$$

Keys "a" through "d" set up the dimension units to be used for input or output (inches or centimeters), and the configuration (straight wire or loop wire). When the loop wire configuration is selected (key "c"), the loop separation, D, must also be entered via key "c."

Keys "A" through "D" provide the program input/output functions. Use of these keys following numeric input signals an input to the program. Use of these keys without numeric entry, or following the clear key (E) signals an output is required from the program. Flag 3 is used to indicate input or output within the program.

User Instructions

STRAIGHT WIRE AND LOOP WIRE INDUCTANCE				
centimeter units	inch units	wire loop, enter D	straight wire	
wire diam d	wire length ℓ	permeability μ	inductance L	clear input mode

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of data card			
2	Select dimension units			
	a) centimeter units		<input type="button" value="F"/> <input type="button" value="A"/>	1.000
	b) inch units		<input type="button" value="F"/> <input type="button" value="B"/>	2.540
3	Select configuration			
	a) wire loop, load loop separation	D	<input type="button" value="F"/> <input type="button" value="C"/>	
	b) straight wire		<input type="button" value="F"/> <input type="button" value="D"/>	
4	To calculate wire diameter, d			
	a) load wire length	ℓ	<input type="button" value="B"/>	
	b) load wire permeability	μ	<input type="button" value="C"/>	
	c) load required inductance	L, μh	<input type="button" value="D"/>	
	d) start solution		<input type="button" value="A"/>	d
5	To calculate wire length, ℓ			
	a) load wire diameter	d	<input type="button" value="A"/>	
	b) load wire permeability	μ	<input type="button" value="C"/>	
	c) load required inductance	L, μh	<input type="button" value="D"/>	
	d) start solution execution		<input type="button" value="B"/>	ℓ
6	To calculate permeability, μ			
	a) load wire diameter	d	<input type="button" value="A"/>	
	b) load wire length	ℓ	<input type="button" value="B"/>	
	c) load required inductance	L, μh	<input type="button" value="D"/>	
	d) start solution execution		<input type="button" value="C"/>	μ
7	To calculate inductance, L			
	a) load wire diameter	d	<input type="button" value="A"/>	
	b) load wire length	ℓ	<input type="button" value="B"/>	
	c) load permeability	μ	<input type="button" value="C"/>	
	d) start solution execution		<input type="button" value="D"/>	L, μh
8	To clear input mode (reset flag 3)		<input type="button" value="E"/>	

Example 3-4.1

Find the inductance of a straight gold wire 0.001 inch in diameter and 0.3 inch long (a hybrid integrated circuit interconnect wire).

```

      GSEK  set inches
      GSEB  set straight wire mode
    .001 GSEA  load wire diameter in inches
    .300 GSEB  load wire length in inches
    1.000 GSEC  load wire relative permeability
      GSED  calculate inductance
    0.010 ***  inductance in microhenries

```

Example 3-4.2

Find the length of a 4/0 copper cable (.528 in diam) having an inductance of 6 microhenries

```

      GSEK  set inches
      GSEB  set straight wire mode
    .528 GSEA  load wire diameter
    1.000 GSEC  load relative permeability of wire
    6.000 GSED  load required inductance
      GSEB  calculate wire length*
    182.258 ***  length, inches

    12.000 ÷
    15.168 ***  length, feet

```

*Computation time takes about 1 minute.

Example. 3-4.3

A pair of 4/0 wires run 20 feet between a capacitor module and an inverter module in an ac traction motor controller. The wire separation is twice the wire diameter. What parasitic inductance does the wire add in series with the capacitors? 4/0 wire is .528 inches in diameter.

```

      GSBK  set inch mode
.528  ENTf  }
      +      } calculate and enter the wire separation,
1.056  ***  } and select wire loop configuration
      GSBK
.528  GSEA  load wire diameter in inches
20.000  ENTi  }
12.000  +      } calculate and load wire length in inches
240.000  ***  }
      GSBK
1.000  GSBK  load permeability of wire
      GSED  calculate inductance of wire loop
3.973  ***  inductance, microhenries

```

If the maximum parasitic inductance that can be tolerated is 2 microhenries, how long can the feeder wires be if the other parameters don't change?

```

2.000  GSED  load required inductance in  $\mu$ h
      GSBK  calculate loop length
120.948  ***  loop length, inches

12.000  +
10.279  ***  loop length, feet

```

Program Listing I

001	*LBLa	SET CM UNIT MODE	056	GT07	goto unit conv and print
002	EEX		057	*LBLb	I/O OF WIRE LENGTH, ℓ
003	ST09	store cm \rightarrow cm conversion	058	EEX	
004	RTN		059	F3?	if numeric input,
005	*LBLb	SET INCH UNIT MODE	060	GT00	goto input subroutine
006	2		061	F0?	jump if loop wire mode
007	.		062	ST01	store "1" for initial guess
008	5	store in \rightarrow cm conversion	063	ST01	store "1" for initial guess
009	4		064	*LBL4	Newton-Raphson loop start
010	ST09		065	RCL1	
011	RTN		066	4	
012	*LBLc	LOAD WIRE LOOP SEPARATION	067	x	calculate and store $f(\ell)$:
013	SF0	indicate wire loop mode	068	RCL0	
014	CF3		069	=	
015	4	goto data entry subroutine	070	LN	
016	GT00		071	EEX	$\ln \left\{ \frac{4\ell}{d} \right\} + \frac{\mu}{4} - 1$
017	*LBLd	SET STRAIGHT WIRE MODE	072	-	
018	CF0	indicate straight wire mode	073	RCL2	
019	RTN		074	+	
020	*LBLA	I/O OF WIRE DIAMETER, d	075	F2?	test for subroutine exit
021	2		076	RTN	
022	EEX		077	ST0E	finish $f(\ell)$ calculation
023	CHS	store 0.002	078	RCL8	
024	3		079	x	
025	ST08		080	1/x	
026	R↓	recover input	081	RCL5	$f(\ell) = \ell - \frac{L}{2 \times 10^{-3} \left\{ \ln \left(\frac{4\ell}{d} \right) + \frac{\mu}{4} - 1 \right\}}$
027	0		082	x	
028	F3?	if numeric input,	083	CHS	
029	GT00	goto data input subroutine	084	RCL1	
030	F0?		085	+	
031	GT01	jump if wire loop mode	086	ST07	
032	RCL1		087	RCL5	calculate and apply $f'(\ell)$:
033	4	calculate and store d for	088	RCL8	
034	x	straight wire case:	089	RCL1	
035	GSB6		090	x	
036	+	$d = \frac{4\ell}{e^{\left(\frac{L}{2\ell \times 10^{-3}} - \frac{\mu}{4} + 1 \right)}}$	091	RCL6	$f'(\ell) = 1 + \frac{L}{(2 \times 10^{-3} \ell) \left\{ \ln \left(\frac{4\ell}{d} \right) + \frac{\mu}{4} - 1 \right\}^2}$
037	RCL2		092	x ²	
038	-		093	x	
039	e ^x		094	=	
040	=		095	EEX	
041	ST00		096	+	
042	GT07	goto unit conversion & print	097	ST=7	calculate correction
043	*LBL1		098	RCL7	apply correction
044	GSB8	calculate and store d for	099	ST-1	
045	GSB6	loop wire case	100	ABS	
046	x		101	EEX	
047	2		102	CHS	test for loop exit
048	=		103	6	
049	-	$d = \frac{2D}{e^{\left(\frac{L}{4\ell \times 10^{-3}} - \frac{\mu}{4} + \frac{D}{\ell} \right)}}$	104	X≠Y?	
050	e ^x		105	GT04	
051	RCL4		106	RCL1	recall and print
052	x		107	GT07	
053	ENT1		108	*LBL1	calculate ℓ for loop wire
054	+		109	RCL5	case
055	ST00		110	RCL8	

REGISTERS									
0 diameter cm	1 length cm	2 $\mu/4$	3	4 wire separation, cm	5 inductance L	6	7 scratch	8 2×10^{-3}	9 1 or 2.54
S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
A	B	C	D	E	scratch	I	index		

111	ENT↑				166	x	calculate μ		
112	+				167	GT02	goto print and space subr		
113	=				168	*LBL0	I/O OF INDUCTANCE, L		
114	RCL4				169	RCL9	undo unit conversion		
115	+				170	=			
116	RCL4				171	5	if numeric input, goto		
117	ENT↑				172	F3?	data input subroutine		
118	+				173	GT00			
119	RCL0				174	F0?	jump if loop wire mode		
120	=				175	GT03			
121	LN				176	SF2	calc: $\ln\left(\frac{4\ell}{d}\right) + \frac{\mu}{4} - 1$		
122	RCL2				177	GSB4			
123	+				178	GT01	jump		
124	=				179	*LBL3	calculate:		
125	ST01	store ℓ			180	RCL4			
126	*LBL7	unit conversion & prt subr			181	ENT↑			
127	RCL9	recall unit conversion			182	+			
128	=				183	RCL0			
129	*LBL2	print and space subroutine			184	=			
130	PRTX	-- can be R/S statement			185	LN			
131	SPC				186	GSB8			
132	RTN				187	+			
133	*LBL0	I/O OF PERMEABILITY, μ			188	ENT↑			
134	4				189	+			
135	=				190	*LBL1	common inductance calculation		
136	RCL9				191	RCL8			
137	=	undo unit conversion			192	x	$\times (2\ell \times 10^{-3})$		
138	2				193	RCL1			
139	F3?	if numeric input, goto			194	x			
140	GT00	data input subroutine			195	ST05	store inductance		
141	F0?				196	GT02	goto print and space subr		
142	GT03	jump if wire loop mode			197	*LBL0	data input subroutine		
143	GSB6				198	ST01	store register index		
144	+	start calculation for			199	R↓	recover input		
145	RCL1	straight wire			200	RCL9	apply unit conversion and		
146	4				201	x	store entry		
147	GT01				202	ST01			
148	*LBL3	loop wire calculation			203	RTN	return to main program		
149	GSB6				204	*LBL6	subroutine to calculate:		
150	2				205	EEX			
151	=				206	RCL5			
152	RCL4				207	RCL8			
153	RCL1				208	=			
154	=				209	RCL1			
155	+				210	=			
156	RCL4	D			211	RTN			
157	2				212	*LBL8	subroutine to calculate:		
158	*LBL1	common calculation routine			213	RCL2			
159	x				214	RCL4			
160	RCL0				215	RCL1			
161	=				216	=			
162	LN				217	-			
163	-				218	RTN			
164	ST02	store $\mu/4$			219	*LBL5	CLEAR INPUT MODE		
165	4				220	CF3			
					221	RTN			

PROGRAM 3-5 AIR-CORE SINGLE-LAYER INDUCTOR DESIGN.

Program Description and Equations Used

This program uses Wheeler's equation [55] to solve for the various parameters relating to single-layer, air-core inductor design. The basic form of Wheeler's equation is:

$$L(\mu\text{h}) = \frac{a^2 n^2}{9a + 10\ell} \quad (\text{use inch dimensions}) \quad (3-5.1)$$

This equation provides answers within 1% accuracy for all values of $2a/\ell$ less than 3, and the results will be about 4% low when $2a/\ell = 5$ (short coils).

There are five parameters that can be used to describe an air-core inductor: the coil radius in inches (a), the coil length in inches (ℓ), the number of turns (n), the winding pitch ($p = \ell/n$), and the inductance in microhenries (L). Of this set of five parameters, only four are independent since ℓ , n , and p are interrelated; hence, given any three independent parameters, the fourth independent parameter, and the remaining dependent parameter can be found. For example, L can be calculated given a , ℓ , and n , or a , n , and p .

Wheeler's equation may be algebraically manipulated to yield the other independent variables.

Solving for ℓ given a , n , and L :

$$\ell = \frac{a^2 n^2 - 9a L}{10 L} \quad (3-5.2)$$

Solving for ℓ given n and p :

$$\ell = n \cdot p \quad (3-5.3)$$

Solving for n given a , ℓ , and L :

$$n = \frac{1}{a} \sqrt{L(9a + 10\ell)} \quad (3-5.4)$$

Solving for n given a , p , and L : find quadratic solution of

$$a^2n^2 - 10Lpn - 9aL = 0 \quad (3-5.5)$$

Solving for p given ℓ and n :

$$p = \ell/n \quad (3-5.6)$$

Solving for p given a , n , and L :

$$p = \frac{1}{10n} \left\{ \frac{a^2n^2}{L} - 9a \right\} \quad (3-5.7)$$

Solving for L given a , n , and p :

$$L = \frac{a^2n^2}{9a + 10np} \quad (3-5.8)$$

Solving for a given ℓ , n , and L : find quadratic solution of

$$n^2a^2 - 9La = 10\ell L = 0 \quad (3-5.9)$$

The program uses these equations as follows. The appropriate input keys are assumed to have been executed prior to an output request. Label "A" inputs or outputs the coil radius in inches, a . The input is stored in R0, and Eq. (3-5.9) is used for output.

Label "B" inputs or outputs the number of turns, n . The input is stored in R1, and if p was previously entered, ℓ is calculated using Eq. (3-5.3). For output, Eq. (3-5.5) is used if p , ℓ , and a are specified, otherwise, Eq. (3-5.4) is used.

Label "C" inputs or outputs the coil length, ℓ . For input, the coil length is stored in R2, flag 0 is cleared, and a new p is calculated and stored using Eq. (3-5.6). For output, if p has been previously entered, use Eq. (3-5.3), otherwise use Eq. (3-5.2).

Label "D" inputs or outputs the winding pitch, p . For input, the new pitch is stored in R3, flag 0 is set, and new ℓ is calculated with Eq. (3-5.3). For output, Eq. (3-5.6) is used.

Label "E" inputs or outputs the coil inductance, L , in microhenries. For input, the value is stored in R4. For output, Eq. (3-5.1) is used, and the new inductance value stored.

Label "c" calculates the wire diameter given the wire AWG with heavy insulation. The wire diameter over heavy insulation bears an

exponential relationship to the wire gauge:

$$\text{Diameter (inches)} = k_1 \cdot e^{k_2 \cdot \text{AWG}} \quad (3-5.10)$$

where $k_1 = 0.31373$

and $k_2 = -.109788$

On the first execution of this routine, the constants k_1 and k_2 are stored into R8 and R9 respectively. Flag 2 is initially set after magnetic card reading to indicate constant storage required, and is reset upon test.

Label "d" calculates the AWG of the wire given the diameter over the insulation in inches:

$$\text{AWG} = \frac{1}{k_2} \cdot \ln \left\{ \frac{\text{Diameter}}{k_1} \right\} \quad (3-5.11)$$

Label "e" is used to clear flag 3 to indicate data output desired.

Keys "A" through "E" leave flag 3 cleared after the associated routine finishes, i.e., data output mode is set unless further numeric entry is made.

The routines under keys "d" and "e" do not alter the state of flag 3. For example, one may load the wire AWG, use key "c" to convert to wire diameter, and then use key "D" to load this value as the winding pitch (close wound coils).

Highest coil Q's are generally obtained when the space between the wires equals the wire diameter (pitch equals twice the wire diameter). Callendar's equation [13] can be used to estimate the Q of a coil with this pitch:

$$Q = \frac{\sqrt{\text{freq in Hz}}}{\frac{2.71}{a} + \frac{2.13}{\ell}} \quad (\text{use inch dimensions}) \quad (3-5.12)$$

For RF coils where the skin depth is less than the wire diameter, Callendar's equation is accurate to within a few percent. For close wound coils, the calculated Q will be high by a factor of 1.9.

HP-67 users may want to make the following program changes to make the final number in the display unambiguous. For example, label "C" causes both the number of turns and the coil length to be printed

with the coil length being displayed last. To change the program so only the number of turns is displayed and printed, change lines 122 through 126 of the program as follows:


```
122  RCL3  
123  *  
124  STO2  
125  RCL1  
126  STO8
```

User Instructions

AIR-CORE, SINGLE-LAYER, SOLENOIDAL INDUCTOR DESIGN				
		AWG \rightarrow diam	diam \rightarrow AWG	clear input mode
coil radius a, in	# of turns n	coil length ℓ , in	pitch $p = \ell/n$	inductance L, μh

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card			
2	Select problem type:			
	a) to find L & p given a, n, & ℓ			
	i) load the coil radius	a, in	A	
	ii) load the number of turns	n	B	
	iii) load the coil length	ℓ , in	C	
	iv) calculate the coil inductance		E	L, μh
	v) calculate the winding pitch		D	p, in/T
	b) to find L & ℓ given a, n, & p			
	i) load the coil radius	a, in	A	
	ii) load the number of turns	n	B	
	iii) load the winding pitch	p, in/T	D	
	iv) calculate the coil inductance		E	L, μh
	v) calculate the coil length		C	ℓ , in
	c) to find n & p given a, ℓ , & L			
	i) load the coil radius	a, in	A	
	ii) load a dummy value for n *	1	B	
	iii) load the winding length	ℓ , in	C	
	iv) load desired inductance	L, μh	E	
	v) calculate the # of turns and the winding pitch		B	n, turns p, in/T
	d) to find n & ℓ given a, n, & L			
	i) load the coil radius	a, in	A	
	ii) load the winding pitch	p, in/T	D	
	iii) load desired inductance	L, μh	E	
	iv) calculate the number of turns and the winding length		B	n, turns ℓ , in
	e) to find ℓ & p given a, n, & L			
	i) load the coil radius	a, in	A	
	ii) load the desired number of turns	n	B	
	iii) load the desired inductance	L, μh	E	
	iv) calculate the inductor length **		C	ℓ , in
	v) calculate the winding pitch		D	p, in/T

User Instructions

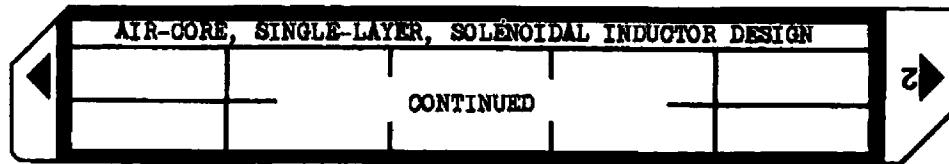

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
2	f) to find a & ℓ given n , p , & L			
	i) load the desired number of turns	n	<input type="button" value="B"/>	
	ii) load the desired winding pitch	p , in/T	<input type="button" value="D"/>	
	iii) load the desired inductance	L , μ h	<input type="button" value="E"/>	
	iv) calculate the coil radius		<input type="button" value="A"/>	a , in
	v) calculate the coil length		<input type="button" value="C"/>	ℓ , in
	g) to find a & p given n , ℓ , & L			
	i) load the desired number of turns	n	<input type="button" value="B"/>	
	ii) load the desired coil length	ℓ , in	<input type="button" value="C"/>	
	iii) load the desired inductance	L , μ h	<input type="button" value="E"/>	
	iv) calculate the coil radius		<input type="button" value="A"/>	a , in
	v) calculate the winding pitch		<input type="button" value="D"/>	p , in/T
3	Go back to any part of step 2, or stop			
4	To convert wire AWG to diameter over heavy (class 2) insulation	AWG	<input type="button" value="f"/> <input type="button" value="C"/>	diam, in
5	To convert wire diameter over heavy insulation to AWG	diam, in	<input type="button" value="f"/> <input type="button" value="D"/>	AWG
6	To clear input mode, i.e., to request output after numeric operations have been performed from the keyboard		<input type="button" value="f"/> <input type="button" value="E"/>	
	Notes:			
	* $p = \ell/n$, a non-zero n is required for proper program operation. The dummy n is replaced with the calculated n under label B.			
	** A negative value for the inductor length means the required inductance cannot be realized with the chosen radius and number of turns. Either increase n or a .			

Example 3-5.1

An air-core coil is to be wound in a $\frac{1}{2}$ inch form using #18 AWG HF wire at a pitch of twice the wire diameter. What number of turns are required for an inductance of 500 nanohenry ($0.5 \mu\text{h}$), and what will the winding length be?

```

.250 GSEr  load coil radius in inches
18.000 GSEc  load wire AWG
0.043 ***  wire diameter over HF insulation

2.000      calculate winding pitch (2 x diam)
      GSED  load winding pitch
.500 GSEr  load required inductance in microhenry
      GSEr  calculate turns and coil length
8.956 ***  number of turns (use 9 turns)
0.776 ***  coil length in inches

```

Example 3-5.2

A 6 turn coil on a 6 inch form is closewound with #4/0 wire. The wire is 0.750 inches over the insulation. What is the coil inductance and length?

```

3.000 GSEr  load the coil radius in inches
6.000 GSEr  load the number of turns
.750 GSED  load winding pitch
      GSEr  calculate inductance
4.500 ***  inductance in microhenries

      GSEr  calculate coil length
4.500 ***  coil length in inches

```

Program Listing I

```

001 *LBLA I/O OF COIL RADIUS, a
002 F3?
003 GT00 jump if numeric entry
004 RCL1
005 X² use quadratic equation
006 ST05 to find a in:
007 9
008 RCL4  $a^2 n^2 - 9aL - 10L^2 = 0$ 
009 X
010 CHS
011 ST06
012 RCL2
013 RCL4
014 X
015 EEX
016 1
017 X
018 CHS
019 ST07
020 GSB9
021 ST00
022 GT08
023 *LBL0
024 ST00
025 RTN
026 *LBLC I/O OF COIL LENGTH,
027 F3?
028 GT00 jump if numeric entry
029 F0?
030 GT01 jump if p entered last
031 RCL0
032 RCL1 calculate and store:
033 X
034 X²
035 RCL4
036 ÷
037 RCL0  $L = \frac{1}{10} \left( \frac{a^2 n^2}{L} - 9a \right)$ 
038 9
039 X
040 -
041 EEX
042 1
043 ÷
044 ST02
045 GT08 goto print and space subr
046 *LBL0
047 CF0 indicate L entered last
048 ST02 store L
049 RCL1
050 ÷ calculate and store
051 ST03  $p = L/n$ 
052 RTN

```

```

053 *LBL1 calculate and store
054 RCL1
055 RCL3  $L = n(L/n)$ 
056 X
057 ST02
058 GT08 goto print and space subr
059 *LBLD I/O OF COIL PITCH, p
060 F3?
061 GT00 jump if numeric entry
062 RCL2
063 RCL1 calculate and store
064 ÷  $p = L/n$ 
065 ST03
066 GT08 goto print and space subr
067 *LBL0
068 ST03 store p
069 RCL1
070 X calculate and store
071 ST02  $L = p \cdot n$ 
072 SF0 indicate p entered last
073 RTN
074 *LBLB I/O OF COIL TURNS, n
075 F3?
076 GT00 jump if numeric entry
077 F0?
078 GT01 jump if p entered last
079 GSB3
080 RCL4 calculate and store n:
081 X
082 JX
083 RCL0  $n = \frac{1}{a} \sqrt{L(9a - 10L)}$ 
084 ÷
085 ST01
086 PRX
087 1/X
088 RCL2
089 X
090 ST03
091 GT08
092 *LBL1 calculate and store n from
093 RCL0 quadratic solution to:
094 X²
095 ST05
096 RCL3
097 RCL4
098 X  $a^2 n^2 - 10Lpn - 9aL = 0$ 
099 EEX
100 1
101 X
102 CHS
103 ST06
104 RCL0
105 RCL4
106 X

```

REGISTERS

0	a	1	n	2	L	3	p	4	L	quadratic	equation	terms	wire AWG	constants
S0		S1		S2		S3		S4		S5	S6	S7	S8	S9
A		B		C		D		E		I				

Program Listing II

NOTE FLAG SET STATUS

107	9	160	*LBL3	9a + 10l calculation subr
108	x	161	RCL0	
109	CHS	162	9	
110	ST07	163	x	
111	GSB9	164	RCL2	
112	ST01	165	EEX	
113	PRTX	166	1	
114	RCL3	167	x	
115	x	168	+	
116	ST02	169	RTN	
117	GT08	170	*LBL6	AWG ← WIRE DIAMETER
118	*LBL0	171	F2?	constant initialization
119	ST01	172	GSB2	needed?
120	F0?	173	RCL9	
121	GT00	174	x	
122	RTN	175	e ^x	diameter = k ₁ · e ^{k₂ · AWG}
123	*LBL0	176	RCL8	
124	RCL3	177	x	
125	x	178	GT08	
126	ST02	179	*LBL4	WIRE DIAMETER ← AWG
127	RTN	180	F2?	constant initialization
128	*LBL0	181	GSB2	needed?
129	F3?	182	RCL8	
130	GT00	183	÷	
131	RCL0	184	LN	
132	RCL1	185	RCL9	AWG = $\frac{1}{k_2} \ln \left\{ \frac{\text{diameter}}{k_1} \right\}$
133	x	186	÷	
134	x2	187	INT	
135	GSB3	188	GT08	
136	÷	189	*LBL2	constant initialization
137	ST04	190	.	
138	*LBL8	191	3	
139	PRTX	192	1	
140	SPC	193	3	
141	RTN	194	0	
142	*LBL0	195	4	
143	ST04	196	ST08	store k ₁
144	RTN	197	R4	recover x register
145	*LBL9	198	.	
146	RCL5	199	1	
147	ST=6	200	0	
148	ST=7	201	9	
149	2	202	7	
150	ST=6	203	3	
151	RCL6	204	3	
152	CHS	205	CHS	
153	ENT↑	206	ST09	store k ₂
154	x2	207	R4	recover x register
155	RCL7	208	RTN	
156	-	209	*LBL5	CLEAR INPUT MODE
157	JX	210	CF3	
158	+	211	RTN	
159	RTN			

NOTE:

Print statements are located at steps 086 and 139 and may be changed to R/S if desired.

NOTE FLAG SET STATUS

LABELS					FLAGS	SET STATUS		
A I/O coil radius	B I/O coil length	C I/O # of turns	D I/O pitch	E I/O inductance	F entered last	FLAGS	TRIG	DISP
a	b	c	d	e	1	ON OFF		
0 local label	1 local label	2 constant storage	3 9a + 10l	4	2 store coefficients	0	DEG	FIX
5	6	7	8 print & space	9 quadratic solution	3 data entry	1	GRAD	SCI
						2	RAD	ENG
						3		n 3

PROGRAM 3-6 AIR-CORE MULTILAYER INDUCTOR DESIGN.

Program Description and Equations Used

This program uses a modification of Bunet's formula [11], Eq. (3-6.1), to design air-core, multilayer solenoidal inductors (inch dimensions).

$$L (\mu h) = \frac{a^2 n^2}{9a + 10\ell + 8.4c + 3.2 c \ell / a} \quad (3-6.1)$$

The coil dimensions are shown in Fig. 3-6.1, and the range of usefulness of the program can be ascertained from Table 3-6.1.

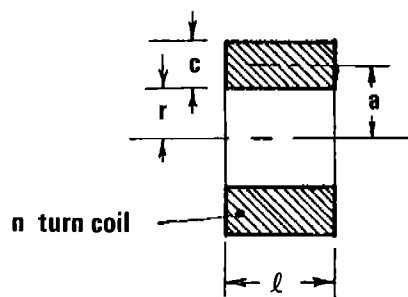


Figure 3-6.1 Multilayer coil dimensions.

Table 3-6.1 Accuracy estimates for Bunet's equation.

c/a ratio	2a/l ratio for 1% accuracy	other accuracies 2a/l %	
1/20	≤ 3	5	4
1/5	≤ 5	10	2
1/2	≤ 2	5	3
1/1	≤ 1.5	5	5

The modification to Eq. (3-6.1) consists of replacing the mid-coil radius, a , by the inner radius, r :

$$a = r + \frac{c}{2} \quad (3-6.2)$$

The coil is generally wound on a coil form, hence, r and ℓ are known from the coil form dimensions. The coil mid-radius, a , is dependent upon the coil buildup, and is generally not known at the inception of the design.

If the wire and insulation occupy a box as shown in Fig. 3-6.2,

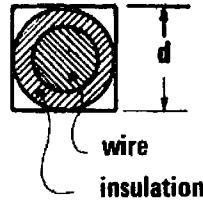


Figure 3-6.2 Wire cross-section.

then the total area occupied by n turns of this wire would be:

$$A_{\text{total}} = n \cdot d^2 \quad (3-6.3)$$

This area is also expressible in terms of the coil dimensions:

$$A_{\text{total}} = c \cdot \ell \quad (3-6.4)$$

Hence,

$$n \cdot d^2 = c \cdot \ell \quad (3-6.5)$$

or

$$c = \frac{n \cdot d^2}{\ell} \quad (3-6.6)$$

A fifth order polynomial in n may be derived to yield the number of turns of wire with diameter d , given the required inductance, L , the coil inner radius, r , and the coil width, ℓ . Taking Eq. (3-6.1), multiplying both sides by the denominator term, and clearing fractions yields:

$$a^3 n^2 - L \{ 9a^2 + (10\ell + 8.4c) a + 3.2c \ell \} = 0 \quad (3-6.7)$$

Substituting Eq. (3-6.2) for a , and Eq. (3-6.6) for c , and collecting terms in like powers of n results in the following 5th order polynomial equation:

$$f(n) = An^5 + Bn^4 + Cn^3 + Dn^2 - En - F = 0 \quad (3-6.8)$$

$$A = \left(\frac{d^2}{2\ell} \right)^3 \quad (3-6.9)$$

$$B = 3r \left(\frac{d^2}{2\ell} \right)^2 \quad (3-6.10)$$

$$C = 3r^2 \left(\frac{d^2}{2\ell} \right) \quad (3-6.11)$$

$$D = r^3 - \left(\frac{d^2}{2\ell} \right)^2 (25.8 L) \quad (3-6.12)$$

$$E = L \left\{ \frac{d^2}{2\ell} (34.8r + 10\ell) + 3.2d^2 \right\} \quad (3-6.13)$$

$$F = rL (10\ell + 9r) \quad (3-6.14)$$

The Newton-Raphson iterative procedure described in Program 1-3 is used to find the largest positive real root for n in Eq. (3-6.8). If the initial guess for n is larger than the largest root, the method will converge to the largest root when the function is a polynomial as in the present case. An initial guess of 10000 turns is used. If a larger number of turns is expected, the user may want to increase the initial guess which is located at step 084 of the program.

If r , c , ℓ , and L are specified, then the solution for n becomes somewhat simpler. Since r and c are both known, a can be calculated from Eq. (3-6.2). With this calculation, all parameters except n are known in Eq. (3-6.1), and n becomes:

$$n = \frac{1}{a} \left\{ L(9a + 10 + c(8.4) + 3.2\ell/a) \right\}^{\frac{1}{2}} \quad (3-6.15)$$

Once n has been calculated, the wire diameter, d , can be calculated from Eq. (3-6.6) as given below:

$$d = \sqrt{\frac{c\ell}{n}} \quad (3-6.16)$$

So far, the two cases for the number of turns have been derived. Likewise, there are two cases for the calculation of L . Given r , ℓ , c , and n , Eqs. (3-6.2) and (3-6.1) may be used to calculate L . If the wire diameter, d , had been specified instead of the coil thickness, c , then

Eqs. (3-6.6) and (3-6.1) are used to calculate L.


Program constants

Since all program steps were used to code the program equations, no room remains for the program constants. These constants are recorded on another magnetic card, and are loaded after the program magnetic card loading. Load the following registers, and record the data on both sides of the data card (2 WDATA commands):

8.4 → R7

3.2 → R8

10. → R9

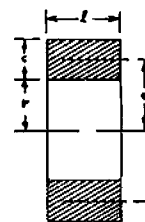

AIR-CORE MULTILAYER INDUCTOR DESIGN				
coil inner radius, r	wire diam, d	winding length, ℓ	number of turns, n	inductance in μh, L
	winding thickness, c			

[illegible]

Example 3-6.1

Find the number of turns of #24 HF wire (0.0224 inches over insulation) to be wound on a bobbin that has a 0.3 inch inner radius and is 0.5 inch wide to obtain an inductance of 200 microhenries. Also find the coil thickness.

```

.30 GSEH  load bobbin inner radius (in)

.0224 GSEK  load wire diameter over insulation (in)

.50 GSEI  load bobbin width (in)

200.00 GSEE  load inductance required (μh)

      GSED  calculate # of turns & coil thickness*
122.65 ***  number of turns (use 123)
0.1231 ***  coil thickness, inches

```

Example 3-6.2

Calculate the inductance of an 18 turn coil of 4/0 wire with 6 turns per layer wound on a 6 inch diameter form. 4/0 wire is 0.75 inch over the insulation.

```

3.00 GSEH  load coil inner radius (in)

.75 GSEK  load wire diameter over insulation (in)

6.00      calculate coil width:
4.50 ***  coil turns per layer x thickness per turn
      GSEC  load coil width

18.00 GSED  load number of turns

      GSEE  calculate inductance
50.6345 *** inductance in microhenries

```

* Requires about a minute to compute.

0	1	2	3	4	5	6	7	8	9
a	r	c	ℓ	L	n	d	8.4	3.2	10
S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
A	B	C	C	D	E	E	I	F	

113	RCLB		169	GT09	jump if input
114	4		170	F0?	if winding thickness loaded,
115	x		171	GT01	skip thickness calculation
116	+		172	RCL6	
117	x		173	X ²	
118	RCLC		174	RCL3	calculate and store
119	3		175	÷	thickness:
120	x		176	RCL5	
121	+		177	x	$c = nd^2/l$
122	x		178	ST02	
123	RCLD		179	*LBL1	
124	ENT↑		180	GSB3	
125	+		181	1/X	calculate and store
126	+		182	RCL0	inductance:
127	x		183	RCL5	
128	RCLC		184	x	$L = \frac{a^2 n^2}{9a + 10l + 8.4c + 3.2 cl/a}$
129	-		185	X ²	
130	ST=2	calc & store $f(n_1)/f'(n_1)$	186	x	
131	RCL2	apply correction:	187	ST04	
132	ST-5	$n_{i+1} = n_i - f(n_1)/f'(n_1)$	188	*LBL2	print and space subroutine
133	ABS		189	DSP4	
134	.	test for loop exit	190	PRTX ←	can be R/S statement
135	1		191	DSP2	
136	X≤Y?		192	*LBL9	OF3 and space subroutine
137	GT08		193	CF3	
138	RCL6		194	SPC	
139	X ²		195	RTN	
140	RCL5	can be R/S statement	196	*LBL3	inductance factor
141	PRTX	print n	197	RCL1	calculation subroutine
142	x		198	RCL2	
143	RCL3	calculate, print and store	199	2	calculate and store:
144	÷	coil thickness, c:	200	÷	$a = r + c/2$
145	ST02		201	+	
146	GT02	$c = nd^2/l$	202	ST00	
147	*LBL0	input storage routine for	203	9	
148	ST05	number of turns input	204	x	
149	GT09	goto OF3, space and return	205	RCL3	calculate:
150	*LBL1	calculate the number of turns	206	RCL9	
151	GSB3	given r, l, c, and L	207	GSB4	$9a + 10l + 8.4c + 3.2 \frac{cl}{a}$
152	RCL4		208	RCL7	
153	x		209	RCL8	
154	JX	$n = \frac{1}{a} \left\{ L(9a + 10l + 8.4c + 3.2 \frac{cl}{a}) \right\}^{1/2}$	210	RCL0	
155	RCL0		211	÷	
156	÷		212	RCL3	
157	ST05		213	GSB4	
158	PRTX ←	can be R/S statement	214	RCL2	
159	1/X		215	*LBL4	x, + subroutine
160	RCL2		216	x	
161	RCL3		217	+	
162	GSB5		218	RTN	
163	JX		219	*LBL5	x, x subroutine
164	ST06		220	x	
165	GT02		221	x	
166	*LBL6	I/O OF INDUCTANCE	222	RTN	
167	ST04	store inductance entry			
168	F3?				

PROGRAM 3-7 CYLINDRICAL SOLENOID DESIGN.

Program Description and Equations Used

This program provides the coil winding particulars and the coil electrical characteristics given the specifications for a cylindrical solenoid. These specifications are:

- 1) Minimum plunger attractive force in pounds (F),
- 2) Initial air gap length in inches (ℓ_{air}),
- 3) Maximum flux density in the air gap (B_{max}) in gauss,
- 4) Maximum coil current density in amperes/in² (Δ),
- 5) Maximum coil buildup, or thickness, (w) in inches,
- 6) Coil excitation voltage (E) in volts, or current (I) in amperes,
- 7) Optionally, the magnetic path area (A_{iron}) in inches², the magnetic path length (ℓ_{iron}) in inches, and the magnetic permeability (μ).

The length of the magnetic path is assumed to be zero unless step 7 is exercised.

The characteristics that the program calculates are:

- 1) Plunger diameter in inches (D_p),
- 2) Number of turns in the coil (N),
- 3) Coil wire AWG using class 2 or heavy insulation,
- 4) Coil length in inches (ℓ_{coil}),
- 5) Coil inductance in henries (L),
- 6) Coil resistance in ohms (R),
- 7) Coil power dissipation in watts (P),
- 8) Actual B in the core and in the air-gap, and
- 9) Actual F.

With the maximum flux density in the air gap and plunger attractive force specified, the area of the air gap can be calculated from:

$$A_{\text{air}} = F \cdot k_1 / (B_{\text{air}}^2) \quad (3-7.1)$$

where k_1 is the constant of proportionality relating flux density in the air gap to pressure in pounds/in²

$$k_1 = 1.73 \times 10^6 \quad (3-7.2)$$

If the plunger area is assumed equal to the air gap area, the plunger diameter can be calculated using:

$$D_p = 2 \cdot \left(A_{\text{air}} / \pi \right)^{\frac{1}{2}} \quad (3-7.3)$$

Once the plunger diameter is known, then a value for the winding thickness may be loaded into the program. The smallest dimension of the winding should not exceed 3 inches to allow adequate thermal conduction for the heat generated with the coil, thus avoiding high internal coil temperatures. If the program calculates a short coil length, then the thickness is not restrained. A long coil restrains the coil thickness to 3 inches or less. Several iterations of the program solution may be required until satisfactory values for coil length and width (thickness) are found.

Given the excitation voltage, inverse current density in the coil (M) in circular mils per ampere, and the coil dimensions as defined by Fig. 3-7.1, the number of turns required is given by Eq. (3-7.4). The derivation of this equation is given later.

$$N = E \cdot M / (\pi (D_p + w)) \quad (3-7.4)$$

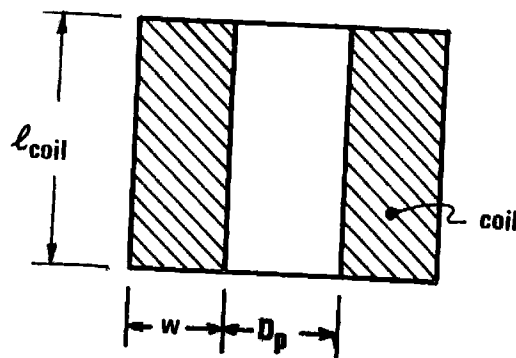


Figure 3-7.1 Solenoid coil dimensions.

If the coil is excited with a current, then the number of turns is:

$$N = (NI)/I \quad (3-7.5)$$

where NI is the coil ampere-turns which is calculated from B_{\max} later.

The cross-sectional area of the coil ($w \cdot \ell_{\text{coil}}$) consists of current carrying wire and noncurrent carrying insulation and space. The shape factor (sf) is the ratio of the current carrying area to the total area of the coil. If the wire plus insulation is assumed to occupy a square with side d as shown in Fig. 3-6.2, and the winding cross-section is occupied by N of these squares, then the shape factor is:

$$sf = \frac{\pi}{4} \left\{ \frac{\text{diameter of bare wire}}{d} \right\}^2 \quad (3-7.6)$$

The diameters of both the bare wire and the wire with insulation bear exponential relationships to the wire AWG as given by Eq. (3-2.1). Substituting these relationships into Eq. (3-7.6) yields:

$$sf = \frac{\pi}{4} \left\{ \frac{a'}{a} e^{\text{AWG}(b' - b)} \right\}^2 \quad (3-7.7)$$

where

$$\frac{\pi}{4} \left\{ \frac{a'}{a} \right\}^2 = .8418900745 \quad (3-7.8a)$$

$$2(b' - b) = -1.21690938 \times 10^{-2} \quad (3-7.8b)$$

The coil has N wires each carrying in current, I ; thus the current density in the coil is:

$$\Delta = (NI)/(sf \cdot \ell_{\text{coil}} \cdot w) \quad (3-7.9)$$

where Δ is specified by the user through M :

$$k_2 = M \cdot \Delta = (\text{cir-mils/A})(\text{A/in}^2) = (4 \times 10^6)/\pi \quad (3-7.10)$$

Solving for the coil length between Eqs. (3-7.9) and (3-7.10) yields:

$$\ell_{\text{coil}} = (NI \cdot M)/(sf \cdot k_2 \cdot w) \quad (3-7.11)$$

The coil ampere-turns, NI , is calculated from B_{\max} using the "Ohm's law" of magnetics:

$$\text{MMF} = \phi \cdot \mathcal{R} \quad (3-7.12)$$

where ϕ is the flux and is continuous throughout the magnetic and air paths and is analogous to electric current. The reluctance, \mathcal{R} , is the magnetic resistance, and the magnetomotive force, MMF, is the magnetic "voltage" source. The total reluctance is the sum of the individual reluctances making up the magnetic circuit and the MMF is proportional to the current in the coil:

$$\text{MMF} = 0.4\mu NI \quad (3-7.13a)$$

$$\mathcal{R} = \sum_i \frac{\ell_i}{\mu_i \cdot A_i} \quad (3-7.13b)$$

The electromagnet model used by this program has two sections, the magnetic path, and the air gap. Usually the air gap reluctance is the dominant term. Noting that the relative permeability for air is unity, and

$$\phi = B_{\text{iron}} \cdot A_{\text{iron}} = B_{\text{max}} \cdot A_{\text{air}} \quad (3-7.14)$$

then solving Eq. (3-7.12) for NI yields:

$$NI = \frac{B_{\text{max}} A_{\text{air}}}{A_{\text{iron}}} \left\{ \frac{\ell_{\text{iron}}}{\mu_{\text{iron}}} + \ell_{\text{air}} \frac{A_{\text{iron}}}{A_{\text{air}}} \right\} \frac{k_3}{0.4\pi} \quad (3-7.15)$$

where $k_3 = 2.54$, the inch to centimeter conversion ratio. The iron area, A_{iron} , refers to the smallest iron area, which may not be next to the air gap.

An iterative method is required to find the wire AWG and coil length. An initial shape factor of 0.5 is assumed, the coil length is obtained using Eq. (3-7.11). The wire diameter over insulation is obtained using

$$d = (w \cdot \ell_{\text{coil}} / N)^{\frac{1}{2}} \quad (3-7.16)$$

The wire AWG is obtained from the wire diameter over insulation from Eq. (3-2.1), and a new shape factor calculated from the AWG using Eq. (3-7.7). The new shape factor replaces the old shape factor and the calculations run again. The iteration is terminated when the new and old shape factors agree within .001.

The coil physical dimensions and number of turns have now been

determined, and other electrical characteristics can be calculated.

$$L = \frac{0.4\pi \cdot N^2 \cdot A_{\text{iron}} \cdot k_3 \times 10^{-8}}{\frac{\ell_{\text{iron}}}{\mu_{\text{iron}}} + \ell_{\text{air}} \frac{A_{\text{iron}}}{A_{\text{air}}}} \quad (3-7.17)$$

$$R = (R/\ell) (\text{mean turn}) (N) \quad (3-7.18)$$

where R/ℓ is obtained from:

$$R/\ell, (\text{ohms/inch}) = k_4 \cdot e^{k_5 \cdot \text{AWG}} \quad (3-7.19)$$

hence,

$$R = N \cdot \pi \cdot (D_p + w) \cdot k_4 \cdot e^{k_5 \cdot \text{AWG}} \quad (3-7.20)$$

For the coil temperature at 60°C, the constants are:

$$\pi \cdot k_4 = 2.9185212367 \times 10^{-5}$$

$$k_5 = 0.2317635483$$

If the coil excitation is a constant voltage, then the coil current will have to be recalculated due to the downward rounding of the wire size to the nearest integral value:

$$I = \frac{E}{R} \quad (3-7.21)$$

The power dissipated in the coil is:

$$P = I^2 R \quad (3-7.22)$$

If constant voltage excitation is used, the peak flux density (B_{max}) and initial plunger attractive force will be slightly larger than the initial values again due to the downward rounding of the wire AWG. The larger wire will have lower resistance causing higher coil current and a higher NI product. Equations (3-7.15) and (3-7.1) are rearranged and used to find B_{iron} and F .

$$B_{\text{iron}} = \frac{0.4\pi NI}{\left\{ \frac{\ell_{\text{iron}}}{\mu_{\text{iron}}} + \ell_{\text{air}} \frac{A_{\text{iron}}}{A_{\text{air}}} \right\} k_3} \quad (3-7.23)$$

$$F = \frac{B_{\max}^2 \cdot A_{\text{air}}}{k_1} = \frac{(B_{\text{iron}} \cdot A_{\text{iron}})^2}{k_1 \cdot A_{\text{air}}} \quad (3-7.24)$$

In addition to the program card, a data card is necessary to load the registers with these constants:

μ_0 default:	500	→	R ₅
B_{\max} default:	15000	→	R ₆
Initial shape factor:	0.5	→	R _E
$(\pi/4)(a'/a)$:	0.8418900745	→	S ₀
$2(b' - b)$:	$-1.216909380 \times 10^{-2}$	→	S ₁
a:	$3.130387015 \times 10^{-1}$	→	S ₂
b:	$-1.097333787 \times 10^{-1}$	→	S ₃
$\pi \cdot k_4$:	$2.985212367 \times 10^{-5}$	→	S ₄
k_5 :	$2.317635483 \times 10^{-1}$	→	S ₅
k_3 :	2.54	→	S ₆
$k_2 = \frac{4}{\pi} \times 10^6$:	1.273239545×10^6	→	S ₇
k_1 :	1.73×10^6	→	S ₈
M default:	1000	→	S ₉

If the user wants to work in centimeter units instead of inch units, then a different set of constants can be loaded. All constants are the same except for the following:

a:	$7.951183018 \times 10^{-1}$	→	S ₂
$\pi \cdot k_4$:	$1.175280459 \times 10^{-5}$	→	S ₄
k_3 :	1.0	→	S ₆
k_2 :	5.012754114×10^5	→	S ₇
k_1 :	1.11613×10^7	→	S ₈


The inverse current density, M, is now in hybrid units. The circular-mils/A must be multiplied by 2.54 before entry, and the current density, Δ , is in A/cm². The plunger attractive force is still in pounds. If this force is desired in kilograms, change k_1 as follows:

k_1 :	2.46064×10^7	→	S ₈
---------	-----------------------	---	----------------

The HP-67 user may wish the program to stop at data output points rather than executing a 5 second "print" halt. To cause the program to

stop at the data output points, change the "print" statements to "R/S" statements at the following line numbers: 047, 084, 131, 144, 160, 176, 180, 185, and 194.

User Instructions

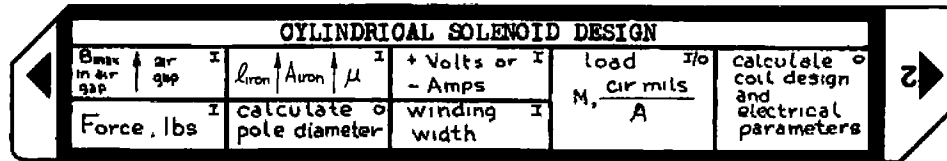

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card and both sides of data card			
2	Load force required (in pounds) at maximum air gap (plunger all the way out)	F	A	
3	Load maximum flux in the iron (gauss) and the air gap in inches	B _{max} l _{air}	ENT f A	
4	Optional, load magnetic circuit parameters: a) load magnetic path length b) load magnetic path minimum area c) load relative permeability If this step is not executed, the program will use A _{iron} = A _{air} and l _{iron} = 0	l _{iron} , in A _{iron} , in ² μ	ENT ENT f B	
5	Calculate pole diameter To change the pole diameter, change B _{max} , a larger B _{max} will result in a smaller pole. B _{max} is material dependent, and generally should not exceed 15000 gauss.		B	pole diameter in inches
6	Load winding thickness	w, in	C	
7	Load excitation voltage or current a) excitation voltage b) excitation current (note neg value)	E, V -I, A	f O f O	
8	Load a value for M, the inverse coil current density in circular-mils per ampere. If no value is loaded, a default value of 1000 will be used. Execution of this step without numeric entry causes currently stored value to be printed and displayed.	M	f D	M Δ

Example 3-7.1

Figure 3-7.2 shows a plunger-type, iron-clad cylindrical solenoid. Design the solenoid to have a 1 inch travel and exert an initial pull of 500 pounds when connected to a 55 volt dc source. The initial flux density in the iron shall be 7000 gauss, and the coil inverse current density shall be 700 circular-mils/A. Assume all the reluctance to be in the air gap.

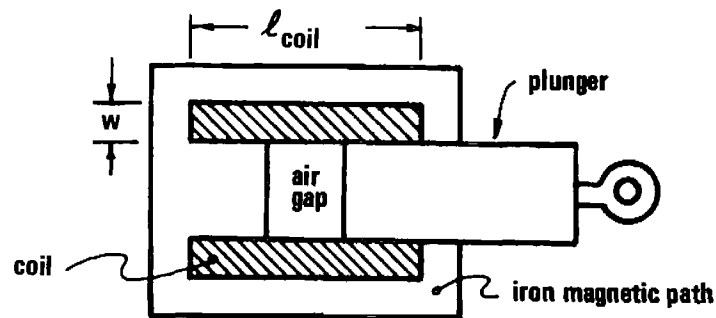


Figure 3-7.2 Plunger-type, iron-clad cylindrical solenoid.

500.00	G524	load initial force required in pounds (F)
7000.00	ENT4	load maximum B field in gauss (B_{\max})
1.00	G5E4	load l_{air}
	G556	calculate plunger diameter required (D_p)
4.74	***	plunger diameter in inches
3.00	G5B0	load winding width in inches (w)
55.00	G5B0	load excitation voltage in volts (E)
700.00	G5B0	load inverse current density, M, in cir-mils/A
700.00	***	M
1915.51	***	Δ , A/in ²
	G5B6	calculate coil design and electrical parameters
1563.00	***	N, the number of turns
12.00	***	AWG of wire with heavy or class 2 insulation
3.57	***	coil length in inches (l_{coil})
1.41	***	coil inductance in henries (L)
5.90	***	coil resistance in ohms (R)
512.43	***	coil power dissipation in watts (P)
7296.69	***	actual maximum flux density in the iron
7296.69	***	B_{\max} , the flux density in the air gap
543.28	***	F, the plunger attractive force actually achieved

Example 3-7.2

A small solenoid is needed which has 0.050 inch travel, exerts an initial pull of 5 pounds, and is used intermittently with a 0.10 duty cycle. The coil excitation current is 3 A, and an initial flux density of 6000 gauss is to be used. Because of the intermittent duty cycle, an M of 100 cir-mils/A is used. The magnetic path is 1.5 inches long, has a cross-sectional area of 0.4 inch², and has a relative permeability of 500. Investigate the solenoid design with and without consideration for the magnetic path reluctance. A much more thorough analysis can be done with Program 3-8.

```

5.000 GSE+ load initial force required in pounds (F)
6000.000 ENT1 load maximum flux density in gauss ( $B_{\max}$ )
.050 GSE+ load initial air gap in inches ( $\ell_{\text{air}}$ )
GSE+ calculate plunger diameter in inches ( $D_p$ )
0.553 *** D
      P
.250 GSE+ load winding width in inches (w)
-3.000 GSE+ load excitation current in A (-I)
100.000 GSED load inverse current density in cir-mils/A (M)
100.000 *** M
12732.395 ***  $\Delta$ , A/inch2

GSE+ calculate coil design etc. without considering iron path
202.000 *** the number of turns (N)
25.000 *** AWG of coil wire with heavy insulation
0.308 *** coil length in inches ( $\ell_{\text{coil}}$ )
0.006 *** coil inductance in henries (L)
1.590 *** coil resistance in ohms (R)
14.311 *** coil power dissipation in watts (P)
5996.237 *** maximum flux density in the iron, gauss
5996.237 ***  $B_{\max}$ , maximum flux density in the air gap, gauss
4.994 *** actual initial force, F, in pounds

```

Rerun program with magnetic (iron) path considered

```

1.500 ENT1 load magnetic path length in inches
.400 ENT1 load magnetic path area in inches2
500.000 GSE+ load relative magnetic permeability

GSE+ calculate coil design and electrical parameters
209.000 *** N
25.000 *** AWG
0.319 ***  $\ell_{\text{coil}}$ 
0.006 *** L
1.645 *** R
14.807 *** P
3597.060 *** B in iron area defined
5988.202 *** B in air gap and in iron pole pieces
4.980 *** F

```

Derivation of Equations Used. The number of coil turns can be calculated from the applied voltage, the desired inverse current density, and the coil inner diameter and thickness. Conveniently, copper has a resistance of 1 ohm per circular mil per inch of length at 60°C; therefore, with a uniform coil temperature of 60°C, the wire resistance is:

$$R = \frac{\ell_w}{M} \quad (3-7.24)$$

where ℓ_w is the winding wire length in the coil in inches, and m is the wire cross-sectional area in circular mils. If M is defined as the inverse current density in circular-mils/A, then the cross-section of a wire carrying a current I is:

$$m = M \cdot I \quad (3-7.25)$$

Since

$$R = \frac{E}{I}, (\text{Ohm's law}) \quad (3-7.26)$$

then

$$\frac{E}{I} = \frac{\ell_w}{M \cdot I} \quad (3-7.27)$$

Rearranging Eq. (3-7.27) and cancelling I yields:

$$E = \frac{\ell_w}{M} \quad (3-7.28)$$

The winding wire length can be found by multiplying the mean turn length by the number of turns:

$$\ell_w = N \cdot \pi \cdot (D_p + w) \quad (3-7.29)$$

where Fig. 3-7.1 defines the coil dimensions D_p and w . Substituting Eq. (3-7.29) into Eq. (3-7.28) and solving for N yields:

$$N = \frac{E \cdot M}{\pi(D_p + w)} \quad (3-7.30)$$

The best reference on the subject known to the author is rather old [47] since it was first published in 1924.

001	*LBLA	LOAD FORCE REQUIRED	056	X	
002	STO7		057	RCL3	
003	RTN		058	=	calculate and store NI
004	*LBLB	LOAD $B_{max} \uparrow l_{air}$	059	GSB9	using Eq. (3-7.15)
005	STO5		060	=	
006	R4		061	STO4	
007	STO8		062	RCL9	
008	GT05	goto CF3 and return subr	063	X<0?	test for current excitation
009	*LBLB	CALCULATE POLE DIAMETER, D_p	064	GT00	
010	RCL7		065	P2S	voltage excitation:
011	RCL8		066	RCL9	calculate the number of
012	X2		067	P2S	turns using Eq. (3-7.4):
013	=		068	X	
014	P2S	$A_{air} = \frac{F \cdot k_1}{B_{air}^2}$	069	RCL0	
015	RCL8		070	RCL0	
016	P2S		071	+	$N = \frac{E \cdot M}{\pi(D_p + w)}$
017	X		072	Pi	
018	STO6	store air gap area	073	X	
019	FI?	minimum magnetic area equals	074	=	
020	STO3	airgap area if flag 1 is set	075	GT01	
021	4		076	*LBL0	current excitation, calculate
022	X		077	RCLA	the number of turns using
023	Pi	$D_p = \sqrt{\frac{4 \cdot A_{air}}{\pi}}$	078	X2Y	Eq. (3-7.5):
024	=		079	=	$N = (NI)/I$
025	JX		080	CHS	
026	STO0	store pole diameter	081	*LBL1	calculate, store and print
027	GT04	goto prt, spe, & CF3 subr	082	INT	the integral number of turns
028	*LBLB	LOAD $l_{iron} \uparrow A_{iron} \uparrow \mu$	083	STO1	
029	CF1	indicate magnetic path used	084	PRTX	
030	STO4		085	*LBL7	iteration loop start
031	R4		086	RCLA	calculate and store coil
032	STO3	store data	087	RCL6	length using Eq. (3-7.11):
033	R4		088	=	
034	STO2		089	RCL0	
035	RTN		090	=	
036	*LBLC	LOAD WINDING WIDTH, w	091	P2S	$l_{coil} = \frac{NI \cdot M}{sf \cdot k_z \cdot w}$
037	STO6		092	RCL9	
038	RTN		093	X	
039	*LBLC	LOAD COIL EXCITATION,	094	RCL7	
040	STO9	+E, or -I	095	P2S	
041	GT05	goto CF3 and return subr	096	=	
042	*LBLD	I/O OF CIRCULAR-MILS/AMP, M	097	STO1	
043	P2S	interchange registers	098	RCL1	calculate wire diameter over
044	F3?	store input if present	099	1/X	insulation using Eq. (3-7.16)
045	STO9		100	RCL0	
046	RCL9	recall and print M	101	X	
047	PRTX		102	RCL1	$d = \sqrt{\frac{w \cdot l_{coil}}{N}}$
048	RCL7	calculate and print Δ :	103	X	
049	X2Y	$\Delta = \frac{M}{k_z}$	104	JX	
050	=		105	P2S	
051	P2S		106	RCL2	calculate and store wire AWG
052	GT04	goto prt, spe, & CF3 subr	107	=	using Eq. (3-2.1)
053	*LBLB	CALCULATE MAIN OUTPUT	108	LN	
054	RCL8		109	RCL3	$AWG = \frac{1}{b} \ln \left\{ \frac{\text{wire diameter}}{a} \right\}$
055	RCL6		110	=	

REGISTERS

0	w	1	l_{coil}	2	l_{iron}	3	A_{iron}	4	μ	5	l_{air}	6	A_{air}	7	F	8	B_{max}	9	+ volts or - amps
S0	$\frac{\pi}{4} \left(\frac{a'}{a} \right)^2$	S1	$2(b' - b)$	S2	a	S3	b	S4	$\pi \cdot k_4$	S5	k_5	S6	$k_3 = 2.54$	S7	$k_2 = \frac{4 \cdot 10^6}{\pi}$	S8	$k_1 = 1.73 \cdot 10^6$	S9	M
A	NI, I	B	AWG	C	R	D	D_p	E	sf	F	N								

111	STOE		166	*LBL0	calculate and print coil power dissipation using Eq. (3-7.21):
112	RCL1	calculate shape factor using Eq. (3-7.7):	167	ABS	
113	x		168	STOA	
114	e ^x		169	X ²	
115	RCL0		170	RCLC	P = I ² R
116	P ² S	$sf = \frac{\pi}{4} \left(\frac{a'}{a} \right)^2 e^{AWG \cdot 2(b'-b)}$	171	x	
117	x		172	PRTX	
118	RCLC	recall old sf and store new sf	173	GSB9	calculate and print new B _{iron} using Eq. (3-7.22):
119	X ² Y		174	RCLA	
120	STOE		175	x	$B_{iron} = \frac{0.4\pi NI/k_3}{\frac{l_{iron}}{\mu_{iron}} + \frac{l_{air} \cdot A_{iron}}{A_{air}}}$
121	-		176	RCL1	
122	ABS		177	x	
123	EEX	test for loop exit	178	PRTX	
124	CHS		179	RCL3	calculate and print:
125	3		180	x	
126	X ² Y?		181	RCL6	$B_{max} = \frac{B_{iron} \cdot A_{iron}}{A_{air}}$
127	GT0?		182	÷	
128	RCLC		183	PRTX	
129	INT	print & store integral AWG	184	X ²	calculate and print new F using Eq. (3-7.23):
130	STOB		185	RCL6	
131	PRTX		186	x	
132	RCL1	recall and print the number of turns	187	P ² S	$F = \frac{B_{max}^2 \cdot A_{air}}{k_1}$
133	PRTX		188	RCL8	
134	SF2	indicate k ₃ on top	189	P ² S	
135	GSB9	calculate and print inductance using Eq. (3-7.17)	190	÷	
136	RCL1		191	*LBL4	print, spc, CF3 subroutine
137	X ²		192	PRTX	
138	x		193	SPC	
139	RCL3	$L = \frac{0.4\pi \cdot N^2 \cdot A_{iron} \cdot k_3 \cdot 10^{-8}}{\frac{l_{iron}}{\mu_{iron}} + \frac{l_{air} \cdot A_{iron}}{A_{air}}}$	194	*LBL5	CF3 and return subroutine
140	x		195	CF3	
141	EEX		196	RTN	
142	0		197	*LBL9	magnetics subroutine to calculate:
143	÷		198	RCL2	
144	PRTX		199	RCL4	
145	RCLB	calculate and print resistance using Eq. (3-7.20)	200	÷	
146	P ² S		201	RCL5	
147	RCL5		202	RCL3	$\frac{0.4\pi}{\frac{l_{iron}}{\mu_{iron}} + \frac{l_{air} \cdot A_{iron}}{A_{air}}} \cdot \frac{k_3(F2+1)}{k_3(F2+0)}$
148	x		203	x	
149	e ^x		204	RCL6	
150	RCL4		205	÷	
151	P ² S	$R = N\pi(Dp+w)k_4 e^{k_5 \cdot AWG}$	206	+	
152	x		207	1/X	
153	RCLD		208	7	} generates 0.4π in 3 steps
154	RCL0		209	2	
155	+		210	D+R	
156	x		211	x	
157	RCL1		212	P ² S	
158	x		213	RCL6	
159	STOC		214	P ² S	
160	PRTX		215	F2?	
161	RCL9		216	1/X	
162	X ² 0?	test for current excitation	217	÷	
163	GT00		218	RTN	
164	RCLC	calculate current using Ohm's law			
165	÷				

LABELS					FLAGS	SET STATUS		
A load F	B calc Dp	C load w	D load M	E calc coil & elect params	0	FLAGS	TRIG	DISP
a B _{max} t _{air} gap	b l _{iron} t _{air} t _M	c load tE, -I	d	e	1 magnetic path data not loaded	ON OFF	DEG	FIX
0 local label	1 local label	2	3	4 out put routine	2 conversion order	1	GRAD	SCI
5 CF3, RTN	6	7 sf iteration routine	8	9 subroutine	3 data entry	2	RAD	ENG
						3		n 2

					NOTE FLAG SET STATUS			
--	--	--	--	--	----------------------	--	--	--

PROGRAM 3-8 CYLINDRICAL SOLENOID ANALYSIS.

Program Description and Equations Used

This program analyzes a cylindrical coil solenoid, or other magnetic circuits having many parts of varying reluctance. The information required to run the program is as follows:

- 1) The air gap in inches (ℓ_{air}),
- 2) The number of turns in the coil (N),
- 3) The AWG of the coil wire,
- 4) The length of the coil in inches (ℓ_{coil}),
- 5) The coil inner diameter in inches (ID_{coil}),
- 6) The plunger outer diameter in inches (OD_p),
- 7) The plunger inner diameter in inches if the plunger is hollow (ID_p),
- 8) The length, area, and permeability of each different magnetic section (ℓ_{iron} , A_{iron} , μ),
 - 8a) If the magnetic section is a cylindrical shell with axial flux flow, the height (h), the ID which may be zero, the OD, and the permeability (μ), can be entered, and the reluctance and cross-sectional area will be returned and automatically loaded into the program,
 - 8b) If the magnetic section consists of a disc (or washer) with radial flux flow, the thickness (t), the ID, the OD, and the permeability can be entered, and the reluctance and minimum cross-sectional area will be returned and automatically loaded into the program, and
- 9) The coil excitation in either volts or amperes (E or -I).

The program will then calculate the following parameters:

- 1) Reluctance and area of each different magnetic section (R & A_{iron}),
- 2) Coil inductance and resistance (R and L),
- 3) Coil circular-mils/A, A/in², and power dissipation M , Δ , & P),
- 4) The flux density in the air gap, and in the magnetic section with the smallest cross-sectional area (B_{air} , B_{iron}), and
- 5) The plunger attractive force in pounds (F).

This program uses the Ohm's law of magnetics as given by Eqs. (3-7.12) and (3-7.13), which combined yield:

$$0.4\pi NI = \phi \cdot \sum_i \frac{\ell_i}{\mu_i A_i} \quad (3-8.1)$$

As magnetic path data is entered, the program keeps a running sum of the reluctances, $\frac{\ell_i}{\mu_i A_i}$, and also stores the smallest magnetic area. The iron part will saturate first where the area is the smallest, and the flux density (B) the highest. The total flux can be found from Eq. (3-8.1):

$$\phi = \frac{0.4\pi NI k_3}{\sum_{\substack{\text{iron} \\ \text{parts}}} \frac{\ell_i}{\mu_i A_i} + \frac{\ell_{\text{air}}}{A_{\text{air}}}} \quad (3-8.2)$$

where

$$A_{\text{air}} = \frac{\pi}{4} \left(OD_p^2 - ID_p^2 \right) \quad (3-8.3)$$

$$k_3 = 2.54$$

The plunger attractive force is found in terms of the flux:

$$F = \frac{\phi^2}{k_1 \cdot k_3 \cdot A_{\text{air}}} \quad (3-8.4)$$

where the air gap area is in inches² and the constant k_1 is:

$$k_1 = 1.73 \times 10^6$$

The inductance of the N turn coil wound on the magnetic circuit is:

$$L = \frac{N^2 k_3}{10^8} \left\{ \frac{0.4\pi}{\sum_{\substack{\text{iron} \\ \text{parts}}} \frac{\ell}{\mu A} + \frac{\ell_{\text{air}}}{A_{\text{air}}}} \right\} \quad (3-8.5)$$

This expression is basically derived in Eqs. (3-1.1) through (3-1.10).

The coil width (w) can be expressed in terms of the coil length (ℓ_{coil}), the number of turns (N), and the wire AWG. The wire is assumed to occupy a box as shown in Fig. 3-6.2.

$$\text{coil area} = w \cdot \ell_{\text{coil}} = N \cdot (\text{wire diameter})^2 \quad (3-8.6)$$

Substituting the exponential relationship between AWG and wire diameter given by Eq. (3-5.10) yields:

$$w = \frac{N}{\ell_{\text{coil}}} \left(a \cdot e^{b \cdot \text{AWG}} \right)^2 \quad (3-8.7)$$

The coil resistance can now be calculated using Eq. (3-7.20):

$$R = N \cdot \pi \left(\text{ID}_{\text{coil}} + w \right) \left(k_4 e^{k_5 \cdot \text{AWG}} \right)$$

The coil power dissipation is:

$$P = I^2 R \quad (3-8.8)$$

If voltage excitation is used, the coil current is calculated using Ohm's law, then the power dissipation is calculated.

The coil circular mils per A is given by:

$$M = 10^6 \cdot \underbrace{\left(a' \cdot e^{b' \cdot \text{AWG}} \right)^2}_{\substack{\text{wire area in} \\ \text{circular mils}}} / I \quad (3-8.9)$$

The coil current density in A/in² is given by Eq. (3-8.10), i.e.:

$$\Delta = \frac{k_2}{M} \quad (3-8.10)$$

Two commonly encountered part shapes in the magnetic path are the cylindrical shell as shown in Fig. 3-8.1 and the disc or washer as shown in Fig. 3-8.2. Two subroutines are provided to calculate the reluctance and minimum cross-sectional area of these two shapes.

Subroutine 1, thin cylindrical shell with permeability μ .

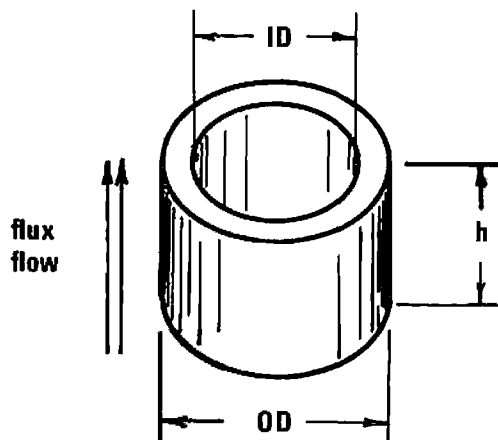


Figure 3-8.1 Thin cylindrical shell.

The cross-sectional area is given by Eq. (3-8.3) and the reluctance is:

$$\mathcal{R} = \frac{h}{\mu A}$$

This subroutine output becomes the input for the program coding under label B, and the reluctance is calculated under label B. The subroutine output is stored in the stack in the same format as data entered from the keyboard for arbitrary magnetic section, i.e.:

stack register	contents
t	not used
z	h
y	cross-sectional area
x	permeability

Subroutine 2, disc or washer with radial flux flow.

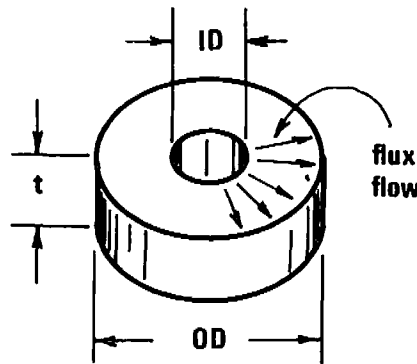


Figure 3-8.2 Disc or washer with radial flux flow.

The disc is composed of an infinite number of annular shells each with infinitesimal thickness dr . The cross-sectional area of each annulus is $2\pi r t$. In this instance, the summation of Eq. (3-8.1) is expressed as an integral:

$$\mathcal{R} = \sum \frac{\ell}{\mu A} = \frac{1}{\mu t} \int_{r_1 = \frac{ID}{2}}^{r_2 = \frac{OD}{2}} \frac{dr}{2\pi r} = \frac{\ln(OD/ID)}{2\pi t \mu} \quad (3-8.11)$$

The disc has the smallest cross-sectional area at the inner diameter, hence:

$$A = A' = \pi \cdot ID \cdot t \quad (3-8.12)$$

This subroutine output becomes the input for the program coding under label B. The data format used with label B is the equivalent length of a constant cross-section magnetic path, the path area, and the path permeability. The equivalent length having the above reluctance and

cross-sectional area A' is:

$$\ell = \mu A' \cdot R = \left(\frac{\pi \cdot ID \cdot t \cdot \mu}{2 \pi \cdot t \cdot \mu} \right) \cdot \ell \ln \frac{OD}{ID} = \frac{ID}{2} \ell \ln \frac{OD}{ID} \quad (3-8.13)$$

Subroutine 2 output is transferred to the program coding under label B using the stack in the same way that subroutine 1 operates.

In addition to the program card, a data card is required to load the registers with the program constants. All registers contain zero except for the following:


a' for AWG	$3.241013109 \times 10^{-1} \longrightarrow S_0$
b' for AWG	$-1.158179256 \times 10^{-1} \longrightarrow S_1$
a for AWG	$3.130387015 \times 10^{-1} \longrightarrow S_2$
b for AWG	$-1.097333787 \times 10^{-1} \longrightarrow S_3$
$\pi \cdot k_4$ for resistance	$2.985212367 \times 10^{-5} \longrightarrow S_4$
k_5 for resistance	$2.317635483 \times 10^{-1} \longrightarrow S_5$
k_3 , cm \rightarrow inch	$2.54 \longrightarrow S_6$
k_2 , $4/\pi \times 10^6$	$1.273239545 \times 10^6 \longrightarrow S_7$
k_1	$1.73 \times 10^6 \longrightarrow S_8$

If metric units are preferred, i.e., linear dimensions in cm, force in kg, current density in A/cm² and inverse current density in hybrid units (circular mil-milli-centimeter/A), change the following constants.

a' for AWG	$8.232173297 \times 10^{-1} \longrightarrow S_0$
a for AWG	$7.951183108 \times 10^{-1} \longrightarrow S_2$
$\pi \cdot k_4$ for resistance	$1.175280459 \times 10^{-5} \longrightarrow S_4$
k_3 cm \rightarrow cm	$1.0 \longrightarrow S_6$
k_2 , $4/(2.54\pi) \times 10^6$	$5.012754114 \times 10^5 \longrightarrow S_7$
k_1	$2.4606 \times 10^7 \longrightarrow S_8$

HP-67 users may want the program to stop instead of executing a "print" statement. This can be accomplished by changing the "print" statements to "R/S" statements at the following line numbers: 102, 105, 124, and 130. To continue program execution after a stop, key a "R/S" command from the keyboard.

User Instructions

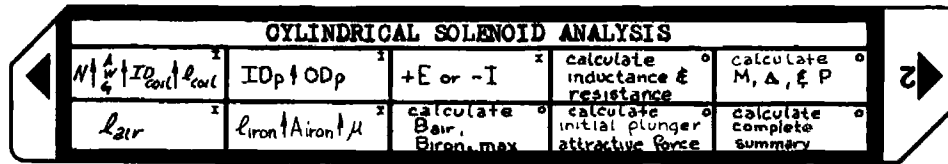

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card and both sides of data card			
2	Load air gap length in inches	l_{air}	A	
3	Load plunger ID and OD in inches. The ID can be zero if the plunger is solid	ID_p OD_p	ENT ↑ f B	
4	Load coil parameters: number of wire turns in coil wire AWG coil ID in inches coil length in inches	N AWG ID_{coil} l_{coil}	ENT ↑ ENT ↑ ENT ↑ f A	
5	Load coil excitation voltage excitation in volts current excitation in A (note minus)	E -I	f Q f Q	
6	Optional step, the main source of reluctance in the magnetic path is the air gap. For added accuracy, the length, area, and permeability of each magnetic section may be entered:			
	effective magnetic path length in inches	l_{iron}	ENT ↑	
	effective magnetic path area in inches ²	A_{iron}	ENT ↑	
	magnetic permeability of path	μ	B	R A
	If the magnetic section is either a cylindrical shell or a disc, then a subroutine can be used to calculate and enter the above parameters from the section dimensions.			
	For cylindrical shells with axial flux flow:			
	load shell height in inches	h	ENT ↑	
	load shell ID in inches (may be zero)	ID	ENT ↑	
	load shell OD in inches	OD	ENT ↑	
	load shell permeability	μ	GSB 1	R A

User Instructions

CYLINDRICAL SOLENOID ANALYSIS			
		CONTINUED	

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
6	continued			
	For discs with radial flux flow:			
	load disc thickness in inches	t	ENT ↑	
	load disc ID in inches	ID	ENT ↑	
	load disc OD in inches	OD	ENT ↑	
	load permeability of material	μ	GSB 2	\mathcal{R} A
	Repeat step 6 for each separate magnetic section in the magnetic circuit.			
7	To calculate the flux density in the air gap and in the smallest iron cross-sectional area (the smallest area has the highest flux dens) If step 6 is omitted, $\mathcal{R}_{iron} = 0$, $A_{iron} = A_{air}$ is assumed, hence, $B_{iron} = B_{air}$		0	B_{air} , G B_{iron} , G
8	To calculate the initial plunger attractive force in pounds		D	F
9	To calculate the electrical inductance and resistance at 60°C of the coil		f D	L, h R, ohms
10	To calculate the coil M, Δ , and power dissipation		f E	M, $\frac{\text{cir-mils}}{\text{A}}$ Δ , A/in^2 P, watts
11	To calculate all the information contained in steps 8, 9, 10, and 11		E	L, h R, ohms M, $\frac{\text{cir-mils}}{\text{A}}$ Δ , A/in^2 P, watts B_{air} , G B_{iron} , G F, lbs
12	To run a new case, goto step 1 and start over			

Example 3-8.1

The cylindrical solenoid shown in cross-section by Fig. 3-8.3 has the following characteristics:

- 1) The coil is 150 turns of #24 AWG HF wire,
- 2) 0.5 A excitation current flows through the coil, and
- 3) The magnetic materials are 1010 mild carbon steel.

For the analysis, neglect the force required to compress the return spring.

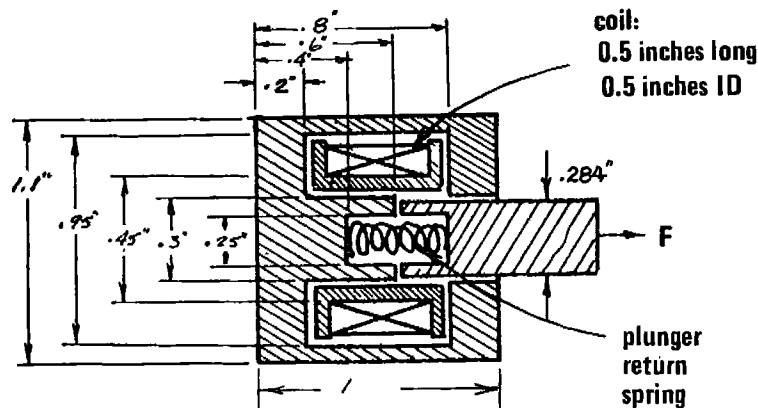


Figure 3-8.3 Cylindrical solenoid construction.

Analyze the solenoid and determine its electrical and magnetic characteristics. Also analyze the solenoid for the same characteristics if the coil is excited by 0.6 Vdc.

The analysis is begun by breaking down the solenoid into its component geometric shapes as shown by Fig. 3-8.4.

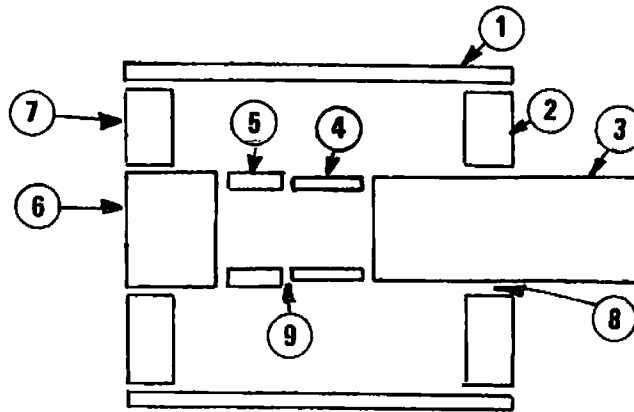


Figure 3-8.4 Component geometric shapes of solenoid.

The component geometric shapes of the solenoid are as follows:

- 1) Cylindrical shell, 1.0" long, 0.95" ID, 1.1" OD, and $\mu = 1000$,
- 2) Disc, 0.2" thick, 0.3" ID, 0.95" OD, and $\mu = 1000$,
- 3) Solid cylinder, 0.2" long (active magnetic part), 0.0" ID, 0.284" OD, and $\mu = 1000$,
- 4) Cylindrical shell, 0.2" long, 0.25" ID, 0.284" OD, and $\mu = 1000$,
- 5) Cylindrical shell, 0.2" long, 0.25" ID, 0.3" OD, and $\mu = 1000$,
- 6) Solid cylinder, 0.4" long, 0.0" ID, 0.3" OD, and $\mu = 1000$,
- 7) Disc, 0.2" thick, 0.3" ID, 0.95" OD, and $\mu = 1000$,
- 8) Disc (air gap), 0.2" thick, 0.284" ID, 0.3" OD, and $\mu = 1$,
- 9) Operating air gap, 0.005" thick, 0.25" ID, 0.284" OD, & $\mu = 1$.

The air gap data is loaded, and the complete summary calculated, then the magnetic path component parts are loaded and the summary run again to show the difference that the magnetic circuit reluctance makes on the electrical and magnetic characteristics. This sequence is repeated with the coil excitation at 0.6 Vdc.

HP-97 PRINTOUT FOR EXAMPLE 3-8.1

.005 GSBa load ℓ_{air} 150. ENT↑ load N 24. ENT↑ load AWG .5 ENT↑ load ID .5 GSBa load ℓ_{coil} .25 ENT↑ load ID _p .284 GSBb load OD _p -.5 GSBc load -I calc all * GSB parameters	solid cylinder .2 ENT↑ length 0. ENT↑ ID .284 ENT↑ OD 1000. GSB1 u 3.157-03 *** R 63.35-03 *** area cylindrical shell .2 ENT↑ length .25 ENT↑ ID .284 ENT↑ OD 1000. GSB1 μ	GSBc calc all params 1.661-03 *** L, h 759.9-03 *** R, ohms 809.2+00 *** M, cir-mils/A 1.574+03 *** Δ , A/in ² 190.0-03 *** P, watts 6.019+03 *** max Biron 6.019+03 *** B _{air} , G 298.6-03 *** F, pounds
2.048-03 *** L, h 759.9-03 *** R, ohms 809.2+00 *** M, cir-mils/A 1.574+03 *** Δ , A/in ² 190.0-03 *** P, watts 7.421+03 *** max Biron 7.421+03 *** B _{air} , G 453.9-03 *** F, pounds	14.03-03 *** R 14.26-03 *** area cylindrical shell .2 ENT↑ length .25 ENT↑ ID .3 ENT↑ OD 1000. GSB1 μ 9.260-03 *** R 21.60-03 *** area	Look at voltage excitation. Set flag 0 so magnetic reluctance is ignored and calculate electrical & magnetic parameters. SF0 .6 GSBc load E GSBc calc params 2.048-03 *** L, h 759.9-03 *** R, ohms 512.4+00 *** M, cir-mils/A 2.485+03 *** Δ , A/in ² 473.7-03 *** P, watts 11.72+03 *** max Biron 11.72+03 *** B _{air} , G 1.132+00 *** F, pounds
* Magnetic reluctance is assumed zero since flag 0 is set. Flag 0 is cleared under label B. load magnetic path data	solid cylinder .4 ENT↑ length 0. ENT↑ ID .3 ENT↑ OD 1000. GSB1 μ 5.659-03 *** R 70.69-03 *** area	Clear flag 0 to use magnetic reluctance. CF0 GSBc calc params 1.661-03 *** L, h 759.9-03 *** R, ohms 512.4+00 *** M, cir-mils/A 2.485+03 *** Δ , A/in ² 473.7-03 *** P, watts 9.505+03 *** max Biron 9.505+03 *** B _{air} , G 744.6-03 *** F, pounds
cylindrical shell 1. ENT↑ length .95 ENT↑ ID 1.1 ENT↑ OD 1000. GSB1 μ 4.141-03 *** R 241.5-03 *** area	disc .2 ENT↑ thickness .3 ENT↑ ID .95 ENT↑ OD 1000. GSB2 μ 917.3-06 *** R 188.5-03 *** min area	disc .2 ENT↑ thickness .284 ENT↑ ID .3 ENT↑ OD 1. GSB2 μ 43.62-03 *** R 178.4-03 *** min area
disc .2 ENT↑ thickness .3 ENT↑ ID .95 ENT↑ OD 1000. GSB2 μ 917.3-06 *** R 188.5-03 *** area	disc .2 ENT↑ thickness .284 ENT↑ ID .3 ENT↑ OD 1. GSB2 μ 43.62-03 *** R 178.4-03 *** min area	disc .2 ENT↑ thickness .284 ENT↑ ID .3 ENT↑ OD 1. GSB2 μ 43.62-03 *** R 178.4-03 *** min area

Program Listing I

001 *LBLA	LOAD AIR GAP IN INCHES	050 *LBLE	CALCULATE B_{air} and B_{iron}
002 ST02	store entry	051 GSB6	calculate R , I , and NI
003 GT00	goto space and return	052 GSB9	calc $(0.4\pi/k_3)/(\sum R_i + l_{air}/A_{air})$
004 *LBLA	LOAD N , AWG , ID_{coil} , l_{coil}	053 RCL4	use A_{air} if magnetic params
005 ST01	store coil length	054 F0?	not entered, otherwise use
006 R4	recover and store ID_{coil}	055 RCL3	min A_{iron}
007 ST0D		056 1/X	take reciprocal area
008 R4	recover and store AWG	057 RCL1	calculate and print ϕ
009 ST0B		058 RCL4	using Eq. (3-7.2)
010 R4	recover and store N	059 X	
011 ST0E		060 ST06	
012 GT00	goto space and return	061 X	calculate and print:
013 *LBL2	SUBROUTINE FOR DISC	062 PZS	
014 R4		063 RCL6	
015 XZY		064 PZS	
016 ST01		065 XZ	
017 ÷		066 ST01	
018 LN	$l_{effective} = \frac{ID}{2} \ln \frac{OD}{ID}$	067 ÷	
019 RCL1		068 PRTX	
020 X		069 RCL6	calculate and print:
021 2		070 RCL3	
022 ÷		071 ÷	
023 XZY		072 RCL1	
024 RCL1		073 ÷	
025 X	$A_{min} = \pi \cdot ID \cdot t$	074 GT08	
026 P1		075 *LBLE	PRINT COMPLETE SUMMARY
027 X		076 GSBd	
028 R4	recover μ	077 GSBc	
029 *LBLE	LOAD l_{iron} , A_{iron} , μ	078 GSBc	
030 XZY	store μ	079 *LBLE	CALCULATE AND PRINT F
031 ST01		080 GSB6	
032 F0?	store A_{iron} on first	081 SF2	
033 ST04	execution of this routine	082 GSB9	
034 X		083 RCL4	
035 ÷		084 X	
036 SPC	$R_i = \frac{l_{iron}}{\mu_i \cdot A_{iron}}$	085 XZ	
037 PRTX		086 RCL3	
038 ST+5	add R_i to \sum	087 ÷	
039 RCL4	test to see if present area	088 PZS	
040 RCL1	is smaller than minimum	089 RCL8	
041 XZY?	stored area, if so, store	090 PZS	
042 ST04	present area	091 ÷	
043 CF0	indicate magnetic params	092 GT08	
044 GSB8	print area and space	093 *LBLE	CALCULATE AND PRINT L & R
045 GT00	goto space and return	094 GSB6	
046 *LBLE	LOAD ID_p , OD_p	095 GSB9	
047 GSB4	calculate and store	096 RCL4	
048 ST03	annular area	097 XZ	
049 GT00	goto space and return	098 X	
NOTE:		099 EEX	
The "print" statements at line numbers		100 8	
037, 102, 105, 124, and 130 may be changed		101 ÷	
to "R/S" statements if desired.		102 PRTX	
		103 RCLC	recall and print resistance
REGISTERS			
0 w	1 l_{coil}	2 l_{air}	3 A_{air}
4 $min A_{iron}$	5 $\sum \frac{l}{\mu A}$	6 ϕ	7 scratch
8 I	9 E		
S0 a'	S1 b'	S2 a	S3 b
S4 πk_4	S5 k_5	S6 k_3	S7 k_2
S8 k_1	S9		
A NI	B AWG	C R	D coil OD
E N	I scratchpad		

Program Listing II

NOTE FLAG SET STATUS

104 *LBL8	print and space subroutine	159 *LBL6	subr to calc R, I, and NI
105 PRTX		160 PZS	
106 GT00		161 RCL2	
107 *LBLc	LOAD COIL EXCITATION	162 RCL3	
108 ST09		163 GSB3	
109 *LBL0	space and return subroutine	164 X ²	$W = \frac{N}{l_{coil}} (a \cdot e^{b \cdot AWG})^2$
110 SPC		165 RCLE	
111 RTN		166 x	
112 *LBLc	CALCULATE AND PRINT M, P	167 RCL1	
113 GSB6		168 ÷	
114 PZS		169 ST00	
115 RCL0		170 RCL0	
116 RCL1		171 +	
117 GSB3		172 RCLE	
118 X ²	$M = 10^6 (a' e^{b' \cdot AWG})^2$	173 x	
119 RCL8		174 PZS	
120 ÷		175 RCL4	$R = N \pi (ID_{coil} + W) k_4 e^{k_5 \cdot AWG}$
121 EEX		176 RCL5	
122 6		177 GSB3	
123 x		178 x	
124 PRTX		179 ST0C	
125 1/X		180 RCL9	
126 PZS		181 X<0?	test for current excitation
127 RCL7	$\Delta = \frac{k_2}{M}$	182 GT00	
128 PZS		183 ÷	$I = E/R$
129 x		184 1/X	
130 PRTX		185 *LBL0	jump destination
131 RCL8		186 ABS	store I
132 X ²		187 ST08	
133 RCLC	$P = I^2 R$	188 RCLE	calculate and store NI
134 x		189 x	
135 GT08		190 ST0A	
136 *LBL1	CYLINDRICAL SHELL SUBR	191 RTN	
137 ST01		192 *LBL9	magnetics subroutine
138 R↓		193 7	
139 GSB4		194 2	0.4π
140 RCL1		195 D→R	
141 GT0B		196 RCL2	
142 *LBL3	subroutine to calculate:	197 RCL3	
143 PZS		198 ÷	
144 RCLB	$R_y \cdot e^{R_x \cdot AWG}$	199 RCL5	
145 x		200 F0?	
146 e ^x		201 CLX	
147 x		202 +	
148 RTN		203 ÷	
149 *LBL4	subroutine to calculate:	204 PZS	
150 X ²		205 RCL6	
151 XZY		206 PZS	
152 X ²		207 F2?	
153 -		208 1/X	
154 P↓	$Area = \frac{\pi}{4} (OD^2 - ID^2)$	209 x	
155 x		210 ST01	
156 4		211 RTN	return to main program
157 ÷			
158 RTN			

LABELS					FLAGS	SET STATUS		
A l_{air}	B l_{iron}	C calculate $B_{air}, \max B_{iron}$	D calc F	E complete summary	0 magnetic parameters entered	FLAGS	TRIG	DISP
a $N \uparrow$	b $ID_p \uparrow OD_p$	c +E or -I	d calc L, R	e calc M, A, ϕ P	1	ON OFF	users choice	FIX SCI ENG
0 local label	1 cylindrical section entry	2 disc section entry	3 wire size subroutine	4 circular section area	2 subroutine control	0 <input type="checkbox"/>	DEG	<input type="checkbox"/>
						1 <input type="checkbox"/>	GRAD	<input type="checkbox"/>
						2 <input type="checkbox"/>	RAD	<input type="checkbox"/>
5	6 R, I & NI subroutine	7	8 print & space subroutine	9 magnetics calc subr	3	3 <input type="checkbox"/>		n <u>3</u>

PROGRAM 3-9 MAGNETIC RELUCTANCE OF TAPERED CYLINDRICAL SECTIONS.

Program Description and Equations Used

This program calculates the magnetic reluctance of tapered cylindrical sections with axial flux flow as shown by Fig. 3-9.1. The magnetic reluctance is analogous to electrical resistance, and is used in the Ohm's law of magnetics as given by Eq. (3-8.1).

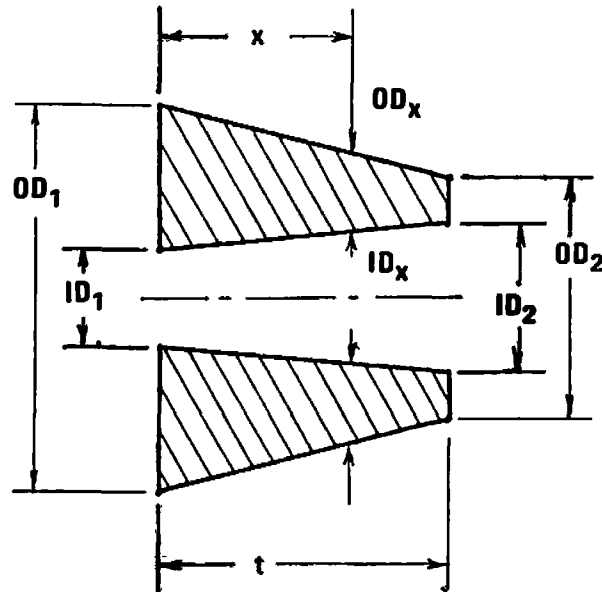


Figure 3-9.1 Tapered cylindrical section and dimensions.

Consider the section to be composed of an infinite number of washers each of infinitesimal thickness dx , then the reluctance of a washer is:

$$d\mathcal{R} = dx/(\mu \cdot A_x) \quad (3-9.1)$$

where

$$A_x = (\pi/4)(OD_x^2 - ID_x^2) \quad (3-9.2)$$

The inner and outer diameters at location x can be found by linearly interpolating between the known end diameters:

$$ID_x = ID_1 + (1/t)(ID_2 - ID_1) \cdot x \quad (3-9.3)$$

$$OD_x = OD_1 + (1/t)(OD_2 - OD_1) \cdot x \quad (3-9.4)$$

Substituting Eqs. (3-9.3) and (3-9.4) into Eq. (3-9.2) and collecting like powers of x results in a quadratic:

$$A_x = (\pi/4)(a + bx + cx^2) \quad (3-9.5)$$

where

$$a = OD_1^2 - ID_1^2$$

$$b = (2/t)\{OD_1(OD_2 - OD_1) - ID_1(ID_2 - ID_1)\}$$

$$c = (1/t^2)\{(OD_2 - OD_1)^2 - (ID_2 - ID_1)^2\}$$

hence,

$$R = \frac{4}{\mu\pi} \int_0^t \frac{dx}{a + bx + cx^2} \quad (3-9.6)$$

The result of this integration can have any one of three forms; let

$$q = b^2 - 4ac \quad (3-9.7)$$

and

$$r = (2cx + b) / \sqrt{|q|} \quad (3-9.8)$$

then if $q > 0$ and $|r| < 1$, the solution is:

$$R = - \frac{8}{\mu\pi \sqrt{|q|}} \tanh^{-1} r \quad (3-9.9)$$

if $q > 0$ and $|r| \geq 1$, the solution is:

$$R = \frac{4}{\mu\pi \sqrt{|q|}} \ell n \left(\frac{r-1}{r+1} \right) \quad (3-9.10)$$

if $q < 0$, the solution for all r is:

$$R = \frac{8}{\mu\pi \sqrt{|q|}} \tan^{-1} r \quad (3-9.11)$$

MAGNETIC RELUCTANCE OF TAPERED CYLINDRICAL SECTIONS				
load $ID_1 \uparrow ID_2$	load $OD_1 \uparrow OD_2$	load section length, t	load permea- bility, μ	print ? calculate R

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of the magnetic card			
2	select print/ no-print option		<div>f</div> <div>E</div> <div>f</div> <div>E</div> <div>f</div> <div>E</div> <div>:</div>	0 (no prt) 1 (print) 0 (no prt) :
3	Load inner diameters	ID ₁ * ID ₂ *	<div>ENT ↑</div> <div>A</div>	
4	Load outer diameters	OD ₁ * OD ₂ *	<div>ENT ↑</div> <div>B</div>	
5	Load section length	t*	<div>C</div>	
6	Load magnetic permeability of material		<div>D</div>	
7	Calculate reluctance		<div>E</div>	R **
	Notes			
	* Any units of the users choosing may be used as long as the same unit is used throughout. If the reluctance is going to be loaded into Program 3-7, then inch units should be used.			
	** The units of reluctance are in inverse dimension units, i.e., inches ⁻¹ , cm ⁻¹ , ft ⁻¹ , etc.			

Example 3-9.1

Given the conical section shown in Fig. 3-9.2, calculate the reluctance in inch units.

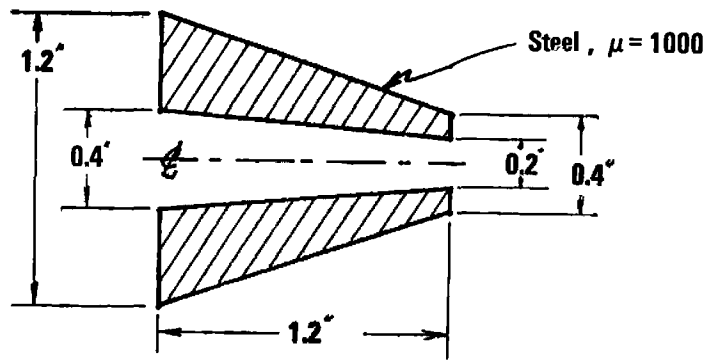


Figure 3-9.2 Tapered conical section.

```

.2 ENT1 ID1
.4 G3EH ID2

.4 ENT1 OD1
.2 G3EH OD2

.2 G3EC t

1000. G3EC μ

3.872-03 *** calculate reluctance
R, in-1

```

Program Listing I

001 *LBLA	LOAD ID ₁ ↑ ID ₂	019 *LBLB	CALCULATE RELUCTANCE
002 ST01		020 RCL3	calculate and store:
003 R↓	store entries	021 RCL2	
004 ST00		022 -	$(OD_2 - OD_1)^2$
005 GT00	goto space and return subr	023 X ²	
006 *LBLB	LOAD OD ₁ ↑ OD ₂	024 ST08	
007 ST03		025 LSTX	calculate and retain in stk:
008 R↓	store entries	026 RCL2	OD ₁ (OD ₂ - OD ₁)
009 ST02		027 X	
010 GT00	goto space and return subr	028 RCL1	calculate w/ register arith:
011 *LBLC	LOAD SECTION LENGTH	029 RCL0	
012 ST04		030 -	$(OD_2 - OD_1)^2 - (ID_2 - ID_1)^2$
013 GT00		031 ENT↑	
014 *LBLD	LOAD PERMEABILITY	032 X ²	
015 ST05		033 ST-8	
016 *LBL0	space and return subroutine	034 R↓	calculate and store b:
017 SPC		035 RCL0	
018 RTN		036 X	
		037 -	
		038 ENT↑	$\frac{2}{t} \{ OD_1(OD_2 - OD_1) - ID_1(ID_2 - ID_1) \}$
		039 +	
		040 RCL4	
		041 ÷	
		042 ST07	
		043 RCL4	finish c calculation
		044 X ²	
		045 ST-8	
		046 RCL7	calculate and store q:
		047 X ²	
		048 RCL2	
		049 X ²	
		050 RCL0	
		051 X ²	
		052 -	$q = b^2 - 4ac$
		053 RCL8	
		054 X	
		055 4	
		056 X	
		057 -	
		058 ST06	
		059 ABS	calculate and store:
		060 JX	$\sqrt{ q }$
		061 ST0A	
		062 RCL4	calculate and store:
		063 GSB0	
		064 ST09	$\int_0^t \frac{dx}{a + bx + cx^2}$
		065 CLX	
		066 GSB0	
		067 ST-9	

REGISTERS									
0 ID ₁	1 ID ₂	2 OD ₁	3 OD ₂	4 t	5 μ	6 scratch	7 b	8 c	9 ∫ ₀ ^t
S0	S1	S2	S3	S4	S5	S6	S7	S8	S9
A $\sqrt{ q }$	B q	C 2cx + b	D	E R	F	G	H	I	J

LABELS					FLAGS	SET STATUS			
A load ID ₁ + ID ₂	B load OD ₁ + OD ₂	C load t	D load permeability	E calculate reluctance	0 r > 1	FLAGS		TRIG	DISP
a	b	c	d	e print / R/S toggle	1 print	ON OFF			
0 local label	1 subroutine destination	2 subroutine destination	3 print / R/S destination	4	2	0	DEG		FIX
						1	GRAD		SCI
						2	RAD		ENG
						3			n 3

Flag 1 should be set (cleared) before magnetic card recording depending upon the user's desire for the program to normally be in the print (R/S) mode after the card read.

Part 4

HIGH FREQUENCY CIRCUIT DESIGN

PROGRAM 4-1 BILATERAL TRANSISTOR AMPLIFIER DESIGN USING S PARAMETERS.

Program Description and Equations Used

When s_{12} , the reverse transmission coefficient, cannot be reduced to near zero using unilateral design methods,* or the unilateral figure of merit is not sufficiently near zero, the bilateral design method must be used. Since s_{12} is related to the capacitive reactance of the transistor base-collector capacity, and this reactance becomes smaller as frequency increases, the bilateral design requirement generally occurs when the amplifier is to be used at UHF frequencies and above.

The bilateral stability factor, K , is computed using Eq. (4-1.1). For the amplifier to be unconditionally stable, K must be greater than one, and the magnitudes of s_{11} and s_{22} must be smaller than one. Since s_{11} and s_{22} are reflection coefficients, this last requirement implies that the input and output impedances are positive. Unconditional stability means the amplifier will not oscillate for any choice of input and output terminations.

$$K = \frac{1 + |\Delta|^2 - |s_{11}|^2 - |s_{22}|^2}{2 |s_{21} \cdot s_{12}|} \quad (4-1.1)$$

$$\Delta = s_{11} \cdot s_{22} - s_{21} \cdot s_{12} \quad (4-1.2)$$

When K is less than one, the amplifier will oscillate with certain source and load impedances, hence, these impedances must be carefully selected. The HP EE pac Program 18 will calculate the stability circles to aid in the termination impedance selection.

The scattering parameters are:

- s_{11} is the input reflection coefficient,
 - s_{12} is the reverse transmission coefficient,
 - s_{21} is the forward transmission coefficient, and
 - s_{22} is the output reflection coefficient.
-

* See the HP EE pac Program 16 for unilateral design methods.

Scattering parameters are obtained from reflection coefficient measurements applied to a two port network with both ports loaded with a reference impedance, Z_o , which is typically 50 ohms resistive. The reflection coefficient is defined by Eq. (1-1.2). For a more comprehensive discussion of s parameters, see Froehner [24], HP application note 95 [32], or Carson [15].

If the proposed amplifier is unconditionally stable, then the maximum gain can be calculated using Eq. (4-1.3)

$$G_{\max} = \left| \frac{s_{21}}{s_{12}} \right| \cdot (K \pm \sqrt{K^2 - 1}) \quad (4-1.3)$$

The negative sign is used when B_1 is positive and vice-versa:

$$B_1 = 1 + |s_{11}|^2 - |s_{22}|^2 - |\Delta|^2 \quad (4-1.4)$$

The source and load reflection coefficients necessary to provide G_{\max} are given by Eqs. (4-1.5) and (4-1.6). These loads present a conjugate match to the transistor.

$$\rho_{MS} = C_1 * \frac{B_1 \pm \sqrt{B_1^2 - 4|C_1|^2}}{2|C_1|^2} \quad (4-1.5)$$

$$\rho_{ML} = C_2 * \frac{B_2 \pm \sqrt{B_2^2 - 4|C_2|^2}}{2|C_1|^2} \quad (4-1.6)$$

$$B_2 = 1 + |s_{22}|^2 - |s_{11}|^2 - |\Delta|^2 \quad (4-1.7)$$

$$C_1 = s_{11} - \Delta \cdot s_{22}^* \quad (4-1.8)$$

$$C_2 = s_{22} - \Delta \cdot s_{11}^* \quad (4-1.9)$$


The minus sign in Eqs. (4-1.5) and (4-1.6) is used when B_1 is positive and vice-versa. The asterisk (*) means the complex conjugate, i.e., the sign of the imaginary part is reversed, or the sign of the angle is reversed for rectangular or polar formats respectively.

Equations (4-1.5) and (4-1.6) are used to calculate reflection coefficients. The corresponding impedances can be obtained if Eq. (1-1.2) is rearranged to provide Z_L in terms of Z_s :

$$Z_L = Z_o \frac{1 + \rho}{1 - \rho} \quad (4-1.10)$$

This routine is contained under label E of the program.

User Instructions

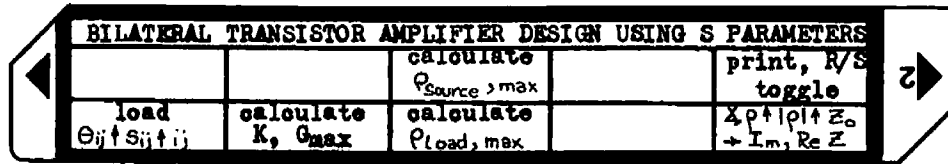

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of magnetic card			
2	Select print or R/S option		<div>F</div> <div>E</div> <div>F</div> <div>E</div> <div>F</div> <div>E</div>	0 (R/S) 1 (print) 0 (R/S) ⋮
3	Load elements of s parameter matrix for $ij = 11, 12, 21, 22$ (any order)			
	a) load angle of s_{ij} in degrees	θ_{ij}°	<div>ENT ↑</div>	
	b) load magnitude of s_{ij}	$ s_{ij} $	<div>ENT ↑</div>	
	c) load subscript	ij	<div>A</div>	
4	Calculate stability factor and maximum gain		<div>B</div>	K $G_{\text{max}}, \text{dB}$
5	Calculate angle and magnitude of load reflection coefficient to obtain G_{max}		<div>C</div>	$\angle \rho_{\text{mL}}$ $ \rho_{\text{mL}} $
	Calculate real and imaginary parts of load impedance	Z_o	<div>E</div>	$\text{Re } Z_L$ $\text{Im } Z_L$
6	Calculate angle and magnitude of source reflection coefficient to obtain G_{max}		<div>F</div> <div>C</div>	$\angle \rho_{\text{mS}}$ $ \rho_{\text{mS}} $
	Calculate real and imaginary parts of source impedance	Z_o	<div>E</div>	$\text{Re } Z_S$ $\text{Im } Z_S$
7	Calculate real and imaginary parts of impedances corresponding to a reflection coefficient and Z_o	$\angle \rho$ $ \rho $ Z_o	<div>ENT ↑</div> <div>ENT ↑</div> <div>E</div>	$\text{Re } Z$ $\text{Im } Z$

Example 4-1.1

Given a 2N3570 transistor operating at $I_c = 4$ mA and $V_{ce} = 10$ V and having the following s parameters at 750 MHz,

$$\begin{bmatrix} s_{11} & s_{12} \\ s_{21} & s_{22} \end{bmatrix} = \begin{bmatrix} 0.277 \angle -59^\circ & 0.078 \angle 93^\circ \\ 1.920 \angle 60^\circ & 0.848 \angle -31^\circ \end{bmatrix}$$

calculate the stability factor, the maximum power gain in dB, the source reflection coefficient and impedance to obtain G_{\max} , and the load reflection coefficient and impedance to obtain G_{\max} .

PROGRAM INPUT	PROGRAM OUTPUT
-59.000 ENT* θ_{11} , angle in degrees	GSBB calculate K & G_{\max}
.277 ENT* s_{11} , magnitude	1.055+00 *** K > 1, uncond stable
11. GSBA ij	12.51+00 *** G_{\max} , dB
93.000 ENT* θ_{12}	GSBC calculate ρ_{MS}
.078 ENT* s_{12}	135.4+00 *** $\angle \rho_{MS}$, degrees
12. GSBA ij	729.6-03 *** $ \rho_{MS} $
64.000 ENT* θ_{21}	50. GSBE calculate Z_s
1.920 ENT* s_{21}	9.065+00 *** Re Z_s , ohms
21. GSBA ij	19.96+00 *** Im Z_s , ohms
-31.000 ENT* θ_{22}	GSBC calculate ρ_{ML}
.848 ENT* s_{22}	33.85+00 *** $\angle \rho_{ML}$, degrees
22. GSBA ij	551.1-03 *** $ \rho_{ML} $
	50. GSBE calculate Z_L
	14.59+00 *** Re Z_L , ohms
	163.1+00 *** Im Z_L , ohms

REGISTERS									
0	1	2	3	4	5	6	7	8	9
C	S ₁₁	Δ S ₁₁	S ₁₂	Δ S ₁₂	sign(B ₁)	Δ	Δ	B ₂ or B ₁	K
Re ρ	Im ρ	Z _o , Z _s	Δ Z _s						
Δ C*, Δ B	S ₂₁	Δ S ₂₁	S ₂₂	Δ S ₂₂	index				

Program Listing II

111	÷			166	-		
112	ENT↑	$ p = \frac{B}{2C} - (\text{sign } B) \sqrt{\left(\frac{B}{2C}\right)^2 - 1}$		167	ST08		
113	X²			168	X=0?		
114	EEX			169	EEX		
115	-			170	ABS		
116	√X			171	LSTX		
117	RCL5			172	÷		
118	X			173	ST05		
119	-			174	RTN		
120	*LBL0	print and space subroutine		175	*LBL8	complex add subroutine	
121	GSB5			176	→R		
122	*LBL3	space subroutine		177	R↓		
123	F0?	space if flag 0 is set		178	R↓		
124	SPC			179	→R		
125	GT06	goto R/S lock		180	X≠Y		
126	*LBL6	CONVERT $X \uparrow p \uparrow Z_0 \rightarrow \text{Im, Re } Z$		181	R↓		
127	PZS			182	+		
128	ST02			183	R↓		
129	R↓			184	+		
130	→R			185	R↑		
131	ST00	Re p		186	→P		
132	EEX			187	RTN		
133	+			188	*LBL9	complex multiply subroutine	
134	X≠Y			189	R↓		
135	ST01	Im p		190	X		
136	X≠Y			191	R↓		
137	→P	1+p		192	+		
138	STx2	$Z_0 \cdot (1+p)$		193	R↑		
139	X≠Y			194	RTN		
140	ST03	X (1+p)		195	*LBL2	subroutine to finish 0	
141	RCL1			196	GSB8	calculation, store results	
142	CHS	-Im p		197	ST00	and print angle of	
143	EEX			198	X≠Y	reflection coefficient	
144	RCL0	Re p		199	CHS		
145	-			200	ST0A		
146	→P	1-p		201	*LBL5	print subroutine	
147	ST÷2	$ Z_0 \cdot (1+p)/(1-p) = Z $		202	F0?		
148	X≠Y			203	PRTX	print and return if flag 0	
149	ST-3	$X(1+p) - X(1-p) = XZ$		204	F0?	is set, otherwise stop	
150	RCL3	XZ		205	RTN		
151	RCL2	Z		206	R/S		
152	PZS			207	RTN		
153	→R	convert to rectangular fmt		208	*LBL6	R/S lock	
154	GSB5	print Re Z		209	R/S	prevents inadvertent use	
155	X≠Y	recover Im Z		210	GT06	of program fens w/ R/S	
156	GT00	print Im Z and space		211	*LBL6	PRINT, R/S TOGGLE	
157	*LBL7	subroutine to calculate:		212	CF0	clear flag 0 to indicate	
158	X²			213	CLX	R/S mode and place a zero	
159	X≠Y	$X^2 - Y^2 - A ^2 + 1 = B$		214	RTN	in the display	
160	X²			215	*LBL6		
161	-			216	SF0	set flag 0 to indicate	
162	EEX	sign(B) → R5		217	EEX	print and continue mode	
163	+			218	RTN	and place a one in display	
164	RCL6						
165	X²						

LABELS					FLAGS	SET STATUS		
A Θ_i, s_{ij}, t_{ij}	B $\rightarrow K, G_{\max}$	C $\rightarrow \rho_{ML}$	D	E $\rho \uparrow Z_0 \rightarrow Z$	0 print	FLAGS	TRIG	DISP
a	b	c $\rightarrow \rho_{ms}$	d	e	1	ON OFF		
0 prt, spc, rtn	1 local label w/ 0, fC	2 subroutine w/ C, fC	3 space, rtn	4	2	0 ■	DEG ■	FIX
5 print, R/S subroutine	6 R/S lock	7 subroutine	8 complex add	9 complex multiply	3	1 ■	GRAD	SCI
						2 ■	RAD	ENG ■
						3 ■		n <u>3</u>

NOTE FLAG SET STATUS

PROGRAM 4-2 UHF OSCILLATOR DESIGN USING S PARAMETERS.

Program Description and Equations Used

At UHF frequencies, the interelement capacities of a UHF transistor can function as the feedback elements to allow the device to oscillate when connected to an external tuned circuit (usually a $\frac{1}{4}$ -wave transmission line section). The emitter circuit is generally left unbypassed while the base circuit is bypassed with a capacitor to provide an ac ground. The collector-emitter capacity provides the necessary feedback to allow the collector to exhibit negative output impedance and oscillate with the external tuned circuit.

The program starts with the common base s parameters, reverses the port ordering so the collector is the input, and calculates the reflection coefficient of the "input." If the magnitude of the reflection coefficient is greater than one, the real part of the input impedance will be negative. The routine under label E provides the conversion from reflection coefficient to impedance, while the routine under label e provides the reverse conversion.

Equation (4-2.1) calculates the input reflection coefficient when the output port is loaded with R_L as shown by Fig. 4-2.1. Equation (4-2.1) holds for any transistor configuration.

$$s_{11}' = s_{11} + \frac{s_{12} \cdot s_{21} \cdot \rho_L}{1 - s_{22} \cdot \rho_L} \quad (4-2.1)$$

where ρ_L is defined by Eq. (1-1.2) with $Z_r = R_L$.

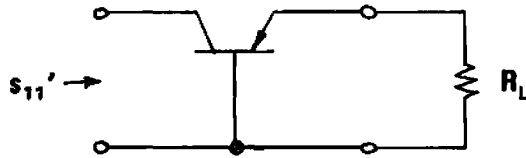


Figure 4-2.1 Common base transistor with collector as input port.

If the tuned source is connected to the collector, and the reflection coefficient of the source is denoted ρ_s , the circuit will oscillate if:

$$\rho_s \cdot s_{11}' \geq 1 \quad (4-2.2)$$

This equation is used in reverse to calculate the source reflection coefficient necessary for oscillation, i.e.:

$$\rho_s = \frac{1}{s_{11}'} \quad (4-2.3)$$

This reflection coefficient can be converted to its equivalent impedance using Eq. (4-1.10). The "Q," or quality factor, of this impedance is the ratio of the imaginary part to the real part, i.e.:

$$Q = \frac{\text{Im } Z_s}{\text{Re } Z_s} \quad (4-2.4)$$

The transistor negative input impedance can also be used to make a reflection amplifier if a circulator is used to separate the input from the output. The noise figure will be poor because of the large unby-passed emitter resistance.


For more information see the HP Journal [33], or HP application note number 95 [32].

Notes for User Instructions. Most UHF transistors are four lead devices (emitter, base, collector, and case). The case is electrically isolated from the transistor, in fact, the transistor chip is so small that it is mounted on the end of the collector lead inside the case. Because

of the fourth element, the case, the parasitic capacities from it to the other leads will introduce errors into the common-emitter to common-base s parameter conversion. See G. Bodway's article [9] on characterization of transistors by means of three port scattering parameters as one way of dealing with this problem.

If the common base s parameters are available, or can be measured, they are the highly preferred form of data input for the program. Common-base parameters notwithstanding, the common-emitter conversion can be used with the knowledge that s_{11}' will not be very accurate.

User Instructions

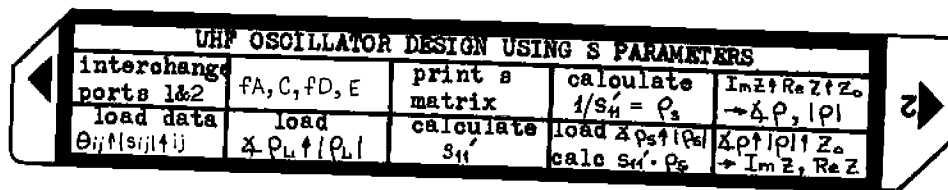

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card or load Program 4-3 if parameter conversion reqd			
2	Load s parameters. If already in common base form, goto step 10 after executing this step. a) load angle of scattering parameter b) load magnitude of scattering parameter c) load subscript of scattering parameter Repeat this step for $ij = 11, 12, 21, 22$ in any order	θ_{ij} $ s_{ij} $ ij	ENT↑ ENT↑ A	
3	To convert common emitter s parameters to common base, load EE1-06A, parameter conversions: $s \leftrightarrow Y, G, Z, H$. (see notes in step 16)			
4	Convert s parameters to Y parameters	Z_o	B	
5	Load Program 4-3 to convert common emitter Y parameters to common base Y parameters			
6	Perform CE to CB conversion		B	
7	Reload EE1-06A to convert Y parameters back to s parameters			
8	Convert Y parameters to s parameters	Z_o	f B	
9	Reload both sides of this program card (4-2)			
10	Calculate load reflection coefficient a) load imaginary part of Z_{emitter} b) load real part of Z_{emitter} c) load reference impedance	Im Z_L Re Z_L Z_o	ENT↑ ENT↑ f E	$\angle \rho_L$ $ \rho_L $

User Instructions



STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
11	Enter load reflection coefficient (if step 10 is used, the reflection coefficient magnitude and angle are already in the stack--- use key "B" alone)	$\angle \rho_L$ $ \rho_L $	ENT B	
12	Interchange port ordering 1 \leftrightarrow 2		f A	
13	Calculate s_{11}'		C	$\angle s_{11}'$ $ s_{11}' $
14	Calculate $\rho_s = 1/s_{11}'$		f D	$\angle 1/s_{11}'$ $ 1/s_{11}' $
15	Convert ρ_s to Z_s ; enter reference impedance To find the minimum resonator Q	Z_0	E ÷	Im Z_s Re Z_s Q_{min}
16	The load reflection coefficient is not erased when Program 4-3 or EE1-06A* is used, hence, for another case, the keystrokes in steps 12, 13, 14, and 15 are contained in user definable key fB, therefore, for another case, do steps 1 through 9, then execute fB * In HP EE pac (supplied by HP)		f B	$\angle s_{11}$ $ s_{11} $ $\angle 1/s_{11}'$ $ 1/s_{11}' $ Im Z_s Re Z_s Q_{min}

Example 4-2.1

A UHF oscillator using a RCA 2N5179 transistor is to operate between 300 MHz and 400 MHz. The transistor is to be operated at 1.5 mA collector current and 4 volts V_{ce} per the manufacturer's recommendations. At 300 MHz the common-emitter y parameters are:

$$\begin{bmatrix} \{(6.5 + j9.0) \times 10^{-3}\} \{ -j1.35 \times 10^{-3} \} \\ \{(32 - j32) \times 10^{-3} \} \{(0.25 + j2.6) \times 10^{-3}\} \end{bmatrix}$$

and at 400 MHz the common-emitter y parameters are:

$$\begin{bmatrix} \{(9.2 + j10.7) \times 10^{-3}\} \{ -j1.8 \times 10^{-3} \} \\ \{(25 - j34) \times 10^{-3} \} \{(0.3 + j4.0) \times 10^{-3}\} \end{bmatrix}$$

The proposed oscillator schematic is shown in Fig. 4-2.2, and biasing networks have been added to achieve the manufacturer's recommended bias. The 100 ohm resistor in series with the RFC lowers the Q of the resonant circuit formed by the RFC and the coax capacity so the circuit will not preferentially oscillate at that lower frequency.

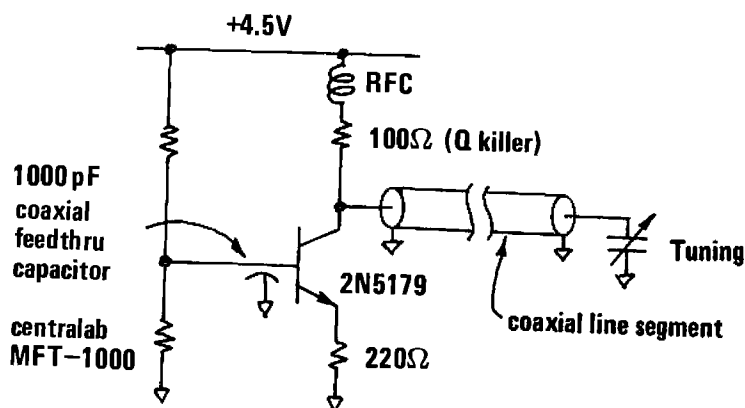


Figure 4-2.2 Oscillator schematic for Example 4-2.1.

HP-97 PRINTOUT FOR EXAMPLE 4-2.1, 300MHz CASE

Load Program 4-3 & load y params			Load Program EE1-06A (EE pac)		
1. GSBe select y parameters			50. GSBe load reference Z & convert y params to s parameters		
5. ENT↑	Im	load y_{ie} and	load this program (Program 4-2)		
6.5 →P	Re	convert to			
1.-03 x		polar format			
11. GSBA	ij				
-90. ENT↑	θ	load y_{re} in	GSBe print s parameters		
1.35-03	mag	polar format			
12. GSBA	ij				
-32. ENT↑	Im	load y_{fe} and			
CHS	Re	convert to	147.6+00 ***	$\angle s_{11}$	
→P		polar format	464.4-03 ***	$ s_{11} $	
1.-03 x			93.63+00 ***	$\angle s_{12}$	
21. GSBA	ij		41.01-03 ***	$ s_{12} $	
2.6 ENT↑	Im	load y_{oe} and	-27.41+00 ***	$\angle s_{21}$	
.25 →P	Re	convert to	1.404+00 ***	$ s_{21} $	
1.-03 x		polar format	-10.62+00 ***	$\angle s_{22}$	
22. GSBA	ij		1.024+00 ***	$ s_{22} $	
GSBE print stored params			load R_L and calculate ρ_L using 50 ohm Z_0		
54.16+00 ***	$\angle y_{11}$	$\angle y_{ie}$			
11.10-03 ***	$ y_{11} $	$ y_{ie} $			
-90.00+00 ***	$\angle y_{12}$	$\angle y_{re}$			
1.350-03 ***	$ y_{12} $	$ y_{re} $	0. ENT↑ Im R_L		
-45.00+00 ***	$\angle y_{21}$	$\angle y_{fe}$	220. ENT↑ Re R_L		
45.25-03 ***	$ y_{21} $	$ y_{fe} $	50. GSBe Z_0		
84.51+00 ***	$\angle y_{22}$	$\angle y_{oe}$	0.000+00 ***	$\angle \rho_L$	
2.612-03 ***	$ y_{22} $	$ y_{oe} $	629.6-03 ***	$ \rho_L $	
GSBB CE → CB conversion			GSBB load ρ_L into program		
GSBE print stored params			GSBB execute design		
-29.31+00 ***	$\angle y_{1b}$				
44.44-03 ***	$ y_{1b} $				
78.69+00 ***	$\angle y_{rb}$				
-1.275-03 ***	$ y_{rb} $		-9.018+00 ***	$\angle s_{11}'$	
-42.35+00 ***	$\angle y_{fb}$		1.027+00 ***	$ s_{11}' $	
-43.64-03 ***	$ y_{fb} $		9.018+00 ***	$\angle 1/s_{11}'$	
84.51+00 ***	$\angle y_{ob}$		973.4-03 ***	$ 1/s_{11}' $	
2.612-03 ***	$ y_{ob} $		616.0+00 ***	Im Z_L	for $Z_0 = 50 \Omega$
			105.9+00 ***	Re Z_L	
			5.817+00 ***	$Q_{min} = \text{Im } Z_L / \text{Re } Z_L$	

A transmission line segment is designed to provide the load reactance of $j616$ ohms to resonate at 300 MHz. The real part of the load reactance is ignored since the Q of the resonant line will be much larger than the minimum Q required. The amplitude of the oscillation will increase until the amplifier becomes non-linear and its power gain is reduced to the point that Eq. (4-2.2) is satisfied with the equals sign.

Because of the high load reactance required, a high Z_o in the resonant line is desired. For the transmission line, use a #12 AWG wire spaced 0.25" off a ground plane as shown by Fig. 4-2.3.

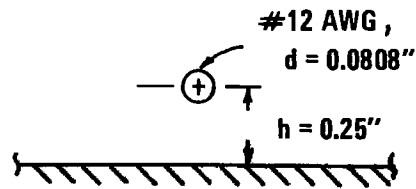


Figure 4-2.3 Air dielectric transmission line.

The characteristic impedance, Z_o , of this line is:

$$Z_o = \frac{138}{\sqrt{\epsilon_r}} \log \frac{4h}{d} \quad (4-2.5)$$

where ϵ_r is the relative dielectric constant of the dielectric, and is unity for air. Using this ϵ_r , and the d and h shown in Fig. 4-2.3, the characteristic impedance of the line is 150.6 ohms.

If the trimmer capacitor at the far end of the line is a 1 - 10 pF piston trimmer, its reactance with 10 pF at 300 MHz is:

$$X_c = -j/(2\pi fC) = -j53.05 \text{ ohms} \quad (4-2.6)$$

The length of transmission line that transforms $-j53.05$ ohms to $j616$ ohms is needed. Equation (1-1.1) can be manipulated to provide the solution for line length i.e.:

$$e^{2\gamma\ell} = \frac{\rho}{\rho_t} \quad (4-2.7)$$

where ρ_t is defined by Eq. (1-2.7). Since the transmission line load impedance is purely imaginary, as is the required input impedance, and the line is essentially lossless, the expressions for the reflection coefficients are the ratios of complex conjugates, and Eq. (4-2.7) can be reduced to the following forms:

$$\ell = \frac{\lambda}{2\pi} \left\{ \tan^{-1} \left(\frac{j \cdot Z_r}{Z_o} \right) - \tan^{-1} \left(\frac{j \cdot Z_s}{Z_o} \right) \right\} \quad (4-2.8)$$

where

$$\gamma = j\beta = j \frac{2\pi}{\lambda}$$

Using Eq. (4-2.8) with $Z_r = -j53.05$ ohms, $Z_s = 616$ ohms, $Z_o = 150.6$ ohms, and $\lambda = 3 \times 10^8 / \text{freq} = 1$ meter = 39.27 inches yields $\ell = 10.46$ inches. This length is too long to be practical. If capacity is added to the transistor collector circuit, less inductance will be required from the transmission line stub, and a shorter stub can be used. If 10 pF is added from the collector to ground, the susceptance of this capacitor will be:

$$B = 2\pi fC = (2\pi)(300 \times 10^6)(10^{-11}) = 18.85 \text{ mmho}$$

This susceptance is subtracted from the susceptance required from the transmission line stub to obtain the new transmission line susceptance and hence, input reactance:

$$B_{\text{line}} = \frac{-1}{616} - 0.01885 = -0.02047 \text{ mho}$$

or

$$X_{\text{line}} = \frac{-1}{B_{\text{line}}} = 48.84 \text{ ohms}$$

Using Eq. (4-2.8) with $Z_s = j48.84$ and the other parameters unchanged yields $\ell = 4.09$ inches, which is much more practical. With this line length, the trimmer capacitor value for oscillation at 400 MHz is calculated as shown by the HP-97 printout in Fig. (4-2.5). Again, neglecting the real part of Z_L , and accommodating the susceptance of the additional 10 pF at the transistor collector, the line must present a reactance of 36.22 ohms to the collector. Using Eq. (4-2.8) and solving for Z_r given $\ell = 4.09$ inches, $\lambda = 29.53$ inches, $Z_s = j36.22$ ohms and $Z_o = 150.6$ ohms yields $Z_r = -j110.8$ ohms. At 400 MHz, $-j110.8$ ohms is the

reactance of a 3.6 pF capacitor, which is within the tuning range of the piston trimmer capacitor. The complete schematic of the oscillator is shown in Fig. 4-2.4, which was breadboarded and does oscillate over the 300 to 400 MHz range. This type of oscillator is often used as the local oscillator in UHF tv tuners.

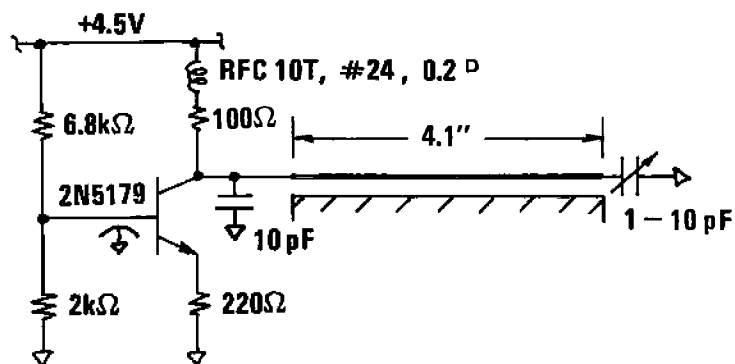


Figure 4-2.4 UHF oscillator schematic.

Load Program 4-3 and load y params			Load Program EE1-06A (EE pao)		
1. GSBe select y parameters			50. GSBk load reference Z & convert y parameters to s parameters		
10.7 ENT↑	Im y _{ie}		Load this program (Program 4-2)		
9.2 +P	Re y _{ie}		GSBc print s parameters		
1.-03 x			139.2+00 ***	4 s ₁₁	
11. GSBA ij			450.8-03 ***	s ₁₁	
-90. ENT↑	4 y _{re}		95.19+00 ***	4 s ₁₂	
1.8-03 ENT↑	y _{re}		77.48-03 ***	s ₁₂	
12. GSBA ij			-36.90+00 ***	4 s ₂₁	
-34. ENT↑	Im y _{fe}		1.369+00 ***	s ₂₁	
25. +P	Re y _{fe}		-15.96+00 ***	4 s ₂₂	
1.-03 x			1.059+00 ***	s ₂₂	
21. GSBA ij			load R _L and calc ρ _L using 50 ohm Z ₀		
4. ENT↑	Im y _{oe}		0. ENT↑	Im R _L	
.3 +P	Re y _{oe}		220. ENT↑	Re R _L	
1.-03 x			50. GSBe	Z ₀	
22. GSBA ij			0.000+00 ***	4 ρ _L	
GSBE print stored values			629.6-03 ***	ρ _L	
49.31+00 ***	4 y _{ie}		GSBB load ρ _L into program		
14.11-03 ***	y _{ie}		GSBb execute design		
-90.00+00 ***	4 y _{re}		-13.06+00 ***	4 s ₁₁ '	
1.800-03 ***	y _{re}		1.067+00 ***	s ₁₁ '	
-53.67+00 ***	4 y _{fe}		13.06+00 ***	4 1/s ₁₁ '	
42.20-03 ***	y _{fe}		937.0-03 ***	1/s ₁₁ '	
85.71+00 ***	4 y _{oe}		403.8+00 ***	Im Z _L for Z ₀ = 50	
4.011-03 ***	y _{oe}		116.3+00 ***	Re Z _L	
GSBB convert CE → CB			3.471+00 ***	Q _{min} = Im Z _L / Re Z _L	
GSBE print CB values					
-31.45+00 ***	4 y _{ib}				
40.44-03 ***	y _{ib}				
82.23+00 ***	4 y _{rb}				
-2.220-03 ***	y _{rb}				
-49.86+00 ***	4 y _{fb}				
-39.24-03 ***	y _{fb}				
85.71+00 ***	4 y _{ob}				
4.011-03 ***	y _{ob}				

Fig. 4-2.5 HP-97 printout for 400 MHz case.

LOAD S PARAMETERS:									
001	*LELA								
002	ENT↑								
003	+								
004	2	calculate storage index							
005	1								
006	-								
007	STOI								
008	R↓	recover and store θ_{ij}							
009	STOI								
010	ISZI	increment index							
011	R↓	recover and store s_{ij}							
012	STOI								
013	GTOS	goto space and return							
014	*LBLB	ENTER LOAD REFLECTION COEF							
015	STOE	store magnitude							
016	XZY								
017	STO7	store angle							
018	GTOS	goto space and return							
019	*LBLC	CALCULATE s_{11}'							
020	RCL3	$ s_{12} $							
021	STO8								
022	RCL4	$\angle s_{12}$							
023	STO9								
024	RCLB	$ s_{21} \quad s_{11}' = s_{11} + \frac{s_{12} s_{21} P_L}{1 - s_{22} P_L}$							
025	STX8								
026	RCLC	$\angle s_{21}$							
027	ST+9								
028	RCL6	$ P_L $							
029	STX8								
030	RCL7	$\angle P_L$							
031	ST+9								
032	RCL6	$\angle s_{22}$							
033	RCL7	$\angle p$							
034	+								
035	RCLD	$ s_{22} $							
036	RCL6	$ p $							
037	x								
038	CHS								
039	+R								
040	EEX								
041	+								
042	+P	$1 - s_{22} \cdot P_L$							
043	ST=8								
044	XZY								
045	ST-9								
046	RCL9	$\left\{ \begin{array}{l} \frac{s_{12} \cdot s_{21} \cdot P_L}{1 - s_{22} \cdot P_L} \\ \text{in polar coordinates} \end{array} \right.$							
047	RCL8								
048	+R								
049	STO8	$\left\{ \begin{array}{l} \frac{s_{12} \cdot s_{21} \cdot P_L}{1 - s_{22} \cdot P_L} \\ \text{in rect coordinates} \end{array} \right.$							
050	XZY								
051	STO9								
052	RCL2	s_{11}							
053	RCL1								
054	+R								
055	ST+8								

REGISTERS									
0	1	2	3	4	5	6	7	8	9
	$ s_{11} $	$\angle s_{11}$	$ s_{12} $	$\angle s_{12}$		$ P_L $	$\angle P_L$	scratch	scratch
S0	scratch	S1 scratch	S2 Im P_L	S3 Re P_L	S4 $Z_0, Z_L $	S5 scratch, $\angle Z_L$	S6 scratch	S7	S8
A	B	C	D	E	F	G	H	I	J
	$ s_{21} $	$\angle s_{21}$	$ s_{22} $	$\angle s_{22}$					

Program Listing II

111 RCL4	166 GSB0	167 GSB0	168 5	169 0	} use 50 ohm Z_0
112 PZS	170 GSB0	171 =	172 GSB5	173 GT09	
113 +R	174 *LBL6	goto space and return subr			
114 XZY	175 RCL1	PRINT S PARAMETER MATRIX			
115 GT08	176 RCL2	S_{11}			
116 *LBL6	177 GSB8				
117 PZS	178 RCL3	S_{12}			
118 ST04	179 RCL4	S_{21}			
119 R4	180 GSB8	S_{22}			
120 ST03	181 RCLB				
121 R4	182 RCLC				
122 ST02	183 GSB8				
123 R4	184 RCLD				
124 R4	185 RCLE				
125 -	186 *LBL8	print subroutine			
126 +P	187 GSB5				
127 ST05	188 XZY				
128 XZY	189 GSB5				
129 ST06	190 *LBL9	space and return subroutine			
130 RCL2	191 F0?	space if flag 0 is set			
131 RCL3	192 SPC				
132 RCL4	193 RTN				
133 +	194 *LBL7	R/S lookup subroutine			
134 +P	195 R/S				
135 ST=5	196 GT07				
136 XZY	197 *LBL5	print or R/S subroutine			
137 ST=6	198 F0?	if flag 0 is set, print			
138 RCL5	199 PRTX	and return			
139 RCL6	200 F0?				
140 PZS	201 RTN				
141 GT08	202 R/S	otherwise stop			
142 *LBL6	203 RTN				
143 RCLE	Notes: Flag 0 controls the print or R/S decision. It should be set or reset to reflect the users choice of printed output, or program halts for output respectively at the time the magnetic card is recorded.				
144 RCL2					
145 ST0E					
146 XZY					
147 ST02					
148 RCLD					
149 RCL1					
150 ST0D					
151 XZY					
152 ST01					
153 RCLC					
154 RCL4					
155 ST0C					
156 XZY					
157 ST04					
158 RCLB					
159 RCL3					
160 ST0B					
161 XZY					
162 ST03					
163 GT07					
164 *LBL6					
165 GSB0					

LABELS					FLAGS	SET STATUS			
A load 3 parameters	B enter load reflection coef	C calculate S_{11}'	D calculate $S_{11}' \rho$	E $\rho, Z_0 \rightarrow Z$	0 print	FLAGS		TRIG	DISP
a interchange ports 1 & 2	b f_A, C, f_D, E	c print s matrix	d calculate $1/S_{11}'$	e $Z, Z_0 \rightarrow \rho$	1	ON OFF			
0	1	2	3	4	2	0 <input type="checkbox"/> <input type="checkbox"/>	DEG <input checked="" type="checkbox"/>	FIX	
						1	GRAD	SCI	
						2	RAD	ENG <input checked="" type="checkbox"/>	
						3		n. 3	
5 print R/S subroutine	6	7 R/S lookup	8 print & space subroutine	9 space subroutine	3				

LABELS					FLAGS	SET STATUS		
A load 3 parameters	B enter load reflection coef	C calculate S_{11}	D calculate $S_{11} \cdot \rho$	E $\rho, Z_0 \rightarrow Z$	0 print	FLAGS		
a interchange ports 1 & 2	b FA, C, FD, E	c print s matrix	d calculate $1/S_{11}$	e Z, Z ₀ → ρ	1	ON OFF	TRIG	DISP
0	1	2	3	4	2	0 <input type="checkbox"/> <input type="checkbox"/>	DEG <input checked="" type="checkbox"/>	FIX
5 print R/S subroutine	6	7 R/S lookup	8 print & space subroutine	9 space subroutine	3	1 <input type="checkbox"/>	GRAD	SCI
						2 <input type="checkbox"/>	RAD	ENG <input checked="" type="checkbox"/>
						3 <input type="checkbox"/>		n 3

PROGRAM 4-3 TRANSISTOR CONFIGURATION CONVERSION.

Program Description and Equations Used

This program allows conversion between common emitter, common base, and common collector configurations of transistor h parameters or y parameters, as well as conversions between the h and the y parameters.

The configuration conversions is done by operating on the y parameters and converting to and from the h parameters for data input and output. To make the program operate in either h or y parameters, the conversion process is skipped for the y parameter case. Label 7 of the program contains the coding that accomplishes the h to y, or y to h conversion. Label 7 is called at the beginning and end of the configuration conversion, and flag 0 is used to indicate whether or not the subroutine under label 7 should be skipped or not.



Figure 4-3.1 Two-port network conventions.

Given a two-port network with port voltages and currents as defined by Fig. 4-3.1, the y and h parameters are defined as follows:

h parameters

$$\begin{bmatrix} E_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ E_2 \end{bmatrix} \quad (4-3.1)$$

y parameters

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \cdot \begin{bmatrix} E_1 \\ E_2 \end{bmatrix} \quad (4-3.2)$$

The network ports correspondence to the transistor elements is shown in Table 4-3.1.

Table 4-3.1 Transistor 2-port correspondences

Configuration	1	1' or 2'	2
CE	B	E	C
CB	E	B	C
CC	B	C	E

The h parameters are converted to y parameters with the following transformation [15]:

$$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} = \frac{1}{h_{11}} \begin{bmatrix} 1 & -h_{12} \\ h_{21} & h_{11}h_{22} - h_{12}h_{21} \end{bmatrix} \quad (4-3.3)$$

Likewise, the y parameters are converted to h parameters in similar fashion:

$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \frac{1}{y_{11}} \begin{bmatrix} 1 & -y_{12} \\ y_{21} & y_{11}y_{22} - y_{21}y_{12} \end{bmatrix} \quad (4-3.4)$$

Since the form of both conversions is identical, the same subroutine is used for both conversions (subroutine 7).

The y matrix representing the present transistor configuration is

transformed into another y matrix representing the new transistor configuration. This new matrix is designated y' for clarity. These transformations are:

For CE → CB or CB → CE,

(4-3.5)

$$\begin{bmatrix} y_{11}' & y_{12}' \\ y_{21}' & y_{22}' \end{bmatrix} = \begin{bmatrix} \{y_{11} + y_{22} + y_{12} + y_{21}\} & \{-(y_{12} + y_{22})\} \\ \{-(y_{21} + y_{22})\} & \{y_{11}\} \end{bmatrix}$$

For CC → CE or CE → CC,

(4-3.6)

$$\begin{bmatrix} y_{11}' & y_{12}' \\ y_{21}' & y_{22}' \end{bmatrix} = \begin{bmatrix} \{y_{11}\} & \{-(y_{11} + y_{12})\} \\ \{-(y_{11} + y_{21})\} & \{y_{11} + y_{22} + y_{21} + y_{12}\} \end{bmatrix}$$

For CC → CB,

(4-3.7)

$$\begin{bmatrix} y_{11}' & y_{12}' \\ y_{21}' & y_{22}' \end{bmatrix} = \begin{bmatrix} \{y_{22}\} & \{-(y_{21} + y_{22})\} \\ \{-(y_{12} + y_{22})\} & \{y_{11} + y_{12} + y_{21} + y_{22}\} \end{bmatrix}$$

For CB → CC,

(4-3.8)


$$\begin{bmatrix} y_{11}' & y_{12}' \\ y_{21}' & y_{22}' \end{bmatrix} = \begin{bmatrix} \{y_{11} + y_{22} + y_{21} + y_{12}\} & \{-(y_{11} + y_{21})\} \\ \{-(y_{11} + y_{12})\} & \{y_{11}\} \end{bmatrix}$$

After the respective conversion is complete, the y' matrix has replaced the y matrix in storage.

In looking over the various conversions, one will notice similarities in the operations used. There are four basic operations used to perform all the conversions:

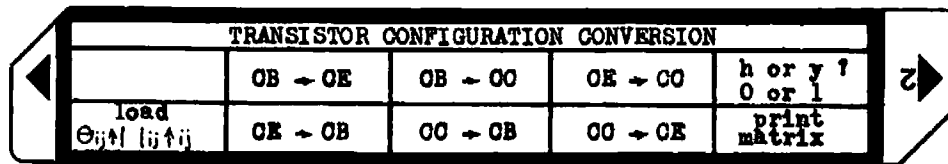- 1) no change;
- 2) $(y_{11} \text{ or } y_{22}) + y_{12}$;
- 3) $(y_{11} \text{ or } y_{22}) + y_{21}$; and
- 4) $y_{11} + y_{22} + y_{12} + y_{21}$.

The choice between y_{11} and y_{22} or y_{12} and y_{21} can be taken care of by interchanging the appropriate y matrix elements prior to these calculations. This matrix reordering is accomplished under label 3. The matrix conversion calculation is done under label 6 (two places); thus, these subroutines are selectively used to achieve all conversions.



STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card			
2	Select h or y matrix mode a) h parameters b) y parameters	0 1	<input type="button" value="F"/> <input type="button" value="E"/> <input type="button" value="F"/> <input type="button" value="E"/>	0 1
3	Load matrix to be converted a) angle of h_{ij} or y_{ij} b) magnitude of h_{ij} or y_{ij} c) subscript repeat this step for $ij = 11, 12, 21, 22$ in any order	θ_{ij} ij ij	<input type="button" value="ENT"/> ↑ <input type="button" value="ENT"/> ↑ <input type="button" value="A"/>	
4	Select conversion desired a) common emitter to common base b) common base to common emitter c) common collector to common base d) common base to common collector e) common collector to common emitter f) common emitter to common collector		<input type="button" value="B"/> <input type="button" value="F"/> <input type="button" value="B"/> <input type="button" value="C"/> <input type="button" value="F"/> <input type="button" value="C"/> <input type="button" value="D"/> <input type="button" value="F"/> <input type="button" value="D"/>	
5	Print converted matrix		<input type="button" value="E"/>	θ_{11} 11 θ_{12} 12 θ_{21} 21 θ_{22} 22

Example 4-3.1

Convert the following common collector h parameter matrix to a common base h parameter matrix:

$$\begin{bmatrix} h_{ic} & h_{rc} \\ h_{fc} & h_{oc} \end{bmatrix} = \begin{bmatrix} 1000 \angle 40^\circ & 10^{-4} \angle -50^\circ \\ 100 \angle 40^\circ & 50 \times 10^{-6} \angle 0 \end{bmatrix}$$

PROGRAM INPUT			PROGRAM OUTPUT		
40. ENT*	$\angle h_{ic}$		0. GSSE	select h parameters	
1000. ENT†	$ h_{ic} $				
11. GSSE	ij		GSSE	execute CC \rightarrow CB conv	
-50. ENT*	$\angle h_{rc}$		GSSE	print stored matrix	
1.-04 ENT†	$ h_{rc} $		-9.971+00 ***	$\angle h_{ib}$	
12. GSSE	ij		22.261+03 ***	$ h_{ib} $	
40. ENT*	$\angle h_{fc}$		-9.967+00 ***	$\angle h_{rb}$	
100. ENT†	$ h_{fc} $		2.261+03 ***	$ h_{rb} $	
21. GSSE	ij		-179.9+00 ***	$\angle h_{fb}$	
0. ENT*	$\angle h_{oc}$		1.000+00 ***	$ h_{fb} $	
50.-06 ENT†	$ h_{oc} $		-49.97+00 ***	$\angle h_{oc}$	
22. GSSE	ij		1.130-03 ***	$ h_{oc} $	

Common base h parameter matrix from HP-97 output:

$$\begin{bmatrix} h_{ib} & h_{rb} \\ h_{fb} & h_{ob} \end{bmatrix} = \begin{bmatrix} 22600 \angle -9.971^\circ & 2261 \angle -9.967^\circ \\ 1.000 \angle -179.9^\circ & 1.130 \times 10^{-3} \angle -49.97^\circ \end{bmatrix}$$

[illegible]

Program Listing II

111 CHS	166 RCL7	calculate and store:
112 RCL6	167 GSB9	
113 RCLD	168 STOD	
114 GSB8	169 R4	$a_{22}' = \frac{\Delta A}{a_{11}}$
115 STOD	170 STOE	
116 R4	171 RTN	return to subroutine call
117 STOE	172 GT02	goto R/S lookup
118 RTN	173 *LBL8	complex addition subroutine
119 *LBL7	174 +R	
120 F0?	175 R4	input and output are in
121 RTN	176 R4	polar co-ordinates
122 RCL2	177 +R	
123 RCL1	178 X*Y	
124 RCLD	179 R4	
125 RCL6	180 +	
126 GSB9	181 R4	
127 STOE	182 +	
128 R4	183 R4	
129 STOE	184 +P	
130 RCL4	185 RTN	
131 RCL3	186 *LBL9	complex multiply subroutine
132 RCLB	187 R4	
133 RCLC	188 X	input and output are in
134 GSB9	189 R4	polar co-ordinates
135 CHS	190 +	
136 RCL7	191 R4	
137 RCL6	192 +R	
138 GSB8	193 +P	
139 STOE	194 RTN	
140 R4	195 *LBL5	PRINT STORED MATRIX
141 STOE	196 RCL1	
142 RCL2	197 RCL2	
143 CHS	198 GSB5	
144 STOE	199 RCL3	
145 RCL1	200 RCL4	
146 1/X	201 GSB5	
147 STOE	202 RCLB	
148 RCL3	203 RCLC	
149 CHS	204 GSB5	
150 RCL4	205 RCLD	
151 GSB9	206 RCL6	
152 STOE	207 *LBL5	print subroutine
153 R4	208 PRTX--	or R/S
154 STOE	209 X*Y	
155 RCL2	210 PRTX--	or R/S
156 RCL1	211 *LBL4	space and return subroutine
157 RCLB	212 SPC	
158 RCLC	213 RTN	
159 GSB9	214 *LBL2	R/S lookup subroutine
160 STOE	215 R/S	
161 R4	216 GT02	
162 STOE	217 *LBL5	SELECT y OR h PARAMETERS
163 RCL2	218 CF0	
164 RCL1	219 X>0?	set flag 0 if "1" entered
165 RCL6	220 SF0	
	221 RTN	return to keyboard control

LABELS					FLAGS	SET STATUS		
A Load data	B CE → CB	C CC → CB	D CC → CE	E print matrix	0 set for y	FLAGS	TRIG	DISP
a	b CB → CE	c CB → CC	d CE → CC	e select y or h	1	ON OFF	DEG	FIX
0	1	2	3 rearrange matrix	4 space & rtn subroutine	2	0 <input type="checkbox"/>	1 <input type="checkbox"/>	2 <input type="checkbox"/>
5 print subroutine	6 [h] → [h]	7 [h] → [y]	8 complex add	9 complex multiply	3	1 <input type="checkbox"/>	GRAD	SCI
						2 <input type="checkbox"/>	RAD	ENG
						3 <input type="checkbox"/>		n 3

PROGRAM 4-4 COMPLEX 2x2 MATRIX OPERATIONS – PART 1.

Program Description and Equations Used

This program is one of two programs to manipulate complex 2x2 matrices. When dealing with high frequency amplifiers employing feedback, and input and output networks, one way of obtaining the overall amplifier response is to operate on the matrices that describe these 2-port networks. Shunt feedback may be included within the transistor transfer matrix through Y matrix addition. Y matrices can be converted to Z matrices using the complex matrix inverse routine. Series feedback is included by adding Z matrices. The input and output networks are included by multiplying ABCD (transmission) matrices.

This program will perform matrix addition ($A + B \rightarrow A$), subtraction ($A - B \rightarrow A$), multiplication ($AB \rightarrow A$), and interchange ($A \rightleftharpoons B$) with 2x2 matrices having complex coefficients. Data entry and output may be in either rectangular or polar format. All data stored and used by the program is in rectangular format. If flag 1 is set, polar format is indicated and the data is converted to and from rectangular format upon data input or output respectively.

The program operation is very straightforward, and matrix operations are done in the conventional manner. Two subroutines are used, one for complex addition and the other for complex multiplication. See [6], [14] for matrix algebra details.

Both this program and the companion program (Program 4-5) share common register storage allocations; thus, matrix manipulations requiring functions contained in different programs are easily accommodated.

Matrix addition and subtraction:

$$\begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \pm \begin{bmatrix} b_{11} & b_{12} \\ b_{21} & b_{22} \end{bmatrix} = \begin{bmatrix} r_{11} & r_{12} \\ r_{21} & r_{22} \end{bmatrix}$$

$$r_{11} = a_{11} \pm b_{11}$$

$$r_{22} = a_{22} \pm b_{22}$$

$$r_{21} = a_{21} \pm b_{21}$$

$$r_{12} = a_{12} \pm b_{12}$$

The R matrix replaces the A matrix at the completion of the routine.

Matrix multiplication:

$$\begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \times \begin{bmatrix} b_{11} & b_{12} \\ b_{21} & b_{22} \end{bmatrix} = \begin{bmatrix} r_{11} & r_{12} \\ r_{21} & r_{22} \end{bmatrix}$$

$$r_{11} = a_{11} b_{11} + a_{12} b_{21}$$

$$r_{12} = a_{11} b_{12} + a_{12} b_{22}$$

$$r_{21} = a_{21} b_{11} + a_{22} b_{21}$$

$$r_{22} = a_{21} b_{12} + a_{22} b_{22}$$

Again, the R matrix replaces the A matrix at the completion of the routine.


Matrix interchange:

$$\begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \begin{matrix} \rightarrow \\ \leftarrow \end{matrix} \begin{bmatrix} b_{11} & b_{12} \\ b_{21} & b_{22} \end{bmatrix} \quad \begin{matrix} a_{11} \leftrightarrow b_{11} \\ a_{12} \leftrightarrow b_{12} \\ a_{21} \leftrightarrow b_{21} \\ a_{22} \leftrightarrow b_{22} \end{matrix}$$

User Instructions

COMPLEX 2x2 MATRIX OPERATIONS - PART 1				
print A	print B	rect/polar 0 / 1	$A \pm B$	
load A	load B	$A + B \rightarrow A$	$A - B \rightarrow A$	$A \times B \rightarrow A$

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of the program card			
2	select polar or rectangular format		<div>f 0</div> <div>f 0</div> <div>f 0</div> <div>⋮</div>	<div>0 (rect)</div> <div>1 (polar)</div> <div>0 (rect)</div> <div>⋮</div>
3	Load A matrix in selected format (step 2) rectangular format shown here a) imaginary part of matrix element b) real part of matrix element c) load element subscript Do this step for subscripts 11, 12, 21, 22 in any order.	<div>Im a_{ij}</div> <div>Re a_{ij}</div> <div>ij</div>	<div>ENT ↑</div> <div>ENT ↑</div> <div>A</div>	
4	Load B matrix in selected format (step 2) polar format shown here a) load angle of matrix element b) load magnitude of matrix element c) load element subscript Do this step for subscripts 11, 12, 21, 22 in any order	<div>$\angle b_{ij}$</div> <div>b_{ij}</div> <div>ij</div>	<div>ENT ↑</div> <div>ENT ↑</div> <div>B</div>	
5	To print matrices in chosen format (say polar) a) A matrix -- use f A b) B matrix -- use f B		<div>f *</div>	<div>\angle_{11} 11</div> <div>\angle_{12} 12</div> <div>\angle_{21} 21</div> <div>\angle_{22} 22</div>

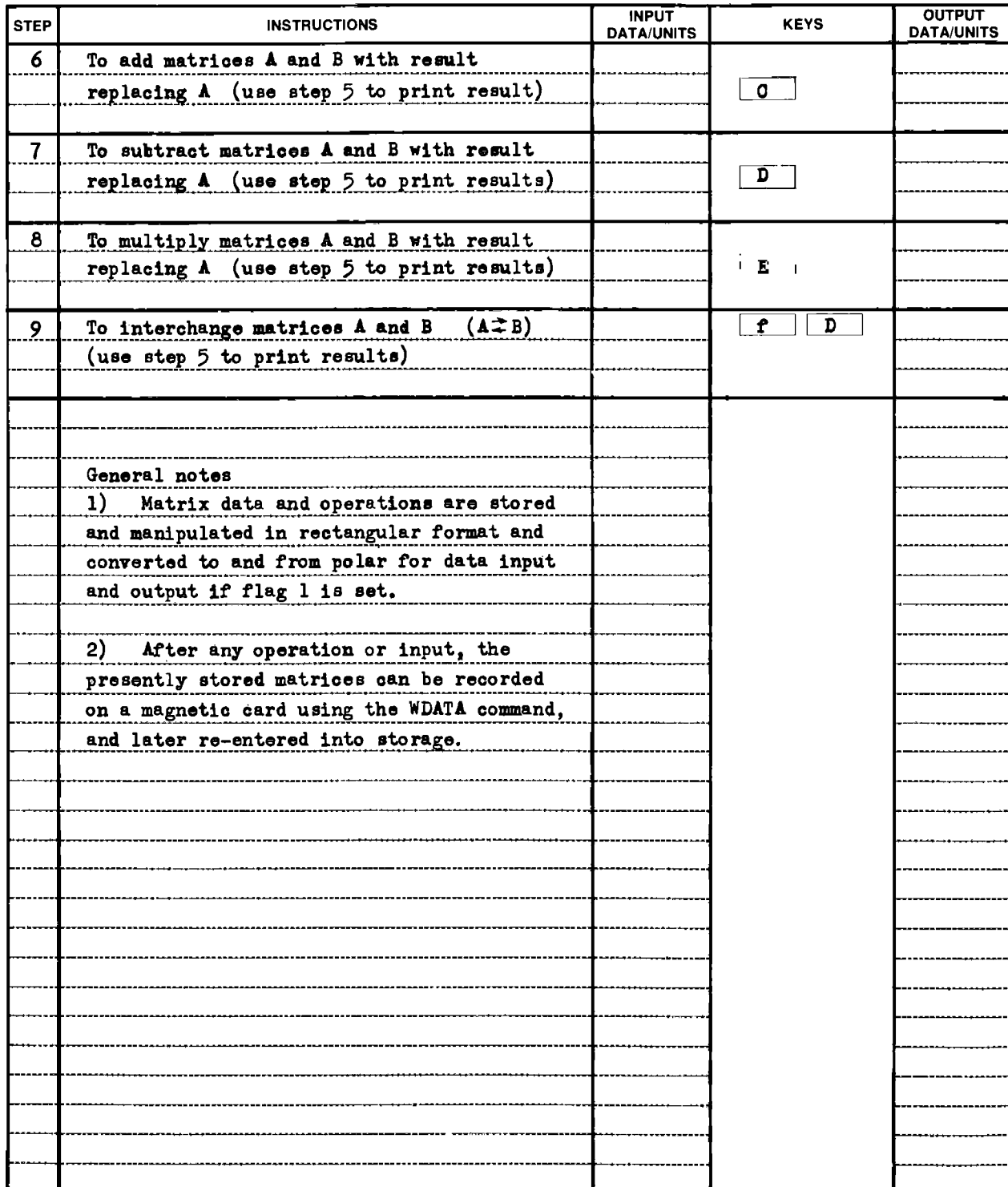

Example 4-4.1

Given

$$A = \begin{bmatrix} (3 + j4) & (4 + j5) \\ (5 + j6) & (2 + j4) \end{bmatrix}, \quad B = \begin{bmatrix} (4 + j5) & (5 + j6) \\ (6 + j7) & (7 + j8) \end{bmatrix}$$

Load the above matrices, store them on a data card, then perform $A + B$, $A - B$, and $A \times B$. The HP-97 printout for the matrix loading is shown below, and the program output is shown on the next page. The B matrix is loaded in scrambled order to demonstrate the free form loading feature of the program.

HP-97 PRINTOUT FOR EXAMPLE 4-4.1 INPUT

A MATRIX LOADING	B MATRIX LOADING
4.00 ENT↑ Im a ₁₁	6.00 ENT↑ Im b ₁₂
3.00 ENT↑ Re a ₁₁	5.00 ENT↑ Re b ₁₂
11.00 GSBA ij	12.00 GSBB ij
5.00 ENT↑ Im a ₁₂	7.00 ENT↑ Im b ₂₁
4.00 ENT↑ Re a ₁₂	6.00 ENT↑ Re b ₂₁
12.00 GSBA ij	21.00 GSBB ij
6.00 ENT↑ Im a ₂₁	8.00 ENT↑ Im b ₂₂
5.00 ENT↑ Re a ₂₁	7.00 ENT↑ Re b ₂₂
21.00 GSBA ij	22.00 GSBB ij
4.00 ENT↑ Im a ₂₂	5.00 ENT↑ Im b ₁₁
2.00 ENT↑ Re a ₂₂	4.00 ENT↑ Re b ₁₁
22.00 GSBA ij	11.00 GSBB ij
	MDTA record data card

HP-97 PRINTOUT FOR EXAMPLE 4.1 OUTPUT

<pre> GSBa print A matrix 4.00 *** Im a11 3.00 *** Re a11 5.00 *** Im a12 4.00 *** Re a12 6.00 *** Im a21 5.00 *** Re a21 4.00 *** Im a22 2.00 *** Re a22 </pre>	<pre> GSBC execute matrix addition GSBa print resultant matrix 9.00 *** Im r11 7.00 *** Re r11 11.00 *** Im r12 9.00 *** Re r12 13.00 *** Im r21 11.00 *** Re r21 12.00 *** Im r22 9.00 *** Re r22 </pre> <p>Note that the R matrix has replaced the A matrix in storage.</p>
<pre> ----- GSBb print B matrix 5.00 *** Im b11 4.00 *** Re b11 6.00 *** Im b12 5.00 *** Re b12 7.00 *** Im b21 6.00 *** Re b21 8.00 *** Im b22 7.00 *** Re b22 </pre>	<pre> ----- Reload A and B matrices by reading data card. GSBD execute mat subtraction GSBa print resultant matrix -1.00 *** Im r11 -1.00 *** Re r11 -1.00 *** Im r12 -1.00 *** Re r12 -1.00 *** Im r21 -1.00 *** Re r21 -4.00 *** Im r22 -5.00 *** Re r22 </pre>
	<pre> ----- Reload A and B matrices by reading data card. GSBE exec mat multiplication GSBa print resultant matrix 89.00 *** Im r11 -19.00 *** Re r11 105.00 *** Im r12 -21.00 *** Re r12 87.00 *** Im r21 -26.00 *** Re r21 104.00 *** Im r22 -29.00 *** Re r22 </pre>

Example 4-4.2

Because the resultant matrix replaces the A matrix in storage, operations may be chained. This example demonstrates that chaining ability starting with the A and B matrices given in Example 4-4.1.

```

GSBE  execute matrix multiplication:  A x B → A
GSBC  execute matrix addition:  AB + B → A
GSBD  execute matrix interchange:  AB + B ↗ B
GSBE  execute matrix multiplication:  B(AB + B) → A
GSBA  print resultant A matrix
651.00 ***  Im a11
-1194.00 *** Re a11

792.00 ***  Im a12
-1401.00 *** Re a12

957.00 ***  Im a21
-1640.00 *** Re a21

1162.00 ***  Im a22
-1923.00 *** Re a22

```

The same data can be outputted (printed) in polar format using the polar-rectangular toggle under label "c" to bring a 1 to the display.

```

GSBC } use polar-rectangular selection toggle
GSBC }
GSBA  print A matrix in polar format
151.40 ***  a11
1359.94 *** |a11|

150.52 ***  a12
1609.37 *** |a12|

149.73 ***  a21
1898.80 *** |a21|

148.86 ***  a22
2246.81 *** |a22|

```

Program Listing I

001	*LBLA	LOAD MATRIX A	056	*LBL0	matrix add/subtract subr
002	SF2	indicate matrix A	057	GSB4	recall matrix B element
003	*LBLB	LOAD MATRIX B	058	F0?	
004	1		059	CHS	change sign of element
005	2		060	XZY	parts if subtraction
006	-		061	F0?	is indicated
007	X>0?	calculate storage register	062	CHS	
008	8	location from subscript	063	XZY	
009	X>0?		064	DSZ1	decrement index
010	-		065	GSB4	recall matrix A element
011	ENT↑		066	GSB2	perform complex addition
012	+		067	GSB5	store result as matrix A
013	3		068	DSZ1	decrement index and
014	+		069	GT00	test for loop exit
015	EEX		070	GT01	goto space and return
016	F2?		071	*LBLB	MATRIX MULTIPLICATION
017	CLX		072	1	
018	+		073	2	calculate and
019	R↓		074	SF2	temporarily store:
020	F1?	if polar data, convert	075	GSB7	
021	+R	to rectangular format	076	3	
022	R↑	recover storage index	077	6	$a_{11} \cdot b_{11} + a_{12} \cdot b_{21} = r_{11}$
023	GSB8	store matrix element	078	GSB7	
024	GT01	goto space and return	079	9	
025	*LBLA	PRINT MATRIX A	080	GSB8	
026	EEX	initialize index register	081	1	
027	ST01	for matrix A	082	4	calculate and
028	GT0e	jump	083	SF2	temporarily store:
029	*LBLB	PRINT MATRIX B	084	GSB7	
030	2	initialize index register	085	3	
031	ST01	for matrix B	086	8	
032	*LBLB	matrix print subroutine	087	GSB7	$a_{11} \cdot b_{12} + a_{12} \cdot b_{22} = r_{12}$
033	GSB4	recall matrix element	088	ST0A	
034	F1?	convert to polar format	089	XZY	
035	+P	if flag 1 is set	090	ST0B	
036	XZY		091	2	
037	PRTX	print matrix element	092	5	calculate and
038	XZY	as complex quantity	093	SF2	temporarily store:
039	PRTX	(may be R/S statements	094	GSB7	
040	SPC	if desired)	095	7	
041	ISZ1	increment index by 2	096	6	
042	ISZ1		097	GSB7	$a_{21} \cdot b_{11} + a_{22} \cdot b_{21} = r_{21}$
043	8		098	ST0C	
044	RCL1		099	XZY	
045	XZY?	test for loop exit	100	ST0D	
046	GT0e		101	4	calculate and store:
047	GT01	goto space and return	102	5	
048	*LBLC	ADD A AND B MATRICES	103	SF2	
049	CF0	indicate matrix addition	104	GSB7	
050	GT0C	jump	105	7	
051	*LBLD	SUBTRACT A AND B MATRICES	106	8	
052	SF0	indicate matrix subtraction	107	GSB7	$a_{21} \cdot b_{12} + a_{22} \cdot b_{22} = r_{22}$
053	*LBLC		108	7	
054	8	initialize index register	109	GSB8	
055	ST01				

REGISTERS																			
0	scratch	1	Re a_{11}	2	Re b_{11}	3	Re a_{12}	4	Re b_{12}	5	Re a_{21}	6	Re b_{21}	7	Re a_{22}	8	Re b_{22}	9	temp Re r_{11}
S0	scratch	S1	Im a_{11}	S2	Im b_{11}	S3	Im a_{12}	S4	Im b_{12}	S5	Im a_{21}	S6	Im b_{21}	S7	Im a_{22}	S8	Im b_{22}	S9	temp Im r_{11}
A temporary Re r_{12}		B temporary Im r_{12}		C temporary Re r_{21}		D temporary Im r_{21}		E		scratchpad		I		index					

Program Listing II

110	9			162	*LBL2	complex add subroutine
111	GSB9	$r_{11} \rightarrow a_{11}$		163	XZY	
112	EEX			164	R↓	
113	GSB8			165	+	
114	RCLB			166	R↓	
115	RCLA			167	+	
116	3	$r_{12} \rightarrow a_{12}$		168	R↑	
117	GSB8			169	RTN	
118	RCLD			170	*LBL7	setup scratchpad index
119	RCLC			171	0	
120	5	$r_{21} \rightarrow a_{21}$		172	*LBL8	store storage index subr
121	GSB8			173	STOI	
122	*LBL1	space and return subroutine		174	R↓	
123	SPC			175	*LBL5	complex storage subroutine
124	RTN			176	STOI	
125	*LBL7	matrix multiply subroutine		177	XZY	
126	EEX			178	PZS	
127	1	recall first matrix element		179	STOI	
128	=			180	PZS	
129	GSB9			181	RTN	
130	RCLI			182	*LBL9	store recall index subr
131	FRC			183	STOI	
132	EEX			184	R↓	
133	1	recall second matrix element		185	*LBL4	complex recall subroutine
134	x			186	PZS	
135	GSB9			187	RCLi	
136	STOE	complex multiplication		188	PZS	
137	R↓			189	RCLi	
138	STOI			190	RTN	
139	R↓			191	*LBLc	POLAR/RECTANGULAR TOGGLE
140	ENT↑			192	CF1	clear flag 1 to indicate
141	R↑			193	CLX	rectangular format and
142	x			194	RTN	place a zero in the display
143	R↑			195	*LBLc	
144	RCLI			196	SF1	set flag 1 to indicate
145	XZY			197	EEX	polar format and place a
146	x			198	RTN	one in the display
147	LSTX			199	*LBLd	MATRIX INTERCHANGE
148	R↓			200	8	initialize index
149	-			201	STOI	
150	R↑			202	*LBL6	
151	RCLC			203	GSB4	
152	x			204	DSZI	recall corresponding
153	R↑			205	GSB4	matrix elements
154	RCLI			206	ISZI	
155	x			207	GSB5	
156	+			208	DSZI	interchange and store
157	XZY			209	R↓	corresponding elements
158	FZP			210	R↓	
159	GT07	jump if first product		211	GSB5	
160	0	recall first product		212	DSZI	decrement index and
161	GSB9	from scratchpad storage		213	GT06	test for loop exit
				214	GT01	goto space and return

LABELS					FLAGS	SET STATUS		
A load A	B load B	C A+B→A	D A-B→A	E A×B→A	0 subtract	FLAGS TRIG DISP		
a print A	b print B	c polar/rect 1 / 0	d A≠B	e print loop start	1 polar	ON OFF	DEG	FIX
0 matrix add/subtract	1 space&rtm	2 complex addition	3	4 complex recall	2 don't continue summation	0 <input type="checkbox"/>	GRAD	SCI
5 complex store	6 A≠B subroutine	7 matrix multiplication	8 store index & complex sto	9 store index & complex rcl	3	1 <input type="checkbox"/>	RAD	ENG <input type="checkbox"/>
						2 <input type="checkbox"/>		n 3
						3 <input type="checkbox"/>		

PROGRAM 4-5 COMPLEX 2x2 MATRIX OPERATIONS – PART 2.

Program Description and Equations Used

This program is the second of two programs to manipulate complex 2x2 matrices. This program will perform matrix inverse ($A^{-1} \rightarrow A$), matrix transpose ($A^T \rightarrow A$), matrix complex conjugate ($A^* \rightarrow A$), and matrix interchange ($A \rightleftharpoons B$). Because the resultant matrix from the matrix operation replaces the A matrix, chaining of matrix operations without data re-entry is easily done.

This program shares common register storage with Program 4-4, hence, matrix operations that require concatenation of routines contained in two different programs can be done without reloading any previous data.

The user may elect to work in either the polar or the rectangular co-ordinate systems, however, all data is stored in rectangular format. If flag 1 is set, the input data is converted from polar to rectangular, and vice-versa for output.

The algorithms used are:

Matrix inverse:

$$A^{-1} = \frac{1}{|A|} \begin{bmatrix} a_{22} & -a_{12} \\ -a_{21} & a_{11} \end{bmatrix} \quad (4-5.1)$$

where $|A|$ is the determinant of A,

$$|A| = a_{11} \cdot a_{22} - a_{21} \cdot a_{12} \quad (4-5.2)$$

Matrix transpose:

$$A^T = \begin{bmatrix} a_{11} & a_{21} \\ a_{12} & a_{22} \end{bmatrix} \quad (4-5.3)$$

Matrix complex conjugate:


$$A^* = \begin{bmatrix} a_{11}^* & a_{12}^* \\ a_{21}^* & a_{22}^* \end{bmatrix}$$

Matrix interchange, see Eq. (4-4.3).

User Instructions

COMPLEX 2x2 MATRIX OPERATIONS - PART 2				
print A	print B	polar/rect 1/0	$A \pm B$	calculate $ A $
load A	load B	$A^{-1} \rightarrow A$	$A^T \rightarrow A$	$A^* \rightarrow A$

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of the program card			
2	Select polar or rectangular format		<div>f 0</div> <div>f 0</div> <div>f 0</div> <div>⋮</div>	<div>0 (rect)</div> <div>1 (polar)</div> <div>0 (rect)</div> <div>⋮</div>
3	Load matrix A in selected format (rect shown)			
	a) load imaginary part of matrix element	Im a_{ij}	ENT↑	
	b) load real part of matrix element	Re a_{ij}	ENT↑	
	c) load subscript of matrix element	ij	A	
	Repeat this step for ij 11, 12, 21, 22 in any order.			
4	Load matrix B in selected format (polar used)			
	a) load angle of matrix element	$\angle b_{ij}$	ENT↑	
	b) load magnitude of matrix element	$ b_{ij} $	ENT↑	
	c) load subscript of matrix element	ij	B	
	Repeat this step for ij 11, 12, 21, 22 in any order.			
5	To print matrices in chosen format (say polar)			
	a) A matrix -- use f A		f *	\angle_{11} $ _{11}$
	b) B matrix -- use f B			\angle_{12} $ _{12}$
				\angle_{21} $ _{21}$
				\angle_{22} $ _{22}$

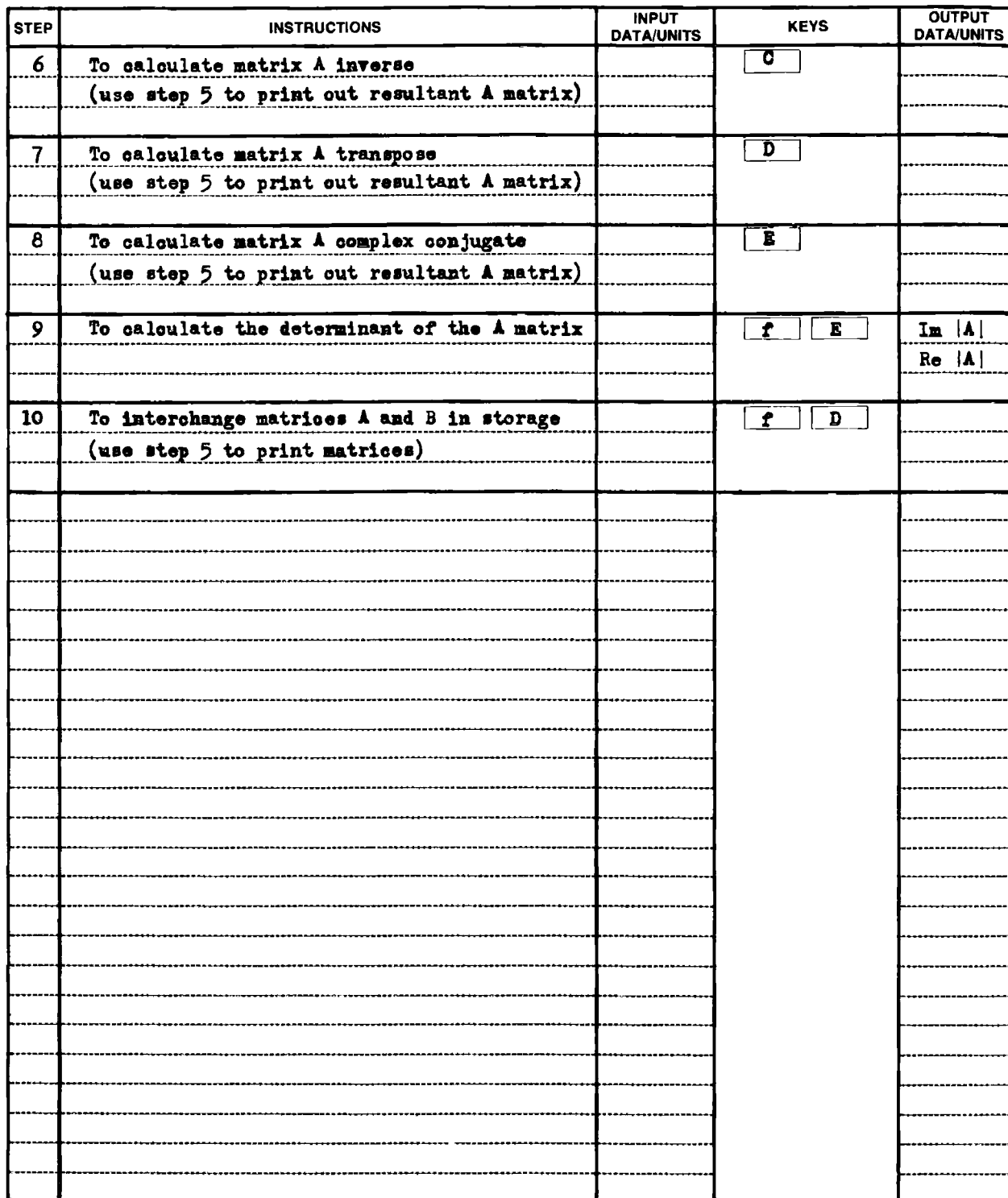

Example 4-5.1

Given the A and B matrices of Example 4-4.1, calculate $B^{-1}AB$. The loading of the A and B matrices is shown in Example 4-4.1, and is omitted here for brevity (they were actually loaded from the magnetic data card from Program 4-4).

Load Program 4-4, and load A and B matrices

GSBE form $AB \rightarrow A$

Load this program (Program 4-5)

GSBa interchange AB and B

GSBC form $B^{-1} \rightarrow A$

Reload Program 4-4

GSBE form $B^{-1}AB \rightarrow A$

GSBa print result

-48.25 *** Im a_{11}
-48.00 *** Re a_{11}

-54.50 *** Im a_{12}
-55.25 *** Re a_{12}

49.50 *** Im a_{21}
45.75 *** Re a_{21}

56.25 *** Im a_{22}
53.00 *** Re a_{22}

001	*LBLA	LOAD MATRIX A																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
-----	-------	---------------	--	--	--	--	--

Program Listing II

109	*LBL0	common output subroutine	164	ISZ1	
110	F1?	convert to polar if required	165	GSB5	
111	→P		166	DSZ1	interchange and store
112	XZY	print both parts of a	167	R4	corresponding matrix
113	PRTX	complex number	168	R4	elements
114	XZY	(may be R/S statements	169	GSB5	
115	PRTX	if desired)	170	DSZ1	decrement index and
116	GT01	goto space and return subr	171	GT06	test for loop exit
117	*LBL2	complex add subroutine	172	GT01	goto space and return subr
118	XZY		173	*LBLD	CALCULATE MATRIX A TRANSPOSE
119	R4		174	3	
120	+		175	GSB9	recall and scratchpad store
121	R4		176	ST0A	a ₁₂
122	+		177	XZY	
123	R4		178	ST0B	
124	RTN		179	5	
125	*LBL3	complex multiply subroutine	180	GSB9	recall a ₂₁ and store in
126	ST0E		181	3	a ₁₂ location
127	R4		182	GSB8	
128	ST0I		183	RCLB	
129	R4		184	RCLA	recall a ₁₂ from scratchpad
130	ENT↑		185	5	and store in a ₂₁ location
131	R4		186	GSB8	
132	x		187	GT01	goto space and return subr
133	R4		188	*LBL9	store recall index subr
134	RCL1		189	ST0I	
135	XZY		190	R4	
136	x		191	*LBL4	complex recall subroutine
137	LSTX		192	PZS	
138	R4		193	RCL1	
139	-		194	PZS	
140	R4		195	RCL1	
141	RCL1		196	RTN	
142	x		197	*LBL8	store storage index subr
143	R4		198	ST0I	
144	RCL1		199	R4	
145	x		200	*LBL5	complex storage subroutine
146	+		201	ST0I	
147	XZY		202	XZY	
148	RTN		203	PZS	
149	*LBLc	POLAR/RECTANGULAR TOGGLE	204	ST0I	
150	CF1	indicate rectangular format	205	PZS	
151	CLX	and place a zero in display	206	RTN	
152	RTN	return to keyboard control	207	*LBL6	CALCULATE MAT A COMPLEX CONJ
153	*LBLc		208	PZS	
154	SF1	indicate polar format and	209	1	reverse the sign of the
155	EEK	place a one in the display	210	CHS	imaginary parts of the
156	RTN	return to keyboard control	211	ST×7	matrix elements
157	*LBLd	MATRIX INTERCHANGE	212	ST×5	
158	8		213	ST×3	
159	ST0I	initialize index	214	ST×1	
160	*LBL6	loop start	215	PZS	
161	GSB4	recall corresponding	216	*LBL1	space and return subroutine
162	DSZ1	matrix elements	217	SPC	
163	GSB4		218	RTN	

LABELS					FLAGS	SET STATUS		
A load A	B load B	C A ¹ →A	D A ^T →A	E A*→A	0	FLAGS	TRIG	DISP
a print A	b print B	c polar/rect	d A≅B	e calc A	1 polar	ON OFF	users choice	
0 complex print	1 space & return	2 complex add	3 complex multiply	4 complex recall	2 used with A	0	DEG	FIX
5 complex store	6 A≅B subroutine	7 common print routine	8 sto index & cmplx store	9 store index & cmplx rcl	3	1	GRAD	SCI
						2	RAD	ENG
						3		n_____

Part 5

**ENGINEERING
MATHEMATICS**

PROGRAM 5-1 ELLIPTIC INTEGRALS AND FUNCTIONS.

Program Description and Equations Used

This program calculates complete elliptic integrals of the first kind and the following elliptic functions: elliptic sine (sn(u,k)), elliptic cosine (cn(u,k)), elliptic delta (dn(u,k)), and elliptic amplitude (am(u,k)).

The elliptic integral of the first kind is defined by Eq. (5-1.1), and the complete elliptic integral of the first kind is defined by Eq. (5-1.2), which can be evaluated using the infinite product shown in Eqs. (5-1.3) through (5-1.6). The product is terminated when k_m becomes smaller than 10^{-10} . Generally this condition is achieved after the 3rd term of the series, hence, the series converges rapidly. As the modulus, k , approaches 1, more iterations are required, e.g., $K(.9) = 2.280549137$ requires 4 iterations and $K(.999) = 4.495596396$ requires 5 iterations.

$$u(\phi, k) = \int_0^{\phi} (1 - k^2 \sin^2 x)^{-1/2} dx \quad (5-1.1)$$

$$K(k) = u\left(\frac{\pi}{2}, k\right) \quad (5-1.2)$$

$$K(k) = \frac{\pi}{2} \prod_{m=0}^{\infty} (1 + k_{m+1}) \quad (5-1.3)$$

$$k_{m+1} = (1 - k_m') / (1 + k_m') \quad (5-1.4)$$

$$k_m' = \sqrt{1 - k_m^2} \quad (5-1.5)$$

$$k_0 \equiv k \quad (5-1.6)$$

The elliptic modulus, k , is commonly expressed three different ways, which leads to some degree of confusion. In the Abramowitz and Stegun tables of elliptic functions [1], the parameters m and θ are used where $m = k^2$, and $\theta = \sin^{-1} k$. The parameter θ is called the modular angle.

The elliptic sine is an elliptic function, and is defined in a somewhat reverse manner from the elliptic integral. Referring to Eq. 5-1.1, given the input $u(\phi, k)$, the limit of integration, ϕ must be found to satisfy the equality, then $\text{sn}(u, k) = \sin \phi$. Likewise, the elliptic cosine is defined; $\text{cn}(u, k) = \cos \phi$. Notice that when $k = 0$, the elliptic sine equals the trigonometric sine and likewise for the respective cosines.

The descending Landen transformation [12], [46] is used to calculate the elliptic sine. Starting with an initial value for $\text{sn}(u_r, k_r)$ as given by Eq. (5-1.7), Eq. (5-1.8) is recursively used to find $\text{sn}(u_0, k_0)$ which is the answer.

$$\text{sn}(u_{m+1}, k_{m+1}) = \sin \left(\frac{\pi u_0}{2K(k)} \right) \quad (5-1.7)$$

$$\text{sn}(u_{r-1}, k_{r-1}) = \frac{(1 + k_r) \text{sn}(u_r, k_r)}{1 + k_r \text{sn}^2(u_r, k_r)} \quad (5-1.8)$$

where

$$r = m+1, m, \dots, 1$$

and k_r is obtained from storage, and was calculated from Eq. (5-1.4) during the complete elliptic integral calculation.

The descending Landen transformation is also the basis for Darlington's elliptic filter algorithms (Program 2-15).

The other elliptic functions are calculated from the elliptic sine as follows:

$$\text{cn}(u, k) = (1 - \text{sn}^2(u, k))^{\frac{1}{2}} \quad (5-1.9)$$

$$\text{dn}(u, k) = (1 - k^2 \cdot \text{sn}^2(u, k))^{\frac{1}{2}} \quad (5-1.10)$$

$$\text{am}(u, k) = \sin^{-1} \text{sn}(u, k) = \phi \quad (5-1.11)$$

Example 5-1.1

Evaluate the following elliptic functions and compare with Abramowitz and Stegun [1] Tables 17.1 and 17.5.

$$K(k); k = \sqrt{0.9}$$

$$\text{sn}(3.09448898, \sin 88^\circ)$$

HP-97 printout

```

      .9  √X
9.486832981-01 *** calculate k
      GSB#
2.578092113+00 *** K(k)

      3.09448898 ENT# load u
      88.  DEG
      SIN calculate k = sin 88°
9.993908270-01 *** sin 88°
      GSB#
9.961546961-01 *** sn(3.09448898, sin 88°)

      DEG
      SIN calculate and print φ = sin-1sn(u,k)
8.500000001+01 ***
```

From Table 17.1 (p. 608 of [1]), $K(m)$ for $m = 0.9$ is:

$$K(m) = 2.57809211334173$$

Rounded to ten significant figures, this figure agrees identically with the program output.

From Table 17.5 (p. 615 of [1]), the elliptic integral of the first kind for $\alpha = 88^\circ$, $\phi = 85^\circ$ is 3.09448898. The program output differs by 1 part in 8.5×10^9 , which exceeds the precision of the input.

Program Listing I

001 *LBLA	COMPUTE COMPLETE ELLIPTIC INT	045 *LBLR	CALCULATE ELLIPTIC SINE
002 GSB2	calculate K(k)	046 GSB3	calculate sn(u,k)
003 GT09	goto output routine	047 GT09	goto output routine
004 *LBL2	K(k) calculation subroutine	048 *LBL3	sn(u,k) calculation subr
005 ST00	store k	049 ST02	store k
006 Pi		050 R4	
007 2	calculate and store:	051 ST03	receiver and store u
008 ÷	$\frac{\pi}{2} \rightarrow R1$	052 RCL2	
009 ST01		053 GSB2	calculate K(k)
010 EEX		054 DSZ1	setup for sn(u,k) calc.
011 1	$10 \rightarrow R8$	055 RAD	
012 ST08		056 RCL3	
013 ST01		057 Pi	form and store initial
014 EEX		058 X	sn value for descending
015 CHS		059 RCL1	Landen transformation:
016 1	$10^{-10} \rightarrow R9$	060 ENT1	$sn(u_{m+1}, k_{m+1}) = sn\left\{\frac{\pi u_0}{2K(k)}\right\}$
017 0		061 +	
018 ST09		062 ÷	
019 *LBL0	K(k) loop start	063 SIN	
020 EEX	calculate and store:	064 ST04	
021 RCL0		065 *LBL1	transformation loop start
022 X ²	$k'_m = (1 - k_m^2)^{1/2}$	066 RCL1	
023 -		067 EEX	recursively use descending
024 JX		068 +	Landen transformation to
025 ST07		069 RCL4	find sn(u ₀ , k ₀):
026 CHS		070 X	
027 EEX	calculate and store:	071 RCL1	$sn(u_{r-1}, k_{r-1}) = \frac{(1+k_r)sn(u_r, k_r)}{1+sn^2(u_r, k_r)}$
028 +		072 RCL4	
029 RCL7	$k_{m+1} = \frac{1 - k'_m}{1 + k'_m}$	073 X ²	
030 EEX		074 X	
031 +		075 EEX	
032 ÷		076 +	
033 ST00		077 ÷	
034 ST01	store k _r for descending	078 ST04	
035 ISZ1	Landen transformation	079 DSZ1	
036 EEX		080 RCL1	
037 +	form $\prod (1 + k_{m+1})$	081 RCL8	test for loop exit
038 STX1		082 X<Y?	
039 RCL9		083 GT01	
040 RCL0	test for loop exit	084 RCL4	recall sn(u, k)
041 X>Y?		085 RTN	return to main program
042 GT00			
043 RCL1	recall K(k)		
044 RTN	return to main program		

REGISTERS									
0 k _i	1 K(k)	2 k ₀	3 u ₀	4 sn(u, k)	5	6	7 scratch	8 10	9 10 ⁻¹⁰
S0 k ₁	S1 k ₂	S2 k ₃	S3 k ₄	S4 k ₅	S5 k ₆	S6	S7	S8	S9
A	B	C	D	E	I				

Program Listing II

```

086 *LBLC  CALCULATE ELLIPTIC COSINE
087 GSB3  calculate sn(u,k)
088 GT06  convert to cn(u,k) & output
089 *LBLD  CALCULATE ELLIPTIC DELTA
090 GSB3  calculate sn(u,k)
091 RCL2  form k*sn(u,k) and convert
092 X     to dn(u,k) then output
093 *LBL6
094 X²    routine to calculate:
095 CHS   (1 - (·)²)½
096 EEX
097 +
098 √X
099 GT09  goto output routine
100 *LBL E  CALCULATE ELLIPTIC AMPLITUDE
101 GSB3  calculate sn(u,k)
102 SIN⁻¹ convert to am(u,k)
103 *LBL9  output subroutine
104 F0?
105 PRTX  print and space if
106 F0?  flag 0 is set
107 SPC
108 RTN  return to main program
109 *LBL7  R/S lookup routine
110 R/S
111 GT07
112 *LBL e  PRINT - R/S TOGGLE
113 F0?  jump if flag 0 is set
114 GT08
115 SF0  set flag 0 and place a 1
116 EEX  in the display
117 GT07  goto R/S lookup routine
118 *LBL8
119 CF0  clear flag 0 and place a
120 CLX  0 in the display
121 RTN  return control to keyboard

```

Flag 0 should be set (cleared) prior to magnetic card recording depending whether the user normally wants the program in the print (R/S) mode.

LABELS					FLAGS	SET STATUS								
A	K(k)	B	sn(u, k)	C	cn(u, k)	D	dn(u, k)	E	am(u, k)	0	print	FLAGS	TRIG	DISP
a		b		c		d		e	print toggle	1		ON OFF		
												0	<input type="checkbox"/> <input type="checkbox"/>	
0	K(k) loop	1	sn loop	2	K(k)	3	sn(u, k)	4		2		1	DEG	FIX <input checked="" type="checkbox"/>
												2	GRAD	SCI
5		6	$\sqrt{1-x^2}$	7	R/s lock	8	print toggle	9	print or R/s	3		3	RAD <input checked="" type="checkbox"/>	ENG
														n <u>9</u>

PROGRAM 5-2 BESSEL FUNCTIONS AND FM OR PHASE MODULATION SPECTRA.

Program Description and Equations Used

This program will calculate the magnitude of the spectral lines arising from a frequency of phase sine-wave modulation process. In addition, the power in the higher sidebands is calculated which can be used to help define the bandwidths necessary for a communication channel carrying frequency division multiplexed data with either frequency modulation (FM), or phase modulation (PM) on the individual subcarriers. Phase modulation is often used to transmit digital data with preconditioning such as Manchester biphasic coding, or doublet modulation.

The spectra of both frequency modulated and phase modulated signals are the same when expressed as a function of the modulation index, m . The modulation index for the FM case is:

$$m_f = \frac{\text{peak carrier deviation from nominal frequency}}{\text{modulation frequency}}$$

Notice that the FM modulation index is modulation frequency dependent. The modulation index for the PM case is:

$$m_p = \begin{cases} \text{carrier phase shift in radians produced by the} \\ \text{modulating frequency.} \end{cases}$$

Also notice that the PM modulation index is modulation frequency independent.

The carrier and carrier sideband levels are described in terms of Bessel functions with the modulation index as the argument. The spacing of the sidebands is equal to the modulating frequency. For example, with a modulation index of 5 and a modulation frequency of 15 kHz, the FM or PM spectra is:

carrier amplitude	$J_0(5),$
first sideband pair	$J_1(5),$
second sideband pair	$J_2(5),$
⋮	
n-th sideband pair	$J_n(5).$

Figure 5-2.1 shows the above concept graphically.

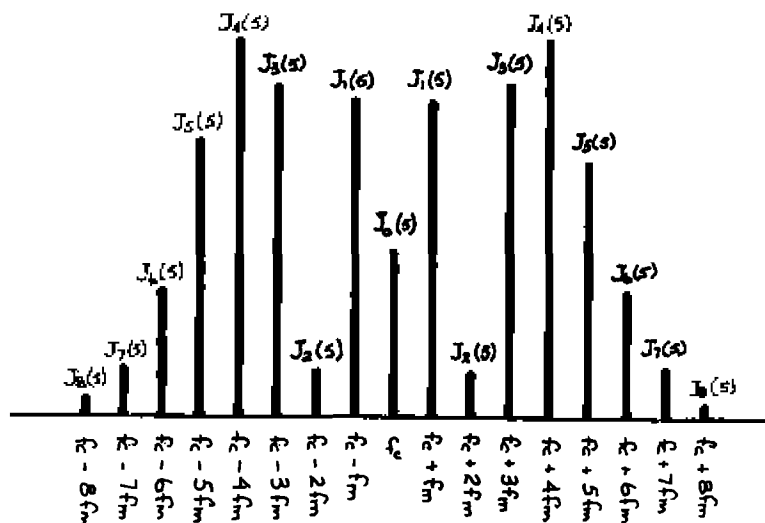


Figure 5-2.1 FM or PM modulation spectra.

A Bessel function identity allows the power remaining in the higher sidebands to be calculated. With FM or PM, all the sidebands carry modulation information in somewhat redundant form. If the higher order sidebands are removed by filtering, the modulation information can still be recovered, but the effective power will be reduced hence, the signal-to-noise ratio decreased; some distortion will also be introduced.

The Bessel function identity is:

$$J_0^2(m) + 2 \sum_{i=1}^{\infty} J_i^2(m) = 1 \quad (5-2.1)$$

The summation is broken into 2 parts and the equation rearranged:

$$\sum_{i=n+1}^{\infty} J_i^2(m) = \frac{1}{2}(1 - J_0^2(m)) - \sum_{i=1}^n J_i^2(m) \quad (5-2.2)$$

Therefore, if the magnitudes of the first n sidebands are known, then the power in the higher sidebands may be calculated since power is proportional to magnitude squared.

When the modulating signal contains 2 sinewaves of different frequencies and amplitudes superposition does not hold, since the resulting

spectra is represented by the products of the Bessel functions of the individual spectra. Let m_1 be the modulation index for modulation frequency f_1 , and likewise, m_2 for f_2 , then the combined modulation spectral components will be as shown in Table 5-2.1.

Table 5-2.1 Spectra for combined modulation

Spectral Component	frequency of component	amplitude of component
Carrier	f_c	$J_0(m_1) \cdot J_0(m_2)$
Simple sidebands of	$f_c \pm f_1$	$J_1(m_1) \cdot J_0(m_2)$
	$f_c \pm f_2$	$J_0(m_1) \cdot J_1(m_2)$
	$f_c \pm 2f_1$	$J_2(m_1) \cdot J_0(m_2)$
	$f_c \pm 2f_2$	$J_0(m_1) \cdot J_2(m_2)$
	\vdots	\vdots
Intermodulation	$f_c \pm f_1 \pm f_2$	$J_1(m_1) \cdot J_1(m_2)$
	$f_c \pm f_1 \pm 2f_2$	$J_1(m_1) \cdot J_2(m_2)$
	$f_c \pm 2f_1 \pm f_2$	$J_2(m_1) \cdot J_1(m_2)$
	\vdots	\vdots

The Bessel function of the first kind is easily evaluated using the summation of an infinite series; however, for values of m larger than 10, computational difficulties arise because of small differences between big numbers, i.e., using Eq. (5-2.3), Table 5-2.2 shows the individual terms for $n = 0$ and $m = 20$.

$$J_n(m) = \left(\frac{m}{2}\right)^n \sum_{i=0}^{\infty} \frac{\left(-\frac{m^2}{4}\right)^i}{i! \cdot (i+n)!} = \left(\frac{m}{2}\right)^n \sum_{i=0}^{\infty} T_j \quad (5-2.3)$$

Table 5-2.2

Infinite series terms.

1.000000000	T_0
-100.0000000	T_1
2500.000000	
-27777.77778	
173611.1111	
-694444.4444	T_5
1929012.346	
-3936759.889	
6151187.327	
-7594058.428	
7594058.428	T_{10}
-6276081.347	
4358389.823	
-2578928.890	
1315780.046	
-584791.1313	T_{15}
228434.0357	
-79042.91893	
24395.96263	
-6757.884387	
1689.471097	T_{20}
-383.1000219	
79.15289702	
-14.96274047	
2.597697998	
-0.415631680	T_{25}
0.061483976	
-0.008434016	
0.001075767	
-0.000127915	
0.000014213	T_{30}
-0.000001479	
0.000000144	
-0.000000013	
0.000000001	

The computed $J_0(20)$ by this method is 0.166021646. Because the range of the numbers exceed 10^{10} , the least significant figures have been lost. Even though the summation was carried out until $T_1 < 10^{-9}$, the answer is only accurate to 2 significant figures. The correct answer to $J_0(20)$ is 0.1670246646, which is computed by a slower, less direct method shown next.

Equation (5-2.4) is the recursion relationship for Bessel functions of the first kind.

$$J_n(m) = \frac{2}{m} (n-1) \cdot J_{n-1}(m) - J_{n-2}(m) \quad (5-2.4)$$

All Bessel functions approach zero as the order becomes large. This characteristic can be used to compute Bessel functions. If $T_{n+2}(m) = 0$ and $T_{n+1}(m) = 10^{-9}$, the recursion relationship can be run backwards to arrive at a result that is proportional to $J_0(m)$. Abramowitz and Stegun [1] has the relations for the minimum starting index

and the constant of proportionality for $J_0(m)$, i.e., given

$$T_i(m) = \frac{2}{m}(i+1) \cdot T_{i+1}(m) - T_{i+2}(m) \quad (5-2.5)$$

then, the minimum starting index is

$$i_{\min} = 2 \cdot \text{INT}\left(\frac{6 + \max(n, z) + (9z/(z+2))}{2}\right) \quad (5-2.6)$$

which for $n=0$ may be reduced to

$$i_{\min} = 2 \cdot \text{INT}\left(\frac{z^2 + 17 \cdot z + 12}{2(z+2)}\right) \quad (5-2.7)$$

where

$$z = 3m/2 \quad (5-2.8)$$

and "INT" means the integral part of the expression. The constant of proportionality is given by Eq. (5-2.9)

$$k = T_0(m) + 2 \sum_{j=1}^{\frac{i_{\min}}{2}} T_{2j}(m) \quad (5-2.9)$$

The first two Bessel functions are then:

$$J_0(m) = \frac{T_0(m)}{k} \quad (5-2.10)$$

$$J_1(m) = \frac{T_1(m)}{k} \quad (5-2.11)$$

With $J_0(m)$ and $J_1(m)$ and the recursion relationship given by Eq. (5-2.4), all the higher order Bessel functions may be evaluated.

User Instructions

BESSEL FUNCTIONS AND FM OR PM MODULATION SPECTRA		Output Format: 0 1 2 ... $J_0(m)$ $J_1(m)$ $J_2(m) \dots$ $(1-J_0^2)/2$ $10 \log \sum_{i=1}^{\infty} J_i^2$ $10 \log \sum_{i=1}^{\infty} J_i^2 \dots$
load m & start	print ?	

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of program card			
2	Select print/no-print (R/S) option		<div>B</div> <div>B</div> <div>B</div>	0 (R/S) 1 (print) 0 (R/S) :
3	Load modulation index and start	m	A	0 $J_0(m)$ $(1-J_0^2)/2$ 1 $J_1(m)$ $10 \log \sum_{i=1}^{\infty} J_i^2(m)$ 2 $J_2(m)$ $10 \log \sum_{i=1}^{\infty} J_i^2(m)$
	remaining power in higher sidebands in dB			
4	To stop analysis (print mode selected)		R/S	

Example 5-2.1

The 400 MHz carrier from a navigation satellite is phase modulated with a 400 Hz sinewave causing 60 degrees peak modulation. What is the modulation index, and what are the amplitudes of the PM sidebands?

The modulation index is the peak modulation expressed in radians:

$$m_p = 2\pi (60/360) = 1.0472 \text{ radians} \quad (5-2.12)$$

HP-97 PRINTOUT FOR EXAMPLE 5-2.1

```

66.  D=F
GSEA  load modulation index and start

      0. *** carrier
0.744072 *** J0(m)
0.225178 *** (1 - J02(m))/2

      1. *** first sideband, fc ± fm
0.455051 *** J1(m)
-11.4 *** relative power in higher sidebands in dB

      2. *** second sideband, fc ± 2fm
0.124972 *** J2(m)
-26.4 ***

      3. ***
0.022322 *** J3(m)
-44.0 ***

      4. ***
0.002964 *** J4(m)
-63.5 ***

      5. ***
0.000313 *** J5(m)
-84.5 ***

```

Notice that 99% of the power is contained in the carrier and the first two sidebands (-26.4 dB = 0.23% remaining power in higher sidebands).

Example 5-2.2

Calculate the sideband structure of a commercial FM station transmitting a 15 kHz signal with 75 kHz peak carrier deviation. The modulation index is:

$$m_f = 75000/15000 = 5 \quad (5-2.13)$$

HP-97 PRINTOUT FOR EXAMPLE 5-2.2

5. GSE- load m_f & start			
0.	***	carrier	
-0.177537	***	$J_0(m)$	
0.464230	***	$(1 - J_0^2(m))/2$	
1.	***	first sidebands	
-0.327579	***	$J_1(m)$	
-1.1	***	power (dB) outside	
2.	***	2nd sideband pair	
0.046565	***	$J_2(m)$	
-1.1	***		
3.	***		
0.364831	***	$J_3(m)$	
-3.0	***		
4.	***		
0.391232	***	$J_4(m)$	
-7.4	***		
5.	***		
0.261141	***	$J_5(m)$	
-13.8	***		
6.	***		
0.131049	***	$J_6(m)$	
-21.8	***		
7.	***		
0.053376	***	$J_7(m)$	
-31.2	***		
8.	***		
0.018405	***	$J_8(m)$	
-41.7	***		
9.	***		
0.005520	***	$J_9(m)$	
-53.3	***		
10.	***		
0.001468	***	$J_{10}(m)$	
-65.7	***		

Notice that one-half the power is contained in the first 3 sidebands and 99% of the power is contained in the first 6 sidebands.

The sideband structure for this example is shown in Fig. 5-2.1.

001	*LBLH	LOAD m AND START				043	*LBL0	calculate T_1 and T_0	
002	STOB	store m				044	GSB1		
003	F0?					045	ST+9	calculate and store $\sum T_{2j}$	
004	SPC	double space if flag 0 set				046	CF2		
005	F0?					047	GSB1	execute recursion formula	
006	SPC					048	F2?		
007	1					049	STO0	test for loop exit	
008	.	calculate minimum starting				050	CLX		
009	5	index plus two				051	STOI	initialize i	
010	x					052	GSB7	print i	
011	ENT↑					053	RCL5		
012	ENT↑					054	RCL9	calculate and print $J_0(m)$:	
013	ENT↑					055	ENT↑		
014	1					056	+		
015	7					057	RCL5	$J_0(m) = \frac{T_0(m)}{k}$	
016	+					058	-		
017	x					059	STO2		
018	2					060	÷		
019	÷	$i_{mn} = 2 \cdot \text{int} \left\{ \frac{Z^2 + 17Z + 12}{2(Z+2)} \right\}$				061	STOI		
020	6					062	GSB6		
021	+					063	X ²	calculate, store and print:	
022	X*Y					064	CHS	$\frac{1 - J_0^2}{2}$	
023	2					065	EEX		
024	+					066	+		
025	÷					067	2		
026	INT					068	÷		
027	ENT↑					069	STO5		
028	+					070	GSB9		
029	2					071	ISZ1	increment and print i	
030	+					072	GSB7		
031	STOI					073	RCLD	calculate, store, and print	
032	2					074	CHS	$J_1(m)$:	
033	RCL0					075	RCL2		
034	÷	calculate and store 2/m				076	÷	$J_1(m) = \frac{T_1(m)}{k}$	
035	STOB					077	STO2		
036	CLX					078	GSB6		
037	STOE	initialize T_{1+2} and $\sum T_{2j}(m)$				079	X ²	calculate and print power	
038	STO9					080	CHS	in higher sidebands	
039	EEX					081	STO6	using Eq. (5-2.2)	
040	CHS					082	RCL5		
041	9	initialize T_{1+1}				083	+		
042	STOD					084	GSB8		

REGISTERS																			
0	m	1	$J_0(m), J_{n-1}(m)$	2	$J_1(m), J_n(m)$	3		4		5	$(1 - J_0^2)/2$	6	$\sum_{i=1}^n J_i^2(m)$	7		8		9	$\sum T_{2j}(m)$
S0		S1		S2		S3		S4		S5		S6		S7		S8		S9	
A	n	B	2/m	C		D	T_i, T_{i+1}	E	T_{i+1}, T_{i+2}	I	i, n								

Program Listing II

085	*LBL2	loop to calc Bessel function
086	RCL1	J_{n-2}
087	CHS	
088	RCL2	J_{n-1}
089	ST01	
090	RCLB	$2/m$
091	X	
092	RCL1	$n-1$ $J_n(m) = \frac{2}{m}(n-1)J_{n-1}(m) - J_{n-2}(m)$
093	X	
094	+	
095	ST02	J_n
096	ISZ1	increment n
097	GSB7	
098	RCL2	
099	GSB6	recall and print $J_n(m)$
100	X ²	
101	ST-6	calculate and print power
102	RCL6	in higher sidebands
103	RCL5	
104	+	
105	GSB8	
106	GT02	
107	*LBL1	$T_i(m)$ recursion subroutine
108	DSZ1	
109	SF2	
110	RCLC	T_{i+2}
111	CHS	
112	RCL1	$i+1$
113	RCLB	$2/m$
114	X	
115	RCLD	T_{i+1} $T_i(m) = \frac{2}{m}(i-1)T_{i+1}(m) - T_{i+2}(m)$
116	ST0E	
117	X	
118	+	
119	ST0D	T_i
120	RTN	
121	*LBL6	print in dsp 6 subroutine
122	DSPE	
123	GT06	
124	*LBL7	print index in dsp 0 subr
125	DSP0	
126	PCL1	
127	*LBL6	
128	F0?	print and return if flag 0
129	PPTV	is set, otherwise stop
130	F0?	
131	RTN	
132	R/S	stop and await R/S command
133	RTN	

134	*LBL8	calculate & prt 10-log subr
135	RCL5	
136	=	
137	LOG	
138	EE ^x	
139	1	
140	A	
141	DSP1	set display format
142	RND	
143	*LBL9	
144	F0?	print and space if flag 0
145	PRT1	is set, otherwise stop
146	F0?	
147	SPC	
148	F0?	
149	RTN	
150	R/S	stop and await R/S
151	RTN	
152	GT04	program block
153	*LBL6	PRINT-R/S TOGGLE
154	F0?	
155	ST03	jump if flag 0 is set
156	SFP	set flag 0 and place
157	EE ^x	a one in the display
158	GT04	goto R/S lookup routine
159	*LBL3	
160	CF0	clear flag 0 and place a
161	CL ^y	zero in the display
162	*LBL4	R/S lookup routine
163	R/S	
164	GT04	

Notes:

Flag 0 should be set or reset prior to magnetic card recording to cause the program to initially be in the print or R/S mode respectively as users desire.

LABELS					FLAGS		SET STATUS		
A load m and start	B R/S - print toggle	C	D	E	0 print	FLAGS		TRIG	DISP
a	b	c	d	e	1	ON OFF			
0 Jo & J ₁ calc loop	1 Jo & J ₁ calc loop	2 output calc loop	3 R/S - print toggle	4 R/S lookup	2 loop exit	0 <input type="checkbox"/> <input type="checkbox"/>	DEG		FIX <input type="checkbox"/>
5	6 dsp 6, print	7 dsp 0, prt I	8 10log, dsp 1	9 print & space	3	1 <input type="checkbox"/> <input type="checkbox"/>	GRAD		SCI <input type="checkbox"/>
						2 <input type="checkbox"/> <input type="checkbox"/>	RAD		ENG <input type="checkbox"/>
						3 <input type="checkbox"/> <input type="checkbox"/>			n <u>0</u>

Note:

Flag 0 should be set or reset prior to magnetic card recording to cause the program to initially be in the print or R/S mode respectively as users desire.

PROGRAM 5-3 CURVE FITTING BY THE CUBIC SPLINE METHOD.

Program Description and Equations Used

This program will fit a cubic spline interpolating curve through 2 to 9 equally spaced points [31]. The cubic spline represents the shape of the curve that would be generated if a clock spring were threaded through the data points. This technique is often used by draftsmen to draw a smooth curve through given points. The shape of such a curve looks natural, and is generally the shape one would attempt to draw by hand.

Let the ordinates, y_i , be given at $x_i = x_1 + (i-1) \cdot h$, where $i = 1, 2, \dots, n$, and h is the point spacing. Furthermore, let $y(x)$ be the interpolating curve that is fitted to these points, and let y_i' and y_i'' represent the first and second derivatives of $y(x)$ evaluated at $x = x_i$. $y(x)$ may be represented piecewise where the function and its first and second derivatives are matched at the boundaries. The first and last segments of the interpolating curve may have their first and second derivatives specified by the user. The individual cubic interpolating polynomial $f_i(x)$ can be expressed in terms of the ordinates y_i and y_{i+1} , and either their first or second derivatives. Both forms will provide the same $y(x)$, but the second derivative form requires simpler calculations.

Assume the third derivative, $y'''(x)$, is constant in each interval, h . This assumption implies that $y''(x)$ is linear in x , i.e.,

$$f_i''(x) = y_i'' \left\{ 1 - \frac{x - x_i}{h} \right\} + y_{i+1}'' \left\{ \frac{x - x_i}{h} \right\} \quad (5-3.1)$$

Equation (5-3.1) is integrated twice with respect to x , and the constants of integration chosen so the boundary conditions are met to the extent that $f_i(x_i) = y_i$ ($i = 1, 2, \dots, n-1$), and $f_{i-1}(x_i) = y_i$ ($i = 2, 3, \dots, n$). The results of this integration yield:

$$\begin{aligned}
f_i(x) &= y_i(1 - (x-x_i)/h) + y_{i+1}(x-x_i)/h \\
&\quad - (h^2/6)(y_i'') \left[1 - (x-x_i)/h - (1 - (x-x_i)/h)^3 \right] \\
&\quad - (h^2/6)(y_{i+1}'') \left[(x-x_i)/h - ((x-x_i)/h)^3 \right] \quad (5-3.2)
\end{aligned}$$

Since the first and second derivatives of the function must also match at the boundaries, Eq. (5-3.2) is differentiated with respect to x and evaluated at x_i :

$$f_i'(x_i) = (y_{i+1} - y_i)/h - (h/6)(2y_i'' + y_{i-1}'') \quad (5-3.3)$$

and

$$f_{i-1}'(x_i) = (y_i - y_{i-1})/h + (h/6)(y_{i-1}'' + 2y_i'') \quad (5-3.4)$$

Equating Eqs. (5-3.3) and (5-3.4) implying boundary match yields:

$$h \cdot y_{i-1}'' = 4h \cdot y_i'' + h \cdot y_{i+1}'' = (6/h)(y_{i-1} - 2y_i + y_{i+1}) \quad (5-3.5)$$

where

$$i = 2, 3, \dots, n-1.$$

This equation set represents $n-2$ equations in n unknowns. If the starting and ending second derivatives are specified (y_1'' and y_n''), then the number of unknowns is reduced by 2, and a solution exists to the equation set. This equation set may be expressed in matrix notation:

$$\begin{bmatrix} 4 & 1 & 0 & 0 & \dots & 0 \\ 1 & 4 & 1 & 0 & \dots & 0 \\ 0 & 1 & 4 & 1 & 0 & \dots \\ \vdots & & & & \vdots & \\ 0 & \dots & 0 & 1 & 4 & 1 \\ 0 & 0 & \dots & 0 & 1 & 4 \end{bmatrix} \cdot \begin{bmatrix} y_2'' \\ y_3'' \\ \vdots \\ y_{n-2}'' \\ y_{n-1}'' \end{bmatrix} = \begin{bmatrix} (6/h^2)(y_1 - 2y_2 + y_3) - y_1'' \\ (6/h^2)(y_2 - 2y_3 + y_4) \\ (6/h^2)(y_3 - 2y_4 + y_5) \\ \vdots \\ (6/h^2)(y_{n-2} - 2y_{n-1} + y_n) - y_n'' \end{bmatrix} \quad (5-3.6)$$

Because of the tridiagonal characteristic of Eq. (5-3.6), a Gauss reduction is an effective method for finding the values of the various second derivatives. Let,

$$d_i = (6/h^2)(y_{i-1} - 2y_i + y_{i+1}) \quad (5-3.7)$$


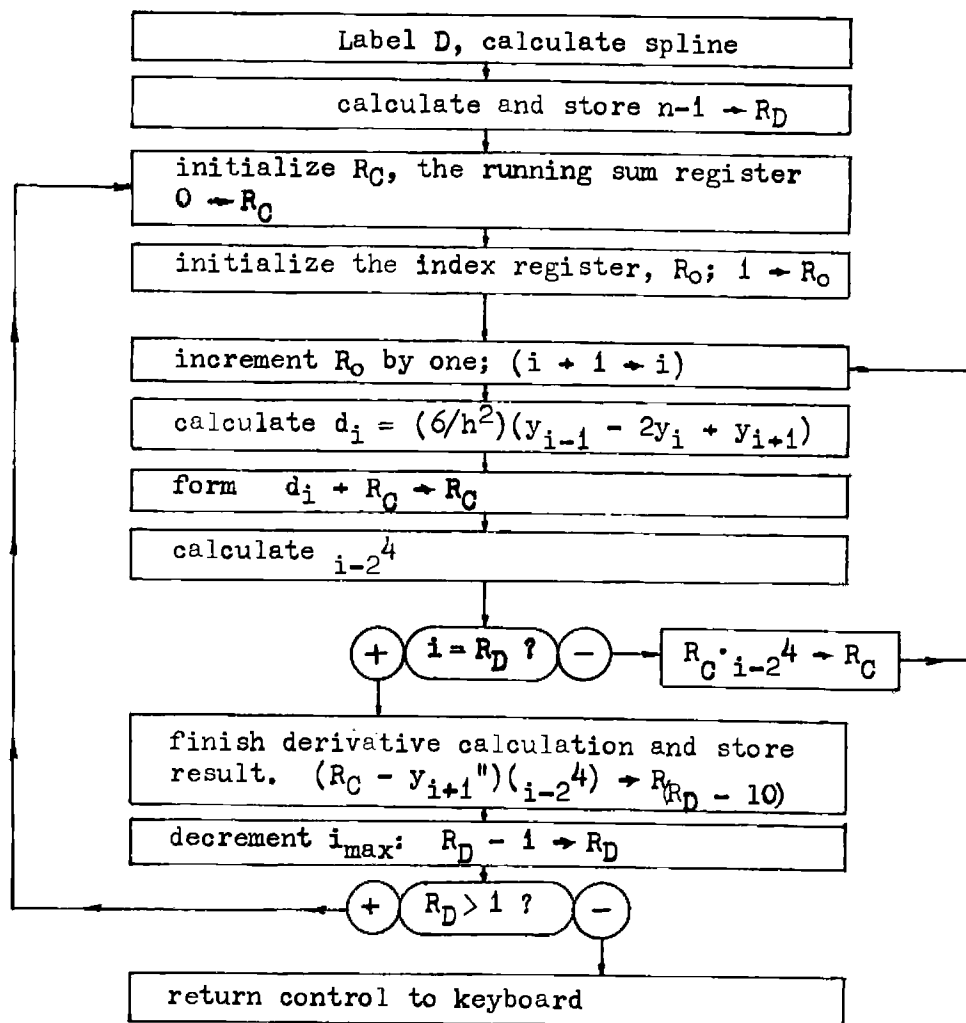


Figure 5-3.1 Flowchart of Gauss reduction algorithm.

User Instructions

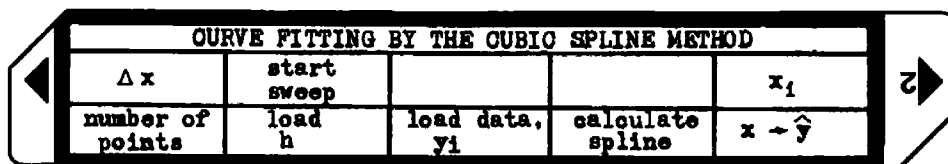

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of magnetic card			
2	Load the number of data points	n	<input type="text" value="A"/>	
3	Load h, the x interval	h	<input type="text" value="B"/>	
4	Load y data	y_1	<input type="text" value="C"/>	2
		y_2	<input type="text" value="C"/>	3
		\vdots		
		y_{n-1}	<input type="text" value="C"/>	n
		y_n	<input type="text" value="C"/>	
5	Calculate spline		<input type="text" value="D"/>	
6	Load first x point	x_1	<input type="text" value="F"/> <input type="text" value="E"/>	
7	Execute single point interpolation	x	<input type="text" value="E"/>	\hat{y}
	Step 7 may be used any number of times			
8	For linear sweep in x and corresponding interpolation of y:			
	a) Load sweep point spacing	Δx	<input type="text" value="F"/> <input type="text" value="A"/>	x_1
	b) Start sweep		<input type="text" value="F"/> <input type="text" value="B"/>	\hat{y}_1
				$x_1 + \Delta x$
				\hat{y}
				$x_1 + 2\Delta x$
				\hat{y}
				\vdots
				\vdots
				$x_1 + (n-1)\Delta x$
				\hat{y}

Example 5-3.1

Fit a cubic spline interpolating curve to the data given in Table 5-3.1. Provide the output sweep with x increments of 0.1.

Table 5-3.1 Data for cubic spline interpolation.

x	1	2	3	4	5	6	7	8	9
y	0	5	9	7	4	3	5	8	9

The HP-97 printer output is shown on the next page, and the interpolated output is plotted in Fig. 5-3.2. The bold points represent the given data.

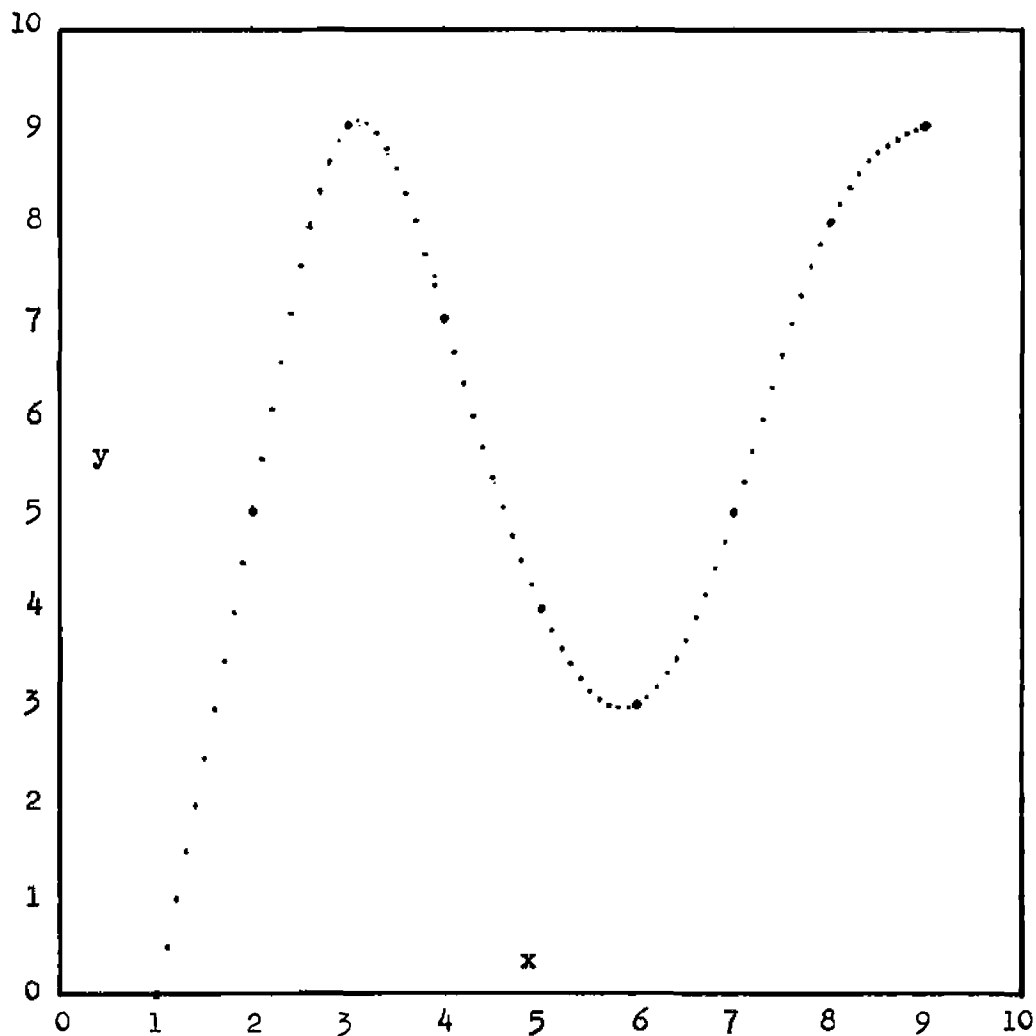


Figure 5-3.2 Cubic spline interpolation of given data.

HP-97 PRINTOUT FOR EXAMPLE 5-3.1

PROGRAM INPUT								
9.000	GSBA	load number of data points						
1.000	GSBE	load h, the x interval						
		load y data points						
0.000	GSBC	y ₁						
5.000	GSBC	y ₂						
9.000	GSBC	y ₃						
7.000	GSBC	y ₄						
4.000	GSBC	y ₅						
3.000	GSBC	y ₆						
5.000	GSBC	y ₇						
8.000	GSBC	y ₈						
9.000	GSBC	y ₉						
	GSBD	execute spline calculation						
1.000	GSBe	load x ₁ , the first x point						
.100	GSBa	load x interval for output sweep						
	GSBb	start sweep						
PROGRAM OUTPUT								
1.000	2.000	3.000	4.000	5.000	6.000	7.000	8.000	9.000
0.000	5.000	9.000	7.000	4.000	3.000	5.000	8.000	9.000
1.100	2.100	3.100	4.100	5.100	6.100	7.100	8.100	x
0.486	5.530	9.059	6.658	3.783	3.073	5.315	8.196	y
1.200	2.200	3.200	4.200	5.200	6.200	7.200	8.200	
0.974	6.058	9.035	6.320	3.587	3.180	5.639	8.361	
1.300	2.300	3.300	4.300	5.300	6.300	7.300	8.300	
1.463	6.574	8.938	5.990	3.415	3.318	5.968	8.500	
1.400	2.400	3.400	4.400	5.400	6.400	7.400	8.400	
1.954	7.067	8.776	5.667	3.267	3.487	6.297	8.615	
1.500	2.500	3.500	4.500	5.500	6.500	7.500	8.500	
2.449	7.529	8.560	5.354	3.147	3.683	6.621	8.710	
1.600	2.600	3.600	4.600	5.600	6.600	7.600	8.600	
2.947	7.948	8.300	5.053	3.054	3.905	6.935	8.788	
1.700	2.700	3.700	4.700	5.700	6.700	7.700	8.700	
3.451	8.315	8.004	4.766	2.992	4.149	7.235	8.853	
1.800	2.800	3.800	4.800	5.800	6.800	7.800	8.800	
3.961	8.619	7.682	4.493	2.961	4.415	7.515	8.907	
1.900	2.900	3.900	4.900	5.900	6.900	7.900	8.900	
4.477	8.851	7.344	4.237	2.963	4.699	7.772	8.955	

Program Listing I

001	*LBLA	LOAD # OF DATA POINTS	056	-	jump if i-2 is zero
002	STOA	store number of data points	057	X=0?	
003	EEX	set y_n to zero	058	GT02	
004	1		059	STOI	initialize I
005	+		060	4	
006	STOI		061	*LBL3	calculate $(i-2)^4$
007	CLX		062	1/X	
008	STOI		063	CHS	
009	EEX	initialize index register	064	4	
010	STOI		065	+	
011	RTN		066	DSZ1	
012	*LBLB	LOAD h, THE x POINT	067	GT03	
013	STOB	SEPARATION	068	GT04	
014	RTN		069	*LBL2	initialize $(i-2)^4$
015	*LBLC	LOAD y DATA	070	4	
016	STOI	store y data	071	*LBL4	store $i-2^4$
017	ISZI	increment storage index	072	1/X	
018	RCL1	recall index to display	073	STOE	
019	RTN	return control to keyboard	074	RCL0	
020	*LBLD	CALCULATE SPLINE	075	RCLD	test for loop exit
021	RCLA	calculate and store n-1	076	X=Y?	
022	EEX		077	GT02	
023	-		078	RCLC	
024	STOD		079	RCLC	$R_0 \cdot i-2^4 - R_0$
025	*LBL0	spline outer loop	080	x	
026	CLX	initialize running sum	081	STOC	
027	STOC		082	GT01	goto inner loop start
028	EEX	initialize index register	083	*LBL2	finish derivative calc
029	STOB		084	RCL0	calculate and store n+10
030	*LBL1	spline inner loop	085	1	as storage index for
031	EEX	increment and store index	086	1	derivative
032	ST+0		087	+	
033	RCL0		088	STOI	
034	EEX		089	RCLC	calculate and store
035	+		090	RCLi	second derivative, y_1''
036	STOI		091	-	
037	RCLi	calculate d_1	092	RCLC	
038	DSZ1		093	1	
039	RCLi		094	RCLD	
040	ENT+		095	EEX	$(R_c - y_{i+1}'')(i-2^4) \rightarrow R_{D+10}$
041	+		096	1	
042	-		097	+	
043	DSZ1		098	STOI	
044	RCLi		099	R1	
045	+	$d_i = \frac{6}{h^2} (y_{i-1} - 2y_i + y_{i+1})$	100	STOI	
046	6		101	EEX	decrement i_{\max}
047	x		102	RCLD	
048	RCLB		103	EEX	
049	X2		104	-	
050	÷		105	STOD	
051	RCLC		106	X>Y?	test for loop exit
052	-	$d_i - R_c \rightarrow R_c$	107	GT00	
053	STOC		108	SFC	
054	RCL0		109	GT08	
055	2				

REGISTERS									
0 Ax for sweep ≠ scratchpad	1 Y_1	2 Y_2	3 Y_3	4 Y_4	5 Y_5	6 Y_6	7 Y_7	8 Y_8	9 Y_9
S0 x_1	S1 current x for sweep	S2 Y_2'	S3 Y_3''	S4 Y_4''	S5 Y_5''	S6 Y_6''	S7 Y_7''	S8 Y_8''	S9 $Y_9'' = 0$
A n	B h	C scratchpad	D index	E scratchpad	F index				

LABELS					FLAGS	SET STATUS		
A load nbr of data points	B load h, the x interval	C load y data	D calculate spline	E $x \rightarrow \hat{y}$	0	FLAGS	TRIG	DISP
a load Δx for sweep	b start sweep	c	d	e load first x point	1	ON OFF	USERS CHOICE	
0 loop destination	1 loop destination	2 initialize i & scratch	3 calculate i	4 gives reduction	2	0	DEG	FIX
						1	GRAD	SCI
						2	RAD	ENG
5	6	7	8	9 loop destination	3	3		n

PROGRAM 5-4 LEAST SQUARES CURVE-FIT TO AN EXPONENTIAL FUNCTION.

Program Description and Equations Used

Many processes both in electrical engineering and in physics have behavior that can be described by an exponential law, e.g., the voltage across a capacitor being charged through a series resistor asymptotically approaches the charging voltage in an exponential manner. When time constants are to be determined from oscilloscope photographs of these phenomena, only part of the entire waveform is available, and some error is introduced transferring the photograph data into numbers. If these errors are random, then a least squares fit can help remove them.

The equation form for the exponential function is given by:

$$x = a(1 - e^{-bt}) \quad (5-4.1)$$

Let d_i represent the difference between the measured point, x_i , and the exponential curve as shown by Fig. 5-4.1 and Eq. (5-4.2).

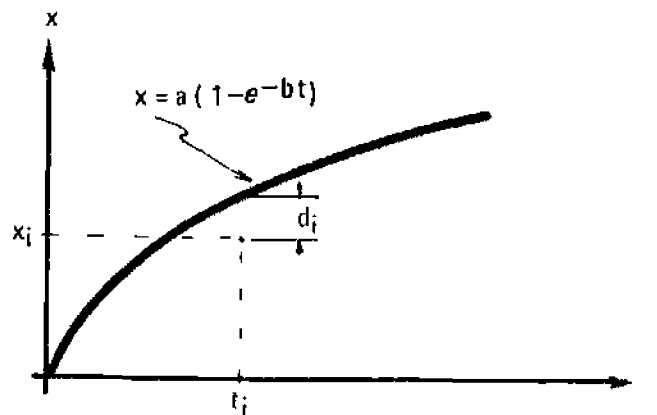


Figure 5-4.1 Exponential function.

$$d_i = x_i - a(1 - e^{-bt_i}) \quad (5-4.2)$$

The object of a least squares fit is to minimize the sum of the

squares of the deviations as implied by Eq. (5-4.3).

$$S = \sum_i d_i^2 = \sum_i (x_i - a(1 - e^{-bt_i}))^2 \quad (5-4.3)$$

The minimum can be found by setting the derivatives of Eq. (5-4.3) to zero, i.e.:

$$\frac{\partial S}{\partial a} = 0, \quad \frac{\partial S}{\partial b} = 0$$

or

$$\frac{\partial S}{\partial a} = -2 \sum_i \{x_i - a(1 - e^{-bt_i})\} \cdot (1 - e^{-bt_i}) = 0 \quad (5-4.4)$$

$$\frac{\partial S}{\partial b} = -2a \sum_i \{x_i - a(1 - e^{-bt_i})\} \cdot (t_i \cdot e^{-bt_i}) = 0 \quad (5-4.5)$$

Equations (5-4.4) and (5-4.5) represent 2 equations in 2 unknowns, a and b . Equation (5-4.4) is solved for a as shown in Eq. (5-4.6) and substituted into Eq. (5-4.5) to yield Eq. (5-4.7)

$$a = \frac{\sum_i x_i (1 - e^{-bt_i})}{\sum_i (1 - e^{-bt_i})^2} \quad (5-4.6)$$

$$g(b) \triangleq \sum_i x_i \cdot t_i e^{-bt_i} \sum_i (1 - e^{-bt_i})^2 - \sum_i x_i (1 - e^{-bt_i}) \sum_i t_i \cdot e^{-bt_i} (1 - e^{-bt_i}) = 0 \quad (5-4.7)$$

To simplify things, the various sums in Eq. (5-4.7) are assigned numbers in the same respective order as they appear.

$$g(b) = \Sigma_1 \Sigma_2 - \Sigma_3 \Sigma_4 = 0 \quad (5-4.8)$$

The object is to find b so $g(b) = 0$. Since Eq. (5-4.7) is nonlinear, an iterative solution is employed to find b . Wegstein's method [29] is used and is flowcharted in Fig. 5-4.2. This method is chosen because no derivatives are required and the convergence is very rapid.

Basically Wegstein's method is Esperti's method where one curve is a straight line (see Program 2-9 for Esperti's method). Equation (5-4.8) will have to be modified as Wegstein's method finds the solution to $f(b) = b$, therefore, let $f(b)$ be as shown in Eq. (5-4.9)

$$f(b) = \frac{\Sigma_3 \Sigma_4}{\Sigma_2} - \Sigma_1 + b \quad (5.4-9)$$

The reason for this form is to try and avoid the small difference between big numbers problem. It is advisable to keep b between 0.1 and 10 for best accuracy. If the data is on a microsecond time scale, enter the time as though it were in seconds and denormalize b after it has been calculated. Likewise for millisecond data.

After b has been found by iteration, a is obtained by using Eq. (5-4.6), which can be expressed in terms of the numbered sums:

$$a = \frac{\Sigma_3}{\Sigma_2} \quad (5.4-10)$$


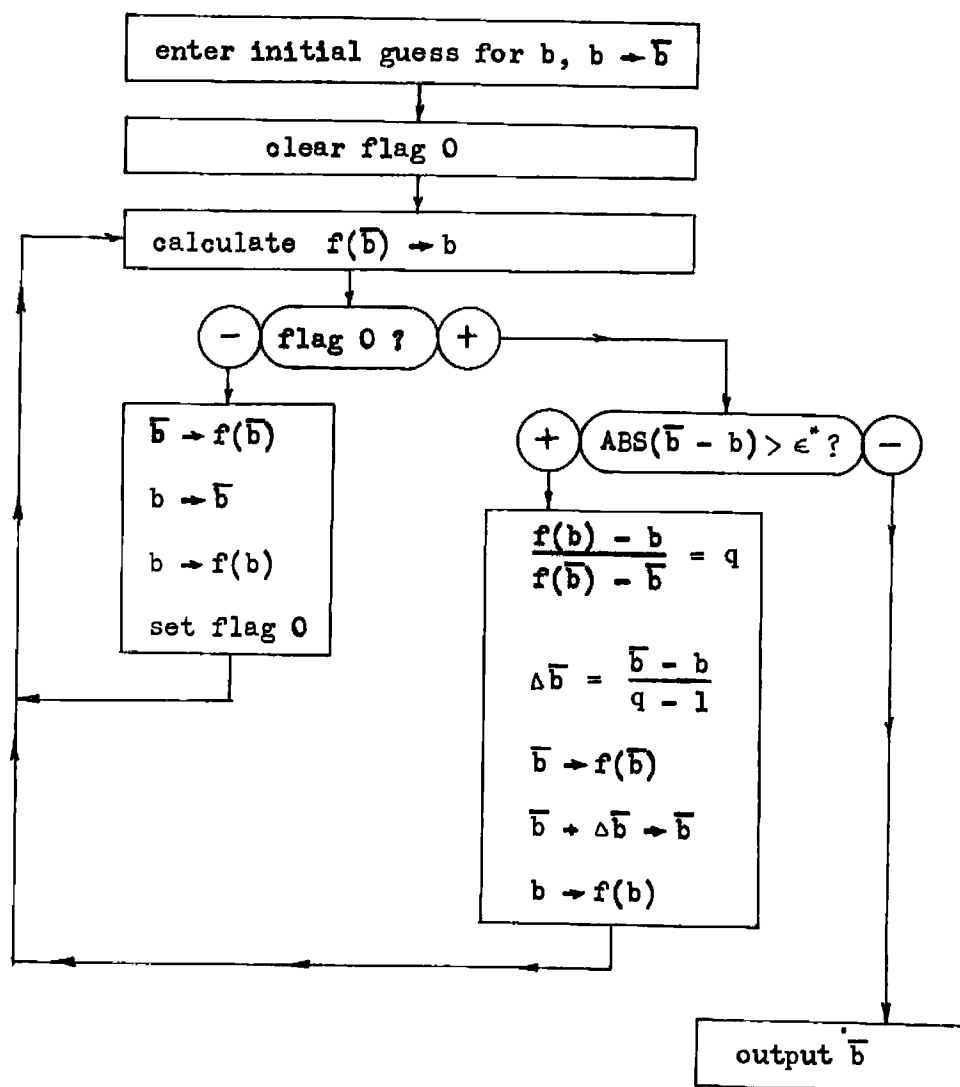


Figure 5-4.2 Flowchart for Wegstein's method.

* For this program, ϵ is chosen at $10^{-6} \cdot \bar{b}$

User Instructions

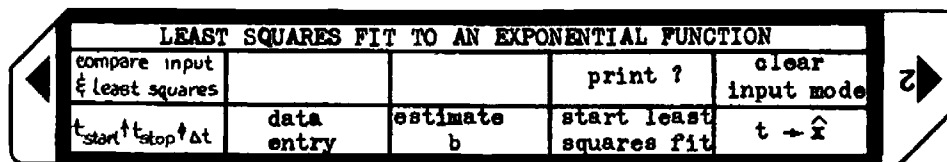

STEP	INSTRUCTIONS	INPUT DATA/UNITS	KEYS	OUTPUT DATA/UNITS
1	Load both sides of magnetic card			
2	Select print or R/S option (toggle)		<div>f</div> <div>D</div> <div>f</div> <div>D</div> <div>f</div> <div>D</div>	0 (R/S) 1 (print) 0 (R/S) : :
3	Load t_{start} , t_{stop} , and t a) time of first data point b) time of last data point c) data point spacing	t_{start} t_{stop} Δt	<div>ENT</div> <div>ENT</div> <div>A</div>	
4	Load data (10 points maximum) load x at t_{start} load x at $t_{start} + \Delta t$: : : load last data point	x_1 x_2 : : : x_n	<div>B</div> <div>B</div> <div>B</div> <div>B</div>	t_{start} $t_{start} + \Delta t$ $t_{start} + 2\Delta t$: t_{stop} $t_{stop} + \Delta t$
5	Load estimate for b ($0.1 \leq b \leq 10$) To examine the currently stored value for b, key "C" without numeric entry. The input mode can be cleared with keys "f", "E".	$b_{estimate}$	<div>C</div>	
6	To clear input mode (used with step 5)		<div>f</div> <div>E</div>	
7	Start least squared fit		<div>D</div>	a b space
8	Optional; compare input data with least squares fit data		<div>f</div> <div>A</div>	t_{start} x_1 \hat{x}_1 : :
9	Calculate linear estimate for x given t	t	<div>E</div>	\hat{x}

Example 5-4.1

A constant voltage was suddenly connected to the field of a large dc traction motor, and an oscilloscope photograph taken of the current. The field time constant is needed to determine loop stability in the overall motor control loop. Table 5-4.1 shows the field current as read from the oscilloscope photo as a function of time.

Table 5-4.1 Motor field current vs. time.

time, seconds	0.1	0.2	0.3	0.4	0.5	0.6	0.7
current, amps	10	18	26	33	39	45	50

Assuming the field to be a simple series LR circuit, find the time constant and the asymptotic field current.

HP-97 PRINTOUT FOR EXAMPLE 5-4.1

.100 ENT↑ load starting time	GSB _a compare input & least squares
.700 ENT↑ load stopping time	0.100 *** time
.100 GSB _A load time increment	10.000 *** I(t) input
	9.587 *** I(t) from least sqs
GSB _B setup for data entry	
10.000 GSB _B load I(.1)	0.200 ***
18.000 GSB _B load I(.2)	18.000 ***
26.000 GSB _B load I(.3)	18.211 ***
33.000 GSB _B load I(.4)	
39.000 GSB _B load I(.5)	0.300 ***
45.000 GSB _B load I(.6)	26.000 ***
50.000 GSB _B load I(.7)	25.971 ***
1.000 GSB _C load b estimate	0.400 ***
	33.000 ***
GSB _D start least sqrs fit	32.953 ***
95.569 *** a (asymptotic current)	0.500 ***
1.057 *** b (1/γ, time constant)	39.000 ***
	39.234 ***
γ = 1/1.057 = 0.9461 seconds	
	0.600 ***
	45.000 ***
	44.885 ***
	0.700 ***
	50.000 ***
	49.969 ***

Address	Instruction	Comment
001	*LBLA	LOAD t _{start} , t _{stop} , Δt
002	STOB	
003	R4	store entries
004	STOD	
005	R4	
006	STOC	
007	GTOb	goto OF3 and R/S lookup subr
008	*LBLC	LOAD b ESTIMATE
009	F3?	if numeric input, store data
010	STOB	
011	RCLB	recall b estimate to display
012	GTOb	goto R/S lookup subroutine
013	*LBLD	START LEAST SQUARES CALO
014	CF0	indicate first time thru loop
015	*LBL9	outer loop start
016	CLX	
017	STO1	initialize sums:
018	STO2	
019	STO3	0 → Σ ₁ → Σ ₂ → Σ ₃ → Σ ₄
020	STO4	
021	9	
022	STO1	initialize index
023	RCLC	
024	RCL0	initialize time register
025	-	
026	STO5	
027	*LBL0	summation loop start
028	ISZ1	increment index
029	RCL0	increment time
030	ST+5	
031	RCLD	
032	RCL5	
033	X>Y?	test for loop exit
034	GT03	
035	RCLB	
036	x	e ^{-bt_i}
037	CHS	
038	e*	
039	STO6	
040	CHS	1 - e ^{-bt_i}
041	EEX	
042	+	
043	STO7	
044	X²	Σ ₂ + (1 - e ^{-bt_i})² → Σ ₂
045	ST+2	
046	RCLi	
047	RCL5	
048	x	Σ ₁ + x _i · t _i · e ^{-bt_i} → Σ ₁
049	RCL6	
050	x	
051	ST+1	
052	RCLi	
053	RCL7	
054	x	Σ ₃ + x _i (1 - e ^{-bt_i}) → Σ ₃
055	ST+3	
056	RCL5	
057	RCL6	
058	x	Σ ₄ + t _i e ^{-bt_i} (1 - e ^{-bt_i}) → Σ ₄
059	RCL7	
060	x	
061	ST+4	
062	GTOb	goto summation loop start
063	*LBL3	start Wegstein solution
064	RCL3	
065	RCL4	
066	x	Σ ₃ · Σ ₄ - Σ ₁
067	RCL2	Σ ₂
068	=	
069	RCL1	
070	-	
071	F0?	jump if not first time
072	GT01	through loop
073	RCLB	b → f(b)
074	STOE	
075	+	
076	STO8	b → b̄ → f(b)
077	STO8	
078	STO9	
079	SF0	not first time thru loop
080	GT09	goto outer loop start
081	*LBL1	jump destination
082	RCLB	
083	+	f(b̄) → b
084	STO8	
085	RCLB	
086	-	
087	RCLB	ABS { (b̄ - b) / b̄ }
088	=	
089	ABS	
090	EEX	
091	CHS	
092	6	test for loop exit
093	X>Y?	
094	GT02	
095	RCL9	
096	RCL8	
097	-	
098	RCLB	q = (f(b) - b) / (f(b̄) - b̄)
099	RCLB	
100	-	
101	=	
102	STOA	
103	RCLB	b̄ → f(b̄)
104	STOE	
105	RCL8	
106	-	
107	RCLA	Δb̄ = (b̄ - b) / (q - 1)
108	EEX	
109	-	
110	=	

REGISTERS									
0 Δt	1 Σ ₁	2 Σ ₂	3 Σ ₃	4 Σ ₄	5 t _i	6 e ^{-bt_i}	7 1 - e ^{-bt_i}	8 b	9 f(b)
S0 x ₀	S1 x ₁	S2 x ₂	S3 x ₃	S4 x ₄	S5 x ₅	S6 x ₆	S7 x ₇	S8 x ₈	S9 x ₉
A a, q	B b̄	C t _{start}	D t _{stop}	E f(b̄)	F index				

Program Listing II

111 RCLB	$\bar{b} + \Delta \bar{b} \rightarrow \bar{b}$	163 *LBL5	print or R/S subroutine
112 +		164 F1?	
113 STOB		165 PRTX	print and return if
114 RCL8	$b \rightarrow f(b)$	166 F1?	flag 1 is set, otherwise
115 ST09		167 RTN	
116 GT09	goto outer loop start	168 R/S	stop and await R/S command
117 *LBL2	Wegstein output	169 RTN	
118 F1?	space if print mode set	170 *LBLB	LOAD DATA
119 SPC		171 9	initialize register index
120 RCL3		172 STOI	
121 RCL2	$a = \frac{\sum a}{\sum z}$	173 *LBLB	data storage loop start
122 =		174 1SZI	increment register index
123 ST0A		175 RCL1	
124 GSB5	gosub print or R/S subr	176 EEX	calculate time for x(t)
125 RCLB	recall b	177 1	
126 GT04	goto print and space subr	178 -	
127 *LBL6	COMPARE INPUT & LEAST SQRS	179 RCL0	
128 RCLC		180 x	
129 RCL0	setup time register	181 RCLC	
130 -	and index register	182 +	
131 ST01		183 R/S	display time & await entry
132 9		184 *LBLB	data storage
133 STOI		185 STOI	store data
134 *LBL7	loop start	186 GT08	goto loop start
135 1SZI	increment register index	187 *LBL6	CF3 and R/S lookup subr
136 RCL0	increment time index	188 CF?	clear flag 3
137 ST-		189 *LBL6	R/S lookup subroutine
138 RCL		190 RTN	
139 RCL5	test for loop exit	191 GT06	
140 X>Y?		192 *LBLd	PRINT OR R/S TOGGLE
141 GT06		193 CF1	clear flag 1 for R/S mode
142 GSB5	output time	194 CLX	and place a zero in display
143 RCL1	recall and output input	195 RTN	return control to keyboard
144 GSB5		196 *LBLd	toggle continued
145 R4	calculate and output	197 SF1	set flag 1 for print mode
146 GSB5	least squares estimate	198 EEX	and place a one in display
147 GT07	goto loop start	199 PTN	return control to keyboard
148 *LBL6	LEAST SQUARES ESTIMATE		
149 RCLB	calculate:		
150 x			
151 CHS			
152 e*			
153 CHS			
154 1	$\hat{x} = a(1 - e^{-bt})$		
155 +			
156 RCLA			
157 x			
158 *LBL4	print and space subroutine		
159 GSB5	gosub print or R/S subr		
160 F1?	space if print mode set		
161 SPC			
162 GT06	goto CF3 and R/S lookup subr		

Notes:

Flag one should be set or reset prior to magnetic card recording depending whether the user wishes the program to normally come up in print or R/S mode after the card read. Step 2 can be skipped in this instance.

LABELS					FLAGS	SET STATUS			
A load times	B load data	C load b estimate	D start least squares	E $t \rightarrow \hat{x}$	0 first time thru Wegstein	FLAGS		TRIG	DISP
a output summary	b	c	d print toggle	e clear flag 3	1 print	ON	OFF	USERS CHOICE DEG FIX GRAD SCI RAD ENG n_____	
0 form sums	1 Wegstein major loop	2 Wegstein output	3 Wegstein start	4 print	2	0	<input checked="" type="checkbox"/>		
5 print or R/S	6 R/S lock	7 summary loop	8 data input loop	9 outer least squares loop	3	1	<input type="checkbox"/>		
						2	<input type="checkbox"/>		

LIST OF ABBREVIATIONS

LIST OF ABBREVIATIONS

alternative or alternate	alt	destination	dest
amplifier	amp	diameter	diam
approximately	approx	display	dsp
arithmetic	arith	distance	dist
attenuation	atten	electrical	elect
		elements	elts
bandpass	BP	enter	ent
bandstop	BS	Equation(s)	Eq(s).
bandwidth	BW	equivalent	equiv
branch	br	evaluation	eval
Butterworth	Buttr	even part of (.)	Ev(.)
		execute	exec
calculation or calculate	calc		
capacitor	cap	feedback	fdbk
Chebyshev	Cheb	Figure	Fig.
circuit	ckt	format	fmt
clear	clr	frequency	freq
coaxial	coax	function	fcn
coefficient	coef		
complex	cmplx	go substitute	go sub
conductance	cond	go to	gto
conjugate	conj		
conversion	conv	henry	h
co-ordinates	co-ords	highpass	HP
decibel	dB	imaginary	imag
decibel ripple	dBR	increment	incr
denominator	den	initialize	init
denormalization	denorm	input/output	I/O
density	dens	integral	int

label	lbl	resistance	resist
level	lvl	return	rtn
linear	lin	review	revu
loop	lp	root sum square	RSS
lowpass	LP	root mean square	RMS
matrix	mat	secondary	sec
minimum	min	section	sect
multiplication	mult	solution	soln
negative	neg	space	spc
numerator	num	specification(s)	spec(s)
odd part of(.)	Odd(.)	square	sq
order	ord	starting frequency	f _{st}
		stopping frequency	f _{sp}
		store	sto
		subroutine	subr
page	pg, p	sweep	swp
parameters	params	temporary	temp
peak	pk	terminating, terminal, or termination	term
polynomial	poly	through	thru
preamplifier	preamp	toggle	tog
primary	pri	total	tot
print	prt	transform	xfm
program	pgm	transformer	xfmr
recall	rcl	transistor	xstr
rectangular	rect	transmitter	xmit
reflection	refl	transmission	xmsn
register(s)	reg(s)	trigonometric	trig
required	reqd		

BIBLIOGRAPHY

- 1 Abramowitz, M., and Stegun, I., Handbook of Mathematical Functions with Formulas, Graphs, and Mathematical Tables, AMS #55, Nat'l Bur. of Stds., Washington, D.C., 1972.
- 2 Amstutz, P., "Elliptic Approximation and Elliptic Filter Design on Small Computers," IEEE Trans. on Ckts. and Systems, vol CAS-25, Dec. 1978, pp. 1001-1011.
- 3 Antoniou, A., "Realization of Gytrators Using Operational Amplifiers and Their Use in RC Active Network Synthesis," Proc IRE (London), vol 116, Nov. 1969, pp. 1838-1850.
- 4 Bashkow, T.R., ch 26 in Mathematical Methods for Digital Computers, Eds. Ralston, A., and Wilf, H., Wiley, N.Y., 1960.
- 5 Belevitch, V., "Tchebycheff Filter and Amplifier Networks," Wireless Engineer, vol 29, April 1952, pp. 106-110.
- 6 Bell, W., Matrices for Scientists and Engineers, Van Nostrand Reinhold, N.Y., 1975.
- 7 Bennett, W.R., "Transmission Network," U.S. Pat 1,849,656, 15 March 1932.
- 8 Blinchikoff, H., and Zverev, A., Filtering in the Time and Frequency Domains, Wiley-Interscience, N.Y., 1976.
- 9 Bodway, G.E., "Circuit Design and Characterization of Transistors by Means of Three Port Scattering Parameters," Microwave Journal, vol 11, no. 15, May 1968.
- 10 Bruton, L., "Network Transfer Functions Using the Concept of Frequency Dependent Negative Resistance," IEEE Trans. on Ckt. Theory, vol CT-16, Aug. 1969, pp. 406-408.
- 11 Bunet, P., "On the Self Inductance of Circular Cylindrical Coils," Revúe General de l'Electricite, Tome xliii, no. 4, Jan. 1938, p. 99.
- 12 Byrd, P., and Friedman, M., Handbook of Elliptic Integrals for Engineers and Physicists, Springer-Verlag, N.Y., 1954.
- 13 Callendar, M., "Q of Solenoid Coils," Wireless Engineer, vol 24, June 1947, p. 185.

- 14 Carnahan, B., Luther, H., Wilkes, J., Applied Numerical Methods, Wiley, N.Y., 1969.
- 15 Carson, R.S., High Frequency Amplifiers, Wiley-Interscience, N.Y., 1975.
- 16 Cohn, S., "Direct Coupled Resonator Filters," Proc. IRE, vol 40, Feb. 1957, pp. 186-196.
- 17 Daniels, R., Approximation Methods for Electronic Filter Design, McGraw-Hill, N.Y., 1974.
- 18 Darlington, S., "Simple Algorithms for Elliptic Filters and a Generalization Thereof," session 3 of IEEE Int. Symp. on Ckts. and Systems Proc., May 1978, pp. 35-39.
- 19 Daryanani, G., Principles of Active Network Synthesis and Design, Wiley, N.Y., 1976.
- 20 Deliyannis, T., "High-Q Factor Circuit with Reduced Sensitivity," Electronic Letters, vol 4, Dec. 1968, p. 577.
- 21 Dishal, M., "Design of Dissipative Band-Pass Filters Producing Exact Amplitude-Frequency Characteristics," Proc IRE, vol 37, Sept. 1949, pp. 1050-1069.
- 22 Doyle, W., "Lossless Butterworth Ladder Networks Operating Between Arbitrary Resistances," J. Math. Phys., vol 37, no. 1, April 1958, pp. 29-37.
- 23 Fano, R.M., "Theoretical Limitations on the Broadband Matching of Arbitrary Impedances," J. Franklin Inst., vol 249, Jan. 1950, pp. 57-83, and vol 249, Feb. 1950, pp. 139-154.
- 24 Froehner, W.H., "Quick Amplifier Design with Scattering Parameters," Electronics Magazine, 16 Oct. 1967.
- 25 Fortescue, Standard Handbook for Electrical Engineers, McGraw-Hill, N.Y., 1922 5th ed., p. 413.
- 26 Geffe, P.R., Designers Guide to Active Filters, Cahners Pub. Co., Boston, MA., 1974.
- 27 Geffe, P.R., "Microcomputer-Aided Filter Design," IEEE Ckts. and Systems Magazine, vol 1, no. 1, Jan. 1979, pp. 5-8.
- 28 Green, E., Amplitude-Frequency Characteristics of Ladder Networks, Marconi's Wireless Telegraph Co. Ltd., Essex, England, 1954.
- 29 Grove, W.E., Brief Numerical Methods, Prentice-Hall, Englewood Cliffs, N.J., 1966.
- 30 Grover, F.W., Inductance Calculations, Working Formulas and Tables, D. Van Nostrand, N.Y., 1946.

- 31 Hamming, R., Numerical Methods for Scientists and Engineers, second edition, McGraw-Hill, N.Y., 1973.
- 32 Hewlett-Packard Application note #95, "S parameters Circuit Analysis and Design," Hewlett-Packard Co., Sept. 1968.
- 33 Hewlett-Packard Journal, "S Parameters for Faster, More Accurate Network Design," vol 18, no. 6, Feb. 1967, p. 3-7.
- 34 Kawakami, M., "Nomographs for Butterworth and Chebyshev Filters," IEEE Trans. on Ckt. Theory, vol CT-10, June 1963, pp. 288-289.
- 35 Kerwin, W., and Heulsman, L., "Design of High Performance Active RC Band Pass Filters," 1966 IEEE Int. Conv. Rec., vol 14, part 10, pp. 74-80.
- 36 Lee, R., Electronic Transformers and Circuits, second ed., Wiley, N.Y., 1961.
- 37 Matthaei, G., "Synthesis of Tchebycheff Impedance-Matching Networks, Filters, and Interstages," IRE Trans. on Ckt. Theory, vol CT-3, Sept. 1956, pp. 163-172.
- 38 Moschytz, G., "Second-Order Pole-Zero Selection for n-th Order Minimum Sensitivity Networks," IEEE Trans. on Ckt. Theory, vol CT-17, Nov. 1970, pp. 527-534.
- 39 Norton, E.L., "Constant Resistance Networks with Applications to Filter Groups," BSTJ, vol 16, April 1937, pp. 178-193.
- 40 Orchard, H.J., "Formulae for Ladder Filters," Wireless Engineer, vol 30, Jan. 1953, pp. 3-5.
- 41 Orchard, H.J., "Computation of Elliptic Functions of Rational Fractions of a Quarter period," IRE Trans. on Ckt. Theory, vol CT-5, Dec. 1958, pp. 352-355.
- 42 Orchard, H.J., and Sheahan, D.F., "Inductorless Bandpass Filters," IEEE Jour. of Solid State Ckts., vol SC-5, June 1970, pp. 108-118.
- 43 Potter, J., and Fich, S., Theory of Networks and Lines, Prentice-Hall, Englewood Cliffs, N.J., 1963.
- 44 Reference Data for Electrical Engineers, Fourth Ed., ITT Corp., New York, N.Y., 1959.
- 45 Saal, R., and Ulbrich, E., "On the Design of Filters by Synthesis," IRE Trans. on Ckt. Theory, vol CT-5, Dec. 1958, pp. 284-327.
- 46 Skwirzynski, J., and Zdunek, J., "Note on Calculation of Ladder Coefficients for Symmetrical and Inverse Impedance Filters on a Digital Computer," IRE Trans. on Ckt. Theory, vol CT-5, Dec. 1958, pp. 328-332.

- 47 Still, A.F., Elements of Electrical Design, McGraw-Hill, N.Y., 1932.
- 48 Szentirmai, G., "Synthesis of Multiple Feedback Active Filters," BSTJ, vol 52, April 1973, pp. 527-555.
- 49 Temes, G., and La Patra, J., Circuit Synthesis and Design, McGraw-Hill, N.Y., 1977.
- 50 Temes, G., and Mitra, S., Eds., Modern Filter Theory and Design, Wiley-Interscience, N.Y., 1973.
- 51 Takahasi, H., "On the Ladder-Type Filter Network with Tchebycheff Response," J. Inst. Elec. Commun. Engrs., Japan, vol 34, Feb 1951, (In Japanese).
- 52 Terman, F.E., Radio Engineers Handbook, McGraw-Hill, N.Y., 1943.
- 53 Weinberg, L., Network Analysis and Synthesis, McGraw-Hill, N.Y., 1962.
- 54 Weinberg, L., and Slepian, P., "Takahasi's Results on Techbycheff and Butterworth Ladder Networks," IRE Trans. on Ckt. Theory, vol CT-7, June 1960, pp. 88-101.
- 55 Wheeler, H.A., "Simple Inductance Formulas for Radio Coils," Proc IRE, vol 16, no. 10, Oct 1928, p. 1398 and subsequent discussion in vol 17, no. 3, March 1929, p. 580.
- 56 White, D.R.J., A Handbook on Electrical Filters, Don White Consultants, Gainesville, VA., 1963.
- 57 Yengst, W.C., Procedures of Modern Network Synthesis, Macmillan, N.Y., 1964.
- 58 Zverev, A.I., Handbook of Filter Synthesis, Wiley, N.Y., 1967.

INDEX

INDEX

- Abramowitz, M., 290, 332, 276, 478, 484
- Active filters, 41-84, 233-280
- Air gap, 337, 391, 400
- Amstutz, P., 293
- Analysis:
- active networks, 41-84, 268-269
 - LC filters, 97-108
 - LRC filters, 75-96
- Antoniou, A., 202
- Approximation:
- Butterworth, 129-140
 - Chebyshev, 129-140
 - elliptic, 281-296
 - narrowband, 185-216
 - maximally flat *see* Butterworth
- AWG of wire, 347, 375
- Balanced structure, 178, 180
- Ball, J., 3
- Bandpass transformations, 165-166, 185-216, 299
- Bandstop transformations, 166-168, 299
- Bartlett's bisection theorem, 101
- Bashkow, T.R., 87
- Belevitch, V., 154
- Bell, W.W., 455
- Bennett, W.R., 154
- Bessel functions, 476, 481
- Bilateral:
- amplifier design, 427
 - network, 163, 185, 199, 217, 233
- Biquad circuits, 235
- Bodway, G., 435
- Bruton, L., 156
- Bunet, P., 383
- Butterworth approximation, 129-130, 134, 136-137, 146, 155, 233, 245-246
- Byrd, P., 292, 476
- Callendar, M., 375
- Capacitance of transformers, 353
- Carnahan, B., 455
- Carson, R.S., 428
- Cascade synthesis, 235
- Characteristic function, 287, 309
- Chebyshev rational function:
- definition, 287-289
 - relation to elliptic functions, 293-294
- Closed loop gain, 255
- Coaxial cable *see* Transmission Line
- Coefficient matching technique, 256-256
- Coefficient sensitivity, *see* Sensitivity
- Cohn, S., 171, 185, 199
- Cubic spline, 491-493

- Daniels, R., 281, 287, 291, 297
 Darlington, S., 293, 325
 Daryanani, G., 254, 255, 272
 Delay (of Butterworth and Chebyshev filters), 141-152
 Decomposition into second order function, 235, 267
 Deliyannis, T., 235, 267
 Dishal, M., 171, 185
 Doyle, W., 22
 Elliptic filter:
 attenuation, 297-299
 characteristic function, 326
 degree, calculation of, 283, 293
 examples, 303, 304, 313, 314
 loss function, 298
 natural modes, 309-311, 326
 transformation to produce loss pole at infinity, 283-284
 Elliptic functions:
 sine (sn), 292, 476
 cosine (cn), 476
 delta (an), 476
 amplitude (am), 476
 Elliptic integrals, 292, 475
 Equiripple filters, 309-324
 Esperti's method, 237-238
 Even part (Ev), 318
 Fano, R.M., 121
 Feedback factor, 267
 Feldtkeller equation, 287, 309
 Ferromagnetic cores, 337
 Fich, S., 36
 Fortescue, 253
 Fourier series for elliptic sine, 292
 Frequency normalization, 163-164
 Frequency-dependent-negative-resistance (FDNR), 156
 Friedman, M., 292, 476
 Froehner, W.H., 428
 Gain-bandwidth of op-amps, 267
 Gain, open loop, 49-54, 268, 271, 272
 Gain-bandwidth product, 272
 Gain sensitivity, 271
 Geffe, P.R., 272, 293
 Green, E., 154
 Grove, W.E., *see* Wegstein's method
 Grover, F.W., 365
 Gyrator, Antoniou, 202
 Hamming, R.W., 3, 491
 Heulsman, L., 235
 Highpass transformation 142-143, 164-165
 h parameters, 447
 Inductance:
 leakage, 353
 of aircore coils, 373, 383
 of solenoids, 395
 of straight wires, 366
 of wire loops, 367
 open circuit, 338
 quality factor (Q), 375
 Inductors:
 active, 202-203
 passive, 337-352

- Input bias current, 260
- Input noise, 109
- Input offset voltage, 260

- Jacobian elliptic functions, 475
- Johnson noise, 109

- Kawakami, M., 129, 133, 134
- Kerwin, W., 235

- Ladder networks, 41, 76, 80, 83, 101, 103, 109
- Landen, descending transformation, 292, 476, 479,
- LaPatra, J., 235
- Least squares fit, 501-503
- Low-pass approximation, *see* Approximation
- Loss function, 297-299
- Luther, H.A., 455

- Magnetic path, 337
- Magnetic saturation, 344
- Matrix algebra, 447-471
- Matthaei, G., 121
- Möbius transformation, 283-284, 299
- Modular elliptic function, 292
- Moschytz, G., 309

- Natural modes:
 - of Butterworth filters, 146
 - of Chebyshev filters, 148
 - of elliptic filters, 328
 - of equiripple filters, 309-312
 - of maximally flat filters, 146
- Negative feedback biquad, 267
- Network, two port, 447
- Newton's method (Newton-Raphson iteration), 57
- Nodal analysis, 56, 258
- Normalized lowpass filter, 153-162
- Norton, E., 154, 211

- Offset voltage, 260
- Open loop gain, 41, 45, 50, 51, 52, 54, 55, 268, 276
- Orchard, H.J., 154, 202, 293
- Ordering of biquads, 244
- Oscillator (design with s parameters), 433

- Passband:
 - bandpass filter, 131
 - bandstop filter, 167
 - highpass filter, 142-143, 253
 - lowpass filter, 147-148
- Passive networks:
 - analysis, 75-108
 - LC filter, 153-216
 - transformation, 217-232
 - transmission lines, 13-40
- Permeability, 337
- Phase delay, 142
- Pole frequency, ω_n , definition, 234
- Pole Q, definition, 234
- Poles, complex conjugate, 234
- Positive feedback biquads *see* Sallen and Key
- Potter, J.I., 36
- Power dissipated in coil, 395

- Q enhancement, 270
- Q factor of inductors, 375
- Quadrangle symmetry, 316

