
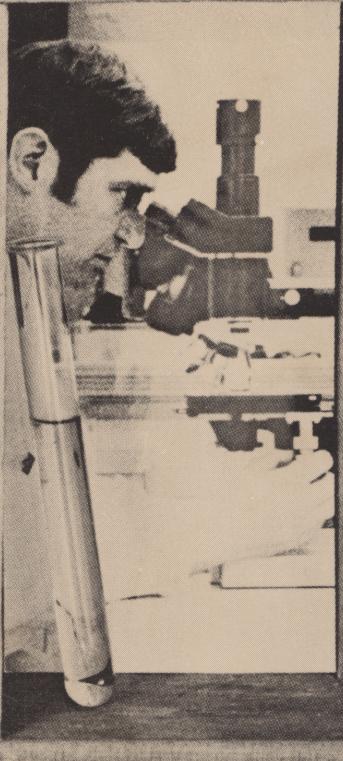


Hewlett-Packard HP-19C/HP-29C SOLUTIONS

ELECTRICAL ENGINEERING

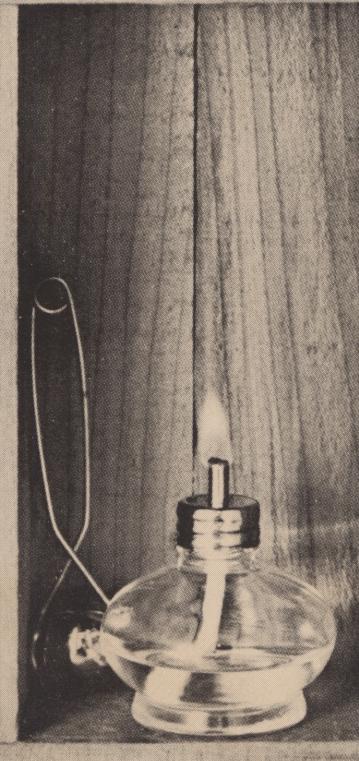

INTRODUCTION

This HP-19C/HP-29C Solutions book was written to help you get the most from your calculator. The programs were chosen to provide useful calculations for many of the common problems encountered.

They will provide you with immediate capabilities in your everyday calculations and you will find them useful as guides to programming techniques for writing your own customized software. The comments on each program listing describe the approach used to reach the solution and help you follow the programmer's logic as you become an expert on your HP calculator.

You will find general information on how to key in and run programs under "A Word about Program Usage" in the Applications book you received with your calculator.

We hope that this Solutions book will be a valuable tool in your work and would appreciate your comments about it.

The program material contained herein is supplied without representation or warranty of any kind. Hewlett-Packard Company therefore assumes no responsibility and shall have no liability, consequential or otherwise, of any kind arising from the use of this program material or any part thereof.

TABLE OF CONTENTS

RESISTIVE/REACTIVE CIRCUIT CALCULATIONS	1
Performs resonance calculations.	
IMPEDANCE OF LADDER NETWORK	5
Computes input impedance of arbitrary ladder network.	
T-ATTENUATOR	8
Computes resistor values for a T-attenuator having specified loss.	
PI-ATTENUATOR	11
Computes resistor values for a PI-attenuator having specified loss.	
WYE-DELTA OR DELTA-WYE TRANSFORMATION	14
Transforms from one topology to the other.	
PI NETWORK IMPEDANCE MATCHING	17
Computes a lossless matching network.	
ACTIVE FILTER DESIGN	20
Computes element values for low-pass and high-pass active filters.	
BUTTERWORTH FILTER DESIGN	24
Computes element values for passive low-pass Butterworth filters between equal terminations.	
STANDARD RESISTANCE VALUES	27
Computes nearest standard value.	
SMITH CHART CONVERSIONS	30
Converts among various radially scaled parameters and also converts between impedance and reflection coefficient.	

RESISTIVE/REACTIVE CIRCUIT CALCULATIONS

This program performs resonance calculations for R-L-C circuits, calculates the reactance of inductive and capacitive branches, the equivalent value of series capacitors or parallel resistors and inductors, and performs power calculations for resistive branches using straightforward manipulations of the following equations:

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$X_C = \frac{1}{2\pi f C}$$

$$X_L = 2\pi f L$$

$$P = I^2 R = E^2 / R$$

$$\frac{A_1 A_2}{A_1 + A_2} = A_3$$

where

f_r = resonant frequency in hertz

L = inductance in henrys

C = capacitance in farads

X_C = capacitive reactance in Ω

X_L = inductive reactance in Ω

P = power in watts

I = current in amps

R = resistance in Ω

E = voltage in volts

A_1, A_2 = the values of two parallel resistors in ohms, two parallel inductors in henrys, or two series capacitors in farads

A_3 = the resultant, equivalent resistance in ohms, inductance in henrys, or capacitance in farads

NOTE: Given a resistance or capacitance, A_1 , the value of the circuit element required to produce a desired resultant resistance or capacitance may be calculated by entering A_1 as a negative value.

EXAMPLES:

1. $C = .01\mu F$, $L = 160\mu H$.
Calculate f_r

2. $L = 2.5h$, $f_r = 60H_z$
Calculate C and X_L at f_r

3. $E = 345v$, $R = 1.25M\Omega$
Calculate P and I

4. $R_1 = 120\Omega$, $R_2 = 240\Omega$
- Find the equivalent resistance of these two resistors in parallel, R_3 .
 - Parallel R_3 with 50Ω .
 - Find the resistance required for a resultant resistance of 25Ω .

SOLUTION:

1E0.-0€ ENT1
0.01-0€ GSE1
125.82+03 *** f_r

60.0000 ENT1
2.5000 GSE2
2.8145-06 *** C

60.0000 ENT1
2.5000 GSE4
942.46+00 *** X_L

345.0000 ENT1
1.25+06 GSE5
95.226-03 *** P

1.25+06 GSE7
276.00-06 *** I

120.0000 ENT1
240.0000 GSE9
80.000+00 *** R₃

50.0000 GSE9
30.769+00 *** 4b
CH3
25.0000 GSE9
133.33+00 *** 4c

User Instructions

Program Listings

<pre> 31 #LBL1 32 X 33 4X 34 GT02 35 *LBL2 36 X#Y 37 GSBB 38 X# 39 X#Y 40 + 41 R/S 42 *LBL2 43 X 44 GT06 45 *LBL4 46 X 47 GSBB 48 1/X 49 R/S 50 *LBL5 51 1/X 52 *LBL6 53 X#Y 54 X# 55 X 56 R/S 57 *LBL7 58 1/X 59 *LBL8 60 X 61 4X 62 R/S 63 *LBL8 64 2 65 X 66 PI 67 X 68 1/X 69 RTN 70 *LBL9 71 X 72 ENT1 73 ENT1 74 LSTX 75 + 76 LSTX 77 + 78 + 79 R/S </pre>	<p>L or C</p> <p>x_L</p> <p>P</p> <p>I or E</p> <p>f_r or x_C</p> <p>A_3 or A_2</p>		<p>*** "Printx" may be inserted or used to replace "R/S".</p>
--	--	--	---

REGISTERS

0	1	2	3	4	5
6	7	8	9	.0	.1
.2	.3	.4	.5	16	17
18	19	20	21	22	23
24	25	26	27	28	29

IMPEDANCE OF A LADDER NETWORK

This program computes the input impedance of an arbitrary ladder network. Elements are added one at a time starting from the right. The first element must be in parallel.

Suppose we have a network whose input admittance is Y_{in} . Adding a shunt R , L , or C , the input admittance becomes

$$Y_{new} = \begin{cases} Y_{in} + \left(\frac{1}{R} + j0 \right) \\ Y_{in} + \left(0 - j \frac{1}{\omega L_p} \right) \\ Y_{in} + \left(0 + j \omega C_p \right) \end{cases}$$

Adding a series R , L , or C , we have


$$Y_{new} = \begin{cases} \left(\frac{1}{Y_{in}} + (R_s + j0) \right)^{-1} \\ \left(\frac{1}{Y_{in}} + (0 + j \omega L_s) \right)^{-1} \\ \left(\frac{1}{Y_{in}} + \left(0 - j \frac{1}{\omega C_s} \right) \right)^{-1} \end{cases}$$

The program converts this admittance to an impedance for display.

NOTE: An erroneous entry may be corrected by entering the negative of the incorrect value.

EXAMPLE:

$$f = 4 \text{ MHz}$$

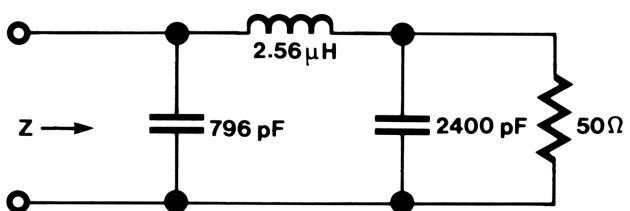

SOLUTION:

```

FIX2
4.+0E 0SB1
50.00 0SB2 |Zin|
50.00 *** XZY
0.00 *** /Zin
2400.-12 GSB5
15.74 *** |Zin|
XZY
-71.66 *** /Zin
2.56-06 GSB2
GSB5
49.65 *** |Zin|
XZY
84.28 *** /Zin
796.-12 GSB5
497.69 *** |Zin|
XZY
8.98 *** /Zin

```

User Instructions

Program Listings

7


01 *LBL1	f	58 GSB0	Convert Y _{in} →Z _{in}
02 2		51 R↓	
03 Y		52 RCL6	
04 PI		53 +	Add admittances
05 X	Clear flag	54 X#Y	or impedances
06 CLRG	W	55 RCL7	
07 ST03		56 +	
08 R/S		57 X#Y	
09 *LBL0	Z↔Y	58 RCL8	
10 R↓		59 X#0?	
11 +P		60 GSB0	
12 1/X		61 R↓	Convert Z→Y
13 X#Y		62 ST01	
14 CHS		63 X#Y	
15 X#Y		64 ST02	
16 +R		65 X#Y	
17 0		66 0	
18 RTN	R,C,L	57 GSB0	Convert Y→Z
19 *LBL2	Set flag (series)	68 ST08	Clear flag
20 ST08		69 R↓	
21 R/S		70 +P	
22 *LBL3		71 R/S	*** Z _{in} / Z _{in}
23 1/X			
24 RCL0			
25 X=0?			
26 GT08	0,Y (parallel)		
27 0			
28 GT08			
29 *LBL4	0,Z (series)		
30 RCL3			
31 X			
32 1/X	X _C or B _L		
33 CHS			
34 0			
35 X#Y			
36 GT08			
37 *LBL5			
38 RCL3			
39 X	X _L or B _C		
40 0			
41 X#Y			
42 *LBL8			*** "Printx" may be inserted.
43 ST07			
44 X#Y			
45 ST06			
46 RCL2			
47 RCL1			
48 RCL0			
49 X#0?			

REGISTERS

0 flag	1 Re[Y _{in}]	2 Im[Y _{in}]	3 ω=2πf	4	5
6 used	7 used	8	9	.0	.1
.2	.3	.4	.5	16	17
18	19	20	21	22	23
24	25	26	27	28	29

T ATTENUATOR

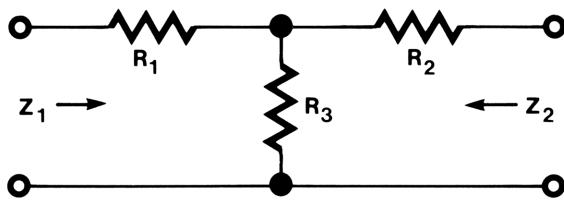The T attenuator can be used to match between two impedances, Z_1 and Z_2 . This program computes the minimum loss of the attenuator and values for the resistors R_1 , R_2 , and R_3 which will yield an attenuator having any desired loss.



The minimum loss in decibels is given by

$$\text{Min Loss} = 10 \log \left(\sqrt{\frac{Z_1}{Z_2}} + \sqrt{\frac{Z_1}{Z_2} - 1} \right)^2$$

where

$$Z_1 \geq Z_2$$

If N is the desired loss of the attenuator expressed as a ratio (loss in dB = $10 \log N$), then

$$R_3 = \frac{2 \sqrt{N Z_1 Z_2}}{N - 1}$$

$$R_1 = Z_1 \left(\frac{N + 1}{N - 1} \right) - R_3$$

$$R_2 = Z_2 \left(\frac{N + 1}{N - 1} \right) - R_3$$

EXAMPLE:

$$Z_1 = 75\Omega$$

$$Z_2 = 50\Omega$$

$$\text{Loss} = 6 \text{ dB}$$

SOLUTION:

75.0000	ENT1	
50.0000	G951	
6.0000	G952	
5.7195+00	***	Min Loss
R18		
43.344+00	***	R1
R12		
1.5715+00	***	R2
R15		
81.973+00	***	R3

NOTE: If the desired loss is less than the minimum loss R_2 will be negative.

User Instructions

Program Listings


81 *LBL1 82 ENR4 83 ST02 84 X#Y 85 ST01 86 R/S 87 *LBL2 88 1 89 0 10 ÷ 11 10X 12 ST07 13 X 14 X 15 TX 16 2 17 X 18 RCL7 19 1 20 ST+7 21 - 22 ST08 23 ÷ 24 ST05 25 RCL1 26 RCL7 27 X 28 RCL8 29 ÷ 30 RCL5 31 - 32 ST03 33 RCL2 34 RCL7 35 X 36 RCL8 37 ÷ 38 RCL5 39 - 40 ST04 41 RCL1 42 RCL2 43 ÷ 44 ENT↑ 45 TX 46 X#Y 47 1 48 - 49 TX	N	50 + 51 X# 52 LOG 53 1 54 0 55 X 56 ST06 57 R/S 58 RCL3 59 R/S 60 RCL4 61 R/S 62 RCL5 63 R/S	*** Min Loss *** R ₁ *** R ₂ *** R ₃
	R ₃		
	R ₁		*** "Printx" may be inserted or used to replace "R/S".

REGISTERS

0	1 Z ₁	2 Z ₂	3 R ₁	4 R ₂	5 R ₃
6 Min Loss	7 N, N+1	8 N-1	9	.0	1
.2	.3	.4	.5	16	17
18	19	20	21	22	23
24	25	26	27	28	29

PI ATTENUATOR

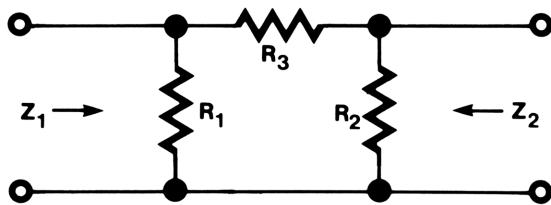The PI attenuator can be used to match between two impedances, Z_1 and Z_2 . This program computes the minimum loss of the attenuator and values for the resistors R_1 , R_2 , and R_3 which will yield an attenuator having any desired loss.



The minimum loss in decibels is given by

$$\text{Min Loss} = 10 \log \left(\sqrt{\frac{Z_1}{Z_2}} + \sqrt{\frac{Z_1}{Z_2} - 1} \right)^2$$

where $Z_1 \geq Z_2$

If N is the desired loss of the attenuator expressed as a ratio (loss in dB = $10 \log N$), then

$$R_3 = \frac{1}{2} (N - 1) \left(\frac{Z_1 Z_2}{N} \right)^{1/2}$$

$$\frac{1}{R_1} = \frac{1}{Z_1} \left(\frac{N + 1}{N - 1} \right) - \frac{1}{R_3}$$

$$\frac{1}{R_2} = \frac{1}{Z_2} \left(\frac{N + 1}{N - 1} \right) - \frac{1}{R_3}$$

EXAMPLE:

$$Z_1 = 75\Omega$$

$$Z_2 = 50\Omega$$

$$\text{Loss} = 6\text{dB}$$

SOLUTION:

```

75.0000 ENT1
50.0000 GEB1
6.0000 GEB2
5.7195+00 *** Min Loss
R/3
2.3862+03 *** R1
R/3
86.517+00 *** R2
R/3
45.747+00 *** R3

```

User Instructions


Program Listings

<pre> 01 *LBL1 02 ENG4 03 ST02 04 X#Y 05 ST01 06 R/S 07 *LBL2 08 1 09 0 10 ÷ 11 10^X 12 ST07 13 ÷ 14 X 15 √X 16 RCL7 17 1 18 ST+7 19 - 20 ST÷7 21 2 22 ÷ 23 X 24 ST05 25 1/X 26 ST08 27 RCL7 28 RCL1 29 ÷ 30 RCL8 31 - 32 1/X 33 ST03 34 RCL7 35 RCL2 36 ÷ 37 RCL8 38 - 39 1/X 40 ST04 41 RCL1 42 RCL2 43 ÷ 44 √X 45 LSTX 46 1 47 - 48 √X 49 + </pre>		N	<pre> 50 X2 51 LOG 52 1 53 0 54 X 55 ST06 56 R/S 57 RCL3 58 R/S 59 RCL4 60 R/S 61 RCL5 62 R/S </pre> <p>*** Min Loss *** R₁ *** R₂ *** R₃</p>
REGISTERS			
0	1 Z ₁	2 Z ₂	3 R ₁
6 Min Loss	7 N, $\frac{N+1}{N-1}$	8 1/R ₃	9 .0 .1
.2	.3	.4	.5 16 17
18	19	20	21 22 23
24	25	26	27 28 29


WYE-DELTA OR DELTA-WYE TRANSFORMATION

This program performs the Y-Δ transform for circuits consisting of resistors, inductors, or capacitors*. The Y-Δ transforms for one-of-a-kind elements are summarized below.

"Δ" Topology

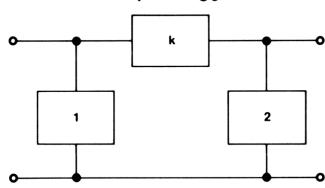

"Y" Topology

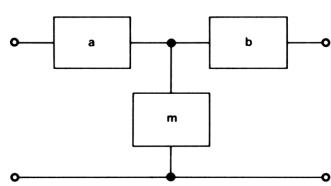

For Capacitors:

$$\text{Y} \rightarrow \Delta \quad C_1 = \frac{C_a C_m}{\Sigma C}$$

$$C_2 = \frac{C_b C_m}{\Sigma C}$$

$$C_k = \frac{C_a C_b}{\Sigma C}$$

$$\Sigma C = C_a + C_b + C_m$$

$$\Delta \rightarrow \text{Y} \quad C_a = \frac{\Sigma C C}{C_2}$$

$$C_b = \frac{\Sigma C C}{C_1}$$

$$C_m = \frac{\Sigma C C}{C_k}$$

$$\Sigma C C = C_1 C_2 + C_2 C_k + C_1 C_k$$

For Inductors: (and Resistors, replace L's by R's)

$$\text{Y} \rightarrow \Delta \quad L_1 = \frac{\Sigma LL}{L_b}$$

$$L_2 = \frac{\Sigma LL}{L_a}$$

$$L_k = \frac{\Sigma LL}{L_m}$$

$$\Sigma LL = L_a L_b + L_b L_m + L_a L_m$$


$$\Delta \rightarrow \text{Y} \quad L_a = \frac{L_1 L_k}{\Sigma L}$$

$$L_b = \frac{L_2 L_k}{\Sigma L}$$

$$L_m = \frac{L_1 L_2}{\Sigma L}$$

$$\Sigma L = L_1 + L_2 + L_k$$

EXAMPLE:

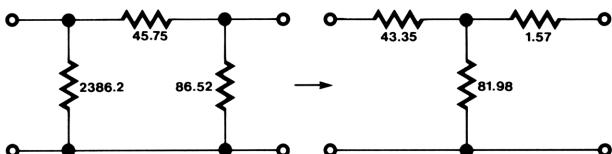

SOLUTION:

2386.20	ENT↑	1
45.75	ENT↑	k
86.52	GSB1	2
	GSB2	
	GSB4	a
43.35	***	
	R/S	m
81.98	***	
	R/S	b
1.57	***	

* Adapted from HP-67/97 Users' Library program #00404D by Bruce Murdock.


User Instructions

Program Listings

01 *LBL1				50 RCL2			
02 ST03				51 X			
03 R1				52 RCL2			
04 ST02				53 RCL3			
05 R4				54 X			
06 ST01				55 +			
07 0				56 RCL1			
08 ST00				57 RCL3			
09 R/S				58 X			
10 *LBL2				59 +			
11 1				60 ST04			
12 ST00				61 RCL3			
13 R/S				62 +			
14 *LBL3				63 ST05			
15 RCL0				64 RCL4			
16 X>0?				65 RCL2			
17 GT00				66 +			
18 *LBL9				67 ST06			
19 RCL1				68 RCL4			
20 RCL2				69 RCL1			
21 +				70 +			
22 RCL3				71 ST07			
23 +				72 *LBL8			
24 ST04				73 RCL5			
25 RCL1				74 R/S			
26 RCL2				75 RCL6			
27 X				76 R/S			
28 RCL4				77 RCL7			
29 +				78 R/S			
30 ST05							
31 RCL1							
32 RCL3							
33 X							
34 RCL4							
35 +							
36 ST06							
37 RCL2							
38 RCL3							
39 X							
40 RCL4							
41 +							
42 ST07							
43 GT00							
44 *LBL4							
45 RCL0							
46 X>0?							
47 GT00							
48 *LBL0							
49 RCL1							
REGISTERS							
0 flag	1 1 or a	2 k or m	3 2 or b	4 Σ or $\Sigma\Sigma$	5 1 or a		
6 k or m	7 2 or b	8	9	.0	.1		
.2	.3	.4	.5	16	17		
18	19	20	21	22	23		
24	25	26	27	28	29		

PI NETWORK IMPEDANCE MATCHING

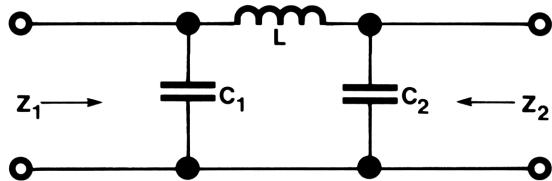A lossless network is often used to match between two resistive impedances Z_1 and Z_2 , as shown



Given the values of Z_1 and Z_2 ($Z_1 > Z_2$), the frequency f , and the desired circuit Q , the values of C_1, C_2 , and L can be found from the following formulas:

$$X_{C1} = \frac{Z_1}{Q}$$

$$C_1 = \frac{1}{2\pi f X_{C1}}$$

$$X_{C2} = \frac{Z_2}{\left[\frac{Z_2}{Z_1} (Q^2 + 1) - 1 \right]^{1/2}}$$

$$C_2 = \frac{1}{2\pi f X_{C2}}$$

$$X_L = \frac{Q Z_1}{Q^2 + 1} \left[1 + \frac{Z_2}{Q X_{C2}} \right]$$

$$L = \frac{X_L}{2\pi f}$$

NOTE: Z_1, Z_2 , and Q must be chosen so that

$$\frac{Z_2}{Z_1} (Q^2 + 1) > 1$$

EXAMPLE:

$$Z_1 = 500\Omega$$

$$Z_2 = 50\Omega$$

$$f = 4\text{MHz}$$

$$Q = 10$$

SOLUTION:

500.0000 ENT↑

50.0000 ENT↑

4.+06 ENT↑

10.0000 GSB1

795.77-12 *** C₁

R/S

2.4006-09 *** C₂

R/S

2.5639-06 *** L

User Instructions

Program Listings


19

01 *LBL1 02 ST04 03 R↓ 04 ST03 05 R↓ 06 ST02 07 R↓ 08 ST01 09 ENG4 10 RCL4 11 RCL1 12 ÷ 13 GSB0 14 RCL2 15 RCL1 16 ÷ 17 RCL4 18 X² 19 1 20 + 21 ST05 22 X 23 1 24 - 25 JX 26 RCL2 27 ÷ 28 ST06 29 GSB0 30 RCL2 31 RCL6 32 X 33 RCL4 34 ÷ 35 1 36 + 37 RCL4 38 RCL1 39 X 40 RCL5 41 ÷ 42 X 43 *LBL0 44 PI 45 2 46 X 47 RCL3 48 X 49 ÷	1/X _{C₂}	50 R/S 51 RTN 52 R/S	***C ₁ , C ₂ , L		
REGISTERS					
0	1 Z ₁	2 Z ₂	3 f	4 Q	5 Q ² +1
6 1/X _{C₂}	7	8	9	.0	.1
.2	.3	.4	.5	16	17
18	19	20	21	22	23
24	25	26	27	28	29

ACTIVE FILTER DESIGN

The transfer function of the active low-pass filter shown is
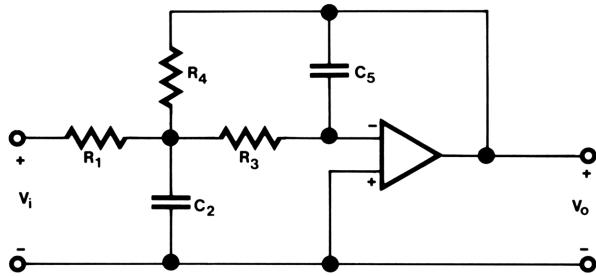
$$\frac{V_o}{V_i}(s) = \frac{-\frac{1}{R_1 R_3 C_2 C_5}}{s^2 + \frac{s}{C_2} \left(\frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_4} \right) + \frac{1}{R_3 R_4 C_2 C_5}}$$



Given

$$G = \left| \frac{V_o}{V_i} \right|, \text{ the desired low frequency gain}$$

f_c , the cutoff frequency in hertz

α , the desired "alpha peaking factor" ($\alpha = 2\zeta$, where ζ is the damping factor)

$C = C_5$, farads

the program computes values for R_1 , C_2 , R_3 and R_4 according to the following equations:

$$R_4 = \frac{\alpha}{4\pi f_c C}$$


$$R_1 = \frac{R_4}{G}$$

$$R_3 = \frac{R_4}{G+1}$$

$$C_2 = \frac{G+1}{R_4 \alpha \pi f_c}$$

The transfer function of the active high-pass filter shown is
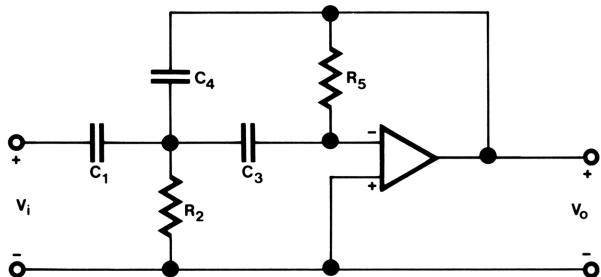
$$\frac{V_o}{V_i}(s) = \frac{-\frac{s^2}{C_4}}{s^2 + \frac{s}{R_5} \left(\frac{C_1}{C_3 C_4} + \frac{1}{C_4} + \frac{1}{C_3} \right) + \frac{1}{R_2 R_5 C_3 C_4}}$$



Given

$$G = \left| \frac{V_o}{V_i} \right|, \text{ the desired high frequency gain}$$

f_c

α

$C = C_1 = C_3$, farads

this program solves the following equations for the values of R_2 , R_5 , and C_4 .²

$$R_2 = \frac{\alpha}{2\pi f_c C \left(2 + \frac{1}{G} \right)}$$

$$R_5 = \frac{2G+1}{\alpha 2\pi f_c C}$$

$$C_4 = \frac{C}{G}$$

NOTES: 1. If α is not specified, $\alpha = \sqrt{2}$ is used, giving component values for a Butterworth filter.

2. These equations derive from the fact that both transfer functions have the form

$$H(s) = \frac{-G \omega_C^2}{s^2 + 2\omega_C s + \omega_C^2},$$

EXAMPLES:

1. Compute R_4 , R_1 , R_3 , and C_2 for a low-pass filter with

$$f_c = 100 \text{ Hz}$$

$$C = .1 \mu\text{F}$$

$$G = 10$$

$$\alpha = \sqrt{2}$$

2. Compute R_2 , C_4 , and R_5 for a high-pass filter with

$$f_c = .1 \text{ Hz}$$

$$C = 10 \mu\text{F}$$

$$G = 1$$

$$\alpha = \sqrt{2}$$

SOLUTIONS:

100.00 $0.1-06$ 10.00 2.00 11253.95 1125.40 1023.09 $2.20-06$	$\text{ENT}\uparrow$ $\text{ENT}\uparrow$ $\text{ENT}\uparrow$ JX GSB1 *** R/S *** R/S *** R/S ***	R_4 R_1 R_3 C_2
--	--	----------------------------------

0.10 $10.-06$ 1.00 2.00 75026.36 $1.00-05$ 337618.62	$\text{ENT}\uparrow$ $\text{ENT}\uparrow$ $\text{ENT}\uparrow$ JX GSB2 *** R/S *** R/S	R_2 C_4 R_5
--	--	-------------------------

User Instructions

Program Listings

01 *LBL1		50 ÷		
02 ST07		51 R/S	*** R ₂	
03 R↓		52 RCL6		
04 R↓		53 RCL5		
05 ST06		54 ST ₇		
06 X		55 ÷		
07 PI		56 R/S	*** C ₄	
08 X		57 RCL7		
09 4		58 1/X		
10 X		59 R/S	*** R ₅	
11 ÷				
12 R/S	*** R ₄			
13 ST04				
14 X ² Y				
15 ÷	*** R ₁			
16 R/S				
17 RCL4				
18 LSTX				
19 1				
20 +				
21 ÷				
22 R/S	*** R ₃			
23 LSTX				
24 RCL6				
25 X				
26 4				
27 X				
28 RCL7				
29 X ²				
30 ÷				
31 R/S	*** C ₂			
32 *LBL2				
33 ST07				
34 R↓				
35 ST05				
36 R↓				
37 ST06				
38 X				
39 2				
40 X				
41 PI				
42 X				
43 STx7				
44 RCL5				
45 1/X				
46 2				
47 +	(2 G+1)/G			
48 ST ₇				
49 X				

REGISTERS


0	1	2	3	4 R ₄	5 G
6 C	7 α	8 2 G+1	9	.0	.1
.2	.3	.4	.5	16	17
18	19	20	21	22	23
24	25	26	27	28	29

BUTTERWORTH FILTER DESIGN

This program computes component values for Butterworth low-pass filters between equal terminations given filter order, termination resistance in ohms, and corner frequency in hertz.

$$C_i = \frac{1}{\pi f_c R} \sin \frac{(2i-1)\pi}{2n}, \quad i = 1, 3, 5, \dots$$
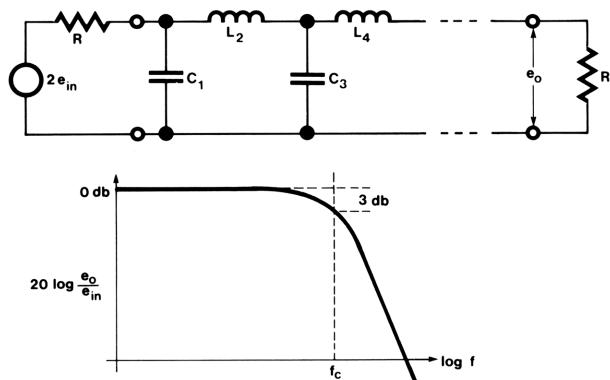
$$L_i = \frac{R}{\pi f_c} \sin \frac{(2i-1)\pi}{2n}, \quad i = 2, 4, 6, \dots$$



NOTE: $n \leq 10$

EXAMPLE:

$$n = 6$$

$$R = 50\Omega$$

$$f_c = 10 \text{ MHz}$$

SOLUTION:

```

6.0000 ENT↑
50.0000 ENT↑
10.+06 GSB1
1.0000+00 *** i
R/S
164.77-12 *** C1
R/S
2.0000+00 ***
R/S
1.1254-06 *** L2
R/S
3.0000+00 ***
R/S
614.93-12 *** C3
R/S
4.0000+00 ***
R/S
1.5373-06 *** L4
R/S
5.0000+00 ***
R/S
450.16-12 *** C5
R/S
6.0000+00 ***
R/S
411.92-09 *** L6

```

User Instructions

25

Program Listings

<pre> 01 *LBL1 02 RAD 03 ENG4 04 ST.3 05 R↓ 06 ST.2 07 R↓ 08 ST.1 09 ST00 10 *LBL0 11 RCL0 12 2 13 x 14 1 15 - 16 PI 17 x 18 RC.1 19 2 20 x 21 ÷ 22 ST01 23 DSZ 24 GT00 25 PI 26 RC.3 27 RC.2 28 x 29 x 30 1/X 31 ST.5 32 2 33 CHS 34 ST.4 35 1 36 ST00 37 *LBL9 38 RC.1 39 RCL0 40 X>Y? 41 GT08 42 R/S 43 RCL i 44 SIN 45 RC.5 46 x 47 R/S 48 RC.2 49 RC.4 </pre>	<p>Sine argument</p> <p>$1/\pi f_c R$</p> <p>i>n?</p> <p>end</p> <p>*** i</p> <p>*** C_i or L_i</p> <p>R</p> <p>± 2</p>	<pre> 50 CHS 51 ST.4 52 YX 53 SX.5 54 ISZ 55 GT09 56 *LBL8 57 0 58 R/S </pre> <p>*** "Printx" may replace "R/S".</p>					
REGISTERS							
0	i	1	2	3	4	5	
6		7	8	9	.0	.1	n
.2	R	.3 f_c	.4 ± 2	.5 $1/\pi f_c R$ or $R/\pi f_c$		17	
18		19	20	21	22	23	
24		25	26	27	28	29	

STANDARD RESISTANCE VALUES*

For a given tolerance, a "step size" is computed which is used to determine two values, one below and one above the non-standard resistance. These are converted by a subroutine to standard values, and the geometric mean of the latter is calculated. If the given non-standard value is below the mean then the lower standard value is selected; otherwise the larger value is selected.

SOLUTION:

NOTE: Incorrect results will be obtained for tolerances other than 5%, 10%, or 20%.

REFERENCE: International Telephone and Telegraph Corp.
Reference Data for Radio Engineers, fourth edition,
 p. 78.

EXAMPLES: Find the closest standard values for the following:

$$R_1 = 432\Omega$$

$$R_2 = 114 \text{ K}\Omega$$

$$R_3 = 3.5 \text{ M}\Omega$$

ENG4		
5.0000 GSE1	5%	
432.0000 GSE2		
430.00+02 ***	R ₁	
114.+03 GSE3		
110.00+03 ***	R ₂	
3.5+06 GSE2		
3.6000+06 ***	R ₃	
10.0000 GSE1	10%	
432.0000 GSE2		
470.00+00 ***	R ₁	
114.+03 GSE3		
120.00+03 ***	R ₂	
3.5+06 GSE2		
3.7000+06 ***	R ₃	
20.0000 GSE1	20%	
432.0000 GSE2		
470.00+00 ***	R ₁	
114.+03 GSE3		
120.00+03 ***	R ₂	
3.5+06 GSE2		
3.3000+06 ***	R ₃	

* Adapted from HP-65 Users' Library program #00915A by Jacob Jacobs.

User Instructions

Program Listings

29

01 *LBL1			50 X	10 EXP R7	
02 1			51 R/S	*** R	
03 2			52 *LBL8	Finds standard R	
04 0			53 .	value from multiple	
05 ÷			54 5	of step size	
06 10 ^x			55 +		
07 ST02	10 to 1/120		56 INT	Round up	
08 R/S			57 ST06		
09 *LBL2			58 2		
10 LOG			59 6		
11 ENT↑			60 X>Y?		
12 INT			61 GT06		
13 ST04			62 4		
14 -			63 7		
15 1			64 RCL6		
16 +			65 X>Y?		
17 10 ^x			66 GT03		
18 ST03			67 1	26<R<47 then add 1	
19 1			68 +		
20 ST-4			69 RTN		
21 1			70 *LBL3		
22 0			71 8		
23 ST05			72 3		
24 *LBL0			73 RCL6		
25 RCL3			74 X>Y?		
26 RCL5			75 RTN		
27 X>Y?	This step >		76 8		
28 GT09	Normal R?		77 2		
29 RCL2			78 RTN		
30 X			79 *LBL7		
31 ST05			80 RCL6		
32 GT00			81 ST07		
33 *LBL9			82 RTN		
34 GSB8			83 *LBL6		
35 ST07	This step		84 RCL6		
36 RCL5			85 RTN		
37 RCL2			86 R/S		
38 ÷					
39 GSB8					
40 ST06	Last step				
41 RCL7					
42 X					
43 IX	✓(This step)*(Last				
44 RCL3	step)				
45 X>Y?					
46 GSB7					
47 RCL7					
48 RCL4					
49 10 ^x					
REGISTERS					
0	1	2 Step size	3 Normal R	4 Exp of R	5 This step
6 Temp	7 Temp	8	9	.0	.1
.2	.3	.4	.5	16	17
18	19	20	21	22	23
24	25	26	27	28	29

SMITH CHART CONVERSIONS

This program allows conversion among standing wave ratio, reflection coefficient, and return loss.

The parameters

σ = voltage standing wave ration

SWR = standing wave ratio expressed in decibels

ρ = reflection coefficient


R.L. = return loss

are related as follows:


$$\text{SWR} = 20 \log \sigma$$

$$\text{R.L.} = 20 \log \frac{1}{\rho}$$

$$\sigma = \frac{1 + \rho}{1 - \rho}$$

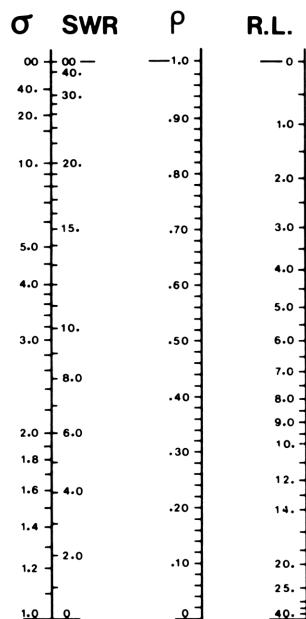

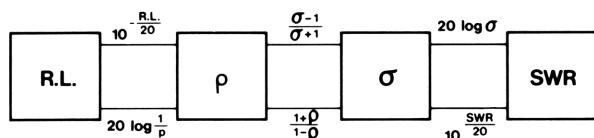These relationships are perhaps more clearly seen in this sketch:



The program also converts between impedance and reflection coefficient using the following relationships:

$$\Gamma = \rho \angle \phi = \frac{\frac{Z}{Z_0} - 1}{\frac{Z}{Z_0} + 1}$$

and

$$Z = Z \angle \theta = Z_0 \frac{1 + \Gamma}{1 - \Gamma}$$

where

Γ = complex reflection coefficient

ρ = $|\Gamma|$

ϕ = $\angle \Gamma$

Z = impedance

Z = $|Z|$

θ = $\angle Z$

Z_0 = characteristic impedance

EXAMPLES:

1. Convert a 6 dB SWR to σ .
2. Convert a 7 dB return loss to SWR
3. A 50Ω system is terminated with an impedance of $62\angle 37^\circ$. What is the reflection coefficient?
4. A reflection coefficient of $.5\angle 7^\circ$ is observed in a 72Ω system. What is the impedance?

SOLUTIONS:

6.00	GSB4	R/S
2.00	*** σ	70.19 *** φ
7.00	GSB3	
	GSB6	
	GSB2	
8.35	*** SWR	72.00 ST01
		7.00 ENT↑
		0.50 GSB7
50.00	ST01	212.50 *** Z
37.00	ENT↑	R/S
62.00	GSBS	9.23 *** θ
0.35	*** ρ	

User Instructions

Program Listings

01 *LBL1	$\rho \rightarrow R.L.$	50 R/S	*** ϕ
02 1/X	$\sigma \rightarrow SWR$	51 *LBL0	$ \angle$
03 *LBL2		52 $\rightarrow R$	$R_e \text{ Im}$
04 LOG		53 ST04	
05 2		54 X \leftrightarrow Y	
06 0		55 ST03	
07 X		56 X \leftrightarrow Y	
08 R/S	*** R.L. or SWR	57 RCL5	Add in rectangular
09 *LBL3	R.L. \rightarrow ρ	58 ST-4	form
10 CHS		59 +	$ 1 \angle 1$
11 *LBL4	SWR \rightarrow σ	60 $\rightarrow P$	
12 2		61 ST02	
13 0		62 R↓	
14 \div		63 RCL3	
15 10 x		64 RCL4	
16 R/S	*** ρ or σ	65 $\rightarrow P$	$ 2 \angle 2$
17 *LBL5	$\sigma \rightarrow \rho$	66 ST \div 2	Divide in polar
18 1/X		67 R↓	form
19 CHS		68 -	\angle'
20 *LBL6		69 RCL2	$ '$
21 1		70 RTN	
22 X \leftrightarrow Y			
23 +			
24 1			
25 LSTX			
26 -			
27 \div			
28 R/S	*** ρ or σ		
29 *LBL7	$\Gamma \rightarrow Z$		
30 1			
31 ST05			
32 R↓			
33 GSB0			
34 RCL1			
35 CHS			
36 X	Reverse \angle		
37 $\rightarrow R$			
38 $\rightarrow P$	*** Z		
39 R/S			
40 X \leftrightarrow Y			
41 R/S	*** θ		
42 *LBL8	$Z \rightarrow \Gamma$		
43 RCL1			
44 CHS			
45 ST05			
46 R↓			
47 GSB0			
48 R/S			
49 X \leftrightarrow Y	*** ρ		

REGISTERS

0	1 Z_0	2 $ 1 , '$	3 Im	4 $R_e, Re-k$	5 k
6	7	8	9	.0	.1
.2	.3	.4	.5	16	17
18	19	20	21	22	23
24	25	26	27	28	29

NOTES

NOTES

In the Hewlett-Packard tradition of supporting HP programmable calculators with quality software, the following titles have been carefully selected to offer useful solutions to many of the most often encountered problems in your field of interest. These ready-made programs are provided with convenient instructions that will allow flexibility of use and efficient operation. We hope that these Solutions books will save your valuable time. They provide you with a tool that will multiply the power of your HP-19C or HP-29C many times over in the months or years ahead.

Mathematics Solutions
Statistics Solutions
Financial Solutions
Electrical Engineering Solutions
Surveying Solutions
Games
Navigational Solutions
Civil Engineering Solutions
Mechanical Engineering Solutions
Student Engineering Solutions

HEWLETT  PACKARD